



**COLLEGE OF ENGINEERING  
PUTRAJAYA CAMPUS  
FINAL EXAMINATION**

**SPECIAL SEMESTER 2013 / 2014**

PROGRAMME	: Bachelor of Electrical & Electronics Engineering (Honours) Bachelor of Electrical Power Engineering (Honours)
SUBJECT CODE	: EEEB273
SUBJECT	: ELECTRONIC ANALYSIS AND DESIGN II
DATE	: April 2014
TIME	: 3 hours

---

**INSTRUCTIONS TO CANDIDATES:**

1. This paper contains **Six** (6) questions in **Nine** (9) pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided.
4. Write answer to different question on **a new page**.
5. For all calculations, assume that  $V_T = 26 \text{ mV}$ .

---

**- MODEL ANSWER -**


---

**THIS QUESTION PAPER CONSISTS OF NINE (9) PRINTED PAGES INCLUDING THIS COVER PAGE.**

## **Question 1 [20 marks]**

## Answers:

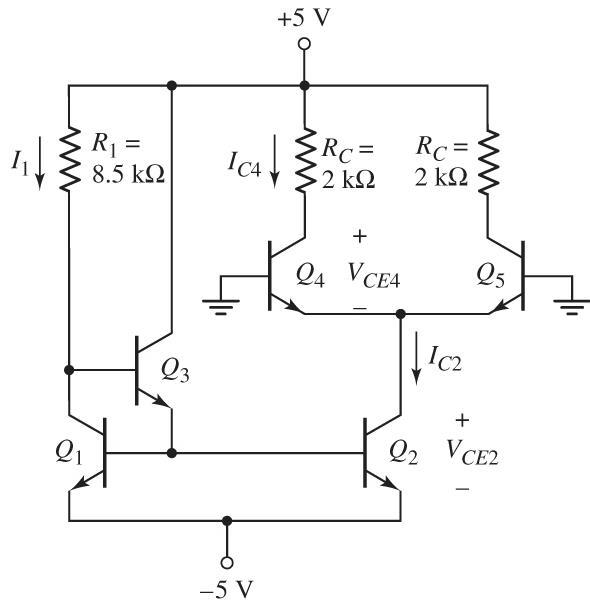- (i) The circuit: [L4] The three-transistor diagram (2 marks)  
The differential amplifier (2 marks)  
The connection of the two circuits (1 mark)



$$(ii) \quad I_1 \approx I_{C2} = \frac{V^+ - V_{BE3} - V_{BE1} - V^-}{R_1} \quad [2]$$

$$I_1 = \frac{5 - 0.7 - 0.7 - 5}{R_1} = 1 \text{ mA}$$

$$R_1 = 8.6 \text{ k}\Omega [2]$$

$$I_{C2} = \frac{I_1}{1 + \left[ \frac{2}{\beta(1 + \beta)} \right]} \cong 1 \text{ mA} [2]$$

$$\frac{I_{C2}}{2} = I_{C4} = 0.5 \text{ mA} [2]$$

$$V_{CE2} = V_E - V^- [1.5]$$

$$= (0 - 0.7) - 5 = 4.3 \text{ V} [1.5]$$

$$V_{CE4} = V^+ - I_{C4}R_C - V_E \quad [2]$$

$$5 - (0.5m)(2k) - (-0.7) = 4.7 \text{ V} [2]$$

**Question 2 [10 marks]****Answers:**

- (i) **Determine**  $I_O$  such that the dc currents in the differential amplifier are balanced. [L3]

[3 marks]

$$I_O = I_{B3} + I_{B4} \quad [1]$$

$$\approx 2 \left( \frac{I_Q}{2} \right) \left( \frac{1}{\beta} \right) \rightarrow \frac{I_Q}{\beta} \quad [1]$$

$$I_O = \frac{0.2m}{100} = 2\mu A \quad [1]$$

- (ii) **Calculate** the open-circuit differential-mode voltage gain. [L3]

[4 marks]

$$r_{o2} = r_{o4} = \frac{V_A}{I_{CQ}} = \frac{100}{0.1m} = 1000k \quad [1]$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.1m}{0.026} = 3.846 \text{ mA/V} \quad [1]$$

$$A_d = g_m(r_{o2} || r_{o4}) \quad [1]$$

$$= 3.846m(1000k)(1000k) \rightarrow 1923 \quad [1]$$

- (iii) **Find** the differential-mode voltage gain if a load resistance  $R_L = 250 \text{ k}\Omega$  is connected to the output. [L3]

[3 marks]

$$A_d = g_m(r_{o2} || r_{o4} || R_L) \quad [1.5]$$

$$A_d = 3.846m(1000k || 1000k || 250k) = 641 \quad [1.5]$$

**Question 3 [15 marks]****Answers:**(a) i. Average current:  $V_p/(\pi R_L)$  [1]

$$I_{ave} = (6)/[(3.141)(200)] = 9.55mA$$
 [1]

ii. Average power delivered to load:

$$P_{Lave} = V_p^2/(2R_L)$$
 [2]

$$= (6)^2/(2(200)) = 90mW$$
 [1]

$$\text{iii. } P_{Qave} = (1/\pi) \int (V_{CC} - V_p \sin \omega t)(V_p/R_L) \sin \omega t \delta \omega t ; \text{ for } 0 \leq \omega t \leq \pi$$
 [2]

$$= \frac{V_{CC}V_p}{\pi R_L} - \frac{V_p^2}{4R_L} = \frac{(10)(6)}{\pi(200)} - \frac{6^2}{4(200)} = 95.51mW - 45mW = 50.5mW$$
 [2]

$$\text{iv. } P_{Save} = 2V_{CC}[V_p/(\pi R_L)] = 2(95.51mW) = 191mW$$
 [2]

$$\eta = P_{Lave}/P_{Save} = 90/191 = 47.1\%$$
 [1]

(b) *Any of the following key-phrases:*(I)  $v_I > +0.7V$ ,  $Q_n$  turns on and operates as emitter follower [1] $I_L$  is positive, supplied thru  $Q_n$ B-E junction of  $Q_p$  is reverse-biased(II)  $v_I < -0.7V$ ,  $Q_p$  turns on and operates as emitter follower [1] $Q_p$  sinks  $I_L$ , which is negativeB-E junction of  $Q_n$  is reverse-biased(III)  $v_O$  remains zero as long as  $-0.7V \leq v_I \leq +0.7V$  [1]**Dead band:** range of input voltage where  $v_O$  is zero

→ Where both transistors are cut-off

**Question 4 [20 marks]****Answers:**

$$\text{i. } r_{\pi 6} = \beta V_T / I_{C6} \text{ where } I_{C6} = I_{C7}/(1+\beta) \quad [2]$$

$$r_{\pi 6} = \beta (1+\beta) V_T / I_{C7} = (90)(91)(0.026)/(0.5m) = 426 \text{ k}\Omega \quad [2]$$

$$r_{\pi 7} = \beta V_T / I_{C7} = (90)(0.026)/0.5m = 4.68 \text{ k}\Omega \quad [2]$$

$$R_i = r_{\pi 6} + (1 + \beta)r_{\pi 7} = 426\text{k}\Omega + (91)(4.68\text{k}\Omega) = 852 \text{ k}\Omega \quad [2]$$

$$\text{ii. } v_{o3} = i_{c7} R_{L7} = (\beta i_{b7}) R_{L7} = \beta(1 + \beta) i_{b6} R_{L7} \quad [2]$$

$$i_{b6} = \frac{v_{o2}}{R_i} \quad [2]$$

$$A_v = \frac{v_{o3}}{v_{o2}} = \frac{\beta(1 + \beta) R_{L7}}{R_i} \quad [2]$$

Find  $\Rightarrow r_{o11}, g_{m11}, r_{\pi 11}, r_{\pi 8} \Rightarrow I_{c11} = I_{c7}, I_{c8} = \text{given}$  [4]

$$r_{o11} = V_A / I_{C7} = 120/0.5m = 240 \text{ k}\Omega$$

$$g_{m11} = V_T / I_{C7} = 0.026/0.5m = 5.2 \text{ k}\Omega$$

$$r_{\pi 11} = \beta V_T / I_{C7} = (90)(0.026)/0.5m = 4.68 \text{ k}\Omega$$

$$r_{\pi 8} = \beta V_T / I_{C8} = (90)(0.026)/2m = 1.17 \text{ k}\Omega$$

$$R_{c11} = r_{o11}(1 + g_{m11} R_E) = (240k)[1 + (5.2k)(4.68k // 0.1k)] = 124T\Omega$$

$$R_{b8} = r_{\pi 8} + (1 + \beta) R_4 = 1.17k + (91)(5k) = 456k\Omega \quad [1]$$

$$R_{L7} = R_{c11} \parallel R_{b8} \cong R_{b8} = 456\text{k}\Omega \quad [2]$$

$$A_v = \frac{90(91)(456k)}{852k} = 4383 \quad [1]$$

**Question 5 [15 marks]****Answers:****Q5(i)**

$$\begin{aligned} I_{C1} &= 8 \mu A & [1] \\ &= I_{C8} / 2 = I_{C9} / 2 &= I_{C10} / 2 & [1] \\ I_{C10} &= 2 \times I_{C10} &= 16 \mu A & [1] \end{aligned}$$

$$\begin{aligned} I_{C10}R_4 &= V_T \ln(I_{REF} / I_{C10}) & [1] \\ I_{REF} &= I_{C10} \exp[I_{C10}R_4 / V_T] & [1] \\ &= (16\mu) \exp[(16\mu \times 5k) / (26m)] & [1] \\ &= 0.347 \text{ mA} & [1] \end{aligned}$$

$$\begin{aligned} I_{REF} &= (V^+ - V - V_{EB12} - V_{BE11}) / R_5 & [1] \\ R_5 &= (V^+ - V - V_{EB12} - V_{BE11}) / I_{REF} & [1] \\ &= (12 - (-12) - 0.6 - 0.6) / (0.347\text{m}) & [1] \\ &= 65.694 \text{ k}\Omega & [1] \end{aligned}$$

**Q5(ii)**

$$\begin{aligned} I_{C6} &= I_{C1} = 8 \mu A & [1] \\ V_{C6} &= V_{BE7} + V_{BE6} + I_{C6}R_2 + V^- & [2] \\ &= 0.6 + 0.6 + (8\mu)(1k) + (-12) & [1] \\ \text{or } V_{C6} &\approx -10.8 \text{ V} & [1] \end{aligned}$$

**Question 6 [20 marks]****Answers:****Q6(a)**

Calculation:

$$A_v = 1 + R_2/(R_{1F} + R_{1V}) \quad [1]$$

$$R_2 = 250 \text{ k}\Omega. \quad R_{1F} \text{ is a fixed-value resistor.}$$

$R_{1V}$  is a potentiometer. Gain is maximum, i.e. 26, when  $R_{1V} = 0 \Omega$ .

$$A_{v1} = 26 = 1 + R_2/(R_{1F} + R_{1V}) = 1 + 250\text{k}/(R_{1F} + 0) \quad [1]$$


$$R_{1F} = 10 \text{ k}\Omega \quad [0.5]$$

Gain is minimum, i.e. 11, when  $R_{1V}$  is maximum.

$$A_{v2} = 11 = 1 + R_2/(R_{1F} + R_{1V}) = 1 + 250\text{k}/(10\text{k} + R_{1V}) \quad [1]$$

$$R_{1V} = 15 \text{ k}\Omega \quad [0.5]$$

Circuit: [2]

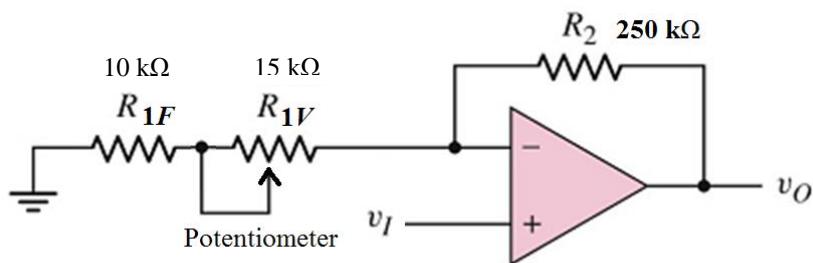**Q6(b)**

Using superposition theorem:

$$v_{I2} = 0: \quad v_{O1}(v_{I1}) = (-R_F/R_1) v_{I1} = (-100\text{k}/100\text{k}) v_{I1} = -v_{I1} \quad [0.5] \quad [0.5] \quad [0.5]$$

$$v_{I1} = 0: \quad v_{O1}(v_{I2}) = (-R_F/R_2) v_{I2} = (-100\text{k}/100\text{k}) v_{I2} = -v_{I2} \quad [0.5] \quad [0.5] \quad [0.5]$$

$$v_{O1} = v_{O1}(v_{I1}) + v_{O1}(v_{I2}) = (-v_{I1}) + (-v_{I2}) = -(v_{I1} + v_{I2}) \quad [0.5] \quad [0.5] \quad [0.5]$$

$$v_O = (-R_F/R_1)v_{O1} = (-100\text{k}/100\text{k})[-(v_{I1} + v_{I2})] = v_{I1} + v_{I2} \quad [0.5] \quad [0.5] \quad [0.5]$$

Note: Student can use any method that leads to the same answer.

**Q6(c)**

$$\mathbf{R}_F / R_1 = 5 \quad \Rightarrow \mathbf{R}_F = 5 R_1 \quad [0.5]$$

$$\text{and} \quad \mathbf{R}_F / R_2 = 10 \quad \Rightarrow \mathbf{R}_F = 10 R_2 \quad [0.5]$$

So, resistor  $R_2$  will be the **smallest** value. Set  $R_2 = 25 \text{ k}\Omega$ . [1]

$$\Rightarrow \quad \mathbf{R}_F = 10 R_2 = 10 \times 25 \text{ k}\Omega = 250 \text{ k}\Omega \quad [0.5]$$

$$\text{and} \quad \mathbf{R}_1 = R_F / 4 = 250 \text{ k}\Omega / 5 = 50 \text{ k}\Omega \quad [0.5]$$

$$R_N = R_1 \parallel R_2 = 50 \text{ k}\Omega \parallel 25 \text{ k}\Omega = 16.667 \text{ k}\Omega$$

$$1 + R_F / R_N = 1 + 250 \text{ k} / (16.667 \text{ k}) = 16$$

$$(1 + R_F / R_N)(R_P / R_A) = (16) (R_P / R_A) = 5 \quad [0.5]$$

$$\text{and} \quad (1 + R_F / R_N)(R_P / R_B) = (16) (R_P / R_B) = 2 \quad [0.5]$$

$$\text{So,} \quad (R_A / R_B) = 2/5. \quad [0.5]$$

$$\text{Choose } \mathbf{R}_A = 80 \text{ k}\Omega, \quad [1]$$

$$\text{then } \mathbf{R}_B = 200 \text{ k}\Omega \quad [1]$$

$$R_P = (2 R_B) / 16 = (5 R_A) / 16$$

$$\Rightarrow \quad \mathbf{R}_P = 25 \text{ k}\Omega \quad [0.5]$$

$$R_P = R_A \parallel R_B \parallel R_C$$

$$\Rightarrow \quad \mathbf{R}_C = 44.45 \text{ k}\Omega \quad [1]$$

**APPENDIX****BASIC FORMULA****BJT**

$$i_C = I_S e^{v_{BE}/V_T}; \text{NPN}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{PNP}$$

$$i_C = \beta i_B = \alpha i_E$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

;Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

**MOSFET**

;N-MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k_n'}{2} \cdot \frac{W}{L}$$

;P-MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k_p'}{2} \cdot \frac{W}{L}$$

;Small signal

$$g_m = 2\sqrt{K_? I_{DQ}}$$

$$r_o \cong \frac{1}{M_{DQ}}$$