



**COLLEGE OF ENGINEERING
PUTRAJAYA CAMPUS
FINAL EXAMINATION**

SPECIAL SEMESTER 2013 / 2014

PROGRAMME : Bachelor of Electrical & Electronics Engineering (Honours)
Bachelor of Electrical Power Engineering (Honours)

SUBJECT CODE : EEEB273

SUBJECT : ELECTRONIC ANALYSIS AND DESIGN II

DATE : April 2014

TIME : 3 hours

INSTRUCTIONS TO CANDIDATES:

1. This paper contains **Six** (6) questions in **Nine** (9) pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided.
4. Write answer to different question on a **new page**.
5. For all calculations, assume that $V_T = 26 \text{ mV}$.

THIS QUESTION PAPER CONSISTS OF NINE (9) PRINTED PAGES INCLUDING THIS COVER PAGE.

Question 1 [20 marks]

Design a differential amplifier using **NPN** bipolar junction transistors (BJT) biased by a three-transistor current source, also using NPN BJT.

The three-transistor NPN BJT current source (consists of Q_1 , Q_2 , Q_3 , and R_1) is biasing the differential amplifier (consists of Q_4 , Q_5 , and resistors R_C) with a **1 mA** constant current.


The transistor parameters are: $\beta = 100$, $V_{BE(\text{on})} = 0.7 \text{ V}$ and $V_A = \infty$. The circuit parameters are: $V^+ = 5 \text{ V}$, $V^- = -5 \text{ V}$. For the differential amplifier $V_{B4} = V_{B5} = 0$, and R_C is given as **2 k Ω** .

- (i) **Draw and label** the circuit diagram of your design clearly. [5 marks]
- (ii) **Show clearly** all calculations and values as accurate as possible with regard to the design. You are required, in particular, to calculate the values of the resistor in the current source, V_{CE2} , and V_{CE4} . [15 marks]

Question 2 [10 marks]

The circuit in **Figure 1** shows a pair of PNP bipolar junction transistors as input devices and a pair of NPN bipolar junction transistors connected as an active load. The biasing current $I_Q = 0.2$ mA, and the transistor parameters are $\beta = 100$, and $V_A = 100$ V.

- (i) **Determine I_O** such that the dc currents in the differential amplifier are **balanced**. [3 marks]
- (ii) **Calculate** the open-circuit differential-mode voltage gain, A_d . [4 marks]
- (iii) **Find** the differential-mode voltage gain if a load resistance $R_L = 250$ k Ω is connected to the output. [3 marks]

 **Figure 1**

Question 3 [15 marks]

(a) An **idealized class-B** output stage, with a complementary pair transistors, as in **Figure 2** has $V^+ = V_{CC} = 10 \text{ V}$, $V^- = -10 \text{ V}$, and $R_L = 200 \ \Omega$. Output signal voltage reads $v_O = 6 \sin \omega t \text{ V}$. The average power supplied by V^+ and V^- to a **class-B** output stage is $2V_{CC}[V_p/(\pi R_L)]$.

Determine the following:

- (i) The average current in the circuit. [2 marks]
- (ii) The average power delivered to the load. [3 marks]
- (iii) The average power dissipated in each transistor. [4 marks]
- (iv) The power conversion efficiency (η) of the output stage. [3 marks]

 


Figure 2

(b) **Describe** the operation of a **class-B** output stage as in **Figure 3**. The cut-in voltage for both transistors is **0.7 V**. How is this output stage different from the **idealized class-B** output stage? [3 marks]

 


Figure 3

Question 4 [20 marks]

Consider the Darlington pair and emitter follower portion of the circuit in **Figure 4**. The parameters are $I_{C7} = I_Q = 0.5 \text{ mA}$, $I_{C8} = 2 \text{ mA}$, $R_4 = 5 \text{ k}\Omega$, and $R_3 = 0.1 \text{ k}\Omega$. For all transistors, the current gain is **90**. Q_{11} has **Early** voltage of **120 V**, while Early voltage for Q_7 is ∞ .

When necessary, redraw circuit or label the circuit parameters and state your assumptions when **finding the values** of the following;

- (i) The input resistance (R_i) of the Darlington pair. [8 marks]
- (ii) The small signal voltage gain of the Darlington pair. [12 marks]

 


Figure 4

Question 5 [15 marks]

Study the bias circuit and input stage of **741 operational amplifier (op-amp)** shown in **Figure 5** carefully. Given that $V^+ = +12\text{ V}$ and $V^- = -12\text{ V}$. Assume V_{BE} for npn = V_{EB} for pnp = 0.6 V (EXCEPT for V_{BE10}). Neglect dc **base currents**.

- (i) **Determine** the value of resistor R_5 if bias current for Q_1 is $8\ \mu\text{A}$, and $V^+ = +12\text{ V}$ and $V^- = -12\text{ V}$. [10 marks]
- (ii) Assuming dc currents in the input stage are exactly **balanced**, therefore dc voltage at collector of $Q_6 =$ dc voltage at collector of Q_5 . **Calculate** V_{C6} . [5 marks]

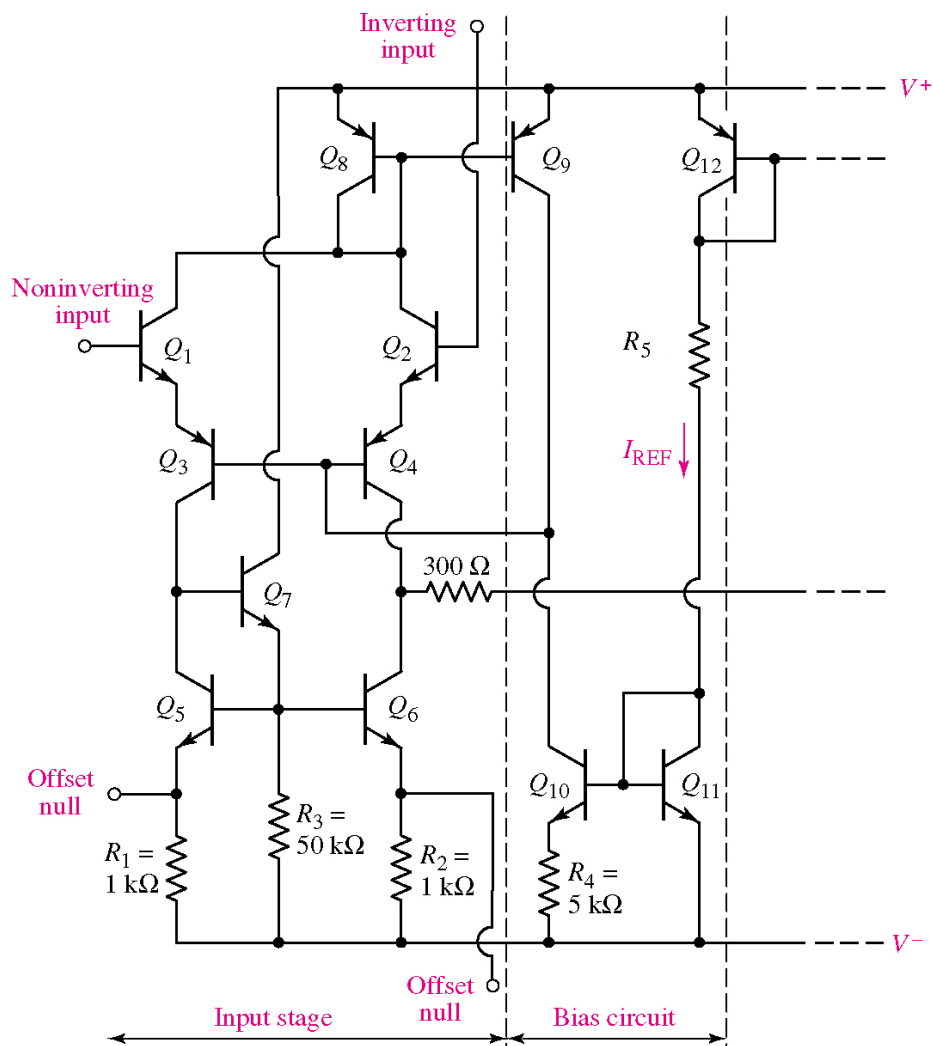


Figure 5

Question 6 [20 marks]

- (a) With a feedback resistor (R_2) of **250 k Ω** , **design** an amplifier using op-amp in non-inverting configuration with a **closed-loop gain** which can be **varied between 11 to 26 V/V**. The closed-loop gain can be varied using a potentiometer (R_{1V}) and a fixed-value resistor (R_{1F}). **Draw clearly** your circuit design.

[6 marks]

- (b) For an **amplifier circuit** using op-amps shown in **Figure 6**, use appropriate ideal op-amp characteristics to **show** that

$$v_O = v_{I1} + v_{I2}$$

when $R_1 = R_2 = R_F = 100 \text{ k}\Omega$.

[6 marks]

 


Figure 6

- (c) For a **generalized summing op-amp** as shown in **Figure 7** the total output voltage (v_O) is the sum of the individual terms, or

$$v_O = -\frac{R_F}{R_1} v_{I1} - \frac{R_F}{R_2} v_{I2} + \left(1 + \frac{R_F}{R_N}\right) \left(\frac{R_P}{R_A} v_{I3} + \frac{R_P}{R_B} v_{I4}\right)$$

where

$$R_N = R_1 \parallel R_2$$

$$R_P = R_A \parallel R_B \parallel R_C$$

With the **smallest resistor value** allowable in the circuit is **25 kΩ**, **design** a summing op-amp similar to **Figure 6b** to produce the output of

$$v_O = -5v_{I1} - 10v_{I2} + 5v_{I3} + 2v_{I4}$$

[8 marks]

 


Figure 7

-END OF QUESTION PAPER-

APPENDIX

BASIC FORMULABJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{NPN}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{PNP}$$

$$i_C = \beta i_B = \alpha i_E$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

;Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

MOSFET

;N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k'_n}{2} \cdot \frac{W}{L}$$

;P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k'_p}{2} \cdot \frac{W}{L}$$

;Small signal

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$