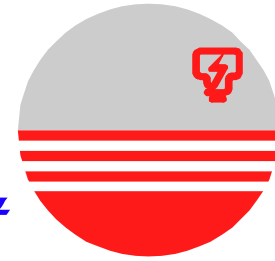


Name:

Student ID Number:

Section: 01 A/B

**UNIVERSITI
TENAGA
NASIONAL**



College of Engineering
Department of Electronics and Communication Engineering

Test 1

SEMESTER 3, ACADEMIC YEAR 2013/2014

Subject Code : **EEEB273**
Course Title : **Electronics Analysis & Design II**
Date : **13 March 2014**
Time Allowed : **2 hours**

Instructions to the candidates:

1. Write your Name and Student ID number. Circle your section number.
2. **Write all your answers using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.**
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**
5. For BJT, use $V_T = 26 \text{ mV}$ where appropriate.
6. Use at least **4 significant numbers** in all calculations.

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.



GOOD LUCK!



| | | | | | |
|--------------|---|---|---|---|-------|
| Question No. | 1 | 2 | 3 | 3 | Total |
| Marks | | | | | |

Question 1 [35 marks]

Figure 1 shows a two-transistor MOS current mirror. The transistor parameters are assumed to be $V_{TP} = -0.4$ V, $k'_p = 60 \mu\text{A}/\text{V}^2$, and $\lambda = 0$. The transistor width-to-length ratios are $(W/L)_1 = 25$, $(W/L)_2 = 15$, and $(W/L)_3 = 5$.

(a) Calculate I_O , I_{REF} , V_{SG1} , and V_{SG3} . [20 marks]

(b) Design the circuit such that $I_O = 80 \mu\text{A}$, $I_{REF} = 220 \mu\text{A}$, and $V_{SD2}(\text{sat}) = 0.35$ V. [15 marks]

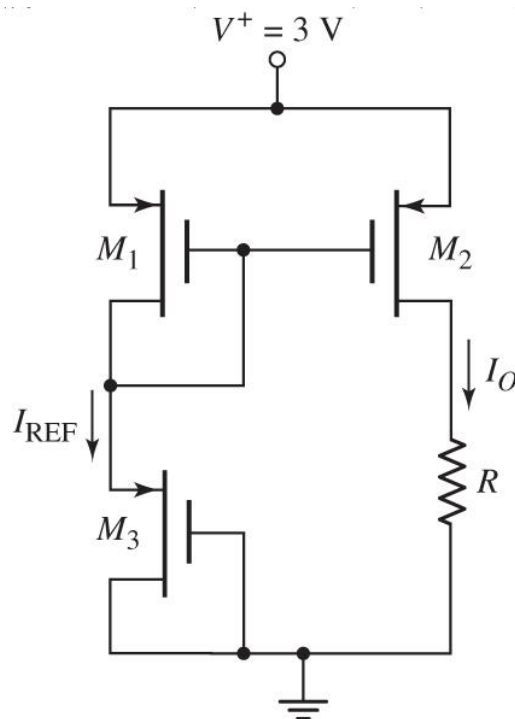


Figure 1

Answers for Question 1**Answers to Q1**

- (a) Calculate
- I_O
- ,
- I_{REF}
- ,
- V_{SG1}
- , and
- V_{SG3}
- .

[20 marks]

$$I_{REF} = \left(\frac{\kappa'_P}{2}\right) \left(\frac{W}{L}\right)_1 (V_{SG1} + V_{TP})^2 = \left(\frac{\kappa'_P}{2}\right) \left(\frac{W}{L}\right)_3 (V_{SG3} + V_{TP})^2 \quad (1) \quad [5]$$

$$V_{SG3} = 3 - V_{SG1} \quad (2) \quad [2]$$

$$\sqrt{25}(V_{SG1} - 0.4) = \sqrt{5}(3 - V_{SG1} - 0.4) \quad [5]$$

$$3.26V_{SG1} = 3.4944 \rightarrow V_{SG1} = 1.08 \text{ V and } V_{SG3} = 1.92 \text{ V} \quad [4]$$

Substituting the values,

$$I_{REF} = \left(\frac{60}{2}\right) (25)(1.08 - 0.4)^2 = 0.347 \text{ mA} \quad [2]$$

$$I_O = \left(\frac{60}{2}\right) (15)(1.08 - 0.4)^2 = 0.208 \text{ mA} \quad [2]$$

- (b) Design the circuit such that
- $I_O = 80 \mu\text{A}$
- ,
- $I_{REF} = 220 \mu\text{A}$
- , and

$$V_{SD2(sat)} = 0.35 \text{ V.}$$

[15 marks]

$$V_{SD2(sat)} = 0.35 = V_{SG2} + V_{TP} - 0.4 \rightarrow V_{SG2} = 0.75 \text{ V} \quad [3]$$

$$I_{REF} = 220 \mu = \left(\frac{60}{2}\right) \left(\frac{W}{L}\right)_1 (0.75 - 0.4)^2 \rightarrow \left(\frac{W}{L}\right)_1 = 59.9 \quad [3]$$

$$I_O = 80 \mu = \left(\frac{60}{2}\right) \left(\frac{W}{L}\right)_2 (0.75 - 0.4)^2 \rightarrow \left(\frac{W}{L}\right)_2 = 21.8 \quad [3]$$

$$V_{SG3} = 3 - 0.75 = 2.25 \text{ V} \quad [3]$$

$$220 = \left(\frac{60}{2}\right) \left(\frac{W}{L}\right)_3 (2.25 - 0.4)^2 \rightarrow \left(\frac{W}{L}\right)_3 = 2.14 \quad [3]$$

Question 2 [25 marks]

Figure 2 shows a differential amplifier has a pair of pnp bipolar as input devices and a pair of npn bipolar connected as an active load. The circuit has $I_Q = 0.2 \text{ mA}$ bias current and the transistor parameters are $\beta = 100$ and $V_A = 100 \text{ V}$.

- (a) Calculate I_O such that the dc currents in the diff-amp are balanced. [6 marks]
- (b) Determine the open-circuit differential-mode voltage gain, A_d . [12 marks]
- (c) Find the differential-mode voltage gain if a load resistance $R_L = 250 \text{ k}\Omega$ is connected to the output. [7 marks]

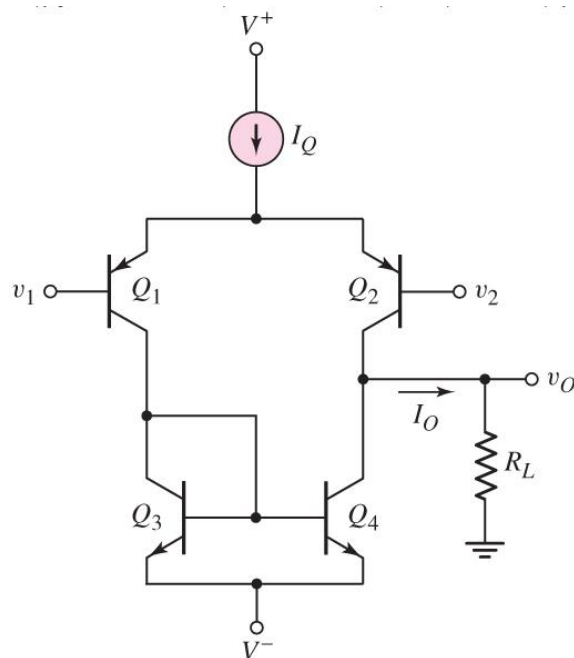


Figure 2

Answers for Question 2

- (a) Calculate I_O such that the dc currents in the diff-amp are balanced. [6 marks]

$$I_U = I_{B3} + I_{B4} \quad [3]$$

$$I_O \approx \frac{I_Q}{\beta} = \frac{0.2\text{mA}}{100} = 2 \mu\text{A} \quad [3]$$

- (b) Determine the open-circuit differential-mode voltage gain, A_d . [12 marks]

$$r_{O2} = r_{O4} = \frac{V_A}{I_{CQ}} = \frac{100}{0.1\text{mA}} = 1000\text{k}\Omega \quad [4]$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.1\text{mA}}{0.026} = 3.846\text{mA/V} \quad [4]$$

$$\therefore A_d = g_m(r_{O2} || r_{O4}) = (3.846\text{mA})(1000\text{k} || 1000\text{k}) = 1923 \quad [4]$$


- (c) Find the differential-mode voltage gain if a load resistance $R_L = 250\text{ k}\Omega$ is connected to the output. [7 marks]

$$A_d = g_m(r_{O2} || r_{O4} || R_L) \quad [3]$$

$$A_d = (3.846\text{mA})(1000\text{k} || 1000\text{k} || 250\text{k}) = 641 \quad [4]$$

Question 3 [20 marks]

The circuit parameters for the **emitter follower** circuit in **Figure 3** is $V^+ = 5\text{ V}$, $V^- = -5\text{ V}$, and $R_L = 1\text{ k}\Omega$. The transistor parameters are $V_{BE(\text{on})} = 0.6\text{ V}$, $V_{CE(\text{sat})} = 0.3\text{ V}$, and $V_A = \infty$. **Neglect** base currents. The **output voltage** is varying from -4.5 V to $+4.5\text{ V}$.

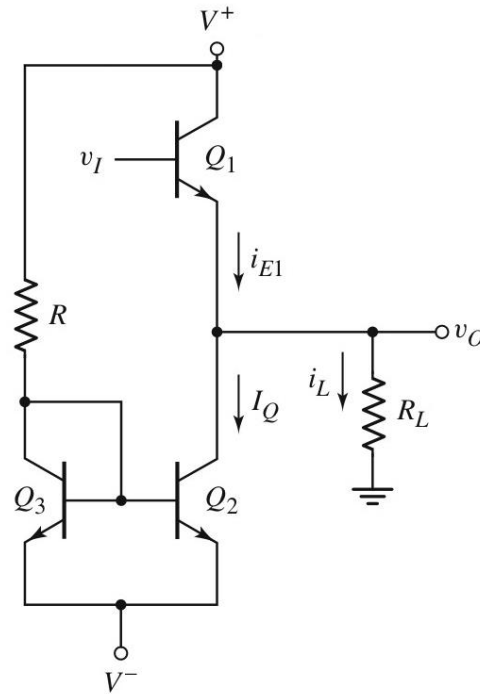**Figure 3**

- (a) **Find** the required I_Q and the value of R . [6 marks]
- (b) For $v_o = 0\text{ V}$, **find** the power dissipated in the transistor Q_1 , and the power dissipated in the current source (Q_2 , Q_3 , and R). [9 marks]
- (c) **Determine** the conversion efficiency for a symmetric sine-wave output voltage with peak value of 8 V . [5 marks]

Answers for Question 3

- i) Find the minimum required I_Q and the value of R. [6 marks]

$$I_{Q\min} = |\text{most negative } I_L| = |v_{\text{omin}}/R_L| \quad [2]$$

$$= |-4.5\text{V}/1\text{k}| = 4.5 \text{ mA} \quad [1]$$

$$R = (V^+ - V_{BE3(\text{on})} - V^-) / I_Q \quad [2]$$

$$= (5 - 0.6 - (-5))/4.5\text{m} = 2.09 \text{ k} \quad [1]$$

- ii) For $v_o = 0$, find the power dissipated in the transistor Q_1 , and the power dissipated in the current source (Q_2 , Q_3 , and R). [9 marks]

$$P_{Q1} = (I_{C1})(V_{CE1}) \quad [1]$$

$$= (I_Q)(V_{C1} - V_{E1}) = (4.5\text{m})(5 - 0) = 22.5 \text{ mW} \quad [1]$$

$$P_{Q2} = (I_{C2})(V_{CE2}) \quad [1]$$

$$= (I_Q)(V_{C2} - V_{E2}) = (4.5\text{m})(0 - (-5)) = 22.5 \text{ mW} \quad [1]$$

$$P_{Q3} = (I_{C3})(V_{CE3}) \quad [1]$$

$$= (I_Q)(V_{BE\text{on}}) = (4.5\text{m})(0.6) = 2.7 \text{ mW} \quad [1]$$

$$P_{\text{Resistor}} = (I)^2(R) \quad [1]$$

$$= (4.5\text{m})^2(2.09\text{k}) = 42.3 \text{ mW} \quad [2]$$

- iii) Determine the conversion efficiency for a symmetric sine-wave output voltage with peak value of 8V. [5 marks]

$$P_L = 0.5(V_p)^2/R_L \quad [1]$$

$$= 0.5(4.5)^2/(1\text{k}) = 10.125 \text{ mW} \quad [1]$$

$$P_S = (V^+ - V^-)(2I_Q) \quad [1]$$

$$= (10)(2 \times 4.5\text{m}) = 90 \text{ mW} \quad [1]$$


$$\text{Power conversion efficiency} = P_L/P_S \times 100\%$$

$$\text{Efficiency} = 10.125\text{m}/90\text{m} \times 100\% = 11.25\% \quad [1]$$

Question 4 [20 marks]

For the circuit in **Figure 4**, the transistor parameters are $\beta = 100$ and $V_A = \infty$. The dc bias currents are as indicated in the figure.

- (a) Determine the input resistance R_i . [12 marks]
- (b) Determine the output resistance R_o . [8 marks]

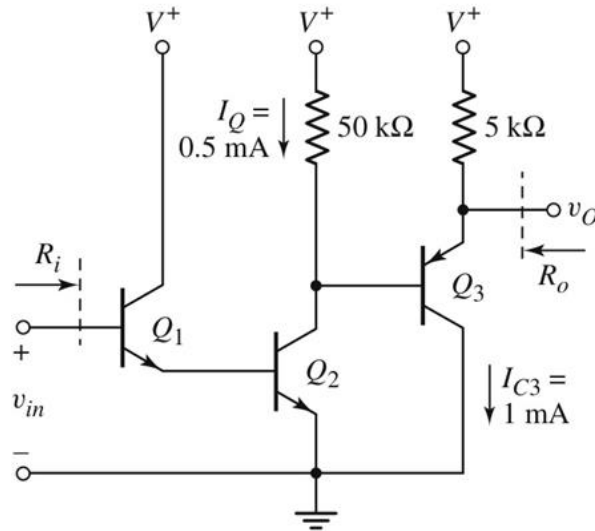**Figure 4**

Answers for Question 4

$$I_{C1} = I_{C2} / (1 + \beta) = 0.5\text{m} / (101) = 4.95\mu\text{A} \quad [2]$$

$$r_{1} = V_T / I_{C1} = (100)(0.026) / 4.95\mu = 530.5\text{k}\Omega \quad [2]$$

$$I_{C2} = I_Q + I_{B3} = 0.5\text{m} + I_{C3} / \beta = 0.5\text{m} + 0.01\text{m} = 0.51\text{mA} \quad [2]$$

$$r_{2} = V_T / I_{C2} = (100)(0.026) / 0.51\text{m} = 5.098\text{k}\Omega \quad [3]$$

$$R_i = r_{1} + (1 + \beta)r_{2} = 530.5\text{k} + (101)(5.2\text{k}) = 1.056\text{M}\Omega \quad [3]$$

$$r_{3} = V_T / I_{C3} = (100)(0.026) / (1\text{m}) = 2.6\text{k}\Omega \quad [2]$$

$$r_{o2} = \hat{O}$$

$$R_{e3} = r_{3} + 50\text{k} // r_{o2} = r_{3} + 50\text{k} = 52.6\text{k}\Omega \quad [3]$$

$$R_o = 5\text{k} // [R_{e3} / (1 + \beta)] = 472\Omega \quad [3]$$

Appendix: BASIC FORMULA

BJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

;Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

MOSFET

;N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{k'_n}{2} \cdot \frac{W}{L}$$

;P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{k'_p}{2} \cdot \frac{W}{L}$$

;Small signal

$$g_m = 2K_n (V_{GSQ} - V_{TN}) = 2\sqrt{K_n I_{DQ}}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$