



**COLLEGE OF ENGINEERING
PUTRAJAYA CAMPUS
FINAL EXAMINATION
SEMESTER 2 2014 / 2015**

PROGRAMME : Bachelor of Electrical & Electronics Engineering (Honours)
Bachelor of Electrical Power Engineering (Honours)

SUBJECT CODE : EEEB273

SUBJECT : ELECTRONIC ANALYSIS AND DESIGN II

DATE : February 2015

TIME : 3 hours

INSTRUCTIONS TO CANDIDATES:

1. This paper contains **Six (6)** questions in **Ten (10)** pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided. Use **pen** to write your answer.
4. Write answer to different question on a **new page**.
5. For all calculations, assume that $V_T = 26 \text{ mV}$.

THIS QUESTION PAPER CONSISTS OF TEN (10) PRINTED PAGES INCLUDING THIS COVER PAGE.

Question 1 [15 marks]

The differential amplifier in Figure 1 is biased by a two-transistor BJT current source (consists of R_1 , Q_3 and Q_4). The transistor parameters are: $\beta = 100$ and $V_{EB(\text{on})} = 0.7 \text{ V}$. The Early voltage for transistors Q_3 and Q_4 is $V_{A3} = V_{A4} = 100 \text{ V}$; while the Early voltage for transistors Q_1 and Q_2 is $V_{A1} = V_{A2} = \infty$. The differential amplifier differential-mode gain is 40 and the common-mode voltage gain is -0.005 . State your assumptions when you answer the following questions:

- (a) Determine v_E and v_{EC1} for common-mode input voltage $v_1 = v_2 = v_{cm} = -2.5 \text{ V}$. [5 marks]
- (b) Determine the output voltage of the differential amplifier if for the inputs $v_1 = 210 \sin \omega t \mu\text{V}$ and $v_2 = 90 \sin \omega t \mu\text{V}$. [6 marks]
- (c) Determine the common-mode input resistance of the differential amplifier if $2R_{icm} = r_{\mu} \parallel [(1 + \beta)(2R_o)] \parallel [(1 + \beta)r_o]$ [4 marks]

 


Figure 1

Q1 (a)

$$V_E = V_1 \text{ ó } V_{BE(on)} = -2.5 - 0.7 = -3.2$$

[1.5]

$$V_{EC1} = v_E \text{ ó } I_{C1} R_C \text{ ó } V_-$$

[1]

$$I_{C1} = [\beta / (1 + \beta)] I_{E1} = [\beta / (1 + \beta)] I_Q / 2 = (100/101)(0.5\text{m}/2) = 0.2475\text{mA}$$

[1.5]

$$V_{EC1} = -3.2 \text{ ó } (0.2475\text{m})(8\text{k}) \text{ ó } (-5) = -0.18\text{V}$$

[1]

Q1(b)

$$A_d = v_o / v_d = g_{m2} R_C / 2$$

OR

$$v_o = (g_{m2} R_C / 2) v_d$$

[2]

$$g_{m2} = I_{C2} / V_T = 0.2475\text{m} / 0.026 = 9.519\text{mA/V}$$

[1]

$$v_d = v_1 \text{ ó } v_2 = 210\sin(\omega t) - 90\sin(\omega t) \mu\text{V} = 120 \sin(\omega t) \mu\text{V}$$

[1.5]

$$v_o = [(9.519\text{m})(8\text{k})(120\mu \sin(\omega t))] / 2 = 4.569 \sin(\omega t) \mu\text{V}$$

[1.5]

Q1(c)

Assume r_{μ} very large

[0.5]

r_{o2} for for the diff-amp transistor is \hat{O}

[0.5]

Thus

$$2R_{icm} \cong (1 + \beta)(2R_o)$$

[1]

R_o is the output of a two-transistor current source

[0.5]

$$R_o = V_A / I_Q = 100 / 0.5\text{m} = 200\text{k}\Omega$$

[1]

$$R_{icm} = (1 + \beta)R_o = (101)(200\text{k}) = 20.20\text{M}\Omega$$

[0.5]

Question 2 [15 marks]

Figure 2 shows a **MOSFET diff-amp with a cascode active load**. Assume that **NMOS** devices are available with the following parameters: $V_{TN} = 0.5 \text{ V}$, $k'_n = 80 \mu\text{A/V}^2$, $\lambda_n = 0.02 \text{ V}^{-1}$, and $(W/L)_1 = (W/L)_2 = 10$. Assume that **PMOS** devices are available with the following parameters: $V_{TP} = -1.0 \text{ V}$, $k'_p = 40 \mu\text{A/V}^2$, and $\lambda_p = 0.02 \text{ V}^{-1}$. The circuit parameters are $V^+ = 5 \text{ V}$ and $V^- = -5 \text{ V}$. The bias current is $I_Q = 0.2 \text{ mA}$.

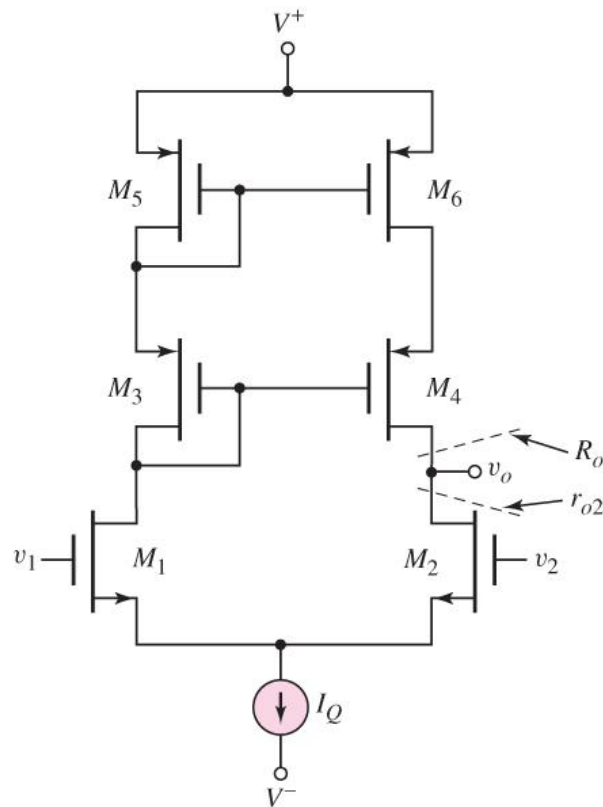


Figure 2

- (a) **Determine** the output resistance, R_o , of the **cascode active load**. [9 marks]
- (b) **Find** the differential-mode voltage gain, A_d . [6 marks]

Q2(a)

$$R_O = r_{O4} + r_{O6} (1 + g_m r_{O4}) \quad \text{OR} \quad R_O \dot{=} g_m r_{O4} r_{O6} \quad [1]$$

$$\text{and} \quad r_o = \frac{1}{\lambda_{DQ}} \quad [1]$$

$$I_{DQ} = I_Q / 2 = 0.2\text{mA} / 2 = 0.1\text{mA} \quad [1]$$

$$r_{O4} = r_{O6} = \frac{1}{\lambda_{DQ}} = \frac{1}{(0.02)(0.1\text{mA})} = 500\text{k}\Omega \quad [2]$$

$$\text{Given that} \quad g_m = 2\sqrt{K_{TM} I_{DQ}} \quad [1]$$

$$g_m = 2\sqrt{\frac{0.08}{2}(10)(0.1\text{mA})} = 0.4 \frac{\text{mA}}{\text{V}} \quad [1]$$

$$\therefore R_O = r_{O4} + r_{O6} (1 + g_m r_{O4}) = 500\text{k} + 500\text{k} (1 + (0.4)(500\text{k})) = \underline{101 \text{ M}\Omega} \quad [2]$$

$$\text{OR} \quad R_O \dot{=} g_m r_{O4} r_{O6} = (0.4)(500\text{k})(500\text{k}) = \underline{100 \text{ M}\Omega} \quad [2]$$

Q2(b)

$$A_d = g_m (r_{O2} || R_O) \quad [2]$$

$$A_d = 0.4\text{mA/V} (500\text{k} || 101\text{M}) \quad [2]$$

$$\underline{A_d = 200} \quad [2]$$

Question 3 [15 marks]

- (a) **Describe** the operation of a **class-B** output stage as in **Figure 3**. The cut-in voltage for both transistors is **0.7 V**. How is this output stage different from the **idealized class-B** output stage? [3 marks]

 


Figure 3

 


Figure 4

- (b) A **class-AB** output stage with BJTs is shown in **Figure 4**. **Reverse saturation current** for every transistor is $I_S = 2 \times 10^{-15}$ A. Assume $+V_{CC} = +5$ V, $-V_{CC} = 0$ V, and $R_L = 1$ k Ω .
- Find** V_{BB} when $v_I = 0$, as such producing $i_{Cn} = i_{Cp} = 1$ mA. [2 marks]
 - Calculate** i_{Cn} , i_{Cp} , and v_I to obtain $v_O = -3.5$ V. [8 marks]
 - Calculate** the power dissipated in R_L . [2 marks]

Q3 Answers:

Q3(a)

Any of the following key-phrases:

- (I) $v_I > +0.7V$, Q_n turns on and operates as emitter follower [1]
 I_L is positive, supplied thru Q_n , B-E junction of Q_p is reverse-biased
- (II) $v_I < -0.7V$, Q_p turns on and operates as emitter follower [1]
 Q_p sinks I_L , which is negative, B-E junction of Q_n is reverse-biased
- (III) v_O remains zero as long as $-0.7V \leq v_I \leq +0.7V$ [1]
Dead band: range of input voltage where v_O is zero
 → Where both transistors are cut-off

Q3(b)

(i) Find V_{BB} :

$$i_{Cn} = I_S \exp(V_{BE}/V_T)$$

$$V_{BE} = V_T \ln(i_{Cn}/I_S) = (26m) \ln(1m/2 \times 10^{-15}) = 0.7004 \text{ V} \quad [1]$$

$$V_{BB} = 2 V_{BE} = 2 \times 0.7004 = 1.40077 \text{ V} \quad [1]$$

(ii) Calculate i_{Cn} , i_{Cp} , and v_I to obtain $v_O = -3.5 \text{ V}$. [Total = 8]

$$v_O = -3.5 \text{ V} = i_L R_L$$

→ $i_L = v_O/R_L = (-3.5V)/(1k) = -3.5 \text{ mA} \quad [1]$
 Therefore, Q_p is conducting and Q_n is OFF.

Approximate value, $i_{Cp} \approx i_L$

$$i_{Cp} = I_S \exp(V_{EB}/V_T) = 3.5 \text{ mA} \quad [0.5]$$

$$V_{EB} = V_T \ln(i_{Cp}/I_S) = (26m) \ln(3.5m/2 \times 10^{-15}) = 0.7329 \text{ V} \quad [0.5]$$

→ $V_{BE} = V_{BB} - V_{EB} = 1.40077 - 0.7329 = 0.6678 \text{ V} \quad [0.5]$
 $i_{Cn} = I_S \exp(V_{BE}/V_T) = (2 \times 10^{-15}) \exp(0.6678/0.026) = 0.2857 \text{ mA} \quad [0.5]$

→ $i_{Cn} = i_{Cp} + i_L$
 $i_{Cp} = i_{Cn} - i_L = 0.2857m - (-3.5m) = 3.7857 \text{ mA} \quad [0.5]$
 $V_{EB} = V_T \ln(i_{Cp}/I_S) = (26m) \ln(3.7857m/2 \times 10^{-15}) = 0.734997 \text{ V} \quad [0.5]$

Actual values:

→ $V_{BE} = V_{BB} - V_{EB} = 1.40077 - 0.734997 = 0.66577 \text{ V} \quad [0.5]$
 $i_{Cn} = I_S \exp(V_{BE}/V_T) = (2 \times 10^{-15}) \exp(0.66577/0.026) = 0.2642 \text{ mA} \quad [0.5]$

→ $i_{Cp} = i_{Cn} - i_L = 0.2642m - (-3.5m) = 3.764 \text{ mA} \quad [1]$

$$v_I = v_O - V_{EB} + V_{BB} / 2 = -3.5 - 0.735 + 0.7004 = -3.535 \text{ V} \quad [2]$$

(iii) The power dissipated in R_L ,

$$P_{RL} = i_L^2 R_L = (3.5)^2 (1k) = 12.25 \text{ mW} \quad [2]$$

Question 4 [20 marks]

Consider the multistage circuit in **Figure 5**. There are three distinctive stages namely the differential amplifier stage, the gain stage, and the output stage. The dc analysis performed by a software tool **LTSpice** on the multistage circuit resulted in an undesired value for the output voltage $v_o = -0.3625 \text{ V}$ (Refer to Appendix A). You are to analyse the dc characteristics of the circuit by **hand analysis** (manual analysis) using only your scientific calculator. Let the bias current from the **Widlar** current source be **0.4 mA**. Following the dc analysis, **identify assumptions** you have made that leads to the undesired output voltage. Thus, **advise** on how to rectify the output voltage to an ideal dc value and how to increase the small signal voltage gain to 10^4 V/V . You may illustrate your ideas by redrawing or redefining the circuit parameters.

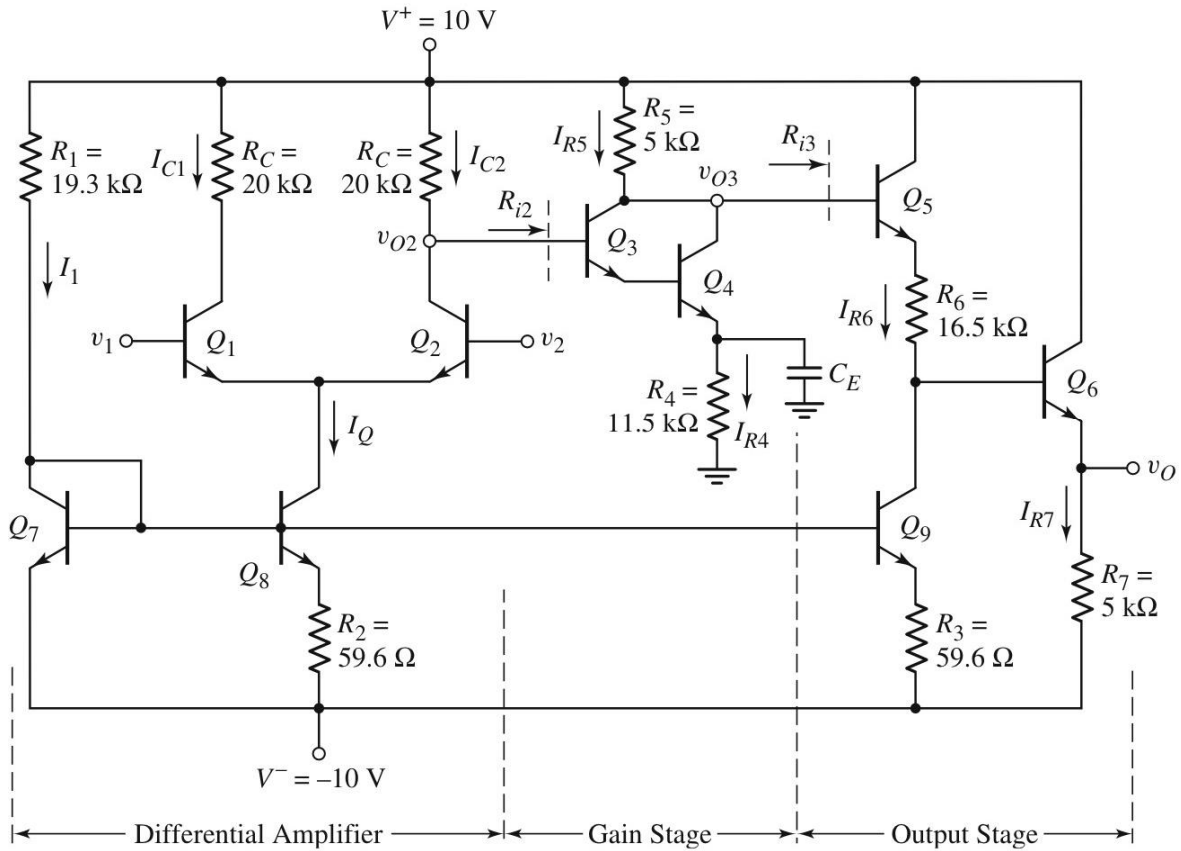


Figure 5

Q4*Input stage:*

$$I_Q = 0.4 \text{ mA}$$

$$I_{C2} = 0.2 \text{ mA} \quad (\text{Neglect base current in Q1 and Q2}) \quad [2]$$

$$v_{o2} = V^+ - I_{C2}R_C = 10 - (0.2\text{m})(20\text{k}) = 6.0\text{V}$$

Gain stage:

$$I_{R4} = [v_{o2} - V_{BE3} - V_{BE4}]/R4 \quad (\text{Assume } V_{BE3} \text{ and } V_{BE4} = 0.7\text{V}) \quad [2]$$

$$I_{R4} = [6 - 2(0.7)]/11.5\text{k} = 0.4\text{mA}$$

$$I_{R4} = I_{R5} \quad (\text{Neglect base currents in Q3 and Q4}) \quad [2]$$

$$v_{o3} = V^+ - (I_{R5}R5) = 10 - (0.4\text{m})(5\text{k}) = 8\text{V}$$

Output Stage:

$$I_{R6} = I_Q \quad (\text{Parallel transistors with } R3 = R2) \quad [2]$$

$$\quad (\text{Neglect base current in Q6}) \quad [2]$$

$$v_{b6} = v_{o3} - V_{BE5} - I_{R6}R6 \quad (\text{Assume } V_{BE5} = 0.7\text{V}) \quad [2]$$

$$v_{b6} = 8 - 0.7 - (0.4\text{m})(16.5\text{k}) = 0.7 \text{ V}$$

$$v_o = v_{b6} - V_{BE7} = 0 \quad (\text{Assume } V_{BE7} = 0.7\text{V}) \quad [2]$$

The solution:

- i. Base currents are neglected in all stages, dc voltage levels have been shifted several times through the stages. If the base currents are taken into account, the actual output voltage, v_o , would not be at the ideal level of zero volt. Instead the dc level should be higher than calculated. In order to adjust the dc level shifts, due to neglecting the base currents, one of the following suggestions can be used to lower the output voltage to zero:
 - a. $R1$ and $R2$ can be reduced to increase I_Q
 - b. R_C can be increased to reduce v_{o2}
 - c. $R5$ can be increased to reduce v_{o3}
 - d. $R6$ can be increased to raise the v_{b6} to a value equals to V_{BE7}
- ii. The assumptions made for $V_{BE} = 0.7 \text{ V}$ for all transistors is also the cause for output voltage to shift several times throughout the stages. If $V_{BE} = 0.6 \text{ V}$ is used in the calculations, the output voltage, v_o would be lower towards a negative value. To increase the output voltage back to zero level, the following can be suggested:
 - a. Increase $R2$ and $R3$ to reduce I_Q
 - b. Reduce R_C to increase v_{o2}
 - c. Reduce $R5$ to increase v_{o3}
 - d. Reduce $R6$ to increase v_{b6}

Marking Criteria:

Every assumption made and mentioned in the analysis deserves 1 mark or capped at [5 marks]

Analysis that leads to a value of $v_o = \pm 0.5 \text{ V}$ [5 marks]Suggest any two solutions in (i) OR (ii) with explanation /reason for suggestions [6 marks]Solution/s to improve gain to 10^4 - use active loads for diff-amp circuit [2 marks]

and specific configuration of active loads [2 marks]

Question 5 [15 marks]

Consider the bias circuit portion of the 741 op-amp in **Figure 6**. Assume that the transistor parameters of $I_S = 5 \times 10^{-16}$ A. The bias voltages are given as ± 15 V.

- (a) **Redesign** the bias circuit to obtain $I_{REF} = 0.4$ mA and $I_{C10} = 40$ μ A. **Determine** the values of V_{BE11} , V_{EB12} , and V_{BE10} . **Neglect** the base currents. [9 marks]
- (b) **Determine** the values of I_{REF} and I_{C10} , using the resistor values found in (a) if $V_{BE(on)} = V_{EB(on)} = 0.6$ V. [6 marks]

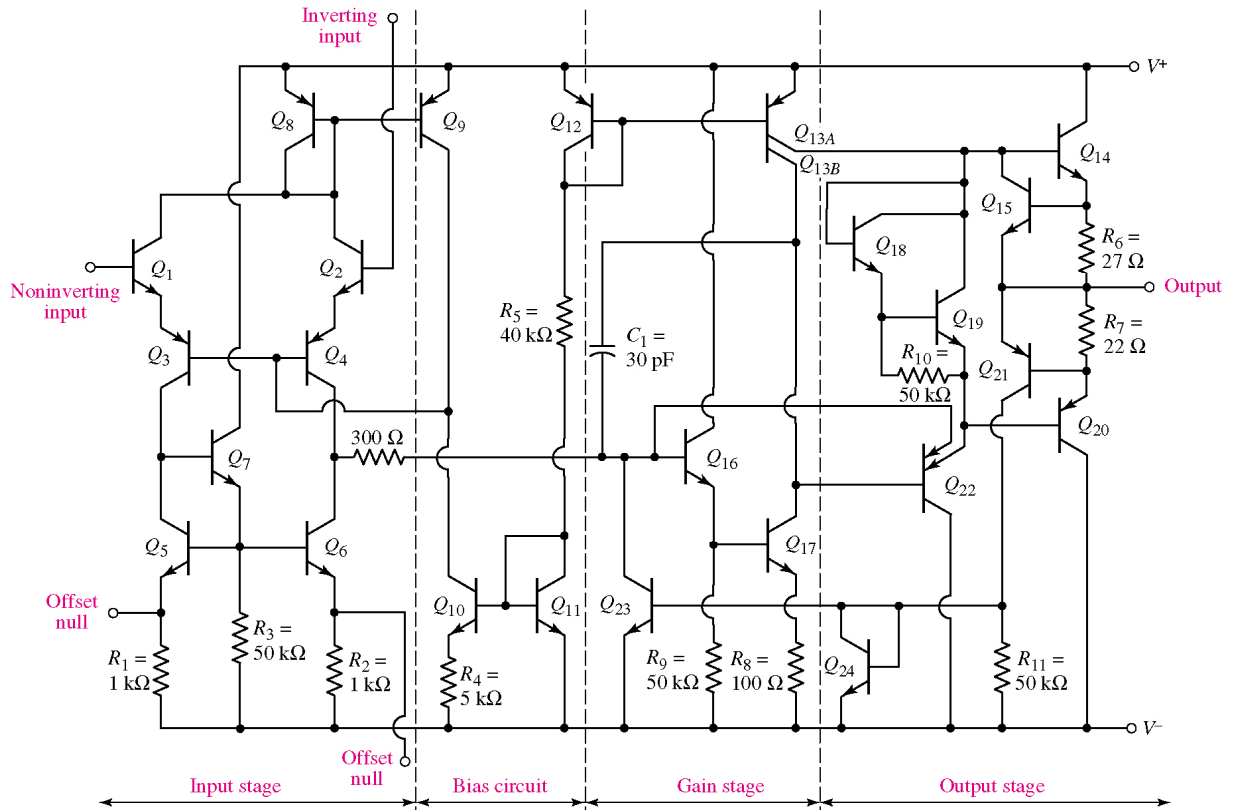


Figure 6

Q5(a)

$$\text{Using the equation, } I_C = I_S \exp^{V_{BE}/V_T} \quad [1]$$

$$V_{BE11} = V_{BE12} = V_T \ln \left(\frac{I_C}{I_S} \right) \quad [1]$$

$$V_{BE11} = 0.026 \ln \left(\frac{0.5 \times 10^{-3}}{5 \times 10^{-6}} \right) = 0.7126 \text{ V} [1]$$

Find R_5 and R_4 ;

$$R_5 = \frac{V^+ - V_{EB12} - V_{BE11} - V^-}{I_{C10}} = \frac{15 - 0.7126 - 0.7126 + 15}{0.4\text{mA}} = 71.44 \text{ k}\Omega [2]$$

$$I_{C10} R_4 = V_T \ln \frac{I_{REF}}{I_{C10}}$$

$$R_4 = \frac{0.026}{0.04\text{mA}} \ln \frac{0.4\text{mA}}{0.04\text{mA}} = 1.497 \text{ k}\Omega [2]$$

$$V_{BE10} = V_{BE11} - I_{C10} R_4 = 0.7126 - 0.04\text{mA}(1.497\text{k}) = 0.6527 \text{ V} [2]$$

Q5(b)

$$I_{REF} = \frac{V^+ - V_{EB12} - V_{BE11} - V^-}{R_5} = \frac{15 - 0.6527 - 0.6527 + 15}{71.44\text{k}} = 0.4017 \text{ mA} [3]$$

$$I_{C10} R_4 = V_T \ln \frac{I_{REF}}{I_{C10}}$$

$$I_{C10}(1.497\text{k}) = (0.026) \ln \frac{0.4017\text{mA}}{I_{C10}} = 0.05987 \text{ mA} [3]$$

Question 6 [20 marks]

(a) With a **feedback resistor (R_2) of 250 k Ω** , design an amplifier using **op-amp** with a **closed-loop gain** which can be **varied between -10 to -25 V/V**. The closed-loop gain can be varied using a **potentiometer (R_{1P})** and a fixed-value resistor (R_{1F}). **Draw clearly** your circuit design. [6 marks]

(b) Refer to **Figure 7**. Op-amp is ideal.

(i) **Derive** the expression for output v_O as a function of inputs v_{I1} and v_{I2} . [4 marks]

(ii) **Calculate** v_O when $R_1 = 50 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, $R_3 = 20 \text{ k}\Omega$, $R_4 = 40 \text{ k}\Omega$, $R_5 = 20 \text{ k}\Omega$, $v_{I1} = +0.25 \text{ V}$, and $v_{I2} = -0.40 \text{ V}$. [2 marks]

 


Figure 7

 


Figure 8

(c) A general output equation for a difference amplifier shown in Figure 8 is

$$v_O = A_d v_d + A_{cm} v_{cm}$$

For the difference amplifier in the Figure 8, the circuit parameters are $R_1 = R_3 = 10 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, and $R_4 = 110 \text{ k}\Omega$ and the output voltage equation is as follows:

$$v_O = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) v_{I2} - \left(\frac{R_2}{R_1}\right) v_{I1}$$


where $v_{I1} = v_{cm} - \frac{v_d}{2}$ and $v_{I2} = v_{cm} + \frac{v_d}{2}$

Find A_d , A_{cm} , and then calculate the $CMRR$ in dB.

[8 marks]

-END OF QUESTION PAPER-

Q6(a)

 

[2]

$$A_v = -R_2/(R_{1F} + R_{1V}) \quad [1]$$

$R_2 = 250 \text{ k}$. R_{1F} is a constant value resistor.

R_{1V} is a potentiometer. Gain is maximum, i.e. -25, when $R_{1V} = 0$.

$$A_{v1} = -25 = -R_2/(R_{1F} + R_{1V}) = -250\text{k}/(R_{1F} + 0) \quad [1]$$

$$R_{1F} = 10 \text{ k} \quad [0.5]$$

$$A_{v2} = -10 = -R_2/(R_{1F} + R_{1V}) = -250\text{k}/(10\text{k} + R_{1V}) \quad [1]$$

$$R_{1V} = 15 \text{ k} \quad [0.5]$$

Q6(b)(i)

$$v_O = \left(1 + \frac{R_2}{R_1}\right)v_1 \quad [0.5]$$

$$v_1 = v_2 \quad [0.5]$$

$$\frac{v_{I1} - v_2}{R_3} + \frac{v_{I2} - v_2}{R_4} = \frac{v_2 - 0}{R_5} \quad [1]$$

$$\frac{v_{I1}}{R_3} + \frac{v_{I2}}{R_4} = v_2 \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right)$$

$$v_2 = \frac{\frac{v_{I1}}{R_3} + \frac{v_{I2}}{R_4}}{\left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right)} \quad [1]$$

$$v_O = \left(1 + \frac{R_2}{R_1}\right) \frac{1}{\left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right)} \left(\frac{v_{I1}}{R_3} + \frac{v_{I2}}{R_4} \right) [1]$$

Q6(b)(ii)

$$v_o = \left(1 + \frac{R_2}{R_1}\right) \frac{1}{\left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}\right)} \left(\frac{v_{I1}}{R_3} + \frac{v_{I2}}{R_4}\right) \quad [0.5]$$

$$v_o = \left(1 + \frac{100k}{50k}\right) \frac{1}{\left(\frac{1}{20k} + \frac{1}{40k} + \frac{1}{20k}\right)} \left(\frac{0.25}{20k} + \frac{-0.40}{40k}\right) \quad [1]$$

$$v_o = (3) \frac{40k}{5} \left(\frac{0.25}{20k} + \frac{-0.40}{40k}\right) = 0.06 \text{ V} \quad [0.5]$$

Q6(c)

$R_1 = R_3 = 10 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, and $R_4 = 110 \text{ k}\Omega$

$$v_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4/R_3}{1 + R_4/R_3}\right) v_{I2} - \left(\frac{R_2}{R_1}\right) v_{I1}$$

$$v_o = \left(1 + \frac{100k}{10k}\right) \left(\frac{110k/10k}{1 + 110k/10k}\right) v_{I2} - \left(\frac{100k}{10k}\right) v_{I1}$$

$$v_o = (1 + 10) \left(\frac{11}{12}\right) v_{I2} - 10v_{I1}$$

2

$$v_o = 10.083v_{I2} - 10v_{I1} = 10.083\left(v_{cm} + \frac{v_d}{2}\right) - 10\left(v_{cm} - \frac{v_d}{2}\right)$$

2

$$v_o = 10.0415v_d + 0.083v_{cm}$$

$A_d = 10.0415$, $A_{cm} = 0.083$

1, 1

$CMRR = 20 \log_{10}[10.0415/0.083] = 41.65 \text{ dB}$

2

APPENDIX A

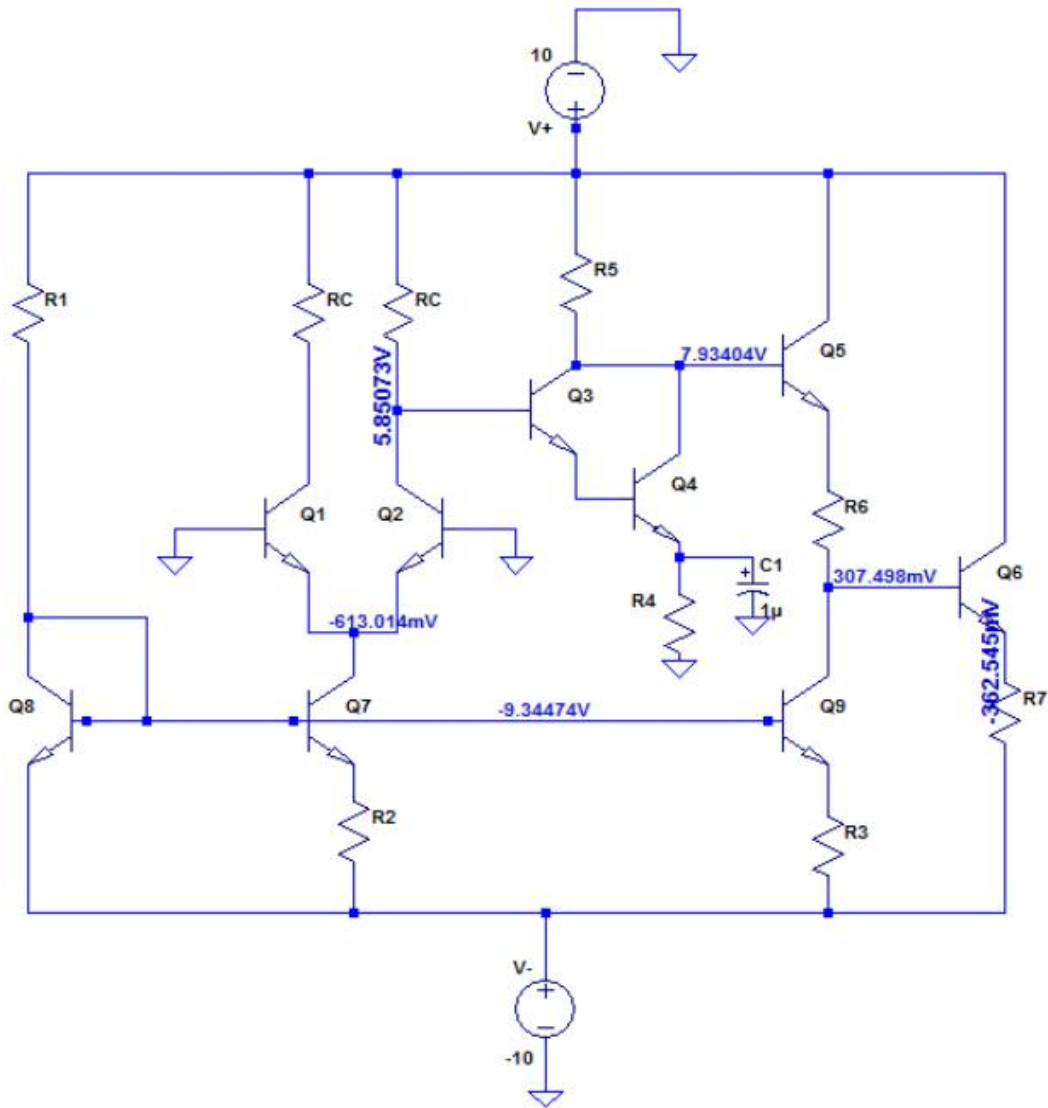


Figure A-1: LTSpice Simulation for Figure 5 in Question 4.

APPENDIX B

BASIC FORMULABJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{NPN}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{PNP}$$

$$i_C = \beta i_B = \alpha i_E$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

;Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

MOSFET

;N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k'_n}{2} \cdot \frac{W}{L}$$

;P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k'_p}{2} \cdot \frac{W}{L}$$

;Small signal

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$