

EEEE273 ó Quiz 7
 SEMESTER 2, ACADEMIC YEAR 2014/2015
 Date: 29 January 2015 Time: 15 minutes

Question:

For the op-amp circuit in **Figure 1**, $R_1 = 50 \text{ k}\Omega$, $R_2 = 200 \text{ k}\Omega$, $R_3 = 25 \text{ k}\Omega$, and $R_4 = 50 \text{ k}\Omega$.

(a) **Find** the voltage gain, A_v , of the circuit. $A_v = v_o / v_I$ **[6 marks]**

(b) **Calculate** v_o when $v_I = 0.5 \text{ V}$. **[4 marks]**

Show clearly all calculations in order to get full marks.

Answer:

| | | | |
|-------|--|---|-----|
| (a) | | | |
| v_1 | $= v_2$ | $= (R_4 / (R_3 + R_4))(v_I)$ | [2] |
| | | $= (50\text{k} / 75\text{k})(v_I) = (2/3)(v_I)$ | [1] |
| v_o | $= (1 + R_2 / R_1)(v_1)$ | | [1] |
| | $= (1 + 200\text{k} / 50\text{k})(2/3)(v_I)$ | | [1] |
| | $= (10/3)(v_I)$ | | [1] |
| A_v | $= v_o / v_I$ | $= 10/3 = 3.333 \text{ V/V}$ | [1] |
| (b) | | | |
| v_o | $= A_v v_I$ | $= (10/3)(v_I)$ | [2] |
| | $= (10/3)(0.5)$ | $= 1.667 \text{ V}$ | [2] |

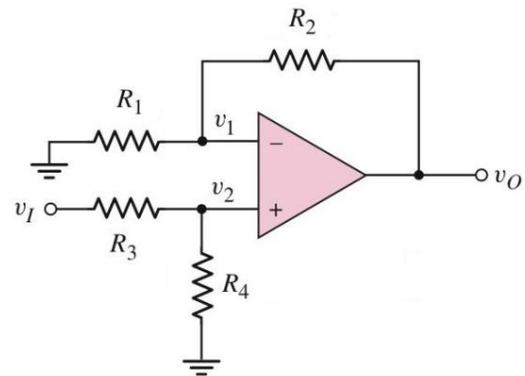


Figure 1

EEEE273 - Quiz 7
 SEMESTER 2, ACADEMIC YEAR 2014/2015
 Date: 29 January 2015 Time: 15 minutes

Question:

For the op-amp circuit in **Figure 1**, $R_1 = 50 \text{ k}\Omega$, $R_2 = 250 \text{ k}\Omega$, $R_3 = 25 \text{ k}\Omega$, and $R_4 = 25 \text{ k}\Omega$.

(a) Find the voltage gain, A_v , of the circuit. $A_v = v_o / v_I$ [6 marks]

(b) Calculate v_o when $v_I = 0.6 \text{ V}$. [4 marks]

Show clearly all calculations in order to get full marks.

Answer:

| | | | |
|-------|--|---|-----|
| (a) | | | |
| v_1 | $= v_2$ | $= (R_4 / (R_3 + R_4))(v_I)$ | [2] |
| | | $= (25\text{k}/50\text{k})(v_I) = (1/2)(v_I)$ | [1] |
| v_o | $= (1 + R_2 / R_1)(v_1)$ | | [1] |
| | $= (1 + 250\text{k}/50\text{k})(1/2)(v_I)$ | | [1] |
| | $= (3)(v_I)$ | | [1] |
| A_v | $= v_o / v_I$ | $= 3 \text{ V/V}$ | [1] |
| (b) | | | |
| v_o | $= A_v v_I$ | $= (3)(v_I)$ | [2] |
| | $= (3)(0.6)$ | $= 1.8 \text{ V}$ | [2] |

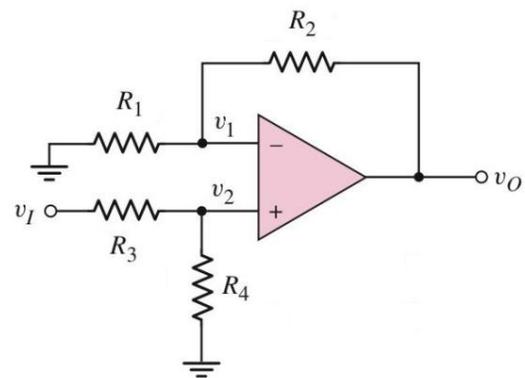


Figure 1

EEEE273 - Quiz 7
 SEMESTER 2, ACADEMIC YEAR 2014/2015
 Date: 29 January 2015 Time: 15 minutes

Question:

For the op-amp circuit in **Figure 1**, $R_1 = 50 \text{ k}\Omega$, $R_2 = 150 \text{ k}\Omega$, $R_3 = 50 \text{ k}\Omega$, and $R_4 = 25 \text{ k}\Omega$.

(a) Find the voltage gain, A_v , of the circuit. $A_v = v_o / v_I$ [6 marks]

(b) Calculate v_o when $v_I = 0.7 \text{ V}$. [4 marks]

Show clearly all calculations in order to get full marks.

Answer:

| | | | |
|-------|--|---|-----|
| (a) | | | |
| v_1 | $= v_2$ | $= (R_4 / (R_3 + R_4))(v_I)$ | [2] |
| | | $= (25\text{k}/75\text{k})(v_I) = (1/3)(v_I)$ | [1] |
| v_o | $= (1 + R_2 / R_1)(v_1)$ | | [1] |
| | $= (1 + 150\text{k}/50\text{k})(1/3)(v_I)$ | | [1] |
| | $= (4/3)(v_I)$ | | |
| A_v | $= v_o / v_I$ | $= 4/3 = 1.333 \text{ V/V}$ | [1] |
| (b) | | | |
| v_o | $= A_v v_I$ | $= (4/3)(v_I)$ | [2] |
| | $= (4/3)(0.7)$ | $= 0.933 \text{ V}$ | [2] |

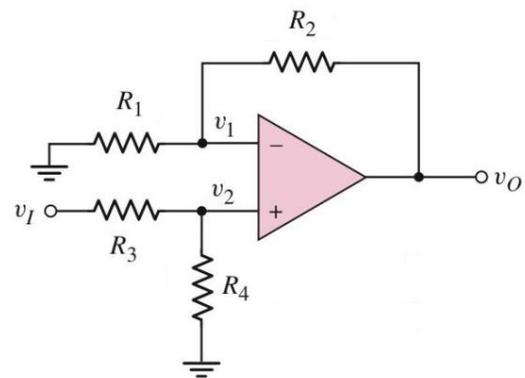


Figure 1

EEEE273 - Quiz 7
 SEMESTER 2, ACADEMIC YEAR 2014/2015
 Date: 29 January 2015 Time: 15 minutes

Question:

For the op-amp circuit in **Figure 1**, $R_1 = 25 \text{ k}\Omega$, $R_2 = 150 \text{ k}\Omega$, $R_3 = 25 \text{ k}\Omega$, and $R_4 = 50 \text{ k}\Omega$.

(a) Find the voltage gain, A_v , of the circuit. $A_v = v_o / v_I$ [6 marks]

(b) Calculate v_o when $v_I = 0.8 \text{ V}$. [4 marks]

Show clearly all calculations in order to get full marks.

Answer:

| | | | |
|-------|--|---|-----|
| (a) | | | |
| v_1 | $= v_2$ | $= (R_4 / (R_3 + R_4))(v_I)$ | [2] |
| | | $= (50\text{k} / 75\text{k})(v_I) = (2/3)(v_I)$ | [1] |
| v_o | $= (1 + R_2 / R_1)(v_1)$ | | [1] |
| | $= (1 + 150\text{k} / 25\text{k})(2/3)(v_I)$ | | [1] |
| | $= (14/3)(v_I)$ | | [1] |
| A_v | $= v_o / v_I$ | $= 4.667 \text{ V/V}$ | [1] |
| (b) | | | |
| v_o | $= A_v v_I$ | $= (4.667)(v_I)$ | [2] |
| | $= (4.667)(0.8) = 3.7336 \text{ V}$ | | [2] |

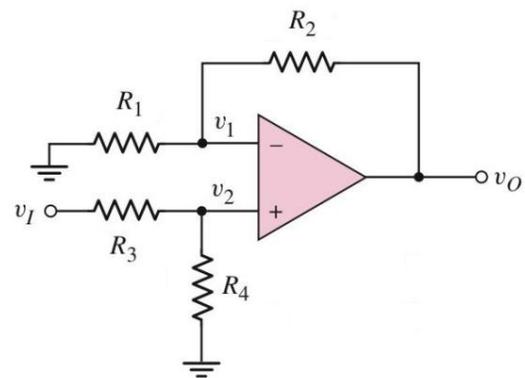


Figure 1