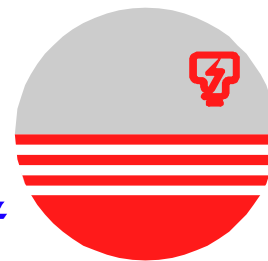


Name: **MODEL ANSWER**
 Student ID Number: **MODEL ANSWER**
 Section: **MODEL ANSWER**
 Lecturer: Dr Azni Wati/ Dr Jamaludin/
 Dr Jehana Ermy

**UNIVERSITI
 TENAGA
 NASIONAL**



College of Engineering
 Department of Electronics and Communication Engineering

Test 1

SEMESTER 2, ACADEMIC YEAR 2014/2015

Subject Code : **EEEB273**
 Course Title : **Electronics Analysis & Design II**
 Date : **6 December 2014**
 Time Allowed : **1½ hours**

Instructions to the candidates:

1. Write your Name, Student ID number, and Section number. Indicate your Lecturer.
2. Write all your answers **using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.**
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**
5. For all calculations, use $V_T = 26 \text{ mV}$ when necessary.

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.



GOOD LUCK!



Question No.	1	2	3	Total
Marks				

BASIC FORMULA

BJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

;Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

MOSFET

;N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{k'_n}{2} \cdot \frac{W}{L}$$

;P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{k'_p}{2} \cdot \frac{W}{L}$$

;Small signal

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

Question 1 [30 marks]

The circuit parameters of a **Widlar** current source shown in **Figure 1** are $V^+ = +5\text{ V}$, and $V^- = -5\text{ V}$. The transistor parameters are $\beta = 120$ and $V_A = 80\text{ V}$. The reference current is **10 times** the bias current and is established by a resistance R_1 . The forward-active operation for transistor Q_1 is $V_{BE1} = 0.7\text{ V}$ at 1 mA . Let the bias current $I_O = 50\text{ }\mu\text{A}$.

- (a) Determine V_{BE1} , V_{BE2} , and R_1 . [12 marks]
- (b) Neglect base currents and calculate the value for emitter resistance R_E . [5 marks]
- (c) Determine the **Widlar** current source output resistance, R_O . [8 marks]
- (d) Determine the percent change in I_O if V_{C2} changes by 5 V . [5 marks]

Answer for Question 1

(a)

$$V_{BE} = V_T \ln(I_C / I_S)$$

$$I_S = I_C / \{\exp(V_{BE} / V_T)\}$$

$$= (1\text{m}) / \{\exp(0.7 / 0.026)\}$$

$$= 2.03 \times 10^{-15}\text{ A}$$

[1]
[1]
[0.5]

$$I_O = 50\text{ }\mu\text{A}$$

$$I_{REF} = 10 \times I_O = 10 \times 50\text{ }\mu\text{A} = 0.5\text{ mA}$$

[2]

At $I_{REF} = 0.5\text{ mA}$,

$$V_{BE1} = V_T \ln(I_{REF} / I_S)$$

$$= (0.026) \ln(0.5\text{m} / 2.03 \times 10^{-15})$$

$$= 0.682\text{ V}$$

[1]
[1]
[0.5]

$$V_{BE2} = V_T \ln(I_O / I_S)$$

$$= (0.026) \ln(50\mu / 2.03 \times 10^{-15})$$

$$= 0.6221\text{ V}$$

[1]
[1]
[0.5]

$$I_{REF} = (V^+ - V_{BE1} - V^-) / R_1$$

$$R_1 = (V^+ - V_{BE1} - V^-) / I_{REF}$$

$$= (5 - 0.682 + 5) / (0.5\text{m})$$

$$= 18.636\text{ k}\Omega$$

[1]
[1]
[0.5]

(b)

$$I_O R_E = V_T \ln(I_{REF} / I_O)$$

$$R_E = (V_T / I_O) \ln(I_{REF} / I_O)$$

$$= (26\text{m} / 50\mu) \ln(0.5\text{m} / 50\mu)$$

$$= 1.198\text{ k}\Omega$$

[2]
[2]
[1]

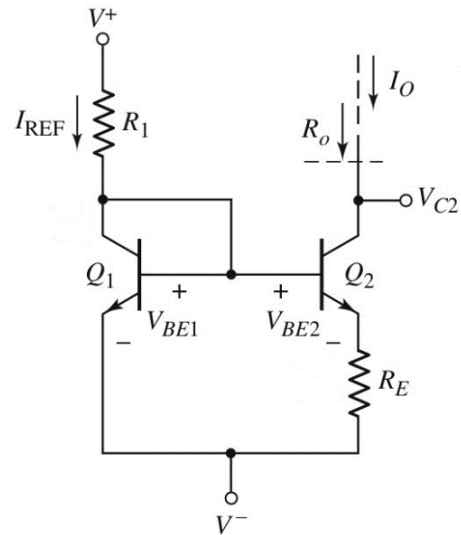


Figure 1

Answer for Question 1

(c)

$$r_{o2} = \frac{V_A}{I_O} = \frac{80}{50\mu} = 1.6 \text{ M}\Omega \quad [1.5]$$

$$g_{m2} = \frac{I_O}{V_T} = \frac{50\mu}{0.026} = 1.923 \text{ mA/V} \quad [1.5]$$

$$r_{\pi2} = \frac{\beta V_T}{I_O} = \frac{(120)(0.026)}{50\mu} = 62.4 \text{ k}\Omega \quad [1.5]$$

$$R'_E = R_E \parallel r_{\pi2} = 1.177 \text{ k}\Omega \quad [1]$$

$$R_O = r_{o2} [1 + g_{m2} (R_E \parallel r_{\pi2})] \quad [1]$$

$$R_O = (1.6\text{M}) [1 + (1.923\text{m})(1.198\text{k} \parallel 62.4\text{k})] = 5.221 \text{ M}\Omega \quad [1.5]$$

(d)

$$\Delta I_O = \frac{1}{R_O} \Delta V_{C2} = \frac{1}{(5.221\text{M})} (5) = 0.958 \text{ A} \quad [3]$$

$$\Delta I_O / I_O = 0.958 / 50 = 0.01916 \Rightarrow 1.916\% \quad [2]$$

Question 2 [30 marks]

The transistors in the circuit shown in **Figure 2** have parameters $V_{TN} = 0.4 \text{ V}$, $V_{TP} = -0.4 \text{ V}$, $k'_n = 80 \mu\text{A/V}^2$, $k'_p = 60 \mu\text{A/V}^2$, and $\lambda_n = \lambda_p = 0$. The transistor width-to-length ratios are $(W/L)_{1,2} = 15$, $(W/L)_3 = 10$, and $(W/L)_4 = 5$.

- (a) **Determine** the I_O , I_{REF} , and $V_{DS2}(\text{sat})$. [20 marks]
- (b) **Calculate** the values of V_{GS1} , V_{GS3} , and V_{SG4} . [10 marks]

Answer for Question 2

$V^+ = 5 \text{ V}$

Q2(b)

Using the equation $I_D = K'_n(V_{GS} - V_{TN})^2$; [1]

Equation for I_{REF} with respect to M_3 and M_4 :

$I_{REF} = \frac{k'_n}{2} \left(\frac{W}{L}\right)_3 (V_{GS3} - V_{TN})^2 = \frac{k'_n}{2} \left(\frac{W}{L}\right)_4 (V_{SG4} + V_{TP})^2$ [2]

$I_{REF} = \frac{80\mu}{2} (10)_3 (V_{GS3} - 0.4)^2 = \frac{60\mu}{2} (5)_4 (V_{SG4} - 0.4)^2$ [2]

Solving the equations in V_{GS3} and V_{SG4} terms:

$V_{SG4} = 1.63299V_{GS3} - 0.25319$... (1) [2]

Equation for I_{REF} with respect to M_3 and M_1 :

$I_{REF} = \frac{k'_n}{2} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TN})^2 = \frac{k'_n}{2} \left(\frac{W}{L}\right)_3 (V_{GS3} - V_{TN})^2$ [2]

$I_{REF} = \frac{80\mu}{2} (15)_1 (V_{GS1} - 0.4)^2 = \frac{80\mu}{2} (10)_3 (V_{GS3} - 0.4)^2$ [2]

$V_{GS3} = 1.22474V_{GS1} - 0.08989$... (2) [2]

Using nodal analysis for LHS:

$V^+ - V_{SG4} - V_{GS3} - V_{GS1} - V^- = 0$; [2]

So, $V_{SG4} + V_{GS3} + V_{GS1} = 10$... (3)

Substitute (1) into (3),

$V_{GS3} = 3.89412 - 0.37979V_{GS1}$... (4) [2]

Substitute (4) into (2);

$V_{GS1} = \underline{2.483 \text{ V}}$ [1]

$V_{GS3} = \underline{2.951 \text{ V}}$ [1]

$V_{SG4} = \underline{4.566 \text{ V}}$ [1]

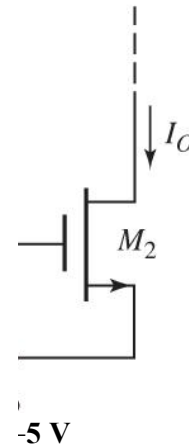


Figure 2

Answer for Question 2

Q2(a)

Based on the calculations above,

$$I_{REF} = \frac{k_n'}{2} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TN})^2 \quad [2]$$

$$I_{REF} = \frac{80\mu}{2} (15)(2.483 - 0.4)^2 \quad [2]$$

$$= \underline{2.603 \text{ mA}} \quad [1]$$

$$I_O = \underline{2.603 \text{ mA}} \quad [2]$$

and

$$V_{DS(sat)} = V_{GS2} - V_{TN} \quad [2]$$

$$= 2.483 - 0.4 = \underline{2.083 \text{ V}} \quad [1]$$

Question 3 [40 marks]

- (a) **Figure 3a** shows a circuit diagram for a BJT differential amplifier (**diff-amp**). Study the circuit diagram carefully. Transistor parameters are: $\beta = \infty$ (neglect base current), $V_A = \infty$, and $V_{BE(\text{on})} = 0.7 \text{ V}$. For the circuit also, voltages measured at v_{C1} and v_{C2} are **4.5 V**. Calculate the value of I_Q and v_{CE2} .

[10 marks]

Answer for Question 3(a)

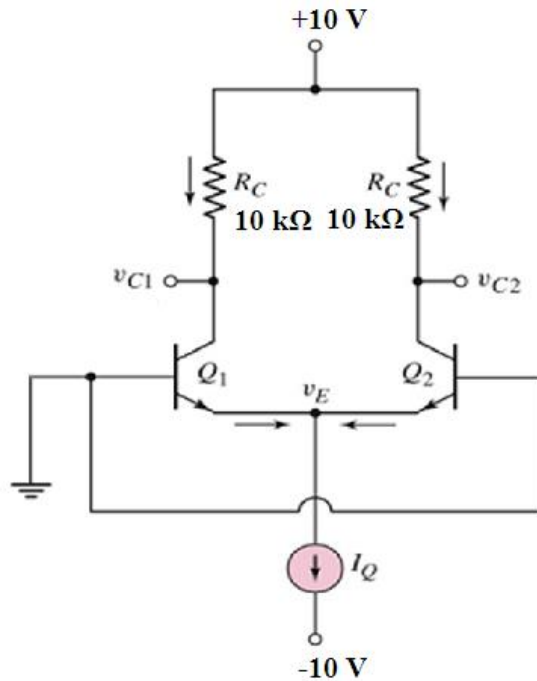


Figure 3a

Q3(a)

Given: $v_{C1} = v_{C2} = 4.5 \text{ V}$

$$10 - I_{C1} R_C = v_{C1} = 4.5 \text{ V} \quad [2]$$

$$\rightarrow I_{C1} = 0.55 \text{ mA} = I_{C2} \quad [1]$$

$$\rightarrow I_Q = I_{C1} + I_{C2} = 1.1 \text{ mA} \quad [2]$$

Given: $v_{C2} = 4.5 \text{ V}$

$$v_{CE2} = v_{C2} - v_E \quad [2]$$

$$v_E = v_{B2} - V_{BE(\text{on})} = 0 - 0.7 = -0.7 \text{ V} \quad [2]$$

$$\rightarrow v_{CE2} = v_{C2} - v_E = 4.5 - (-0.7) = 5.2 \text{ V} \quad [1]$$

(b) For a basic BJT differential amplifier shown in **Figure 3b**, the circuit parameter values are: $V^+ = +10\text{ V}$, $V^- = -10\text{ V}$, $I_Q = 1\text{ mA}$, and $R_C = 12\text{ k}\Omega$. The transistor parameters in the differential pair are $\beta = \infty$ (neglect base currents), $V_A = \infty$, and $V_{BE}(\text{on}) = 0.7\text{ V}$. The constant current source in the **Figure 3b** (that is providing the current I_Q) is implemented using a **cascode current source**.

(i) For all transistors in the **cascode current source**, $V_A = 120\text{ V}$ and $\beta = 100$. What is the value of the **output resistance (R_o)** looking into the constant current source?
[5 marks]

(ii) Calculate the differential-mode voltage gain (A_d) taken as **one-sided output voltage** at v_{C2} .
[5 marks]

(iii) Calculate the common-mode voltage gain (A_{cm}) using the following formula when all transistors in the **cascode current source** have $V_A = \infty$ (or that the **cascode current source is an ideal current source**):

$$A_{cm} = \frac{-\beta R_C}{r_\pi + 2(1 + \beta)R_o} \quad [5\text{ marks}]$$

(iv) It is given that the input voltages for the differential amplifier are $v_{B1} = 210 \times 10^{-6} \sin \omega t\text{ V}$ and $v_{B2} = 190 \times 10^{-6} \sin \omega t\text{ V}$. Calculate differential-mode input voltage (v_d), common-mode input voltage (v_{cm}), and the output voltage (v_o) of the differential amplifier using values of A_d and A_{cm} from (ii) and (iii) above.
[15 marks]

Answer for Question 3(b)

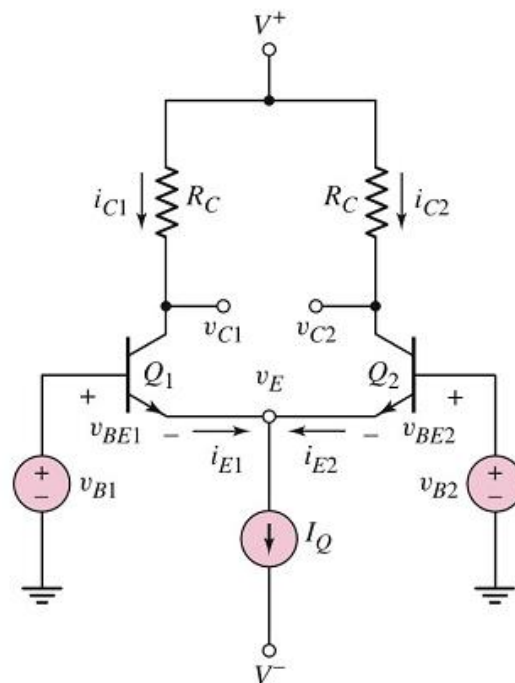


Figure 3b

Answer for Question 3 (Cont.)

Q3(b)

(i)

$\beta = 100, I_Q = 1 \text{ mA}$

For cascode current source

$$R_O = (\beta r_{OCasc}) \quad [2]$$

$$r_{OCasc} = V_A / I_Q \quad [1]$$

$$= (120)/(1\text{m}) = 120 \text{ k}\Omega \quad [1]$$

$$R_O = (\beta r_{OCasc}) = 100 \times 120\text{k} \\ = 12 \text{ M}\Omega \quad [1]$$

(ii)

$$A_d = g_{m2} R_C / 2 \quad [2]$$

$$g_{m2} = (I_Q / 2) / V_T \quad [1]$$

$$= 0.5 \text{ mA} / 26 \text{ mV} = 19.23 \text{ mA/V} \quad [1]$$

$$A_d = (19.23 \text{ m} \times 12\text{k}) / 2 \\ = 115.38 \text{ V/V} \quad [1]$$

(iii)

For cascode current source that has transistors with $V_A = \infty$,

$$R_O = (\beta V_A / I_Q) = (100 \times \infty) / (1\text{m}) = \infty \quad [2]$$

$$A_{cm} = \frac{-\beta R_C}{r_\pi + 2(1 + \beta)R_o} = \frac{-(\infty)(12\text{k})}{r_\pi + 2(1 + \infty)(\infty)} = 0$$

→ $A_{cm} = \{\text{use formula}\} = \text{Value} / \infty = 0 \quad [3]$

(iv)

$$v_d = v_{B1} - v_{B2} \quad [2]$$

$$= 210 \times 10^{-6} \sin \omega t - 190 \times 10^{-6} \sin \omega t \quad [2]$$

$$= 20 \times 10^{-6} \sin \omega t \text{ (V)} \quad [1]$$

$$v_{cm} = (v_{B1} + v_{B2}) / 2 \quad [2]$$

$$= (210 \times 10^{-6} \sin \omega t + 190 \times 10^{-6} \sin \omega t) / 2 \quad [2]$$

$$= 200 \times 10^{-6} \sin \omega t \text{ (V)} \quad [1]$$

$$v_o = A_d \times v_d + A_{cm} \times v_{cm} \quad [2]$$

$$= (115.38)(20 \times 10^{-6} \sin \omega t) + (0)(200 \times 10^{-6} \sin \omega t) \quad [2]$$

$$= 2307.6 \times 10^{-6} \sin \omega t \text{ V} \quad [1]$$

