

Name:

Student ID Number:

Section:

Lecturer: Dr. Jamaludin Bin Omar

EEEE273 - Quiz 4 ☺☺☺
SEMESTER 1, ACADEMIC YEAR 2015/2016
Date: 30 July 2015

Take home quiz. Deadline of submission: 3 August 2015, 5 pm.

You may refer to notes and textbook.

WRITE your answer on clean papers, computer printed answer will not be accepted.

Question:

Consider a simple BJT operational amplifier in **Figure 1**. The circuit parameters are $I_{C7} = I_Q = 0.25$ mA, $I_{C8} = 1$ mA, $R_4 = 10$ k Ω , and $R_3 = 0.2$ k Ω . Assume $\beta = 120$ for all transistors and the **Early voltage** for Q_7 and Q_{11} is 100 V.

- (a) Find the values of I_1 and R_1 if $V^+ = 10$ V, $V^- = -10$ V, and $V_{BE} = V_{EB} = 0.7$ V for all transistors **EXCEPT** Q_7 and Q_{11} . [2 marks]
- (b) Determine the **overall gain** (A_v) of the multistage amplifier in the **Figure 1**. Assume that voltage gain for the input stage (differential amplifier with active load) is A_{v1} , voltage gain for the gain stage (Darlington pair) is A_{v2} , and voltage gain for the output stage (Emitter follower) is $A_{v3} = 1$. [6 marks]
- (c) Calculate the output resistance (R_o) of the multistage amplifier in the **Figure 1**. [2 marks]

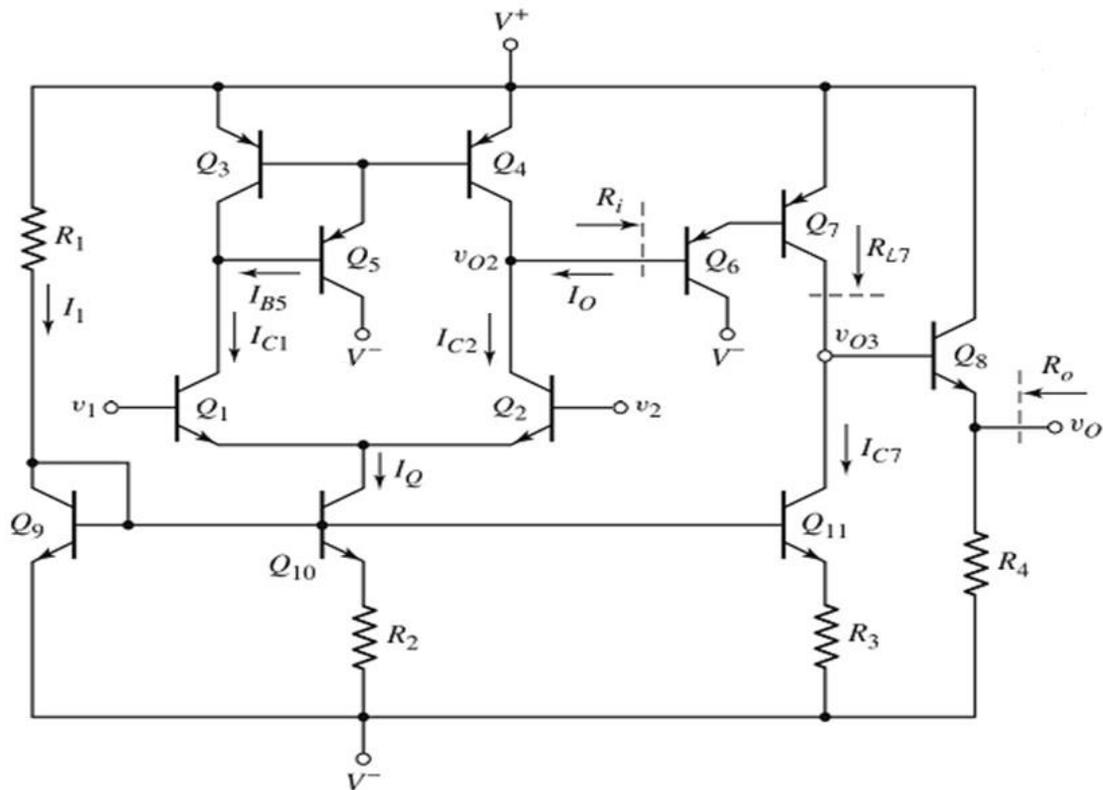


Figure 1

Name:

Student ID Number:

Section:

Lecturer: Dr. Jamaludin Bin Omar

EEEE273 - Quiz 4 ☺☺ ☺
SEMESTER 1, ACADEMIC YEAR 2015/2016
Date: 30 July 2015

Take home quiz. Deadline of submission: 3 August 2015, 5 pm.

You may refer to notes and textbook.

WRITE your answer on clean papers, computer printed answer will not be accepted.

Question:

Consider a simple BJT operational amplifier in **Figure 1**. The circuit parameters are $I_{C7} = I_Q = 0.25$ mA, $I_{C8} = 1$ mA, $R_4 = 10$ k Ω , and $R_3 = 0.2$ k Ω . Assume $\beta = 120$ for all transistors and the **Early voltage** for Q_7 and Q_{11} is 120 V.

- (d) Find the values of I_1 and R_1 if $V^+ = 12$ V, $V^- = -12$ V, and $V_{BE} = V_{EB} = 0.7$ V for all transistors **EXCEPT** Q_7 and Q_{11} . [2 marks]
- (e) Determine the **overall gain** (A_v) of the multistage amplifier in the **Figure 1**. Assume that voltage gain for the input stage (differential amplifier with active load) is A_{v1} , voltage gain for the gain stage (Darlington pair) is A_{v2} , and voltage gain for the output stage (Emitter follower) is $A_{v3} = 1$. [6 marks]
- (f) Calculate the output resistance (R_o) of the multistage amplifier in the **Figure 1**. [2 marks]

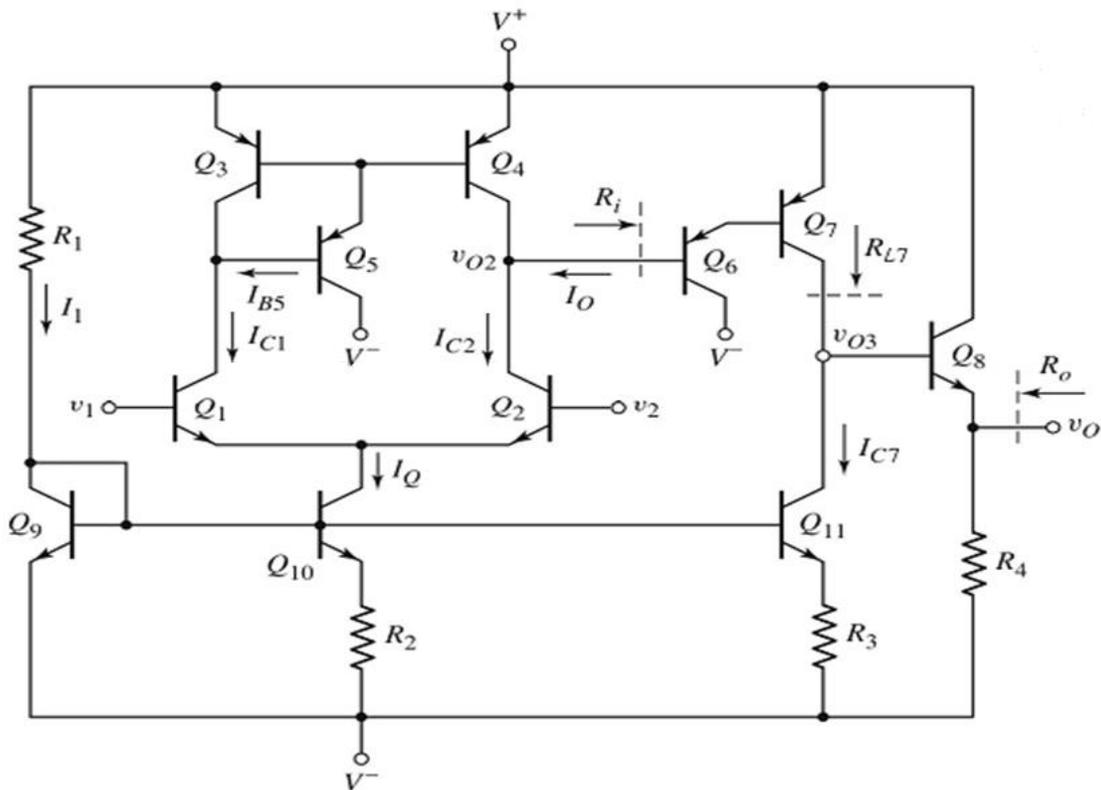


Figure 1

Name:

Student ID Number:

Section:

Lecturer: Dr. Jamaludin Bin Omar

EEEE273 - Quiz 4 ☺☺
SEMESTER 1, ACADEMIC YEAR 2015/2016
Date: 30 July 2015

Take home quiz. Deadline of submission: 3 August 2015, 5 pm.

You may refer to notes and textbook.

WRITE your answer on clean papers, computer printed answer will not be accepted.

Question:

Consider a simple BJT operational amplifier in **Figure 1**. The circuit parameters are $I_{C7} = I_Q = 0.25$ mA, $I_{C8} = 1.2$ mA, $R_4 = 10$ k Ω , and $R_3 = 0.2$ k Ω . Assume $\beta = 120$ for all transistors and the **Early voltage** for Q_7 and Q_{11} is 110 V.

- (g) Find the values of I_1 and R_1 if $V^+ = 12$ V, $V^- = -12$ V, and $V_{BE} = V_{EB} = 0.7$ V for all transistors **EXCEPT** Q_7 and Q_{11} . [2 marks]
- (h) Determine the **overall gain** (A_v) of the multistage amplifier in the **Figure 1**. Assume that voltage gain for the input stage (differential amplifier with active load) is A_{v1} , voltage gain for the gain stage (Darlington pair) is A_{v2} , and voltage gain for the output stage (Emitter follower) is $A_{v3} = 1$. [6 marks]
- (i) Calculate the output resistance (R_o) of the multistage amplifier in the **Figure 1**. [2 marks]

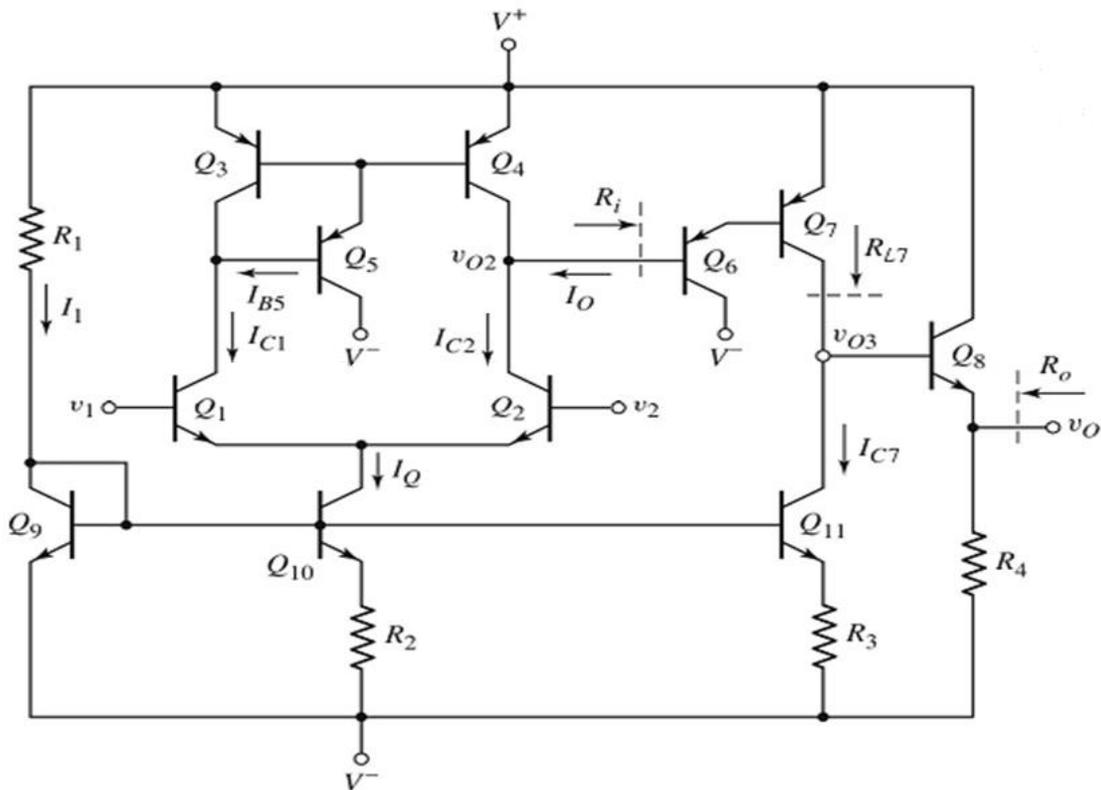


Figure 1

Name:

Student ID Number:

Section:

Lecturer: Dr. Jamaludin Bin Omar

EEEE273 - Quiz 4 ☺ ☺☺
SEMESTER 1, ACADEMIC YEAR 2015/2016
Date: 30 July 2015

Take home quiz. Deadline of submission: 3 August 2015, 5 pm.

You may refer to notes and textbook.

WRITE your answer on clean papers, computer printed answer will not be accepted.

Question:

Consider a simple BJT operational amplifier in **Figure 1**. The circuit parameters are $I_{C7} = I_Q = 0.2$ mA, $I_{C8} = 1.2$ mA, $R_4 = 10$ k Ω , and $R_3 = 0.2$ k Ω . Assume $\beta = 120$ for all transistors and the **Early voltage** for Q_7 and Q_{11} is 110 V.

- (j) Find the values of I_1 and R_1 if $V^+ = 8$ V, $V^- = -8$ V, and $V_{BE} = V_{EB} = 0.7$ V for all transistors EXCEPT Q_7 and Q_{11} . [2 marks]
- (k) Determine the overall gain (A_v) of the multistage amplifier in the **Figure 1**. Assume that voltage gain for the input stage (differential amplifier with active load) is A_{v1} , voltage gain for the gain stage (Darlington pair) is A_{v2} , and voltage gain for the output stage (Emitter follower) is $A_{v3} = 1$. [6 marks]
- (l) Calculate the output resistance (R_o) of the multistage amplifier in the **Figure 1**. [2 marks]

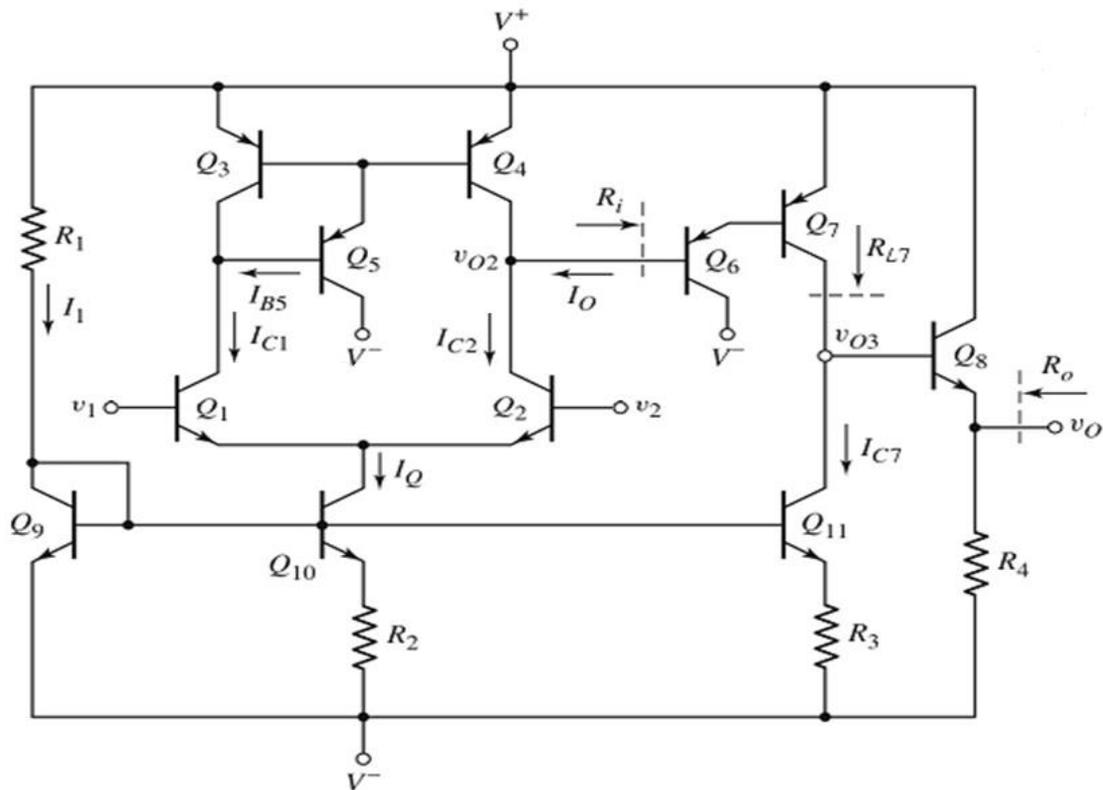


Figure 1

