

EEEE273 ó Quiz 7
 SEMESTER 1, ACADEMIC YEAR 2015/2016
 Date: 7 September 2015 Time: 15 minutes

Question:

For the op-amp circuit in **Figure 1**, $R_1 = 50 \text{ k}\Omega$, $R_2 = 200 \text{ k}\Omega$, $R_3 = 25 \text{ k}\Omega$, and $R_4 = 50 \text{ k}\Omega$.

(a) **Find** the voltage gain, A_v , of the circuit. $A_v = v_o / v_I$ **[6 marks]**

(b) **Calculate** v_o when $v_I = 0.5 \text{ V}$. **[4 marks]**

Show clearly all calculations in order to get full marks.

Answer:

(a)			
	v_1	$= v_2 = (R_4 / (R_3 + R_4))(v_I)$	[2]
		$= (50\text{k} / 75\text{k})(v_I) = (2/3)(v_I)$	[1]
	v_o	$= (1 + R_2 / R_1)(v_1)$	[1]
		$= (1 + 200\text{k} / 50\text{k})(2/3)(v_I)$	[1]
		$= (10/3)(v_I)$	[1]
	A_v	$= v_o / v_I = 10/3 = 3.333 \text{ V/V}$	[1]
(b)			
	v_o	$= A_v v_I = (10/3)(v_I)$	[2]
		$= (10/3)(0.5) = 1.667 \text{ V}$	[2]

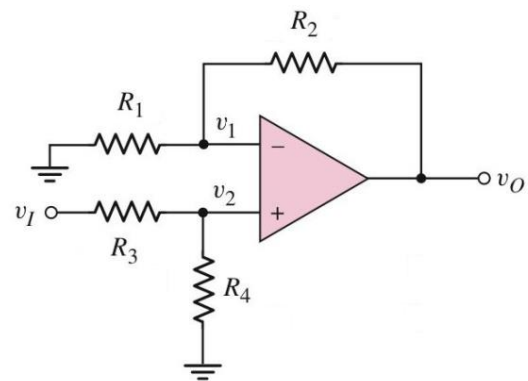


Figure 1

EEEE273 - Quiz 7
 SEMESTER 1, ACADEMIC YEAR 2015/2016
 Date: 7 September 2015 Time: 15 minutes

Question:

For the op-amp circuit in **Figure 1**, $R_1 = 50 \text{ k}\Omega$, $R_2 = 250 \text{ k}\Omega$, $R_3 = 25 \text{ k}\Omega$, and $R_4 = 25 \text{ k}\Omega$.

(a) **Find** the voltage gain, A_v , of the circuit. $A_v = v_o / v_I$ **[6 marks]**

(b) **Calculate** v_o when $v_I = 0.6 \text{ V}$. **[4 marks]**

Show clearly all calculations in order to get full marks.

Answer:

(a)	v_1	$= v_2$	$= (R_4 / (R_3 + R_4))(v_I)$	[2]
			$= (25\text{k}/50\text{k})(v_I) = (1/2)(v_I)$	[1]
	v_o	$= (1 + R_2 / R_1)(v_1)$		[1]
		$= (1 + 250\text{k}/50\text{k})(1/2)(v_I)$		[1]
		$= (3)(v_I)$		[1]
	A_v	$= v_o / v_I$	$= 3 \text{ V/V}$	[1]
(b)	v_o	$= A_v v_I$	$= (3)(v_I)$	[2]
		$= (3)(0.6)$	$= 1.8 \text{ V}$	[2]

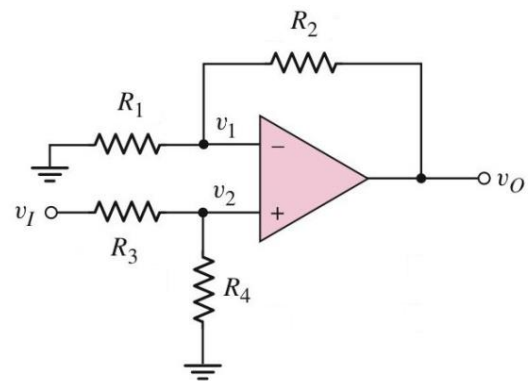


Figure 1

EEEE273 - Quiz 7 ..
 SEMESTER 1, ACADEMIC YEAR 2015/2016
 Date: 7 September 2015 Time: 15 minutes

Question:

For the op-amp circuit in **Figure 1**, $R_1 = 50 \text{ k}\Omega$, $R_2 = 150 \text{ k}\Omega$, $R_3 = 50 \text{ k}\Omega$, and $R_4 = 25 \text{ k}\Omega$.

(a) **Find** the voltage gain, A_v , of the circuit. $A_v = v_o / v_I$ **[6 marks]**

(b) **Calculate** v_o when $v_I = 0.7 \text{ V}$. **[4 marks]**

Show clearly all calculations in order to get full marks.

Answer:

(a)	$v_1 = v_2 = (R_4 / (R_3 + R_4))(v_I)$	[2]
	$= (25\text{k}/75\text{k})(v_I) = (1/3)(v_I)$	[1]
v_o	$= (1 + R_2 / R_1)(v_1)$	[1]
	$= (1 + 150\text{k}/50\text{k})(1/3)(v_I)$	[1]
	$= (4/3)(v_I)$	[1]
A_v	$= v_o / v_I = 4/3 = 1.333 \text{ V/V}$	[1]
(b)	$v_o = A_v v_I = (4/3)(v_I)$	[2]
	$= (4/3)(0.7) = 0.933 \text{ V}$	[2]

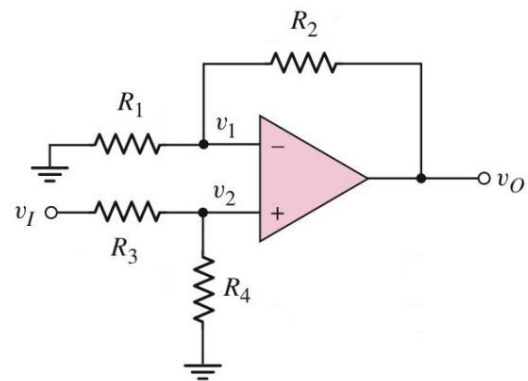


Figure 1

EEEE273 - Quiz 7
 SEMESTER 1, ACADEMIC YEAR 2015/2016
 Date: 7 September 2015 Time: 15 minutes

Question:

For the op-amp circuit in **Figure 1**, $R_1 = 25 \text{ k}\Omega$, $R_2 = 150 \text{ k}\Omega$, $R_3 = 25 \text{ k}\Omega$, and $R_4 = 50 \text{ k}\Omega$.

(a) **Find** the voltage gain, A_v , of the circuit. $A_v = v_o / v_I$ **[6 marks]**

(b) **Calculate** v_o when $v_I = 0.8 \text{ V}$. **[4 marks]**

Show clearly all calculations in order to get full marks.

Answer:

(a)	$v_1 = v_2$	$= (R_4 / (R_3 + R_4))(v_I)$	[2]
		$= (50\text{k}/75\text{k})(v_I) = (2/3)(v_I)$	[1]
	$v_o = (1 + R_2 / R_1)(v_1)$		[1]
	$= (1 + 150\text{k}/25\text{k})(2/3)(v_I)$		[1]
	$= (14/3)(v_I)$		[1]
	$A_v = v_o / v_I$	$= 4.667 \text{ V/V}$	[1]
(b)	$v_o = A_v v_I$	$= (4.667)(v_I)$	[2]
	$= (4.667)(0.8) = 3.7336 \text{ V}$		[2]

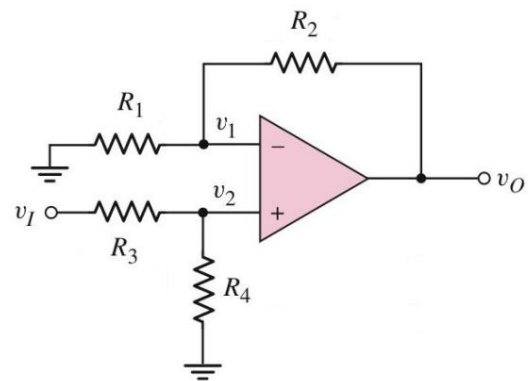


Figure 1