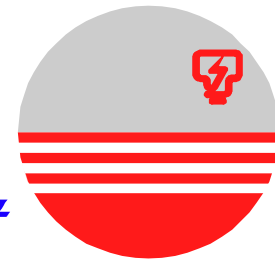


Name:
 Student ID Number:
 Section:
 Lecturer: Dr Azni Wati/ Dr Fazrena Azlee/
 Dr Jehana Ermy/ Dr Jamaludin
 Table Number:

**UNIVERSITI
 TENAGA
 NASIONAL**



College of Engineering
 Department of Electronics and Communication Engineering

Test 1 – MODEL ANSWERS

SEMESTER 1, ACADEMIC YEAR 2015/2016

Subject Code : **EEEE273**
 Course Title : **Electronics Analysis & Design II**
 Date : **5 July 2015**
 Time Allowed : **1½ hours**

Instructions to the candidates:

1. Write your Name and Student ID number. Circle Lecturer for your section.
2. Write all your answers using pen. **DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.**
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.

☺ **GOOD LUCK!** ☺

| Question Number | Q1 | Q2 | Q3 | Total |
|-----------------|-----------|-----------|-----------|------------|
| Marks | 40 | 30 | 30 | 100 |

BASIC FORMULA FOR TRANSISTOR

BJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

;Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

MOSFET

;N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{k'_n}{2} \cdot \frac{W}{L}$$

;P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{k'_p}{2} \cdot \frac{W}{L}$$

;Small signal

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

Question 1 [40 marks]

For all **BJT current sources** in **this question**, all transistors are matched and have same parameters. The transistor parameters are: $\beta = 50$, $V_{BE(on)} = 0.6 \text{ V}$, and $V_A = 150 \text{ V}$. The circuit parameters for the current sources are: $V^+ = 10 \text{ V}$, $V^- = -10 \text{ V}$, and $R_1 = 24 \text{ k}\Omega$.

- (a) Calculate reference current (I_{REF}), output current (I_O), and output resistance (R_O) for **Three-transistor** current source, **Wilson** current source, and **Cascode** current source. **Show all calculations clearly and do not forget to put proper Units for I_{REF} , I_O , and R_O .**

[36 marks]

- (b) Based on I_O and I_{REF} relationships and R_O , **which current source** has the most stable I_O , **which current source** has the medium stable I_O , and **which current source** has the least stable I_O from the three current sources given in **part (a)**? **Explain** why you had said that.

[4 marks]

Answer for Question 1

Question 1(a) [36 marks]

| Three-transistor current source | Wilson current source | Cascode current source |
|--|--|--|
| $I_{REF} = (V^+ - 2 V_{BE} - V^-)/R_1$ $= (10 - 2 \times 0.6 - (-10))/(24\text{k})$ $= 0.783 \text{ mA}$ | $I_{REF} = (V^+ - 2 V_{BE} - V^-)/R_1$ $= (10 - 2 \times 0.6 - (-10))/(24\text{k})$ $= 0.783 \text{ mA}$ | $I_{REF} = (V^+ - 2 V_{BE} - V^-)/R_1$ $= (10 - 2 \times 0.6 - (-10))/(24\text{k})$ $= 0.783 \text{ mA}$ |
| $I_O = I_{REF}/(1 + 2/(\beta(1+\beta)))$ $= (0.783\text{m})/(1+2/(50 \times 51))$ $= 0.783 \text{ mA}$ | $I_O = I_{REF}/(1 + 2/(\beta(2+\beta)))$ $= (0.783\text{m})/(1+2/(50 \times 52))$ $= 0.783 \text{ mA}$ | $I_O = I_{REF}/(1 + 4/\beta)$ $= (0.783\text{m})/(1+4/(50))$ $= 0.725 \text{ mA}$ |
| $r_{O2} = V_A / I_O$ $= 150/(0.783\text{m})$ $= 191.57 \text{ k}\Omega$ | $r_{O3} = V_A / I_O$ $= 150/(0.783\text{m})$ $= 191.57 \text{ k}\Omega$ | $r_{O4} = V_A / I_O$ $= 150/(0.725\text{m})$ $= 206.89 \text{ k}\Omega$ |
| $R_O = r_{O2}$ $= 191.57 \text{ k}\Omega$ | $R_O = (\beta r_{O3})/2$ $= (50 \times 191.57\text{k})/2$ $= 4.789 \text{ M}\Omega$ | $R_O = \beta r_{O4}$ $= 50 \times 206.89\text{k}$ $= 10.3445 \text{ M}\Omega$ |

[4 marks each box, Total 36 marks]

Question 1(b) [4 marks]

Most stable: Wilson, medium: Cascode, least: 3-transistor.

I_O for Wilson is approximately equal to I_{ref} although R_O is the middle.

Although I_O for Cascode is less than I_{ref} , its R_O is highest.

3-transistor has smallest R_O although its I_O is similar to Wilson.


Any explanation that makes sense may be accepted!

[4 marks]

Question 2 [30 marks]

The circuit shown in **Figure 2** is a PMOS version of a two-transistor current source. Assume that the transistor parameters are $V_{TP} = -0.4 \text{ V}$, $k'_p = 80 \mu\text{A}/\text{V}^2$, and $\lambda = 0$. The transistor width-to-length ratios are $(W/L)_1 = 30$, $(W/L)_2 = 15$, and $(W/L)_3 = 10$.

- (a) Determine I_O , I_{REF} , V_{SG1} , and V_{SG3} [18 marks]
- (b) Calculate the maximum value of V_{D2} such that M_2 remains biased in the saturation region. [6 marks]
- (c) Find the largest value of R such that M_2 remains biased in the saturation region. [6 marks]

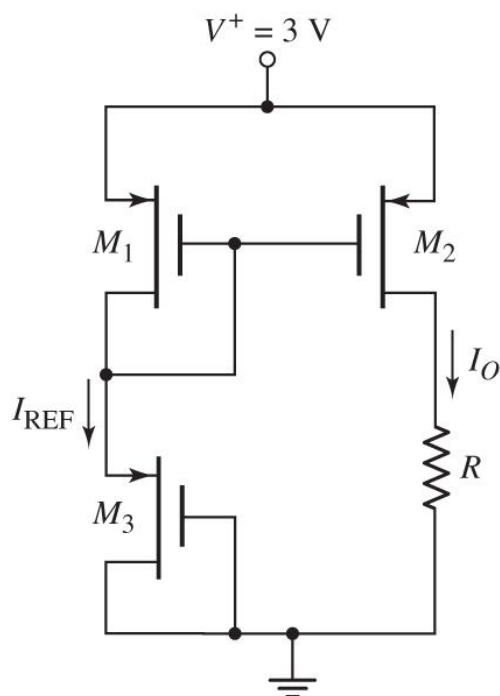Answer for Question 2**Figure 2**

Answer for Question 2

Question 2(a) [18 marks]

$I_{D1} = I_{D3} = I_{REF}$ [2 marks]

$I_{D1} = (1/2) k_{\phi} (W/L)_1 (V_{SG1} + V_{TP})^2 = (1/2)(80\mu)(30)(V_{SG1} - 0.4)^2$ eqn 1 [2 marks]

$I_{D3} = (1/2) k_{\phi} (W/L)_3 (V_{SG3} + V_{TP})^2 = (1/2)(80\mu)(10)(V_{SG3} - 0.4)^2$ eqn 2 [2 marks]

$V^+ - V_{SG1} - V_{SG3} = 0$, so $V_{SG3} = V^+ - V_{SG1}$.. eqn 3 [2 marks]

Solve simultaneous equations: $I_{D1} = I_{D3} = I_{REF}$

$(1/2)(80\mu)(30)(V_{SG1} - 0.4)^2 = (1/2)(80\mu)(10)(V_{SG3} - 0.4)^2$, replace V_{SG3} into eqn 2

~~$(1/2)(80\mu)(30)(V_{SG1} - 0.4)^2 = (1/2)(80\mu)(10)(3 - V_{SG1} - 0.4)^2$~~
 $(30)(V_{SG1} - 0.4)^2 = (10)(2.6 - V_{SG1})^2$ [2 marks]

$V_{SG1} = -2.605V$ or $1.205V$, choose $V_{SG1} = 1.205V$ since $V_{SG} > |V_{TP}|$ [2 marks]

$I_{REF} = I_{D1} = (1/2) k_{\phi} (W/L)_1 (V_{SG1} + V_{TP})^2 = (1/2)(80\mu)(30)(1.205 - 0.4)^2 = 0.78mA$ [2 marks]

$I_O = I_{D2} = (1/2) k_{\phi} (W/L)_2 (V_{SG2} + V_{TP})^2 = (1/2)(80\mu)(15)(1.205 - 0.4)^2 = 0.39mA$,
or, $I_O = (W/L)_2 / (W/L)_1 \times I_{REF} = 15/30 \times 0.78mA = 0.39mA$ [2 marks]

$V_{SG3} = 3 - V_{SG1} = 3 - 1.205 = 1.795V$ [2 marks]

Question 2(b) [6 marks]

$V_{D2} = V^+ - V_{SD2}$ [1 mark]

$V_{D2(max)} = V^+ - V_{SD2(min)} = V^+ - V_{SD2(sat)}$ [2 marks]

$V_{SD2(sat)} = V_{SG2} + V_{TP} = 1.205 + (-0.4) = 0.805V$ [2 marks]

So $V_{D2(max)} = 3 - 0.805 = 2.195V$ [1 marks]

Question 2(c) [6 marks]

$V_R = V_{D2} = V^+ - V_{SD2} = I_O \times R$ [2 marks]

$V_R(max) = V_{D2(max)} = 2.195 = I_O \times R$ [2 marks]

$R = 2.195 / I_O = 2.195 / 0.39mA = 5.63k\Omega$ [2 marks]

Question 3 [30 marks]

Figure 3 shows a circuit diagram for a **BJT** differential amplifier (diff-amp). The circuit parameter values are: $V^+ = +10\text{ V}$, $V^- = -10\text{ V}$, and $R_C = 10\text{ k}\Omega$. The transistor parameters are: $\beta = \infty$ (neglect base current), $V_A = \infty$, and $V_{BE(\text{on})} = 0.7\text{ V}$.

- (a) Assume that Q_1 and Q_2 are **matched pair** and operating at the same temperature.

By defining
$$v_d = v_{B1} - v_{B2}$$

Show that
$$i_{C1} = \frac{I_Q}{1 + e^{-v_d/V_T}} \quad \text{and} \quad i_{C2} = \frac{I_Q}{1 + e^{+v_d/V_T}}$$
 [10 marks]

- (b) The circuit has voltages measured at $v_{C1} = v_{C2} = 4.0\text{ V}$, for $v_{B1} = v_{B2} = 0\text{ V}$. **Find I_Q .** [6 marks]

- (c) If $v_{B1} = 1.2\text{ mV}$ and $v_{B2} = -2.0\text{ mV}$

- (i) **Calculate v_d and v_{cm} .** [4 marks]

- (ii) **Calculate i_{C1} and i_{C2} .** [5 marks]

- (iii) **Find v_o if the diff-amp gain $A_d = 40$ and $A_{cm} = -0.05$.** [5 marks]

Answer for Question 3

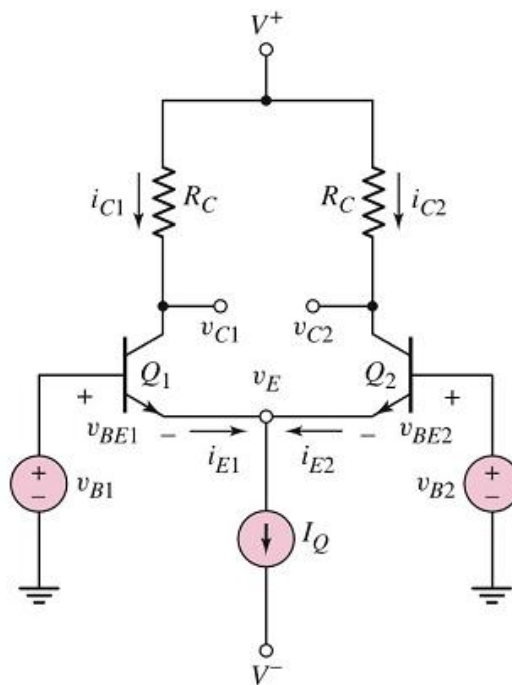


Figure 3

Answer for Question 3(a)

$$i_{C1} = I_S e^{v_{BE1}/V_T} \quad [1]$$

$$i_{C2} = I_S e^{v_{BE2}/V_T} \quad [1]$$

$$I_Q = i_{C1} + i_{C2} = I_S [e^{v_{BE1}/V_T} + e^{v_{BE2}/V_T}] \quad [3]$$

$$v_{BE2} - v_{BE1} = (v_{B2} - v_E) - (v_{B1} - v_E) = v_{B2} - v_{B1} = -v_d \quad [1]$$

$$\frac{i_{C1}}{I_Q} = \frac{1}{1 + e^{(v_{BE2} - v_{BE1})/V_T}} = \frac{1}{1 + e^{-v_d/V_T}} \quad [2]$$

$$\frac{i_{C2}}{I_Q} = \frac{1}{1 + e^{-(v_{BE2} - v_{BE1})/V_T}} = \frac{1}{1 + e^{+v_d/V_T}} \quad [2]$$

Answer for Question 3(b)

$$v_{C1} = V^+ \text{ ó } i_{C1} R_C \quad [1]$$

$$4.0 \text{ V} = 10 \text{ ó } (i_{C1})(10\text{k}) \quad [1]$$

$$i_{C1} = 0.6 \text{ mA} \quad [1]$$

$$\beta = \hat{O}$$

$$i_{C1} = i_{E1} = I_Q / 2 \quad [1]$$

$$I_Q = 2xi_{C1} = 2x0.6 \text{ mA} \quad [1]$$

$$= 1.2 \text{ mA} \quad [1]$$

Answer for Question 3(c)

$$v_{B1} = 1.2 \text{ mV and } v_{B2} = -2.0 \text{ mV}$$

$$\begin{aligned} \text{(i) } v_d &= v_{B1} - v_{B2} \\ &= 1.2\text{m ó } (-2\text{m}) = 3.2 \text{ mV} \end{aligned} \quad [2]$$

$$\begin{aligned} v_{cm} &= (v_{B1} + v_{B2}) / 2 \\ &= (1.2\text{m} + (-2\text{m})) / 2 = -0.4 \text{ mV} \end{aligned} \quad [2]$$

$$\begin{aligned} \text{(ii) } i_{C1} &= I_Q / [1 + \exp(-v_d/V_T)] \\ &= 1.2\text{m} / [1 + \exp(-3.2\text{m}/0.026)] \\ &= 0.6369 \text{ mA} \end{aligned} \quad [2.5]$$

$$\begin{aligned} i_{C2} &= I_Q / [1 + \exp(+v_d/V_T)] \\ &= 1.2\text{m} / [1 + \exp(+3.2\text{m}/0.026)] \\ &= 0.5631 \text{ mA} \end{aligned} \quad [2.5]$$

$$\text{(iii) } v_o = A_d \times v_d + A_{cm} \times v_{cm} \quad [2]$$

$$= (40)(3.2\text{m}) + (-0.05)(-0.4\text{m}) \quad [2]$$

$$= 128.02 \text{ mV} \quad [1]$$