

Name:

Student ID Number:

Section:

Lecturer: Dr. Jamaludin Bin Omar

EEEE273 - Quiz 5

SEMESTER 2, ACADEMIC YEAR 2015/2016

Date: 31 December 2015

**Take home quiz.** Deadline of submission: 4 January 2016, 5 pm.


You may refer to notes and textbook.

**WRITE** your answer on clean papers, computer printed answer will not be accepted.

**Question:**

Consider a simple BJT operational amplifier in **Figure 1**. The circuit parameters are  $I_{C7} = I_Q = 0.25$  mA,  $I_{C8} = 1.2$  mA,  $R_4 = 12$  k $\Omega$ , and  $R_3 = 0.2$  k $\Omega$ . Assume  $\beta = 120$  for all transistors and the **Early voltage** for  $Q_7$  and  $Q_{11}$  is 110 V.

- (a) Find the values of  $I_1$  and  $R_1$  if  $V^+ = 10$  V,  $V^- = -10$  V, and  $V_{BE} = V_{EB} = 0.7$  V for all transistors **EXCEPT**  $Q_7$  and  $Q_{11}$ . [2 marks]
- (b) Determine the overall gain ( $A_v$ ) of the multistage amplifier in the **Figure 1**. Assume that voltage gain for the input stage (differential amplifier with active load) is  $A_{v1}$ , voltage gain for the gain stage (Darlington pair) is  $A_{v2}$ , and voltage gain for the output stage (Emitter follower) is  $A_{v3} = 1$ . [6 marks]
- (c) Calculate the output resistance ( $R_o$ ) of the multistage amplifier in the **Figure 1**. [2 marks]

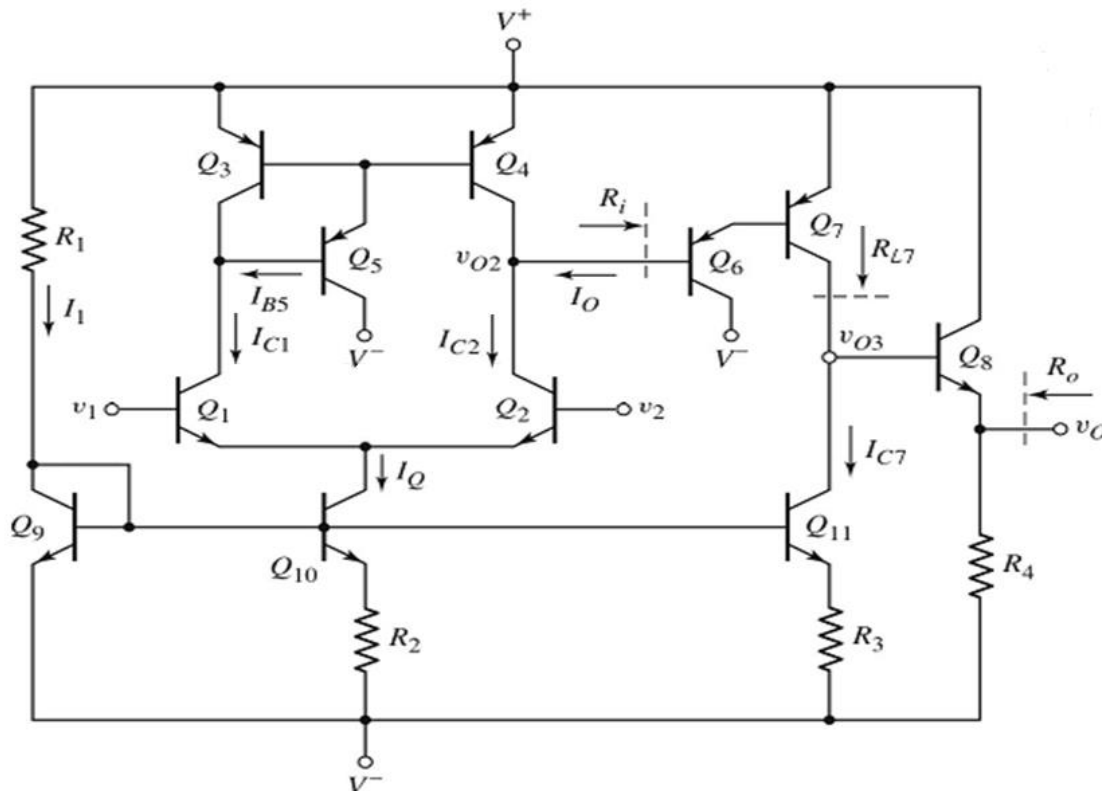

**Figure 1**

Name:

Student ID Number:

Section:

Lecturer: Dr. Jamaludin Bin Omar

EEEE273 - Quiz 5

SEMESTER 2, ACADEMIC YEAR 2015/2016

Date: 31 December 2015

**Take home quiz.** Deadline of submission: 4 January 2016, 5 pm.


You may refer to notes and textbook.

**WRITE** your answer on clean papers, computer printed answer will not be accepted.

**Question:**

Consider a simple BJT operational amplifier in **Figure 1**. The circuit parameters are  $I_{C7} = I_Q = 0.25$  mA,  $I_{C8} = 1.2$  mA,  $R_4 = 12$  k $\Omega$ , and  $R_3 = 0.2$  k $\Omega$ . Assume  $\beta = 120$  for all transistors and the **Early voltage** for  $Q_7$  and  $Q_{11}$  is 110 V.

- (d) Find the values of  $I_1$  and  $R_1$  if  $V^+ = 11$  V,  $V^- = -11$  V, and  $V_{BE} = V_{EB} = 0.7$  V for all transistors **EXCEPT**  $Q_7$  and  $Q_{11}$ . [2 marks]
- (e) Determine the overall gain ( $A_v$ ) of the multistage amplifier in the **Figure 1**. Assume that voltage gain for the input stage (differential amplifier with active load) is  $A_{v1}$ , voltage gain for the gain stage (Darlington pair) is  $A_{v2}$ , and voltage gain for the output stage (Emitter follower) is  $A_{v3} = 1$ . [6 marks]
- (f) Calculate the output resistance ( $R_o$ ) of the multistage amplifier in the **Figure 1**. [2 marks]

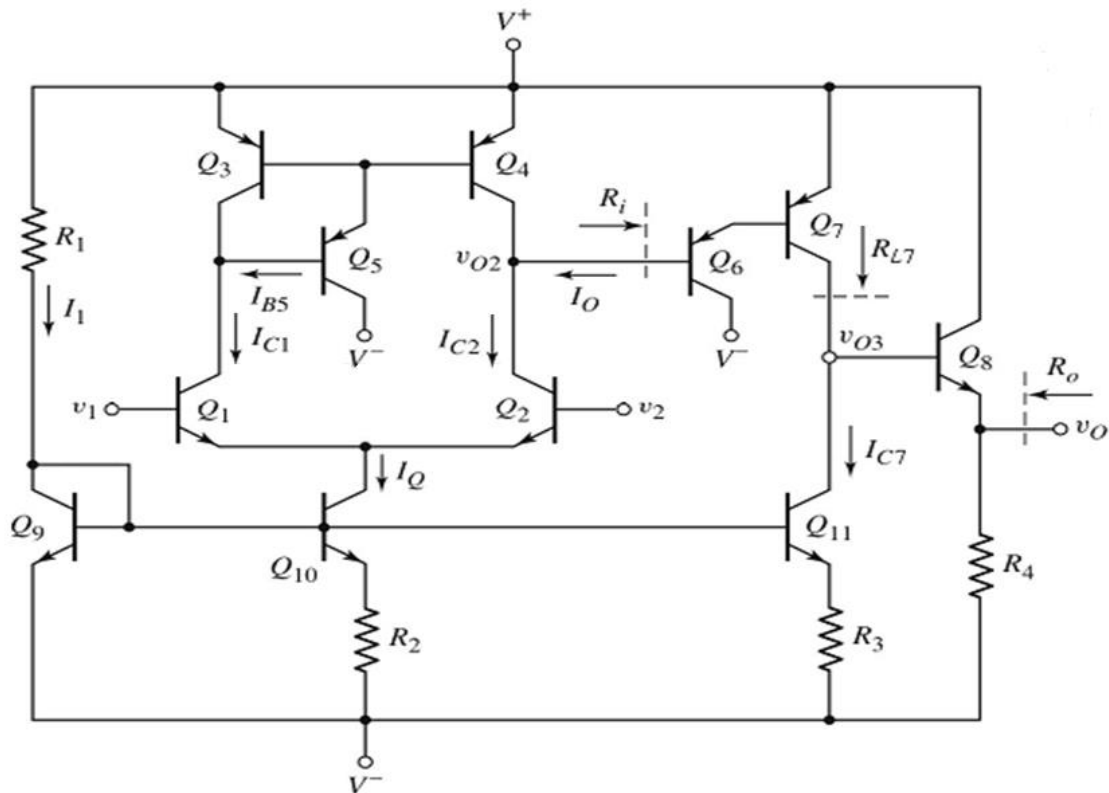

**Figure 1**

Name:

Student ID Number:

Section:

Lecturer: Dr. Jamaludin Bin Omar

EEEE273 - Quiz 5

SEMESTER 2, ACADEMIC YEAR 2015/2016

Date: 31 December 2015

**Take home quiz.** Deadline of submission: 4 January 2016, 5 pm.


You may refer to notes and textbook.

**WRITE** your answer on clean papers, computer printed answer will not be accepted.

**Question:**

Consider a simple BJT operational amplifier in **Figure 1**. The circuit parameters are  $I_{C7} = I_Q = 0.25$  mA,  $I_{C8} = 1$  mA,  $R_4 = 12$  k $\Omega$ , and  $R_3 = 0.2$  k $\Omega$ . Assume  $\beta = 120$  for all transistors and the **Early voltage** for  $Q_7$  and  $Q_{11}$  is 120 V.

- (g) Find the values of  $I_1$  and  $R_1$  if  $V^+ = 9$  V,  $V^- = -9$  V, and  $V_{BE} = V_{EB} = 0.7$  V for all transistors **EXCEPT**  $Q_7$  and  $Q_{11}$ . [2 marks]
- (h) Determine the overall gain ( $A_v$ ) of the multistage amplifier in the **Figure 1**. Assume that voltage gain for the input stage (differential amplifier with active load) is  $A_{v1}$ , voltage gain for the gain stage (Darlington pair) is  $A_{v2}$ , and voltage gain for the output stage (Emitter follower) is  $A_{v3} = 1$ . [6 marks]
- (i) Calculate the output resistance ( $R_o$ ) of the multistage amplifier in the **Figure 1**. [2 marks]

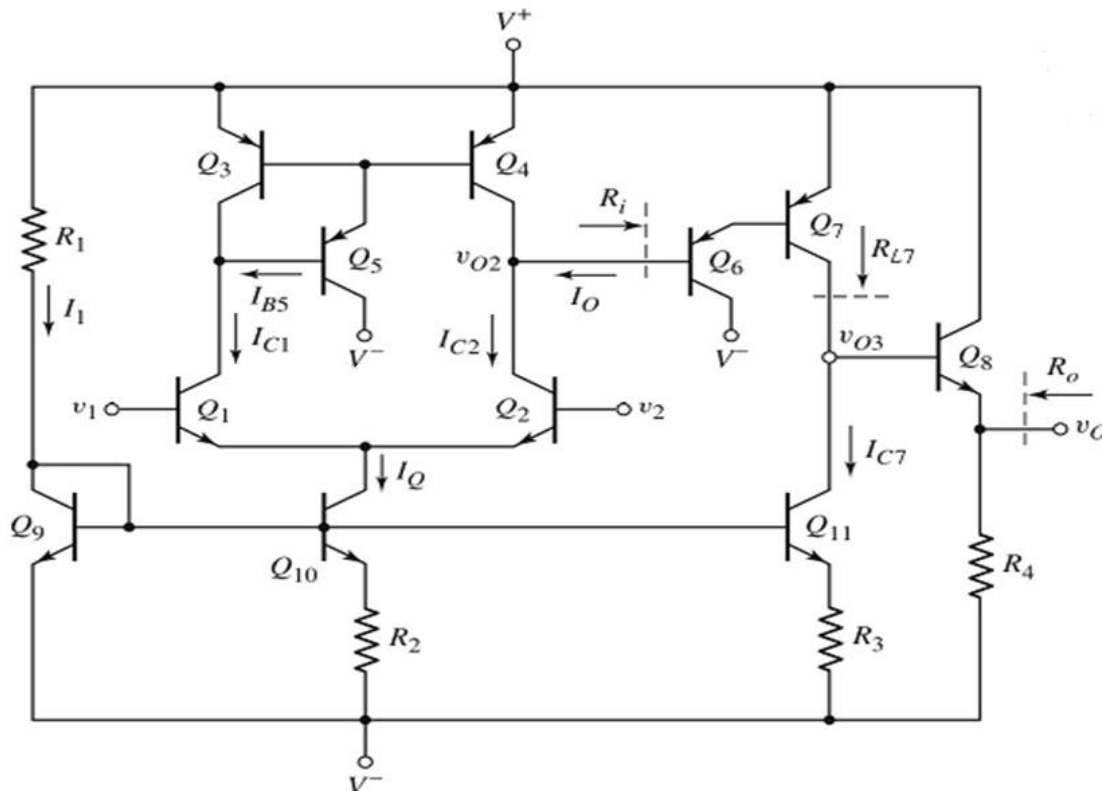

**Figure 1**

Name:

Student ID Number:

Section:

Lecturer: Dr. Jamaludin Bin Omar

EEEE273 - Quiz 5

SEMESTER 2, ACADEMIC YEAR 2015/2016

Date: 31 December 2015

**Take home quiz.** Deadline of submission: 4 January 2016, 5 pm.


You may refer to notes and textbook.

**WRITE** your answer on clean papers, computer printed answer will not be accepted.

**Question:**

Consider a simple BJT operational amplifier in **Figure 1**. The circuit parameters are  $I_{C7} = I_Q = 0.25$  mA,  $I_{C8} = 1.1$  mA,  $R_4 = 10$  k $\Omega$ , and  $R_3 = 0.2$  k $\Omega$ . Assume  $\beta = 110$  for all transistors and the **Early voltage** for  $Q_7$  and  $Q_{11}$  is 110 V.

- (j) Find the values of  $I_1$  and  $R_1$  if  $V^+ = 9$  V,  $V^- = -9$  V, and  $V_{BE} = V_{EB} = 0.7$  V for all transistors **EXCEPT**  $Q_7$  and  $Q_{11}$ . [2 marks]
- (k) Determine the overall gain ( $A_v$ ) of the multistage amplifier in the **Figure 1**. Assume that voltage gain for the input stage (differential amplifier with active load) is  $A_{v1}$ , voltage gain for the gain stage (Darlington pair) is  $A_{v2}$ , and voltage gain for the output stage (Emitter follower) is  $A_{v3} = 1$ . [6 marks]
- (l) Calculate the output resistance ( $R_o$ ) of the multistage amplifier in the **Figure 1**. [2 marks]

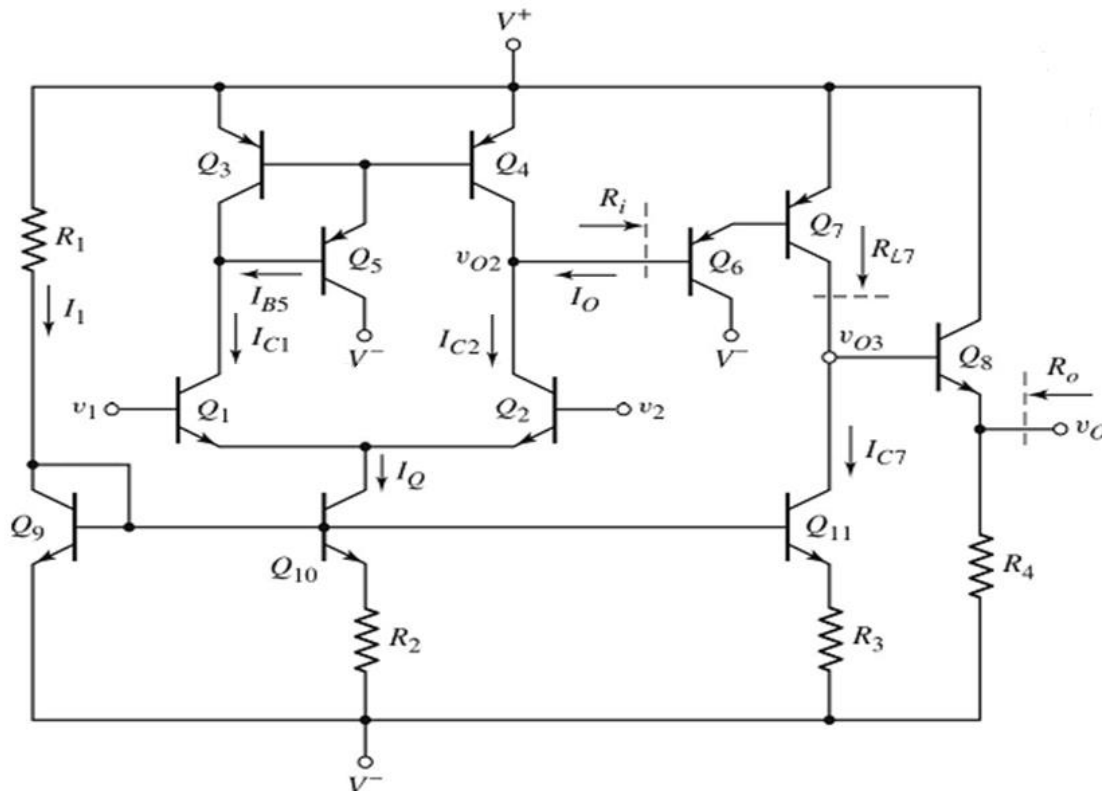

**Figure 1**

Name:

Student ID Number:

Section:

Lecturer: Dr. Jamaludin Bin Omar

EEEE273 - Quiz 5

SEMESTER 2, ACADEMIC YEAR 2015/2016

Date: 31 December 2015

**Take home quiz.** Deadline of submission: 4 January 2016, 5 pm.

You may refer to notes and textbook.

**WRITE** your answer on clean papers, computer printed answer will not be accepted.


**Question:**

Consider a simple BJT operational amplifier in **Figure 1**. The circuit parameters are  $I_{C7} = I_Q = 0.2$  mA,  $I_{C8} = 1.1$  mA,  $R_4 = 11$  k $\Omega$ , and  $R_3 = 0.2$  k $\Omega$ . Assume  $\beta = 110$  for all transistors and the **Early voltage** for  $Q_7$  and  $Q_{11}$  is 120 V.

(m) Find the values of  $I_1$  and  $R_1$  if  $V^+ = 11$  V,  $V^- = -11$  V, and  $V_{BE} = V_{EB} = 0.7$  V for all transistors **EXCEPT**  $Q_7$  and  $Q_{11}$ . [2 marks]

(n) Determine the overall gain ( $A_v$ ) of the multistage amplifier in the **Figure 1**. Assume that voltage gain for the input stage (differential amplifier with active load) is  $A_{v1}$ , voltage gain for the gain stage (Darlington pair) is  $A_{v2}$ , and voltage gain for the output stage (Emitter follower) is  $A_{v3} = 1$ . [6 marks]

(o) Calculate the output resistance ( $R_o$ ) of the multistage amplifier in the **Figure 1**. [2 marks]

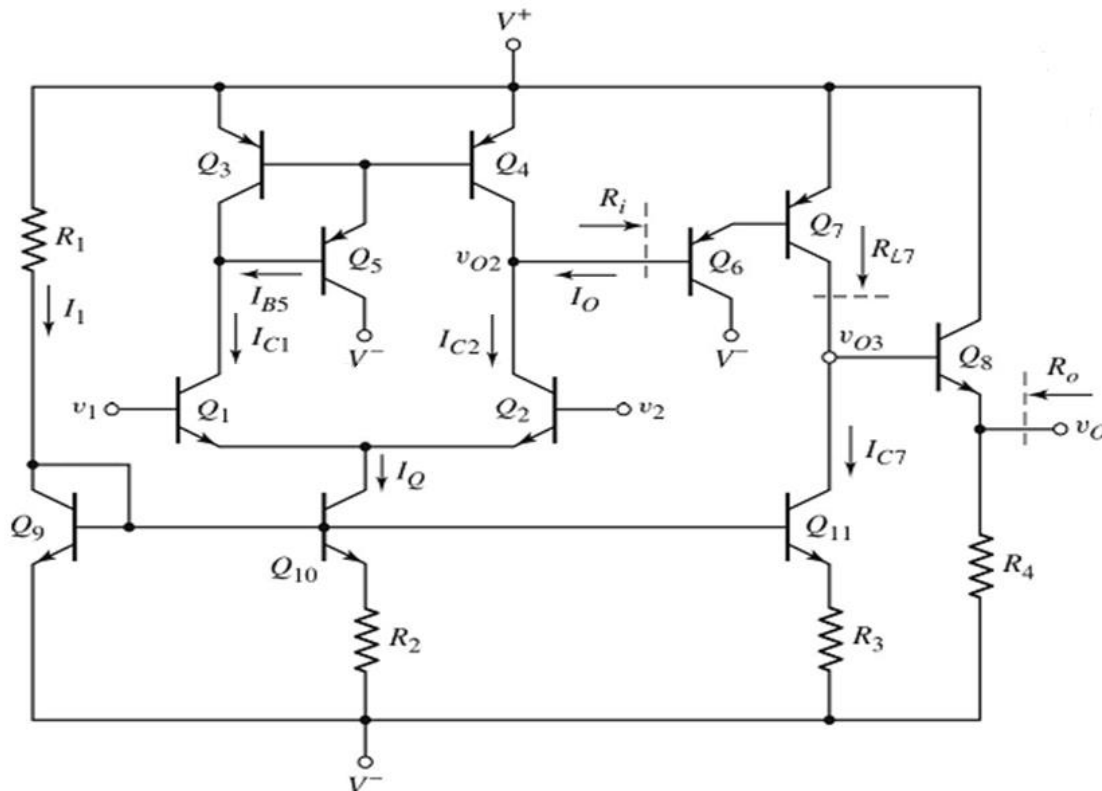

**Figure 1**