

EEEE273 - Quiz 7  
 SEMESTER 2, ACADEMIC YEAR 2015/2016  
 Date: 21 January 2016 Time: 15 minutes

**Question:**

Refer to **ideal** inverting op-amp in **Figure 1**. Calculate its closed-loop voltage gain ( $A_d = v_o / v_I$ ) range if  $R_1 = 20 \text{ k}\Omega$  and  $R_2$  is a potentiometer (having variable resistance) with value from  $20 \text{ k}\Omega$  to  $50 \text{ k}\Omega$ .

Show your calculation clearly.

[10 marks]

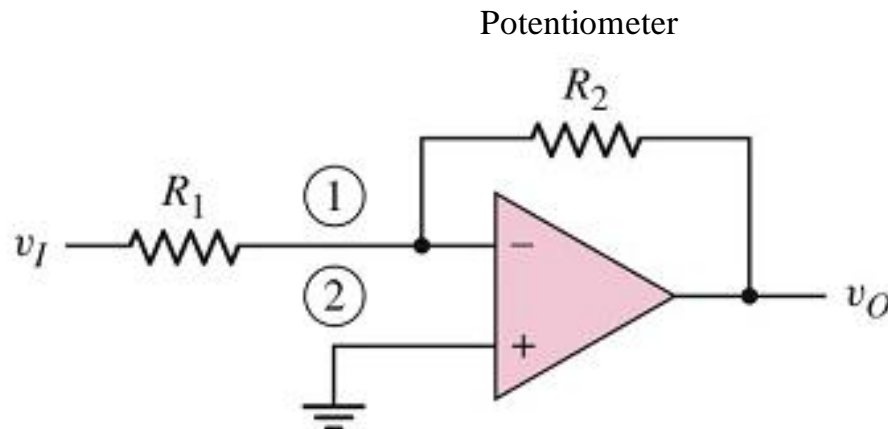


Figure 1

**Answer:**

$$A_d = v_o / v_I = - R_2 / R_1 \quad [1]$$

$R_2$  is a potentiometer, so  $R_2 (\text{min}) = 20 \text{ k}\Omega$  and  $R_2 (\text{max}) = 50 \text{ k}\Omega$  [1, 1]

$$R_1 = 20 \text{ k}\Omega \quad [1]$$

$$A_d(\text{min}) = - R_2 (\text{min}) / R_1 = -20\text{k}/20\text{k} = -1 \text{ V/V} \quad [2, 1]$$

$$A_d(\text{max}) = - R_2 (\text{max}) / R_1 = -50\text{k}/20\text{k} = -2.5 \text{ V/V} \quad [2, 1]$$

EEEEB273 - Quiz 7  
 SEMESTER 2, ACADEMIC YEAR 2015/2016  
 Date: 21 January 2016 Time: 15 minutes

**Question:**

Refer to **ideal** inverting op-amp in **Figure 1**. Calculate its closed-loop voltage gain ( $A_d = v_o / v_I$ ) range if  $R_1 = 15 \text{ k}\Omega$  and  $R_2$  is a potentiometer (having variable resistance) with value from  $10 \text{ k}\Omega$  to  $40 \text{ k}\Omega$ .

Show your calculation clearly.

[10 marks]

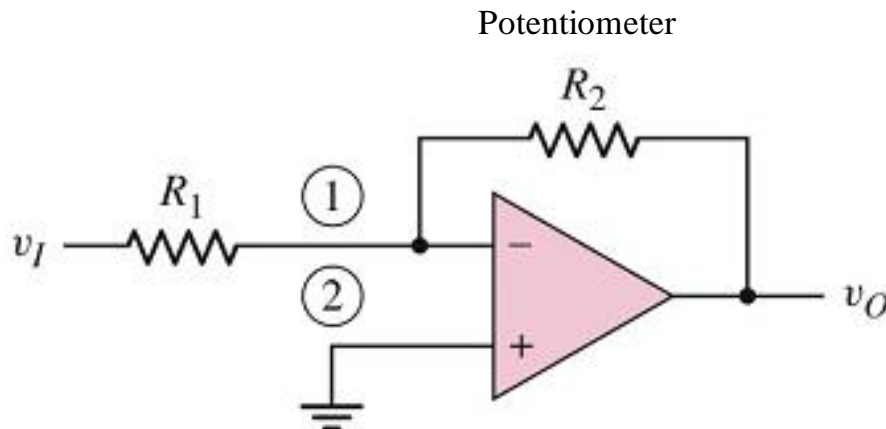


Figure 1

**Answer:**

$$A_d = v_o / v_I = -R_2 / R_1 \quad [1]$$

$R_2$  is a potentiometer, so  $R_2 (\text{min}) = 10 \text{ k}\Omega$  and  $R_2 (\text{max}) = 40 \text{ k}\Omega$  [1, 1]

$$R_1 = 15 \text{ k}\Omega \quad [1]$$

$$A_d(\text{min}) = -R_2 (\text{min}) / R_1 = -10\text{k}/15\text{k} = -0.667 \text{ V/V} \quad [2, 1]$$

$$A_d(\text{max}) = -R_2 (\text{max}) / R_1 = -40\text{k}/15\text{k} = -2.667 \text{ V/V} \quad [2, 1]$$

EEEEB273 - Quiz 7  
 SEMESTER 2, ACADEMIC YEAR 2015/2016  
 Date: 21 January 2016 Time: 15 minutes

**Question:**

Refer to **ideal** inverting op-amp in **Figure 1**. Calculate its closed-loop voltage gain ( $A_d = v_o / v_I$ ) range if  $R_2 = 20 \text{ k}\Omega$  and  $R_1$  is a potentiometer (having variable resistance) with value from  $20 \text{ k}\Omega$  to  $50 \text{ k}\Omega$ .

Show your calculation clearly.

[10 marks]

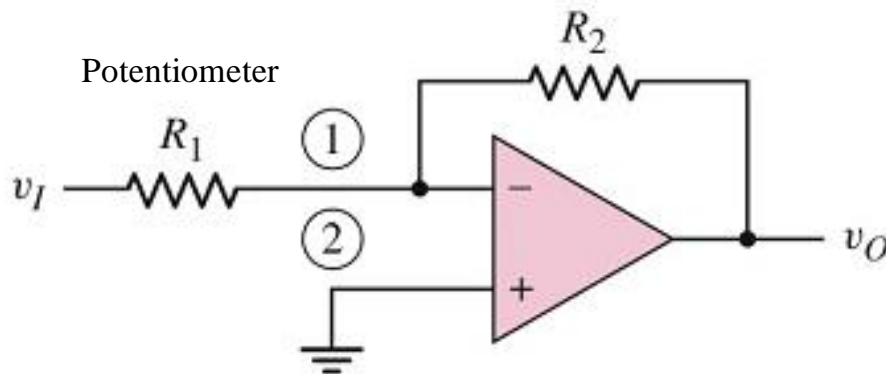


Figure 1

**Answer:**

$$A_d = v_o / v_I = - R_2 / R_1 \quad [1]$$

$$R_1 \text{ is a potentiometer, so } R_1 (\text{min}) = 20 \text{ k}\Omega \text{ and } R_1 (\text{max}) = 50 \text{ k}\Omega \quad [1, 1]$$

$$R_2 = 20 \text{ k}\Omega \quad [1]$$

$$A_d(\text{min}) = - R_2 / R_1(\text{max}) = -20\text{k}/50\text{k} = -0.4 \text{ V/V} \quad [2, 1]$$

$$A_d(\text{max}) = - R_2 / R_1 (\text{min}) = -20\text{k}/20\text{k} = -1 \text{ V/V} \quad [2, 1]$$

EEEE273 - Quiz 7  
 SEMESTER 2, ACADEMIC YEAR 2015/2016  
 Date: 21 January 2016 Time: 15 minutes

**Question:**

Refer to **ideal** inverting op-amp in **Figure 1**. Calculate its closed-loop voltage gain ( $A_d = v_o / v_I$ ) **range** if  $R_2 = 15 \text{ k}\Omega$  and  $R_1$  is a potentiometer (**having variable resistance**) with value from **10 kΩ** to **40 kΩ**.

Show your calculation clearly.

[10 marks]

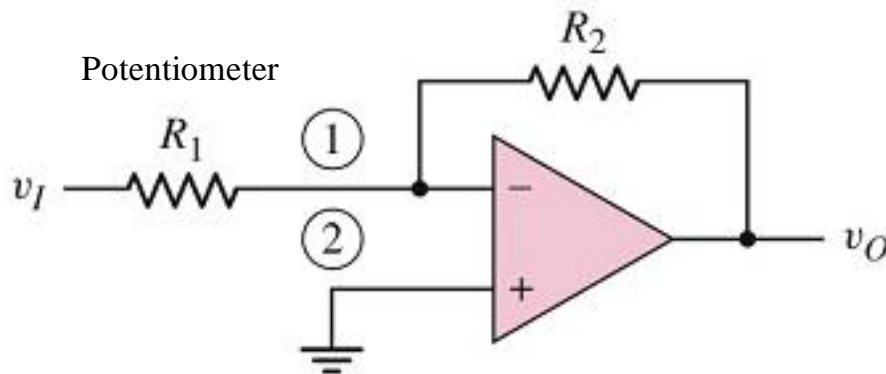


Figure 1

**Answer:**

$$A_d = v_o / v_I = - R_2 / R_1 \quad [1]$$

$$R_1 \text{ is a potentiometer, so } R_1 (\text{min}) = 10 \text{ k}\Omega \text{ and } R_1 (\text{max}) = 40 \text{ k}\Omega \quad [1, 1]$$

$$R_2 = 15 \text{ k}\Omega \quad [1]$$

$$A_d(\text{min}) = - R_2 / R_1(\text{max}) = -15\text{k}/40\text{k} = -0.375 \text{ V/V} \quad [2, 1]$$

$$A_d(\text{max}) = - R_2 / R_1 (\text{min}) = -15\text{k}/10\text{k} = -1.5 \text{ V/V} \quad [2, 1]$$