

Name:
Student ID Number:
Section:
Lecturer: Dr Azni Wati/ Dr Jehana Ermy/
Dr Jamaludin
Table Number:



College of Engineering
Department of Electronics and Communication Engineering

Test 2 – Model Answer

SEMESTER 2, ACADEMIC YEAR 2015/2016

Subject Code : EEEB273
Course Title : Electronics Analysis & Design II
Date : 9 January 2016
Time Allowed : 1 hour 45 minutes

Instructions to the candidates:

1. Write your Name and Student ID number. Circle Lecturer for your section.
2. Write all your answers using pen. **DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.**
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.

() **GOOD LUCK!** ()

Question Number	Q1	Q2	Q3	Total
Marks				

Answer for Question 1 (Cont.)

Q1(a) [6 marks]

M1 & M2: Diff Amp	[2]
M3 ó M6: Active load	[4]

Q1(b) [8 marks]

$$V_{cm(max)} = V^+ - V_{SG5} \text{ ó } V_{SG3} \text{ ó } V_{DS1(sat)} + V_{GS1} \quad [1]$$

$$V_{DS1(sat)} = V_{GS1} - V_{TN}$$

Thus,

$$V_{cm(max)} = V^+ - V_{SG5} \text{ ó } V_{SG3} + V_{TN} \quad [2]$$

$$V_{SG5} = V_{SG3} = \quad [1]$$


$$= \sqrt{\frac{I_{D5}}{K_p}} - V_{TP} = \sqrt{\frac{\frac{I_o}{2}}{\frac{k_p}{2}(W/L)}} - (-1) = \sqrt{\frac{0.23m}{2}} + 1 = 0.5362 + 1 = 1.5362 \quad [3]$$

$$V_{cm(max)} = 10 - 1.5362 - 1.5362 + 1 = 7.9276V \quad [1]$$

Q1(c) [6 marks]

Indicate ac grounds [2]

Indicate ac currents in diff-amp [2]

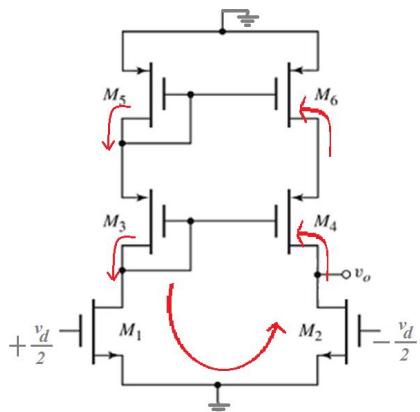Labels of inputs $v_d/2$ and $\delta v_d/2$ [2]

Q1(d) [8 marks]

$$g_{m4} = 2\sqrt{K_p I_{D4}} = 2\sqrt{\left(\frac{k_p}{2}\right)\left(\frac{W}{L}\right)_4 I_{D4}}$$
$$g_{m4} = 2\sqrt{\left(\frac{80}{2}\right)(10)(0.115m)} = 0.4289mA/V \quad [2]$$
$$r_{o4} = r_{o6} = \frac{1}{\lambda_p I_{D4}} = \frac{1}{(0.01)(0.23m/2)} = 869.56k\Omega \quad [4]$$
$$R_o = g_{m4} r_{o4} r_{o6} = (0.4289m)(869.56k)(869.56k) = 324.3M\Omega \quad [2]$$

Q1(e) [8 marks]

$$A_d = g_{m2}(r_{o2} \parallel R_o) \quad [1]$$
$$g_{m2} = 2\sqrt{K_n I_{D2}} = 2\sqrt{\left(\frac{k_n}{2}\right)\left(\frac{W}{L}\right)_2 I_{D2}}$$
$$g_{m2} = 2\sqrt{\left(\frac{100}{2}\right)(5)(0.115m)} = 0.3391mA/V \quad [2]$$
$$r_{o2} = \frac{1}{\lambda_n I_{D2}} = \frac{1}{(0.015)(0.115m)} = 579.71k\Omega \quad [2]$$
$$A_d = (0.3391m)(579.71k \parallel 324.3M) = 196.17 \quad [3]$$

Q1(f) [4 marks]

Output resistance of diff-amp is r_{o2}/R_o , therefore it can be changed by changing the configuration or circuit used for the active load. The larger output resistance from the active load circuit (R_o) results in larger diff-amp output resistance and vice versa. [4 marks for any logical discussions that creates R_o with diff-amp output resistance]

Answer for Question 2

Q2(a) [10 marks]

$$R_i = r_{\pi 6} + r_{\pi 7}(1 + \beta_p) \quad [2]$$

$$r_{\pi 6} = \frac{\beta_p V_T}{I_{C6}} = \frac{90x26mV}{0.25mA/91} = 851.76k\Omega \quad [2]$$

$$I_{C6} = \frac{\beta_p}{1 + \beta_p} I_{E6} = \frac{\beta_p}{1 + \beta_p} I_{B7} = \frac{\beta_p}{1 + \beta_p} \frac{I_{C7}}{\beta_p} = \frac{I_{C7}}{1 + \beta_p} = \frac{0.25mA}{1 + 90} = 0.002747mA \quad [2]$$

$$r_{\pi 7} = \frac{\beta_p V_T}{I_{C7}} = \frac{90x26mV}{0.25mA} = 9.36k\Omega \quad [2]$$

$$R_i = 851.76k + (9.36k)(1 + 90) = 1.70352M\Omega \quad [2]$$

Q2(b) [20 marks]

$$R_o = R_4 \left| \left(\frac{r_{\pi 8} + Z}{(1 + \beta_n)} \right) \right| \quad [2]$$

$$Z = \frac{r_{\pi 9} + (R_{c11} \| R_{c7})}{(1 + \beta_n)} \quad [2]$$

$$R_{c11} = r_{o11}(1 + g_{m11}(r_{\pi 11} \| R_3)) \quad [2]$$

$$r_{o11} = V_{A11} / I_{C11} = 120V / 0.25mA = 480k\Omega \quad [1]$$

$$g_{m11} = I_{C11} / V_T = 0.25mA / 26mV = 9.615mA/V \quad [1]$$

$$r_{\pi 11} = \beta_n V_T / I_{C11} = (120x26mV) / 0.25mA = 12.48k\Omega \quad [1]$$

$$r_{\pi 11} \| R_3 = 12.48k \| 200 = 196.84\Omega$$

$$R_{c11} = (480k)(1 + 9.615m(196.84)) = 1388.45k\Omega \quad [1]$$

$$R_{c7} = r_{o7} = V_{A7} / I_{C7} = 60V / 0.25mA = 240k\Omega \quad [2]$$

$$R_{c11} \| R_{c7} = 1388.45k \| 240k = 204.62k\Omega \quad [1]$$

$$r_{\pi 9} = \beta_n V_T / I_{C9} = (120x26mV) / (1mA / 121) = 377.5k\Omega \quad [1]$$

$$I_{C9} = \frac{\beta_n}{1 + \beta_n} I_{E9} = \frac{\beta_n}{1 + \beta_n} I_{B8} = \frac{\beta_n}{1 + \beta_n} \frac{I_{C8}}{\beta_n} = \frac{I_{C8}}{1 + \beta_n} = \frac{1mA}{121} = 0.008264mA \quad [1]$$

$$Z = \frac{r_{\pi 9} + R_{c11} \| R_{c7}}{(1 + \beta_n)} = \frac{377.5k + 204.62k}{(1 + 120)} = 5.108k\Omega \quad [2]$$

$$r_{\pi 8} = \beta_n V_T / I_{C8} = \frac{120x26mV}{1mA} = 3.12k\Omega \quad [1]$$

$$R_o = R_4 \left| \left(\frac{r_{\pi 8} + Z}{(1 + \beta_n)} \right) \right| = 5k \left| \left(\frac{3.12k + 5.108k}{(1 + 120)} \right) \right| = 67.08\Omega \quad [2]$$

Answer for Question 3

(a) Using the formula,

(6 marks)

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right);$$

[2]

$$V_{BE} = V_T \ln\left(\frac{i_{Cn}}{I_S}\right) = (0.026) \ln\left(\frac{1m}{2 \times 10^{-15}}\right) = 0.7004 \text{ V}$$

[2]

$$\text{So, } V_{BB} = 2V_{BE} = 2(0.7004) = 1.401 \text{ V}$$

[2]

(b) The power dissipated in each transistor, P_Q **(3 marks)**

$$P_Q = i_C \cdot v_{CE} = (1m)(5) = 5 \text{ mW}$$

[2,1]

(c) When $v_O = -3.5 \text{ V}$,**(12 marks)**

$$i_{Cp} \approx |i_L| = |v_O/R_L| = |-3.5V/1k\Omega| = 3.5 \text{ mA}$$

[2]

$$V_{EB} = V_T \ln\left(\frac{i_{Cp}}{I_S}\right) = (0.026) \ln\left(\frac{3.5m}{2 \times 10^{-15}}\right) = 0.7330 \text{ V}$$

[2]

$$V_{BB} = V_{BB} - V_{EB} = 1.40077 - 0.73296 = 0.6678 \text{ V}$$

[2]

$$i_{Cn} = (2 \times 10^{-15}) \exp\left(\frac{0.6678}{0.026}\right) = 0.2857 \text{ mA}$$

[2]

$$\text{Then, } i_{Cp} \approx i_{Cn} + i_L = 0.2857 \text{ mA} + 3.5 \text{ mA} = 3.7857 \text{ mA}$$

[2]

Using the new sets of values, - this is second iteration and optional. If marking first iteration only, the 4 marks will be redistributed in the above (V_{BE} , V_{EB} , i_{Cn} and i_{Cp}).

$$V_{EB} = V_T \ln\left(\frac{i_{Cp}}{I_S}\right) = (0.026) \ln\left(\frac{3.7857 \text{ mA}}{2 \times 10^{-15}}\right) = 0.73499 \text{ V}$$

[1]

$$V_{BB} = V_{BB} - V_{EB} = 1.40077 - 0.73499 = 0.66578 \text{ V}$$

[1]

$$i_{Cn} = (2 \times 10^{-15}) \exp\left(\frac{0.66578}{0.026}\right) = 0.2642 \text{ mA}$$

[1]

$$i_{Cp} = i_{Cn} + i_L = 0.2642 \text{ mA} + 3.5 \text{ mA} = 3.764 \text{ mA}$$

[1]

$$v_I = v_O - v_{EB} + V_{BB}/2 = -3.5 - 0.7330 + 0.7004 = -3.533 \text{ V}$$

[2]

(d) For power dissipation in:

(9 marks)

$$Q_n : P_{Qn} = i_{Cn} v_{CEn} = (0.2857 \text{ mA})(5 - (-3.5)) = 2.43 \text{ mW}$$

[2,1]

$$Q_p : P_{Qp} = i_{Cp} v_{ECp} = (3.7857 \text{ mA})(-3.5 - (-5)) = 5.68 \text{ mW}$$

[2,1]

$$R_L : P_{RL} = i_L^2 R_L = (3.5 \text{ mA})^2 (1 \text{ k}) = 12.25 \text{ mW}$$

[2,1]