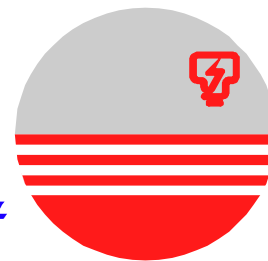


Name:  
Student ID Number:  
Section:  
Lecturer: Dr Azni Wati/ Dr Jehana Ermy/  
Dr Jamaludin  
Table Number:

**UNIVERSITI  
TENAGA  
NASIONAL**



**College of Engineering**  
Department of Electronics and Communication Engineering

**Test 2**

**SEMESTER 2, ACADEMIC YEAR 2015/2016**

Subject Code : **EEEB273**  
Course Title : **Electronics Analysis & Design II**  
Date : **9 January 2016**  
Time Allowed : **1 hour 45 minutes**

**Instructions to the candidates:**

1. Write your Name and Student ID number. Circle Lecturer for your section.
2. Write all your answers using pen. **DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.**
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**

**NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.**



**GOOD LUCK!**



Question Number	Q1	Q2	Q3	Total
Marks				


**Question 1** [40 marks]

**Figure 1** shows a MOSFET differential amplifier with active load circuit biased with constant current source  $I_Q$ . It is given that  $V^+ = 10\text{ V}$ ,  $V^- = -10\text{ V}$ , and  $I_Q = 0.23\text{ mA}$ .

Also, the NMOS transistor parameters are:  $V_{TN} = 1\text{ V}$ ,  $k'_n = 100\ \mu\text{A}/\text{V}^2$  and  $\lambda_n = 0.015\text{ V}^{-1}$ , and the PMOS transistor parameters are:  $V_{TP} = -1\text{ V}$ ,  $k'_p = 80\ \mu\text{A}/\text{V}^2$  and  $\lambda_p = 0.01\text{ V}^{-1}$ . Given that the transistors aspect ratios  $(W/L)_{1,2} = 5$  and  $(W/L)_{3,6} = 10$ .

- (a) **State** the function of each transistor  $M_1$  to  $M_6$  in the **Figure 1**. [6 marks]
- (b) **Determine** the maximum **common-mode voltage input**,  $v_{cm}(\text{max})$ , that can be applied such that the transistors are **still biased in saturation region**. [8 marks]
- (c) **Draw the ac equivalent circuit** for the differential-mode input ( $v_1 = +v_d/2$  and  $v_2 = -v_d/2$ ). **Indicate** the resultant ac currents in all transistors. [6 marks]
- (d) **Determine** the output resistance  $R_o$  in the **Figure 1**. [8 marks]
- (e) **Calculate** the differential-mode voltage gain ( $A_d$ ) of the diff-amp. [8 marks]
- (f) **Comment** how the output resistance of the diff-amp can be changed. [4 marks]

**Answers for Question 1**

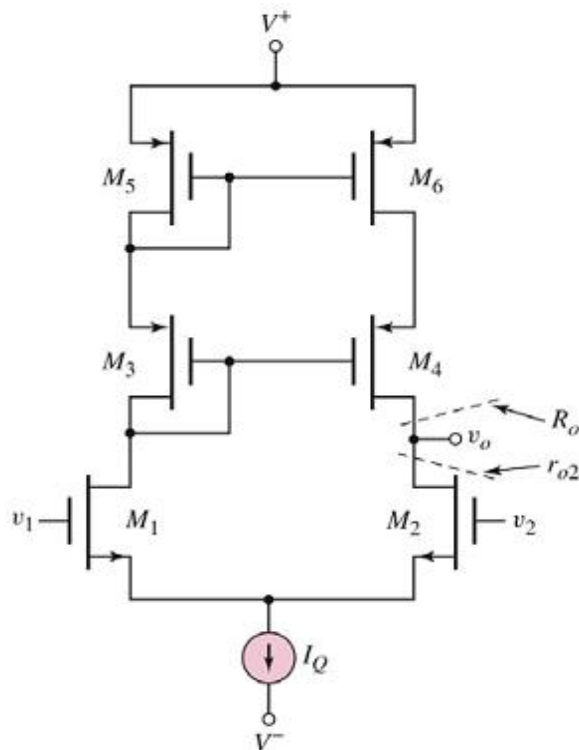

**Figure 1**

**Answer for Question 1 (Cont.)**

**Answer for Question 1 (Cont.)**

**Answers:**


**Question 2** [30 marks]

The circuit in **Figure 2** shows a **Darlington** pair emitter-follower configuration. Assume  $\beta = 120$  for all NPN transistors and  $\beta = 90$  for all PNP transistors. Let  $V_{A7} = 60 \text{ V}$  for  $Q_7$ ,  $V_{A11} = 120 \text{ V}$  for  $Q_{11}$ , and  $V_A = \infty$  for all other transistors.

Given that  $R_3 = 200 \text{ }\Omega$ ,  $R_4 = 5 \text{ k}\Omega$ ,  $I_{C7} = I_{C11} = 0.25 \text{ mA}$ , and  $I_{C8} = 1 \text{ mA}$ .

(a) **Calculate** the value of  $R_i$  of the circuit in the **Figure 2**. [10 marks]

(b) **Find** the value of  $R_o$  of the circuit in the **Figure 2**. [20 marks]

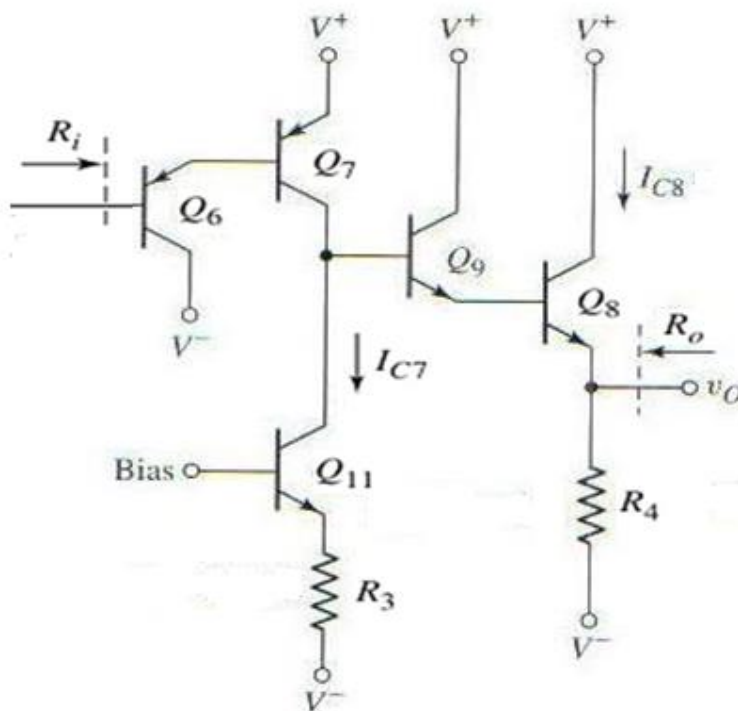

**Figure 2**

**Answer for Question 2**


**Answer for Question 2 (Cont.)**

**Question 3** [30 marks]

**Figure 3** shows a simplified **class-AB** output stage with BJTs. The circuit parameters are  $V_{CC} = 5$  Volts and  $R_L = 1 \text{ k}\Omega$ . The saturation current is  $I_S = 2 \times 10^{-15} \text{ A}$ .

- (a) When  $v_I = 0$ , calculate the value for  $V_{BB}$  that gives  $i_{Cn} = i_{Cp} = 1 \text{ mA}$ . [6 marks]
- (b) Find the power dissipated in transistors  $Q_n$  and  $Q_p$  when  $v_I = 0$ . [3 marks]
- (c) Determine  $i_L$ ,  $i_{Cn}$ ,  $i_{Cp}$ , and  $v_I$  if  $v_O = -3.5 \text{ V}$ . [12 marks]
- (d) Based on answers in part (c), calculate the power dissipated in  $Q_n$ ,  $Q_p$ , and  $R_L$ . [9 marks]

**Answer for Question 3**

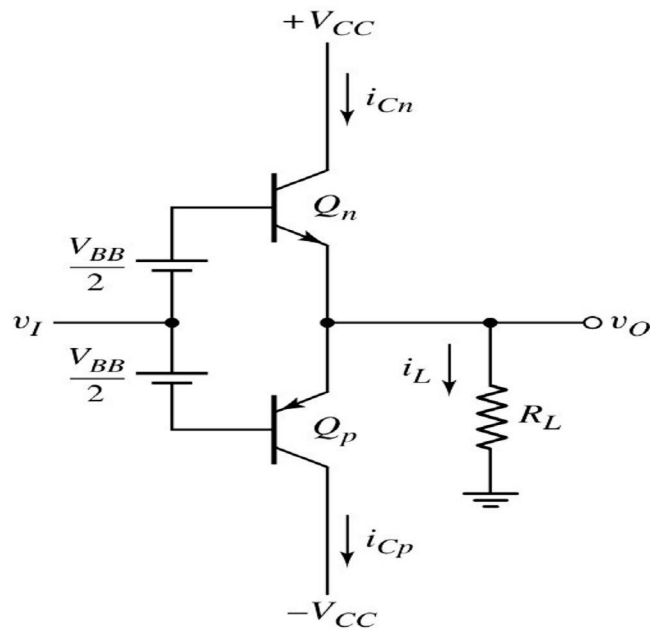

**Figure 3**



**Answer for Question 3 (Cont.)**

## BASIC FORMULA FOR TRANSISTOR

### BJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

### MOSFET

; N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{k'_n}{2} \cdot \frac{W}{L}$$

; P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{k'_p}{2} \cdot \frac{W}{L}$$

; Small signal

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$