



**COLLEGE OF ENGINEERING
PUTRAJAYA CAMPUS
FINAL EXAMINATION
SEMESTER 1 2016 / 2017**

PROGRAMME : Bachelor of Electrical & Electronics Engineering (Honours)
Bachelor of Electrical Power Engineering (Honours)

SUBJECT CODE : EEEB273

SUBJECT : ELECTRONIC ANALYSIS AND DESIGN II

DATE : September 2016

TIME : 3 Hours

INSTRUCTIONS TO CANDIDATES:

1. This paper contains **FIVE** (5) questions.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided. Use **pen** to write your answer.
4. Write answer to different question on a **new page**.

***THIS QUESTION PAPER CONSISTS OF EIGHT (8) PRINTED PAGES INCLUDING
THIS COVER PAGE.***

QUESTION 1 [20 MARKS]

(a) Consider the Widlar current-source circuit with multiple output shown in **Figure 1**. Assume that $V_{BE1(on)} = 0.7 \text{ V}$. The circuit parameters are $R_1 = 10 \text{ k}\Omega$, $R_{E2} = 1 \text{ k}\Omega$, and $R_{E3} = 2 \text{ k}\Omega$.

Calculate I_{REF} , I_{O2} , and I_{O3} .

[10 marks]

 


Figure 1

(b) The circuit shown in **Figure 2** has circuit and transistor parameters as $V^+ = +3 \text{ V}$, $V^- = -3 \text{ V}$, $R_D = 360 \text{ k}\Omega$, $V_{TP} = -0.4 \text{ V}$, $K_p = 30 \mu\text{A}/\text{V}^2$, and $\lambda = 0$. The bias current is given as $I_Q = 12 \mu\text{A}$. Calculate voltage V_{SD1} for $v_1 = v_2 = 0$.

[10 marks]

 


Figure 2

QUESTION 2 [20 MARKS]

(a) The differential amplifier shown in **Figure 3** is biased by a **0.20 mA** constant current source (i.e. $I_Q = 0.20 \text{ mA}$). It is to be redesigned to use an active load in order to increase its differential-mode voltage gain (A_d). The active load to be used is a **2-Transistor Current Source** using **PMOS transistors** to replace the resistors (R_D) in the differential amplifier. Let supply voltages be $\pm 5\text{V}$.

Assume that NMOS devices are available with the following parameters: $K_n = 400 \mu\text{A}/\text{V}^2$, $V_{TN} = 0.5 \text{ V}$, and $\lambda_n = 0.02 \text{ V}^{-1}$

Assume that PMOS devices are available with the following parameters: $K_p = 200 \mu\text{A}/\text{V}^2$, $V_{TP} = -1 \text{ V}$, and $\lambda_p = 0.02 \text{ V}^{-1}$

(i) **Draw the new circuit** incorporating the **active load's full circuit diagram**. Label the circuit correctly and clearly with appropriate symbols and numbering for transistors used in circuit. Leave I_Q symbol as it is in **Figure 3**. **[4 marks]**

(ii) Determine the **differential-mode voltage gain** (A_d) of the circuit. **[6 marks]**

 


Figure 3

(b) Consider an **idealized class-B** output stage as shown in **Figure 4**. The output stage is to deliver **50 W of average power to the load** at a **maximum output voltage of 11.3 V**. Let the power supply voltages be ± 12 volts. The average current supplied by the supply units can be calculated by using $I_{av} = I_p / \dots$.

- (i) Calculate the **peak output current, I_p** . **[4 marks]**
- (ii) Calculate the **total average power supplied** by the supply units **[4 marks]**
- (iii) Calculate the **power conversion efficiency** for this circuit. **[2 marks]**

 


Figure 4

QUESTION 3 [20 MARKS]

Figure 5 shows a multistage amplifier circuit with transistor parameters of $\beta = 120$ and $V_A = \infty$, $V_{BE(on)} = V_{EB(on)} = 0.7V$. It is given that $V^+ = 10 V$.

- (a) Explain the functions of transistors Q_1 , Q_2 and Q_3 in the multistage amplifier. **[5 marks]**
- (b) The circuit is such that **zero dc output voltage** is established. Calculate the value of resistors R_{C2} and R_{C3} if currents $I_Q = 0.5 \text{ mA}$ and $I_{C3} = 1 \text{ mA}$. **[10 marks]**
- (c) **Determine** the output resistance, R_o . **[5 marks]**

 


Figure 5

QUESTION 4 [20 MARKS]

Consider a **standard 741 operational amplifier** (op-amp) circuit as shown in **Figure 6a**. Study **Figure 6a** carefully and observe labelling and values for the resistors in the circuit. Load resistance $R_L = 2 \text{ k}\Omega$ is connected to the Output of the 741 op-amp. The op-amp is supplied by $\pm 15 \text{ V DC}$ voltages.

The transistors have $\beta_n = 200$, $\beta_p = 50$, **Early voltages** $V_{AN} = V_{AP} = 50 \text{ V}$, $V_{BE(\text{on})} = V_{EB(\text{on})} = 0.6 \text{ V}$, and the reverse saturation current $I_S = 5 \times 10^{-16} \text{ A}$.

From **DC analysis**, bias currents for selected transistors are $I_{C13A} = 0.18 \text{ mA}$, $I_{C13B} = 0.54 \text{ mA}$, $I_{C16} = 15.8 \mu\text{A}$, $I_{C17} = 0.54 \text{ mA}$, $I_{C20} = 0.138 \text{ mA}$, and $I_{C22} = 0.18 \text{ mA}$.

Figure 6b shows the AC equivalent circuit for the gain stage of the 741 op-amp. **Figure 6c** shows the AC equivalent circuit for the output stage of the 741 op-amp, which is used to calculate R_{i3} in the **Figure 6b**.

With small-signal analysis, the voltage gain for the gain stage (A_{v2}) of the 741 op-amp can be calculated using the following formula:

$$A_{v2} = \frac{v_{o2}}{v_{o1}} = \frac{-\beta_n (1 + \beta_n) R_9 (R_{act2} \parallel R_{i3} \parallel R_{o17})}{R_{i2} (R_9 + R_{b17})}$$

Where:

$$R_{act2} = r_{o13B}$$

$$R_{i3} = r_{\pi22} + (1 + \beta_p) [R_{19} \parallel R_{20}]$$

$$R_{19} \cong R_{13A}$$

$$R_{20} = r_{\pi20} + (1 + \beta_p) R_L$$

$$R_{b17} = r_{\pi17} + (1 + \beta_n) R_8$$

Calculate the voltage gain for the gain stage (A_{v2}) of the 741 op-amp if R_8 is **short circuit**. Neglect base current in your calculations. Apply appropriate assumptions and recall standard formula for parameters which are not given above. **[20 marks]**

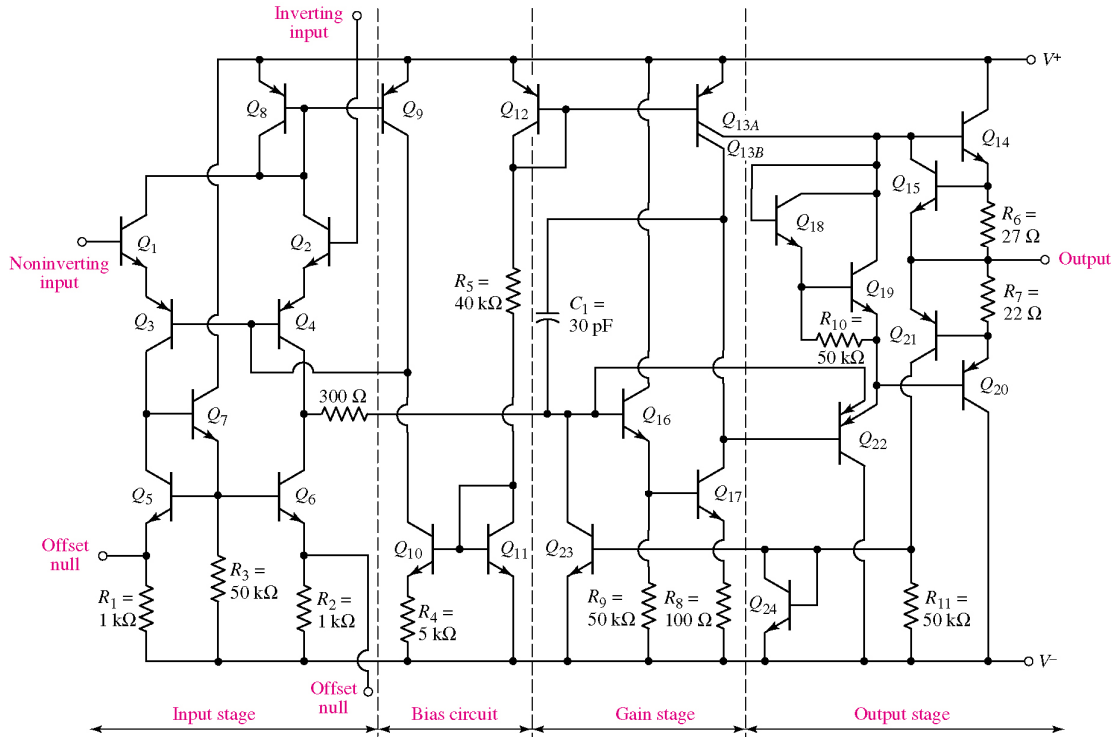


Figure 6a

 


Figure 6b

 


Figure 6c

QUESTION 5 [20 MARKS]

- (a) Briefly describe **two characteristics of an ideal op amp**. **[4 marks]**
- (b) State **three applications** for the ideal op amp. **[3 marks]**
- (c) Refer to the **generalised summing amplifier** using ideal op amp in **Figure 7**. The output voltage is given by:

$$v_O = -\frac{R_F}{R_1}v_{I1} - \frac{R_F}{R_2}v_{I2} + \left(1 + \frac{R_F}{R_N}\right)\left[\frac{R_P}{R_A}v_{I3} + \frac{R_P}{R_B}v_{I4}\right]$$

Where $R_N = R_1 // R_2$ and $R_P = R_A // R_B // R_C$

Design the summing amplifier for $v_O = 2v_{I1} - 10v_{I2} + 3v_{I3} - v_{I4}$

Use **500kΩ** for the **largest resistor** value. Design the circuit such that the **input impedance seen by each source** is the largest value possible. **[13 marks]**

 


Figure 7

-END OF QUESTION PAPER-

APPENDIX:

A) BASIC FORMULA FOR TRANSISTOR

BJT

$$i_C = I_S e^{v_{BE}/V_T} \quad ; \text{NPN}$$

$$i_C = I_S e^{v_{EB}/V_T} \quad ; \text{PNP}$$

$$i_C = \beta i_B = \alpha i_E$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

MOSFET

; N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k'_n}{2} \cdot \frac{W}{L}$$

; P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k'_p}{2} \cdot \frac{W}{L}$$

; Small signal

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

B) HYBRID- EQUIVALENT CIRCUITS

