

Seat Number:

Name:

Student ID Number:

Section: 01/02/03/04/05/06 A/B

Lecturer: Dr Fazrena / Dr Jamaludin /

Dr Azni Wati / Dr Jehana / Ms Zarrin

**UNIVERSITI
TENAGA
NASIONAL**



College of Engineering
Department of Electronics and Communication Engineering

Test 1 SOLUTION

SEMESTER 1, ACADEMIC YEAR 2016/2017

Subject Code : **EEEEB273**
Course Title : **Electronics Analysis & Design II**
Date : **15 July 2016**
Time Allowed : **1½ hour**

Instructions to the candidates:

1. Write your Name and Student ID number. Circle your section number.
2. Write all your answers using pen. **DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.**
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.** Use both sides of the question paper to write your answers.
5. For all calculations, assume that $V_T = 26 \text{ mV}$.

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.



GOOD LUCK!



Question No.	1	2	3	Total
Marks				

Question 1 [40 marks]

(a) The Widlar current source is shown in **Figure 1**. It is given that $V^+ = 12V$, $V^- = -12V$, $R_I = 50k\Omega$ and $V_{BE1} = 0.68V$ at $1mA$.

i) **By clearly stating any assumptions, derive** the relationship between I_o and I_{REF} for a Widlar current source to achieve the equation below:

[8 marks]

$$I_o R_E = V_T \ln\left(\frac{I_{REF}}{I_o}\right)$$

ii) **Design** the current source to provide output current of $3\mu A$ by determining I_{REF} , I_{C1} , I_{C2} , V_{BE2} and R_E .

[12 marks]

Answers for Question 1(a)i)

Neglecting base currents, $I_B = 0$, $I_C = I_E$ [1mark]
 $I_{C1} = I_{REF} = I_{E1}$, $I_{C2} = I_O = I_{E2}$ [1mark]
 $I_{C1} = I_S \exp(V_{BE1}/V_T) = I_{REF}$ [1mark]
 $I_{C2} = I_S \exp(V_{BE2}/V_T) = I_O$ [1mark]
 $V_{BE1} = V_T \ln(I_{REF}/I_S)$ and $V_{BE2} = V_T \ln(I_O/I_S)$ [1mark]

KVL in B-E Loop:
 $V_{BE1} = V_{BE2} + I_{E2}R_E$ [1mark]
 $V_{BE1} = V_{BE2} + I_O R_E$
 $I_O R_E = V_{BE1} - V_{BE2}$ [1mark]
 $= V_T \ln(I_{REF}/I_S) - V_T \ln(I_O/I_S)$
 $= V_T \ln(I_{REF}/I_O)$ [1mark]

Answers for Question 1(a)ii)

$I_{REF} = [V^+ - V_{BE1} - V^-] / R_I = [12 - 0.68 - (-12)]/50k$
 $= 0.4664 \text{ mA}$ [2marks]

Calculate I_S :
 $I_C = 1mA$ when $V_{BE1} = 0.68 \text{ V}$
 $1m = I_S \exp [0.68/26m]$
 $I_S = 4.308 \times 10^{-15} \text{ A}$ [2marks]

Recalculate V_{BE1} :
 $V_{BE1} = V_T \ln(I_{REF}/I_S) = 26m \ln(0.4664m/4.308 \times 10^{-15})$
 $= 0.6602V$ [2marks]

Recalculate I_{REF} :
 $I_{REF} = [12 - 0.6602 - (-12)]/50k = 0.4668 \text{ mA}$ [1mark]
 Therefore, $I_{C1} = I_{REF} = 0.4668 \text{ mA}$ [1mark]
 $I_{C2} = I_O = 3 \text{ uA}$ [1mark]
 $V_{BE2} = V_T \ln(I_O/I_S) = 26m \ln(3 \text{ uA} / 4.308 \times 10^{-15}) = 0.5289 \text{ V}$ [1mark]


Calculating R_E :
 $R_E = (V_T / I_O) \ln(I_{REF}/I_O) = (26m/3 \text{ uA}) \ln(0.4668 \text{ mA} / 3 \text{ uA})$
 $= 43.74 \text{ k}\Omega$ [2marks]

(b) Design a **pnp version of the Wilson current source** using a resistor, R_1 , to establish the current, I_{REF} . The circuit parameters are $V^+ = 10\text{ V}$, $V^- = -10\text{ V}$, and the transistor parameters are: $V_{EB(on)} = 0.6\text{ V}$, $\beta = 80$, and $V_A = \infty$.

- i) **Sketch** the circuit of the design. [8 marks]
- ii) What is I_{REF} , if the load current, I_O is **0.8 mA**? [8 marks]
- iii) **Compare and contrast** the stability of the **Wilson current source** to a **three-transistor current source**. [4 marks]

Answers for Question 1(b)

(i) $V^+ = 10\text{ V}$

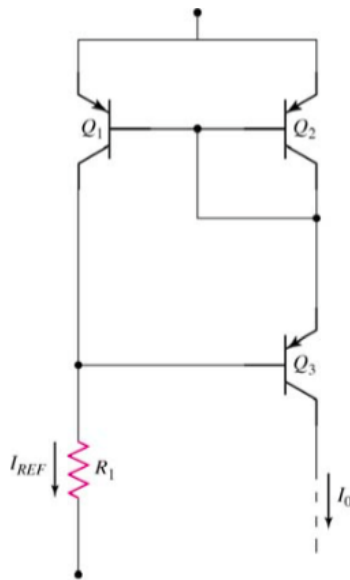

$V^- = 10\text{ V}$

Q1, Q2 and Q3 placement: [4 marks]
Insertion of R_1 [2 marks]
Labels of I_{REF} and I_O [2 marks]

(ii) $I_O = I_{REF} \left[\frac{1}{\left(1 + \frac{2}{\beta(\beta+2)}\right)} \right] \dots [2\text{ marks}]$

For $I_O = 0.8\text{ mA}$, substitute into eqn.,

$$I_{REF} = I_O \left[1 + \frac{2}{\beta(\beta+2)} \right]$$

$$I_{REF} = (0.8\text{ m}) \left[1 + \frac{2}{(80)(82)} \right]$$

$$I_{REF} = \mathbf{0.8002\text{ mA} [2\text{ marks}]}$$

For R_1 ;

$$R_1 = \frac{V^+ - V_{BE1} - V_{BE3} - V^-}{I_{REF}} \dots [2\text{ marks}]$$

$$R_1 = \frac{10 - 0.6 - 0.6 - (-10)}{0.8002\text{ m}}$$

$$= \mathbf{23.49\text{ k}\Omega [2\text{ marks}]}$$

(iii) The stability of the circuits:

Wilson: $R_O = \frac{\beta}{2} r_{O3}$, and [1 mark]

3TCS: $R_O = r_{O2}$ [1 mark]

Therefore, Wilson current source has more stability than 3TCS by a factor of $\beta/2$.

[2 marks]

Question 2 [30 marks]

(a) Consider the basic two-transistor NMOS current source in **Figure 2**. The circuit parameters are $V^+ = 2.5\text{V}$, $V^- = -2.5\text{V}$, and $I_{REF} = 120\mu\text{A}$. The transistor parameters are $V_{TN} = 0.8\text{V}$, $k'_n = 80\mu\text{A/V}^2$, $(W/L)_1 = 3$, $(W/L)_2 = 4.5$, and $\lambda = 0.01\text{V}^{-1}$. Calculate I_{D2} at $V_{DS2} = 3\text{V}$. [15 marks]

(b) **Redesign** the NMOS current source circuit in **Figure 2** such that the **minimum voltage at $V_{D2} = -2.0\text{V}$** , $I_{REF} = 60\mu\text{A}$, and the load current $I_O = 100\mu\text{A}$. [15 marks]

Answers for Question 2(a)

$$I_{REF} = \frac{k'_n}{2} \left(\frac{W}{L} \right)_1 (V_{GS1} - V_{TN})^2 \quad (1)$$

$$V_{GS1} = \sqrt{\frac{2I_{REF}}{k'_n(W/L)_1}} + V_{TN} = \sqrt{\frac{2(120\mu)}{(80\mu)(3)}} + 0.8 = 2\text{V} \quad (3)$$

$$V_{GS1} = V_{GS2}$$

$$I_{D2} = \frac{k'_n}{2} \left(\frac{W}{L} \right)_2 (V_{GS2} - V_{TN})^2 = \frac{80\mu}{2} (4.5)(2 - 0.8)^2 = 180\mu\text{A} \quad (3)$$

$$I_{D2} = 180\mu\text{A at } V_{DS2} = 2\text{V}$$

$$\text{At } V_{DS2} = 3\text{V}$$

$$I_{D2(new)} = I_{D2} + \Delta I_{D2} = 180\mu\text{A} + \frac{\Delta V_{DS2}}{R_o} \quad (3)$$

$$\text{where } R_o = \frac{1}{\lambda I_{DQ}} = \frac{1}{(0.01)(180\mu)} = 555.6\text{k}\Omega \quad (2)$$

$$\Delta V_{DS2} = 3 - 2 = 1\text{V} \quad (1)$$

$$I_{D2(new)} = 180\mu\text{A} + \frac{1}{555.6\text{k}} = 181.8\mu\text{A} \quad (2)$$

Answers for Question 2 (b)

$$\begin{aligned}V_{D2} &= V_{DS2} + V_{S2} = V_{DS2} + V^- \\V_{D2min} &= V_{DS2(sat)} + V^- \\V_{DS2(sat)} &= V_{D2min} - V^- \\&= -2 - (-2.5) = 0.5V\end{aligned}\quad [3marks]$$

$$\begin{aligned}\text{Also, } V_{DS2(sat)} &= V_{GS2} - V_{TN} \\V_{GS2} &= V_{DS2(sat)} + V_{TN} \\&= 0.5 + 0.8 = 1.3V = V_{GS1}\end{aligned}\quad [3marks]$$

$$\begin{aligned}I_{D1} &= I_{REF} = 60 \text{ uA} \\I_{D1} &= (kn^2/2)(W/L)_1(V_{GS1}-V_{TN})^2 \\60\text{u} &= (80\text{u}/2) (W/L)_1(1.3-0.8)^2 \\(W/L)_1 &= 6\end{aligned}\quad [3marks]$$

$$\begin{aligned}I_{D2} &= I_O = 100 \text{ uA} \\I_{D2} &= (kn^2/2)(W/L)_2(V_{GS2}-V_{TN})^2 \\100\text{u} &= (80\text{u}/2) (W/L)_2(1.3-0.8)^2 \\(W/L)_2 &= 10\end{aligned}\quad [3marks]$$

$$\begin{aligned}R &= [V^+ - V_{GS1} - V^-] / I_{REF} \\&= [2.5 - 1.3 - (-1.2)]/60\text{u} \\&= 61.67\text{k}\Omega\end{aligned}\quad [3marks]$$


Question 3 [30 marks]

The basic BJT differential pair is shown in **Figure 3**. The circuit parameter values are: $V^+ = +12\text{ V}$, $V^- = -12\text{ V}$, $I_Q = 1.2\text{ mA}$, and $R_C = 12\text{ k}\Omega$. The transistor parameters in the differential pair are $\beta = \infty$ (neglect base currents), $V_A = \infty$, and $V_{BE}(\text{on}) = 0.7\text{ V}$. The constant current source in **Figure 3** that is providing the current I_Q is implemented using the **cascode current source**.

- (a) **Sketch the full differential pair circuit** that includes the circuit for the **cascode current source**. [10 marks]
- (b) **Determine i_{C1} and v_{CE2}** for common-mode voltages $v_{B1} = v_{B2} = v_{CM} = -3.5\text{ V}$. [10 marks]
- (c) It is given that the input voltages for the differential amplifier are $v_{B1} = 210 \times 10^{-6} \sin \omega t\text{ V}$ and $v_{B2} = 180 \times 10^{-6} \sin \omega t\text{ V}$. **Calculate** the differential-mode input voltage (v_d) and common-mode input voltage (v_{cm}) of the differential amplifier. Then, find the **maximum and minimum values of v_d and v_{cm}** . [10 marks]

Answers for Question 3

(a)

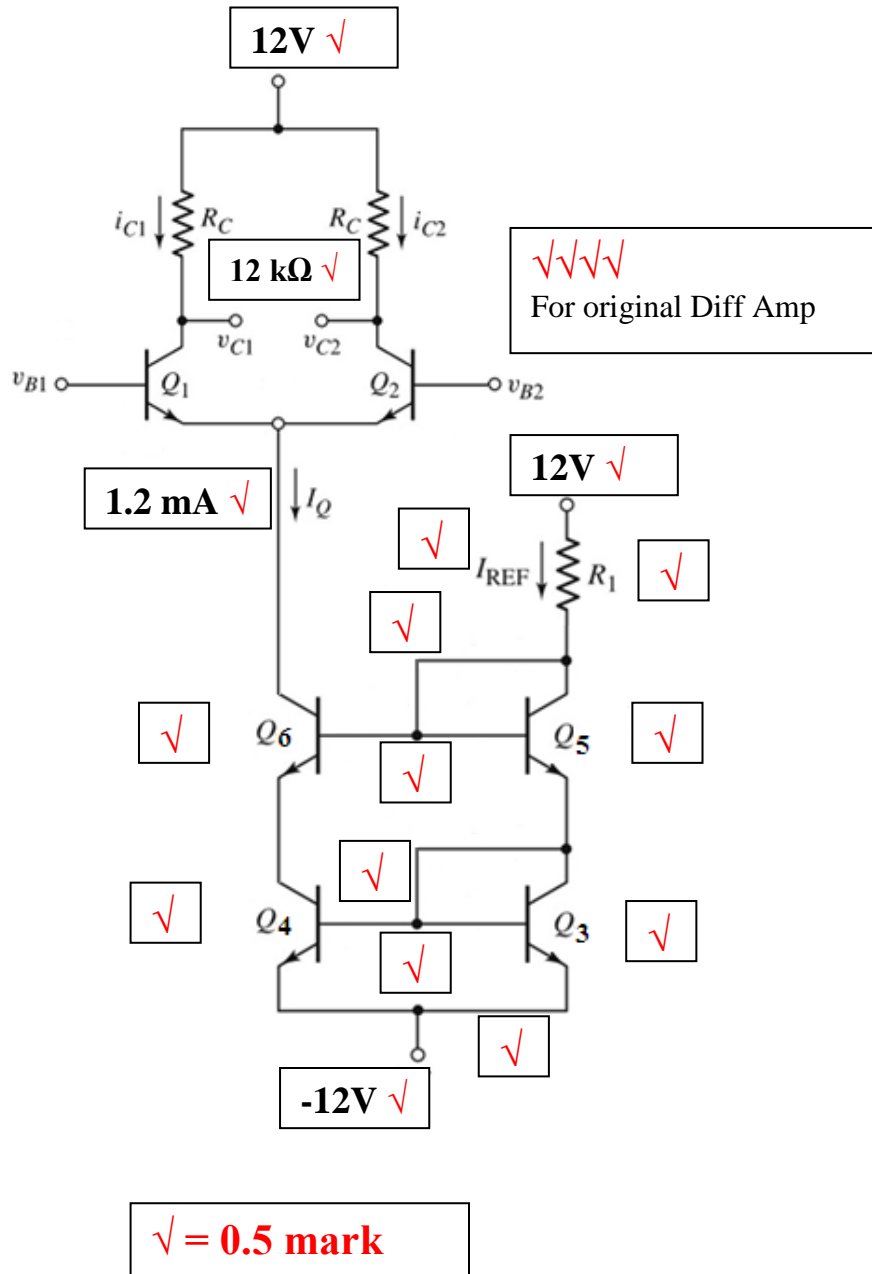

(b)

$$\beta = \infty$$

$$i_{C1} = i_{E1} = I_Q / 2 = 1.2\text{mA} / 2 = 0.6 \text{ mA} \quad [1, 1]$$

$$v_{B1} = v_{B2} = v_{CM}$$

$$i_{C2} = i_{C1} = 0.6 \text{ mA} \quad [1]$$

$$v_{C2} = V^+ - i_{C2} R_C \quad [1]$$

$$= 12 - (0.6\text{mA})(12\text{k}) = 4.8 \text{ V} \quad [1]$$

For $v_{CM} = -3.5 \text{ V}$

$$v_E = v_{CM} - V_{BE}(\text{on}) \quad [1]$$

$$= -3.5 - 0.7 = -4.2 \text{ V} \quad [1]$$

$$v_{CE2} = v_{C2} - v_E \quad [2]$$

$$= 4.8 - (-3.5) = 8.3 \text{ V} \quad [1]$$

(c)

$$v_d = v_{B1} - v_{B2} \quad [1]$$

$$= 210 \times 10^{-6} \sin \omega t - 180 \times 10^{-6} \sin \omega t \quad [1]$$

$$= 30 \times 10^{-6} \sin \omega t \text{ V} \quad [1]$$

$$v_d(\text{max}) = 30 \times 10^{-6} (1) = 30 \mu\text{V} \quad \{\sin \omega t = 1\} \quad [1]$$

$$v_d(\text{min}) = 30 \times 10^{-6} (-1) = -30 \mu\text{V} \quad \{\sin \omega t = -1\} \quad [1]$$

$$v_{cm} = (v_{B1} + v_{B2}) / 2 \quad [1]$$

$$= (210 \times 10^{-6} \sin \omega t + 180 \times 10^{-6} \sin \omega t) / 2 \quad [1]$$

$$= 195 \times 10^{-6} \sin \omega t \quad [1]$$

$$v_{cm}(\text{max}) = 195 \times 10^{-6} (1) = 195 \mu\text{V} \quad \{\sin \omega t = 1\} \quad [1]$$

$$v_{cm}(\text{min}) = 195 \times 10^{-6} (-1) = -195 \mu\text{V} \quad \{\sin \omega t = -1\} \quad [1]$$