

Name:
 Student ID Number:
 Section:
 Lecturer: Dr Fazrena Azlee/Dr Azni Wati/
 Dr Jamaludin/Dr Jehana Ermy/ Ms Zarrin

**UNIVERSITI
 TENAGA
 NASIONAL**



College of Engineering
 Department of Electronics and Communication Engineering

Test 2

SEMESTER 1, ACADEMIC YEAR 2016/2017

Subject Code : **EEEB273**
 Course Title : **Electronics Analysis & Design II**
 Date : **19 August 2016**
 Time Allowed : **1½ hours**

Instructions to the candidates:

1. Write your Name, Student ID number, and Section number. Indicate your Lecturer.
2. Write all your answers **using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.**
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**
5. For all calculations, use $V_T = 26 \text{ mV}$ when necessary.

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.



GOOD LUCK!



Question No.	1	2	3	Total
Marks				

BASIC FORMULA

BJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

;Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

MOSFET

;N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{k'_n}{2} \cdot \frac{W}{L}$$

;P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{k'_p}{2} \cdot \frac{W}{L}$$

;Small signal

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

Question 1 [30 marks]

A differential amplifier is shown in **Figure 1**. The circuit parameters are given as $V^+ = 10\text{ V}$, $V^- = -10\text{ V}$, and $I_Q = 1.5\text{ mA}$. The NMOS transistor parameters are $V_{TN} = 0.4\text{ V}$, $k'_n = 100\ \mu\text{A/V}^2$, $\lambda_n = 0.025\text{ V}^{-1}$, $(W/L)_{1,2} = 5$ and $(W/L)_8 = 20$. The PMOS transistor parameters are $V_{TP} = -0.4\text{ V}$, $k'_p = 40\ \mu\text{A/V}^2$, $\lambda_p = 0.04\text{ V}^{-1}$ and $(W/L)_{3,4} = 10$.

- i. Determine the **range of the output voltage, v_o** , for the differential amplifier. [15 marks]
- ii. Define **common mode rejection ratio, CMRR**. How can the circuit in **Figure 1** be **redesigned to improve** its CMRR? Explain what will happen to the **range of the output voltage** calculated in part i) if the circuit is redesigned. [5 marks]
- iii. Find the **output resistance, R_o** , of the differential amplifier. [10 marks]

Answer for Question 1

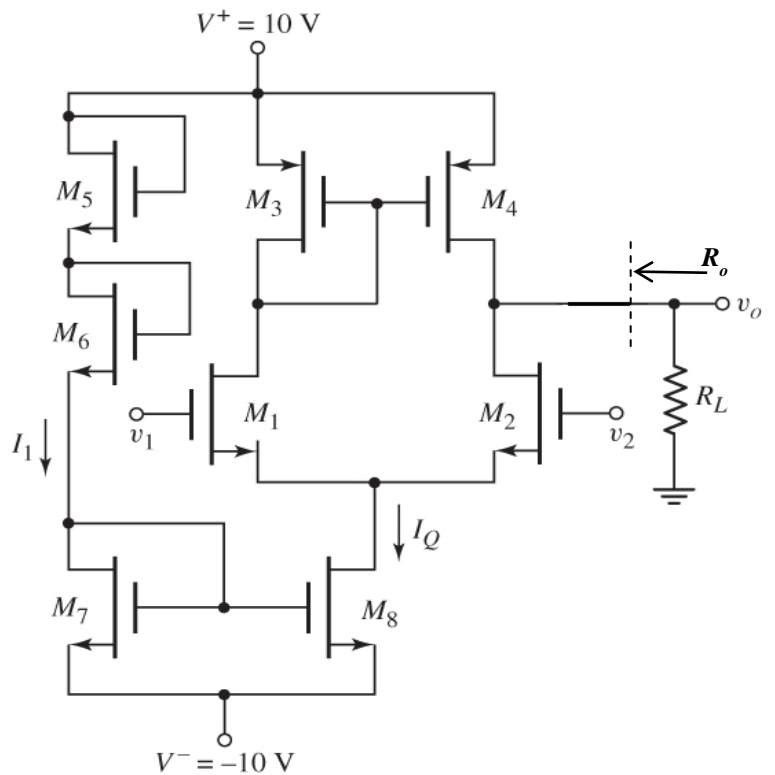


Figure 1

Answer for Question 1 (continue)

Question 2 [30 marks]

(a) The circuit in **Figure 2** has a pair of npn bipolar transistors as input devices and three-pnp-bipolar-transistor circuit connected as an active load. The differential amplifier circuit is biased with a constant current source $I_Q = 0.2 \text{ mA}$ that has an output resistance $R_{OCS} = 50 \text{ M}\Omega$. The transistor parameters are: $\beta = 100$, $V_{A1} = V_{A2} = 100 \text{ V}$, $V_{A3} = V_{A4} = 60 \text{ V}$, and $V_{A5} = \infty$.

- i. **Calculate the open-circuit differential-mode voltage gain A_d .** [12 marks]
- ii. **Determine R_L such that the differential-mode voltage gain is reduced to 80% of its open-circuit value.** [8 marks]

Answer for Question 2(a)

 


Figure 2

(b) Refer to **Figure 3**. It is given that $I_Q = I_{R4} = I_{R6} = 0.4 \text{ mA}$, and $I_{R7} = 2 \text{ mA}$. Neglect base currents and assume $V_{BE(\text{on})} = 0.7 \text{ V}$ for all transistors except Q_8 and Q_9 in the Widlar circuit. From small-signal analysis, $R_{i2} = 1.3 \text{ M}\Omega$. Calculate the overall gain of the circuit, $A_d = v_o/v_d$. State any assumptions. Assume $\beta = 100$ and $V_A = \infty$. It is given that the gain of the Darlington Pair can be calculated using:

$$A_{V2} = \left(\frac{I_{R4}}{2V_T} \right) (R_5 \parallel R_{i3}) \quad [10 \text{ marks}]$$

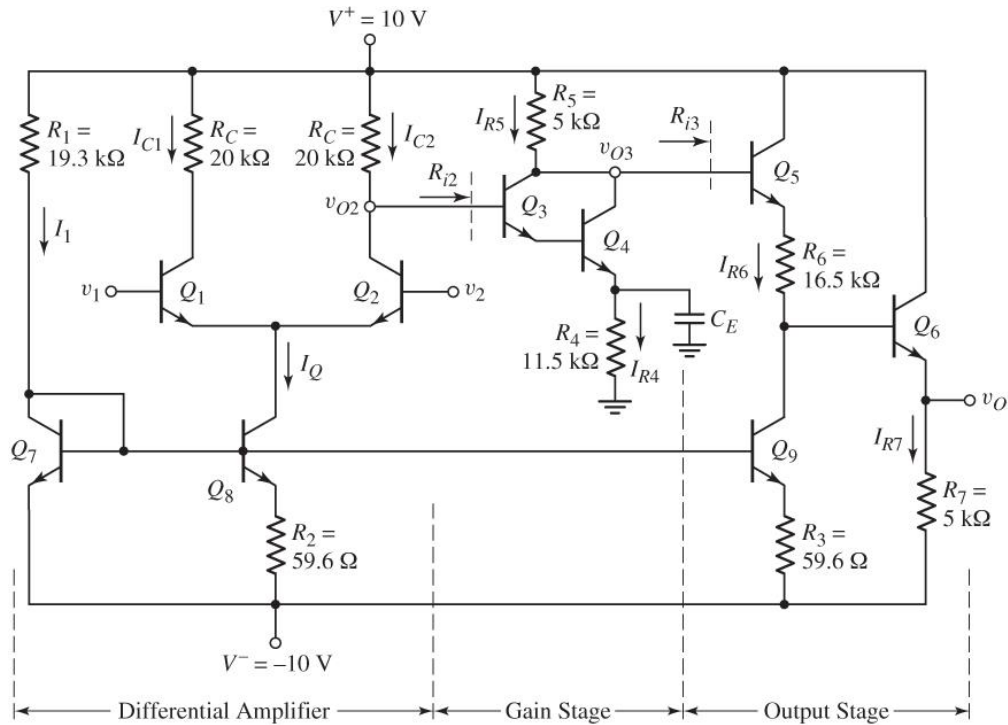


Figure 3

Answer for Question 2(b)

Question 3 [40 marks]

- (a) **Compare and contrast** the output stage classes (namely **class-A**, **class-B**, and **class-AB**). You might consider the **keywords**: percent (%) of time the output transistors are conducting; the power conversion efficiency; quiescent bias current; power dissipation. [15 marks]

Answer for Question 3(a)

(b) Consider the emitter follower of the **class-A** output stage shown in **Figure 4**. The circuit parameters are: $V^+ = 7.5 \text{ V}$, $V^- = -7.5 \text{ V}$, and $R_L = 2 \text{ k}\Omega$. Assume all transistors are matched with $V_{BE(on)} = 0.7 \text{ V}$ and $V_{CE(sat)} = 0.5 \text{ V}$. Neglect base currents in your calculations.

- i) Find the value of R_1 that gives the maximum possible output range. [10 marks]
- ii) Sketch the output current waveform (i_{C1}) for one complete input cycle. [5 marks]
- iii) Calculate the power conversion efficiency, η , for this output stage. [10 marks]

Answer for Question 3(b)

 


Figure 4