



**COLLEGE OF ENGINEERING
PUTRAJAYA CAMPUS
FINAL EXAMINATION**

SEMESTER 2 2016 / 2017

MODEL ANSWER

PROGRAMME : Bachelor of Electrical & Electronics Engineering (Honours)
Bachelor of Electrical Power Engineering (Honours)

SUBJECT CODE : EEEB273

SUBJECT : ELECTRONIC ANALYSIS AND DESIGN II

DATE : January/February 2017

TIME : 3 hours

INSTRUCTIONS TO CANDIDATES:

1. This paper contains **FIVE (5) questions in NINE (9) pages.**
 2. Answer **ALL** questions.
 3. Write **ALL** answers in the answer booklet provided. **Use pen** to write your answer.
 4. Write answer to different question on **a new page**.
 5. **Show clearly all calculations, complete with proper Unit for every parameter.**
-

THIS QUESTION PAPER CONSISTS OF *NINE (9)* PRINTED PAGES INCLUDING THIS COVER PAGE.

Answers to QUESTION 1 [20 marks]a) R_o (output resistance of Widlar CS) [Total = 8]

$$R_2 = (V_T \ln[I_1/I_{C4}])/I_{C4} = (0.026 \ln[0.5m/200\mu]/200\mu = 119\Omega) \quad [2]$$

$$g_{m4} = I_{C4}/V_T = I_Q/(V_T) = (200\mu)/0.026 = 7.692 \text{ mA/V} \quad [1]$$

$$r_{\pi4} = \beta V_T / I_{C4} = 100(0.026)/200\mu = 13k\Omega \quad [1]$$

$$r_{\pi4} \| R_2 = 118\Omega \quad [1]$$

$$r_{o4} = V_A/I_{C4} = 100/200\mu = 0.5M\Omega \quad [1]$$

$$R_o = r_{o4}[1 + g_{m4}(r_{\pi4} \| R_2)] = 0.5M[1 + 7.692m(118)] = 954k\Omega \quad [2]$$

b) Value of R_C [Total = 4]

$$v_{o2} = V^+ - I_{C2}R_C \quad [1]$$

$$R_C = (V^+ - v_{o2})/I_{C2} = (10-8)/(0.5 * I_{C4}) = 2/100\mu = 20k\Omega \quad [3]$$

c) Differential-mode input resistance, R_{id} [Total = 4]

$$r_{\pi2} = \beta V_T / I_{C2} = 100(0.026)/100\mu = 26k\Omega \quad [2]$$

$$R_{id} = 2 r_{\pi2} = 2(26k) = 52k\Omega \quad [2]$$


d) Common-mode input resistance, R_{icm} [Total = 4]

$$\text{Assume } r_\mu = \infty. r_O = V_A/I_{CQ1} = \infty / I_{CQ1} = \infty. \quad [1]$$

$$\text{Thus, } R_{icm} \approx (1+\beta)R_o = (101)(954k) = 96.4M\Omega \quad [2, 1]$$

Answers to QUESTION 2 [20 marks]

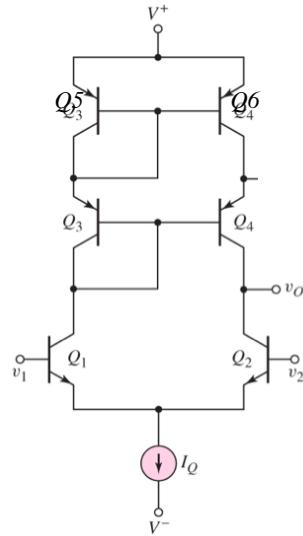- (a) Cascode current source labeled for *pnp* transistors [2 marks]
 Labelled the R_{OAL} [1 mark]



- (b) Calculate R_{OAL} :
 $I_O = I_{CQ}/2 = 0.2m/2 = 0.1 \text{ mA}$ [1 mark]
 $r_{o4} = V_{AP}/I_O = 120/0.1m = 1.200 \text{ M}\Omega$ [1 mark]
 $R_{OAL} = \beta r_{o4} = (80)(1.200\text{M}) = 96.00 \text{ M}\Omega$ [2 marks]

With two-transistor current source,

$$R_{OAL} = r_{o4} = V_{AP}/I_O = 120/0.1m = 1.200 \text{ M}\Omega \quad [1 \text{ mark}]$$

Thus, the output resistance is smaller than the former [2 marks]

- (c) $v_O = g_m v_d R_O$ [1 mark]
 $R_O = R_{OAL} \parallel r_{o2}$ [1 mark]
 $r_{o2} = V_{AN}/I_O = 100/0.1m = 1.000 \text{ M}\Omega$ [1 mark]
 $R_O = 96\text{M} \parallel 1 \text{ M} = 0.9897 \text{ M}\Omega$ [1 mark]
 $g_{m2} = I_O/V_T = 0.1m/0.026 = 3.846 \text{ mA/V}$ [1 mark]
 $A_d = g_{m2} R_O = (3.846m)(0.9897\text{M}) = 3806$ [1 mark]
- (d) $v_O = A_d v_d = (3806)(10 \sin \omega t) \text{ m} = 38.06 \sin \omega t \text{ V}$ [2, 2 marks]

Answers to QUESTION 3(a) [10 marks]

- (i) Calculation of i_L , i_{Cp} , i_{Cn} , and v_I . [6 marks]
- $$v_O = -4 \text{ V} = i_L R_L$$
- $\Rightarrow i_L = v_O / R_L = (-4\text{V}) / (1\text{k}\Omega) = -4 \text{ mA}$ [0.5]
- Therefore, Q_p is conducting and Q_n is OFF.
- Approximate value $i_L \approx i_{Cp} = I_S \exp(V_{EBP}/V_T) = 4 \text{ mA}$ [0.5]
- $$V_{EBP} = V_T \ln(i_{Cp}/I_S) = (26\text{m}) \ln(4\text{m} / 2 \times 10^{-15}) = 0.7364 \text{ V}$$
- [0.5]
- $$V_{BEN} = V_{BB} - V_{EBP} = 1.4 - 0.7364 = 0.6636 \text{ V}$$
- [0.5]
- $\Rightarrow i_{Cn} = I_S \exp(V_{BEN}/V_T) = (2 \times 10^{-15}) \exp(0.6636/0.026) = 0.2429 \text{ mA}$ [0.5]
- $$i_{Cn} = i_{Cp} + i_L$$
- [0.5]
- Actual value of $i_{Cp} = i_{Cn} - i_L = 0.2429 \text{ m} - (-4\text{m}) = 4.2429 \text{ mA}$ [0.5]
- $$V_{EBP} = V_T \ln(i_{Cp}/I_S) = (26\text{m}) \ln(4.2429 \text{ m} / 2 \times 10^{-15}) = 0.73796 \text{ V}$$
- [0.5]
- $$V_{BEN} = V_{BB} - V_{EBP} = 1.4 - 0.73796 = 0.66204 \text{ V}$$
- [0.5]
- $\Rightarrow i_{Cn} = I_S \exp(V_{BEN}/V_T) = (2 \times 10^{-15}) \exp(0.66204/0.026) = 0.2288 \text{ mA}$ [0.5]
- $v_I = v_O + V_{BEN} - V_{BB} / 2 = -4 + 0.66204 - 0.7 = -4.03796 \text{ V}$
- OR $v_I = v_O - V_{EBP} + V_{BB} / 2 = -4 - 0.73796 + 0.7 = -4.03796 \text{ V}$ [1]

- (ii) Calculation of power dissipation in transistor Q_n and Q_p : [4 marks]

$$P_{Qn} = i_{Cn} V_{CEn}$$
 [1]
$$V_{CEn} = +V_{CC} - v_O = +6 - (-4) = 10 \text{ V}$$
 [0.5]

$\Rightarrow P_{Qn} = (0.2288 \text{ mA})(10 \text{ V}) = 2.288 \text{ mW}$ [0.5]

$$P_{Qp} = i_{Cp} V_{ECp}$$
 [1]
$$V_{ECp} = v_O - (-V_{CC}) = -4 - (-6) = 2 \text{ V}$$
 [0.5]

$\Rightarrow P_{Qp} = (4.2429 \text{ mA})(2 \text{ V}) = 8.4858 \text{ mW}$ [0.5]

Answers to QUESTION 3(b) [10 marks]

$$R_i = r_{\pi 1} + (1 + \beta) r_{\pi 2}$$
 [1 mark]
$$r_{\pi 2} = \beta v_T / I_Q = (120)(0.026) / 1\text{m} = 3.120 \text{ k}\Omega$$
 [1 mark]
$$I_{C1} = \frac{\beta}{1+\beta} I_{B2} = I_Q / (1 + \beta) = 1\text{m} / (1 + 120) = 8.26 \mu\text{A}$$
 [1 mark]
$$r_{\pi 1} = \beta v_T / I_{C1} = (120)(0.026) / (1\text{m} / (1 + 120)) = 377.52 \text{ k}\Omega$$
 [1 mark]

Thus, $R_i = 377.52\text{k} + (1 + 120)(3.12\text{k}) = \underline{755.04 \text{ k}\Omega}$ [1 mark]

$$R_O = 5\text{k} \parallel (r_{\pi 3} + 10\text{k}) / (1 + \beta)$$
 [2 marks]
$$R_{\pi 3} = \beta v_T / I_{C3} = (120)(0.026) / 2\text{m} = 1.56 \text{ k}\Omega$$
 [1 mark]

Thus, $R_O = 5\text{k} \parallel (1.56\text{k} + 10\text{k}) / (121)$

$$= 5\text{k} \parallel 0.095537\text{k} = \underline{0.09375 \text{ k}\Omega}$$
 [2 marks]

Answers to QUESTION 4(a) [10 marks]**Q4(a)(i) [5 marks]**

$$I_{C10} = I_{C9} = 10 \times 10^{-6} \text{ A}, I_{REF} = 1 \times 10^{-3} \text{ A} \quad [1]$$

$$R_4 = \frac{V_T}{I_{C10}} \ln \frac{I_{REF}}{I_{C10}} \quad [1]$$

$$R_4 = \frac{0.026}{10 \times 10^{-6}} \ln \frac{1 \times 10^{-3}}{10 \times 10^{-6}} = 11.97 \text{ k}\Omega \quad [0.5]$$

$$R_5 = \frac{V^+ - V_{EB12} - V_{BE11} - V^-}{I_{REF}} \quad [1]$$

$$V_{EB12} = V_{BE11} = V_T \ln \frac{I_{REF}}{I_S} = 0.026 \ln \frac{1 \times 10^{-3}}{10^{-14}} = 0.658 \text{ V} \quad [1]$$

$$R_5 = \frac{15 - 0.658 - 0.658 - (-15)}{1 \text{ m}} = 28.68 \text{ k}\Omega \quad [0.5]$$

Q4(a)(ii) [3 marks]

$$I_{C1} = \frac{I_{C8}}{2} = \frac{I_{C9}}{2} = \frac{10 \mu\text{A}}{2} = 5 \mu\text{A} \quad [1]$$

$$I_{C6} = I_{C1} = 5 \mu\text{A} \quad [0.5]$$

$$r_{\pi 6} = \frac{\beta V_T}{I_{C6}} = \frac{200 \times 0.026}{5 \mu} = 1.04 \text{ M}\Omega \quad [1.5]$$

Q4(a)(iii) [2 marks]**Apply balanced concept, $\text{vc6} = \text{vc5}$**

$$\text{Vc6} = \text{Vc5} \quad [0.5]$$

$$V_{C6} = V_{C5} = V^- + I_{C6} R_2 + V_{BE6} + V_{BE7} \quad [1]$$

$$V_{C6} = (-15) + (5 \mu\text{A})(1 \text{ k}\Omega) + 0.6 + 0.6 = -13.795 \text{ V} \quad [0.5]$$

Answers to QUESTION 4(b) [10 marks]**Q4(b)(i) [4 marks]**

$$I_Q = I_{D6} = I_{D5}$$

1

$$I_{D5} = K_p (V_{SG5} + V_{TP})^2 = (100\mu\text{A}/\text{V}^2) \times (1.5 - 0.5)^2 = 100\mu\text{A}$$

2

$$\Rightarrow I_Q = I_{D5} = 100\mu\text{A} = 0.1\text{mA}$$

1

1

Q4(b)(ii) [6 marks]

$$A_d = g_{m2}(r_{o2} \parallel r_{o4})$$

1

$$g_{m2} = \sqrt{2K_p I_Q} = \sqrt{2(100\mu)(100\mu)} = 141.42\mu\text{A/V}$$

0.5

$$r_{o2} = \frac{1}{\lambda_p I_{D2}} = \frac{1}{0.02 \times 50\mu} = 1\text{M}\Omega$$

0.5

0.5

$$r_{o4} = \frac{1}{\lambda_n I_{D4}} = \frac{1}{0.01 \times 50\mu} = 2\text{M}\Omega$$

0.5

0.5

$$A_d = (141.42\mu)(1\text{M} \parallel 2\text{M}) = 94.286$$

0.5

0.5

$$A_{v2} = g_{m7}(r_{o7} \parallel r_{o8})$$

$$g_{m7} = 2\sqrt{K_{n7} I_{D7}} = 2\sqrt{(125\mu)(100\mu)} = 223.6\mu\text{A/V}$$

0.5

0.5

$$r_{o7} = \frac{1}{\lambda_n I_{D7}} = \frac{1}{0.01 \times 100\mu} = 1\text{M}\Omega$$

0.5

0.5

$$r_{o8} = \frac{1}{\lambda_p I_{D8}} = \frac{1}{0.02 \times 100\mu} = 0.5\text{M}\Omega$$

0.5

0.5

$$A_{v2} = (223.6\mu)(1\text{M} \parallel 0.5\text{M}) = 74.53$$

0.5

0.5

$$A_v = A_d A_{v2} = 94.286 \times 74.53 = 7027.45$$

1

1

Answers to QUESTION 5(a) [6 marks]

Calculation:

$$A_v = 1 + R_2/(R_{1F} + R_{1V}) \quad [1]$$

$$R_2 = 250 \text{ k}\Omega.$$

R_{1F} is a fixed-value resistor.

R_{1V} is a potentiometer.

Gain is maximum, i.e. $A_v(\max) = 51$, when $R_{1V} = 0 \Omega$.

$$A_v(\max) = 51 = 1 + R_2/(R_{1F} + R_{1V}) = 1 + 250\text{k}/(R_{1F} + 0) \quad [1]$$


$$R_{1F} = 5 \text{ k}\Omega \quad [0.5]$$

Gain is minimum, i.e. $A_v(\min) = 11$, when R_{1V} is maximum.

$$A_v(\min) = 11 = 1 + R_2/(R_{1F} + R_{1V}) = 1 + 250\text{k}/(5\text{k} + R_{1V}) \quad [1]$$

$$R_{1V} = 20 \text{ k}\Omega \quad [0.5]$$

Circuit: [2]

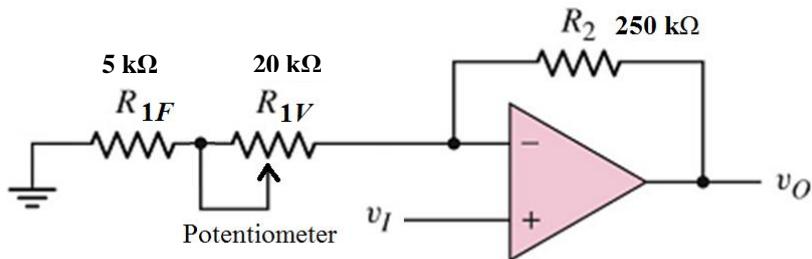Answers to QUESTION 5(b) [4 marks]

$R_1 = 75 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, $R_3 = 80 \text{ k}\Omega$, and $R_4 = 200 \text{ k}\Omega$.

$$v_{O1} = (-R_2/R_1)v_I \quad [1]$$

$$v_{O1} / v_I = -(100\text{k}/75\text{k}) = -1.333 \text{ V/V} \quad [1]$$

$$v_O = (-R_4/R_3)v_{O1} = (-R_4/R_3)(-R_2/R_1)v_I \quad [1]$$

$$\begin{aligned} v_O / v_I &= (R_4/R_3)(R_2/R_1) \\ &= [(200\text{k}/80\text{k})(100\text{k}/75\text{k})] = 3.333 \text{ V/V} \quad [1] \end{aligned}$$

Answers to QUESTION 5(c) [10 marks]

Q5(c)(i) $R_3 = R_4 = 100 \text{ k}\Omega$

$$A_v = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1 + R_{1POT}} \right) = \frac{100k}{100k} \left(1 + \frac{2R_2}{R_1 + R_{1POT}} \right) = \left(1 + \frac{2R_2}{R_1 + R_{1POT}} \right)$$

[1]

A_v is maximum (i.e. $A_v = 100$) when $R_{1POT} = 0$, i.e.

$$100 = \left(1 + \frac{2R_2}{R_1 + 0} \right) \quad [1]$$

$$99 R_1 = 2 R_2 \quad \text{Eqn 1} \quad [0.5]$$

A_v is minimum (i.e. $A_v = 10$) when $R_{1POT} = 100 \text{ k}\Omega$, i.e.

$$10 = \left(1 + \frac{2R_2}{R_1 + 100k} \right) \quad [1]$$

$$9(R_1 + 100k) = 2R_2 \quad \text{Eqn 2} \quad [0.5]$$

$$\{\text{Eqn 1}\} = \{\text{Eqn 2}\}$$

$$99 R_1 = 9 R_1 + 900k \quad [1]$$

$$\Rightarrow R_1 = 10 \text{ k}\Omega \quad [1]$$

$$\Rightarrow R_2 = (99 R_1) / 2 = 495 \text{ k}\Omega \quad [1]$$

Q5(c)(ii) $v_{I1} = 1.45 \text{ V}, v_{I2} = 1.13 \text{ V}, R_4 = 2 R_3, R_{1POT} = 40 \text{ k}\Omega$

$$A_v = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1 + R_{1POT}} \right) = \frac{2R_3}{R_3} \left(1 + \frac{2(495k)}{10k + 40k} \right) = 41.6 \quad [1.5]$$

$$v_O = A_v(v_{I2} - v_{I1}) = (41.6)(1.13 - 1.45) = -13.312V \quad [1.5]$$