



**COLLEGE OF ENGINEERING
PUTRAJAYA CAMPUS
FINAL EXAMINATION
SEMESTER 2 2016 / 2017**

PROGRAMME : Bachelor of Electrical & Electronics Engineering (Honours)
Bachelor of Electrical Power Engineering (Honours)

SUBJECT CODE : EEEB273

SUBJECT : ELECTRONIC ANALYSIS AND DESIGN II

DATE : January/February 2017

TIME : 3 hours

INSTRUCTIONS TO CANDIDATES:

1. This paper contains **FIVE (5)** questions in **NINE (9)** pages.
2. Answer **ALL** questions.
3. Write **ALL** answers in the answer booklet provided. Use **pen** to write your answer.
4. Write answer to different question on a **new page**.
5. Show clearly all calculations, complete with proper **Unit** for every parameter.

THIS QUESTION PAPER CONSISTS OF NINE (9) PRINTED PAGES INCLUDING THIS COVER PAGE.

Question 1 [20 marks]

Consider a BJT differential amplifier with the circuit shown in **Figure 1**. The transistor parameters are $\beta = 100$, $V_A = \infty$ for Q_1 and Q_2 , and $V_A = 100$ V for Q_3 and Q_4 .

At input voltages of $v_1 = v_2 = 0$, $I_{C4} = 200 \mu\text{A}$, and $I_1 = 0.5 \text{ mA}$, output voltage is $v_{O2} = 8 \text{ V}$.

Neglect the base currents.

- (a) **Find** the output resistance (R_O) of the current source. [8 marks]
- (b) **Determine** the value of R_C . [4 marks]
- (c) **Find** the differential-mode input resistance, R_{id} . [4 marks]
- (d) **Find** the common-mode input resistance, R_{icm} . [4 marks]

 


Figure 1

Question 2 [20 marks]

Figure 2 shows a BJT differential amplifier with a bias current, $I_Q = 0.2 \text{ mA}$. The differential amplifier increases its gain by applying a BJT cascode current source comprising **pnp** transistors as an active load. The circuit parameters are $V^+ = 10 \text{ V}$ and $V^- = -10 \text{ V}$. The transistor parameters are given as $\beta = 80$, $V_{BE(\text{on})} = 0.7 \text{ V}$, $V_{AN} = 100 \text{ V}$, and $V_{AP} = 120 \text{ V}$.

- (a) **Draw** the differential amplifier circuit with the added cascode current source as the active load. [3 marks]
- (b) **Determine** the output resistance, R_{OAL} , of the cascode current source. Later, **compare** the output difference for the circuit above should the active load is replaced by a two-transistor current source. [7 marks]
- (c) **Find** the differential-mode voltage gain, A_d , of the circuit. [6 marks]
- (d) **Calculate** the output voltage of the circuit with a $v_d = 10 \sin(\omega t) \text{ mV}$. [4 marks]

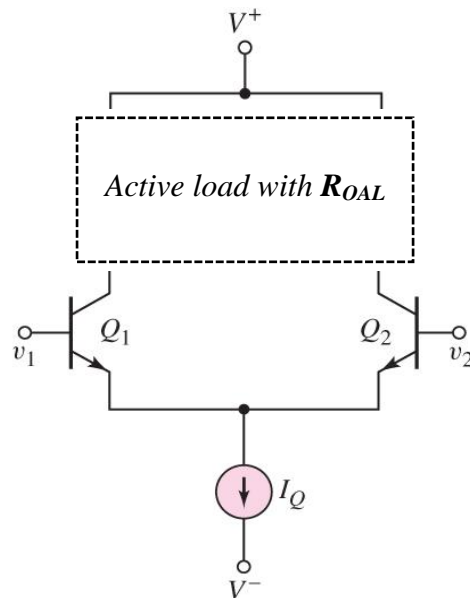


Figure 2

Question 3 [20 marks]

(a) A class-AB output stage with BJTs is shown in **Figure 3**. Reverse saturation current for every transistor is $I_S = 2 \times 10^{-15}$ A. Assume $+V_{CC} = +6$ V and $-V_{CC} = -6$ V. Let $R_L = 1$ k Ω and $V_{BB} = 1.40$ V. For the case of the output voltage $v_O = -4$ V:

- (i) Determine i_L , i_{Cp} , i_{Cn} , and v_I . [6 marks]
- (ii) Calculate the power dissipated in transistor Q_n and Q_p . [4 marks]

 


Figure 3

 


Figure 4

(b) **Figure 4** shows a circuit with the transistor parameters as $\beta = 120$, and $V_A = \infty$. The bias currents in the transistors are indicated on the figure. Determine the input resistance (R_i) and the output resistance (R_o) of the circuit. [10 marks]

Question 4 [20 marks]

- (a) Study the input stage and bias circuit of the 741 op-amp in **Figure 5**. The circuit parameters are $V^+ = +15\text{ V}$, $V^- = -15\text{ V}$, and $I_{C9} = 10\text{ }\mu\text{A}$. The transistor parameters are $\beta = 200$, $V_{BE6} = V_{BE7} = 0.6\text{ V}$, and the reverse saturation current $I_S = 10^{-14}\text{ A}$ for each transistor. Ignore the base currents and assume the DC currents in the input stage are **exactly balanced**.

Given that the current flowing through resistor R_5 is **1 mA**.

- (i) **Determine** the values of resistor R_4 and R_5 . [5 marks]
- (ii) **Calculate** values for current I_{C1} and resistance $r_{\pi6}$. [3 marks]
- (iii) **Determine** the DC voltage at the collector of Q_6 (i.e. V_{C6}). [2 marks]

 


Figure 5

- (b) Consider the MC14573 op-amp in **Figure 6**. Assume transistor parameters of $V_{TN} = 0.5 \text{ V}$, $V_{TP} = -0.5 \text{ V}$, $K_n = 125 \mu\text{A/V}^2$, $K_p = 100 \mu\text{A/V}^2$, $\lambda_n = 0.01 \text{ V}^{-1}$, $\lambda_p = 0.02 \text{ V}^{-1}$ and the circuit parameters of $V^+ = +10 \text{ V}$ and $V^- = -10 \text{ V}$.

Given that $V_{SG5} = 1.5 \text{ V}$:

- (i) **Find** the DC bias currents I_Q . [4 marks]
- (ii) **Determine** the overall small signal differential-mode voltage gain for the MC14573 op-amp in **Figure 6**. Gain for the output stage consists of transistor M_7 and M_8 is given

by equation
$$A_{v2} = g_{m7}(r_{o7} \parallel r_{o8}).$$
 [6 marks]

 
 


Figure 6

Question 5 [20 marks]

- (a) With a **feedback resistor (R_2)** of **250 k Ω** , **design** an amplifier using op-amp in non-inverting configuration with a **closed-loop gain** which can be **varied from 11 to 51 V/V**. The closed-loop gain can be varied using a **potentiometer (R_{1V})** and a **fixed-value resistor (R_{1F})**. **Draw and label clearly** your circuit design. [6 marks]

- (b) Consider the two inverting op-amp circuit connected in cascade as shown in **Figure 7**. Let **$R_1 = 75 \text{ k}\Omega$** , **$R_2 = 100 \text{ k}\Omega$** , **$R_3 = 80 \text{ k}\Omega$** , and **$R_4 = 200 \text{ k}\Omega$** . Calculate **$v_{O1}/v_I$** and **$v_O/v_I$** for the circuit. [4 marks]

**Figure 7**

- (c) **Figure 8** shows a design for an **instrumentation amplifier** using op-amps. In the design, R_{1POT} is a **100 kΩ potentiometer** (or a variable resistor) used to provide variable resistance so that differential voltage gain (A_v) of the instrumentation amplifier can be adjustable. With analysis, it can be shown that output voltage (v_o) is given by

$$v_o = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1 + R_{1POT}} \right) (v_{I2} - v_{I1})$$

 


Figure 8

- (i) With $R_3 = R_4 = 100 \text{ k}\Omega$, **design an instrumentation amplifier** using the circuit as shown in the **Figure 8** to realize a differential voltage gain (A_v) adjustable from **10 to 100**. (Hints: A_v is smallest when R_{1POT} is at maximum value, and vice versa. You are required to determine the value of R_1 and R_2 in the circuit). [7 marks]
- (ii) **Calculate** A_v and v_o when $v_{I1} = 1.45 \text{ V}$, $v_{I2} = 1.13 \text{ V}$, $R_4 = 2 R_3$, R_{1POT} is set at **40 kΩ**, and the values of R_1 and R_2 are found in step (i) above. [3 marks]

-END OF QUESTION PAPER-

APPENDIX:

A) BASIC FORMULA FOR TRANSISTOR

BJT

$$i_C = I_S e^{v_{BE}/V_T} \quad ; \text{NPN}$$

$$i_C = I_S e^{v_{EB}/V_T} \quad ; \text{PNP}$$

$$i_C = \beta i_B = \frac{\beta}{\beta + 1} i_E$$

$$i_E = i_B + i_C$$

;Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

MOSFET

;N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k'_n}{2} \cdot \frac{W}{L}$$

;P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k'_p}{2} \cdot \frac{W}{L}$$

;Small signal


$$g_m = 2\sqrt{K_n I_{DQ}} \quad ; \text{N – MOSFET}$$

$$g_m = 2\sqrt{K_p I_{DQ}} \quad ; \text{P – MOSFET}$$


$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

B) HYBRID- π EQUIVALENT CIRCUITS

BJT

 

MOSFET

 

C) QUADRATIC FORMULA

$$Ax^2 + Bx + C = 0 \quad \rightarrow \quad x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$