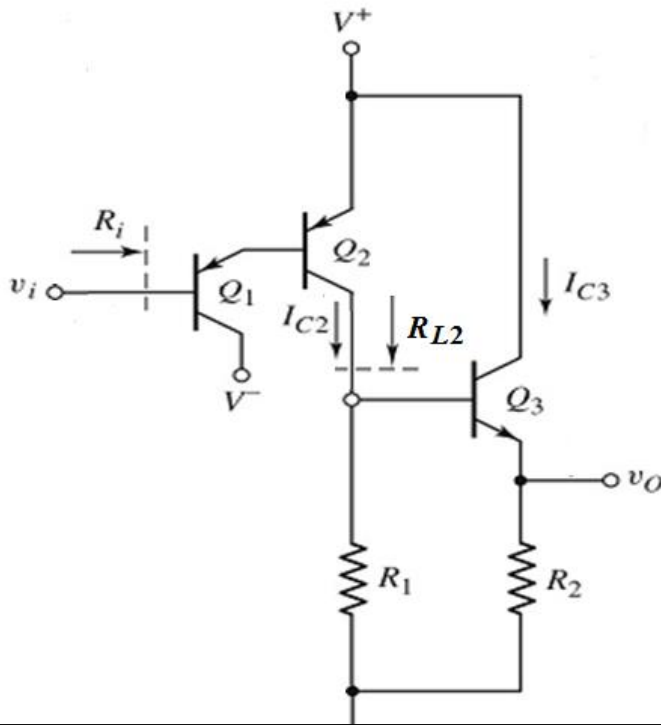


Question:

Study the gain stage and simple output stage circuit shown in **Figure 1** carefully. The transistor parameters are: $\beta = 100$ and $V_A = 120$ V. Neglect base currents.

Let $R_1 = 50$ k Ω , $R_2 = 5$ k Ω , $I_{C2} = 0.5$ mA, and $I_{C3} = 1$ mA. Determine the input resistance (R_i) of the gain stage and the equivalent load resistance of the gain stage connected to the collector of Q_2 , i.e. R_{L2} shown in the **Figure 1**. [10 marks]

Write your answer using pen, with proper Units for all the parameters.



$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$


R_i	$= r_{\pi 1} + (1 + \beta) r_{\pi 2}$	[2]
$r_{\pi 2}$	$= (\beta V_T) / I_{C2} = (100 \times 0.026) / 0.5\text{m} = 5.2 \text{ k}\Omega$	[1]
I_{C1}	$= I_{C2} / (1 + \beta)$	[1]
$r_{\pi 1}$	$= (\beta V_T) / I_{C1} = (\beta(1 + \beta) V_T) / I_{C2}$ $= (100 \times 101 \times 0.026) / 0.5\text{m} = 525.2 \text{ k}\Omega$	[1]
R_i	$= r_{\pi 1} + (1 + \beta) r_{\pi 2}$ $= 525.2\text{k} + (101)(5.2\text{k}) = 1050.4 \text{ k}\Omega$	[1]
R_{L2}	$= R_1 \parallel [r_{\pi 3} + (1 + \beta) R_2]$	[2]
$r_{\pi 3}$	$= (\beta V_T) / I_{C3} = (100 \times 0.026) / 1\text{m} = 2.6 \text{ k}\Omega$	[1]
R_{L2}	$= (50\text{k}) \parallel [2.6\text{k} + (1 + 100)(5\text{k})] = 45.51 \text{ k}\Omega$	[1]

Question:

Study the gain stage and simple output stage circuit shown in **Figure 1** carefully. The transistor parameters are: $\beta = 100$ and $V_A = 120$ V. Neglect base currents.

Let $R_1 = 40$ k Ω , $R_2 = 8$ k Ω , $I_{C2} = 0.4$ mA, and $I_{C3} = 1$ mA. Determine the input resistance (R_i) of the gain stage and the equivalent load resistance of the gain stage connected to the collector of Q_2 , i.e. R_{L2} shown in the **Figure 1**. [10 marks]

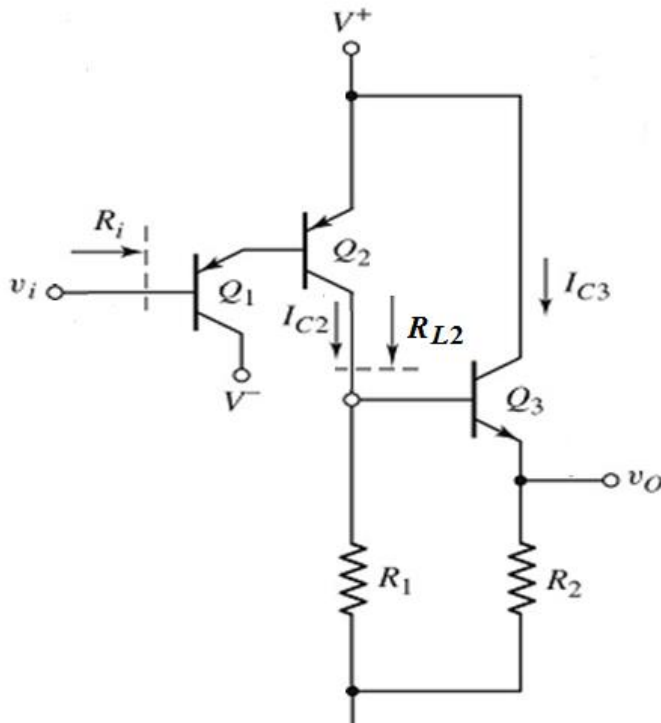Write your answer using pen, with proper Units for all the parameters.



$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

$$R_i = r_{\pi 1} + (1 + \beta) r_{\pi 2} \quad [2]$$

$$r_{\pi 2} = (\beta V_T) / I_{C2} = (100 \times 0.026) / 0.4 \text{ m} = 6.5 \text{ k}\Omega \quad [1]$$

$$I_{C1} = I_{C2} / (1 + \beta) \quad [1]$$

$$r_{\pi 1} = (\beta V_T) / I_{C1} = (\beta(1 + \beta) V_T) / I_{C2} = (100 \times 101 \times 0.026) / 0.4 \text{ m} = 656.5 \text{ k}\Omega \quad [1]$$

$$R_i = r_{\pi 1} + (1 + \beta) r_{\pi 2} = 656.5 \text{ k} + (101)(6.5 \text{ k}) = 1313 \text{ k}\Omega \quad [1]$$

$$R_{L2} = R_1 \parallel [r_{\pi 3} + (1 + \beta) R_2] \quad [2]$$

$$r_{\pi 3} = (\beta V_T) / I_{C3} = (100 \times 0.026) / 1 \text{ m} = 2.6 \text{ k}\Omega \quad [1]$$


$$R_{L2} = (40 \text{ k}) \parallel [2.6 \text{ k} + (1 + 100)(8 \text{ k})] = 38.12 \text{ k}\Omega \quad [1]$$

Question:

Study the gain stage and simple output stage circuit shown in **Figure 1** carefully. The transistor parameters are: $\beta = 100$ and $V_A = 120$ V. Neglect base currents.

Let $R_1 = 55$ k Ω , $R_2 = 8$ k Ω , $I_{C2} = 0.3$ mA, and $I_{C3} = 1$ mA. Determine the input resistance (R_i) of the gain stage and the equivalent load resistance of the gain stage connected to the collector of Q_2 , i.e. R_{L2} shown in the **Figure 1**. [10 marks]

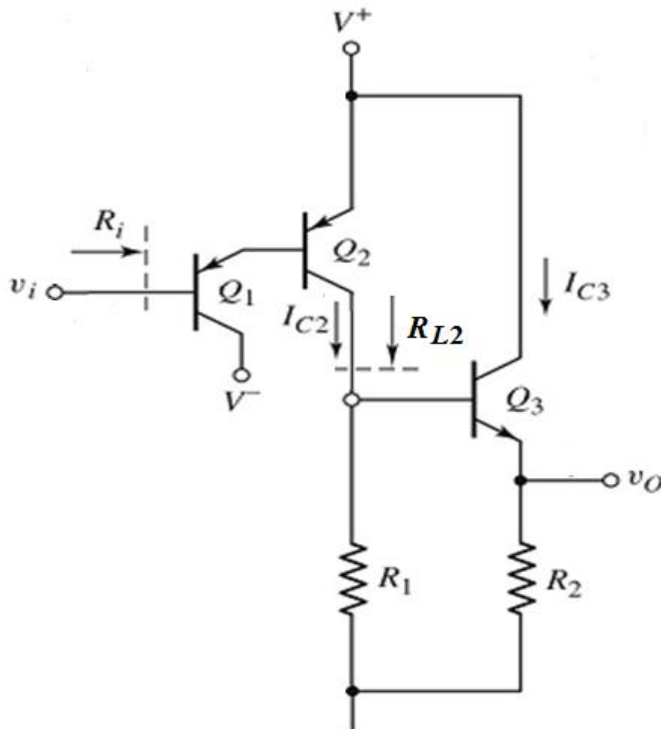Write your answer using pen, with proper Units for all the parameters.



$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$


R_i	$= r_{\pi 1} + (1 + \beta) r_{\pi 2}$	[2]
$r_{\pi 2}$	$= (\beta V_T) / I_{C2} = (100 \times 0.026) / 0.3\text{m} = 8.667 \text{ k}\Omega$	[1]
I_{C1}	$= I_{C2} / (1 + \beta)$	[1]
$r_{\pi 1}$	$= (\beta V_T) / I_{C1} = (\beta(1 + \beta) V_T) / I_{C2}$ $= (100 \times 101 \times 0.026) / 0.3\text{m} = 875.333 \text{ k}\Omega$	[1]
R_i	$= r_{\pi 1} + (1 + \beta) r_{\pi 2}$ $= 875.333\text{k} + (101)(8.667\text{k}) = 1750.666 \text{ k}\Omega$	[1]
R_{L2}	$= R_1 \parallel [r_{\pi 3} + (1 + \beta) R_2]$	[2]
$r_{\pi 3}$	$= (\beta V_T) / I_{C3} = (100 \times 0.026) / 1\text{m} = 2.6 \text{ k}\Omega$	[1]
R_{L2}	$= (55\text{k}) \parallel [2.6\text{k} + (1 + 100)(8\text{k})] = 51.5 \text{ k}\Omega$	[1]

Question:

Study the gain stage and simple output stage circuit shown in **Figure 1** carefully. The transistor parameters are: $\beta = 100$ and $V_A = 120$ V. Neglect base currents.

Let $R_1 = 45$ k Ω , $R_2 = 10$ k Ω , $I_{C2} = 0.6$ mA, and $I_{C3} = 1$ mA. Determine the **input resistance (R_i)** of the gain stage and the **equivalent load resistance** of the gain stage connected to the collector of Q_2 , i.e. R_{L2} shown in the **Figure 1**. [10 marks]

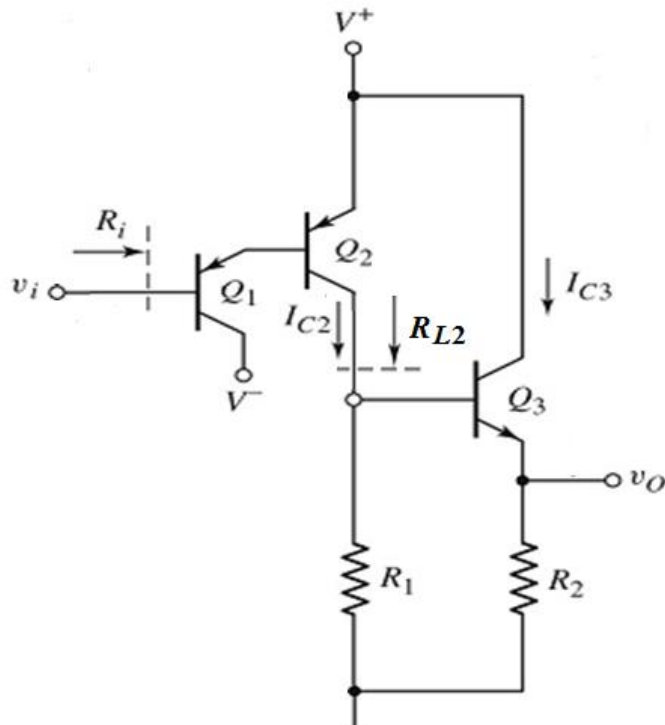Write your answer using pen, with proper Units for all the parameters.



$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

R_i	$= r_{\pi 1} + (1 + \beta) r_{\pi 2}$	[2]
$r_{\pi 2}$	$= (\beta V_T) / I_{C2} = (100 \times 0.026) / 0.6\text{m} = 4.333 \text{ k}\Omega$	[1]
I_{C1}	$= I_{C2} / (1 + \beta)$	[1]
$r_{\pi 1}$	$= (\beta V_T) / I_{C1} = (\beta(1 + \beta) V_T) / I_{C2}$ $= (100 \times 101 \times 0.026) / 0.6\text{m} = 437.667 \text{ k}\Omega$	[1]
R_i	$= r_{\pi 1} + (1 + \beta) r_{\pi 2}$ $= 437.667\text{k} + (101)(4.333\text{k}) = 875.333 \text{ k}\Omega$	[1]
R_{L2}	$= R_1 \parallel [r_{\pi 3} + (1 + \beta) R_2]$	[2]
$r_{\pi 3}$	$= (\beta V_T) / I_{C3} = (100 \times 0.026) / 1\text{m} = 2.6 \text{ k}\Omega$	[1]
R_{L2}	$= (45\text{k}) \parallel [2.6\text{k} + (1 + 100)(10\text{k})] = 43.08 \text{ k}\Omega$	[1]