

Question:

Consider the MC14573 op-amp in **Figure 1**. Assume transistor parameters of $V_{TN} = 0.5$ V, $K_n = 125 \mu\text{A/V}^2$ and $\lambda_n = 0.01 \text{ V}^{-1}$ for N-MOSFET; and $V_{TP} = -0.5$ V, $K_p = 100 \mu\text{A/V}^2$, and $\lambda_p = 0.02 \text{ V}^{-1}$ for P-MOSFET. Given that $V_{SG5} = 1.5$ V:

- (a) Find the quiescent bias currents for all transistors in the **Figure 1**. [4 marks]
 (b) Determine the overall small signal differential-mode voltage gain for the MC14573 op-amp in the **Figure 1**. Gain for the output stage consists of transistor M_7 and M_8 is given by equation:
 $A_{v2} = -g_{m7}(r_{o7} \parallel r_{o8})$. [6 marks]

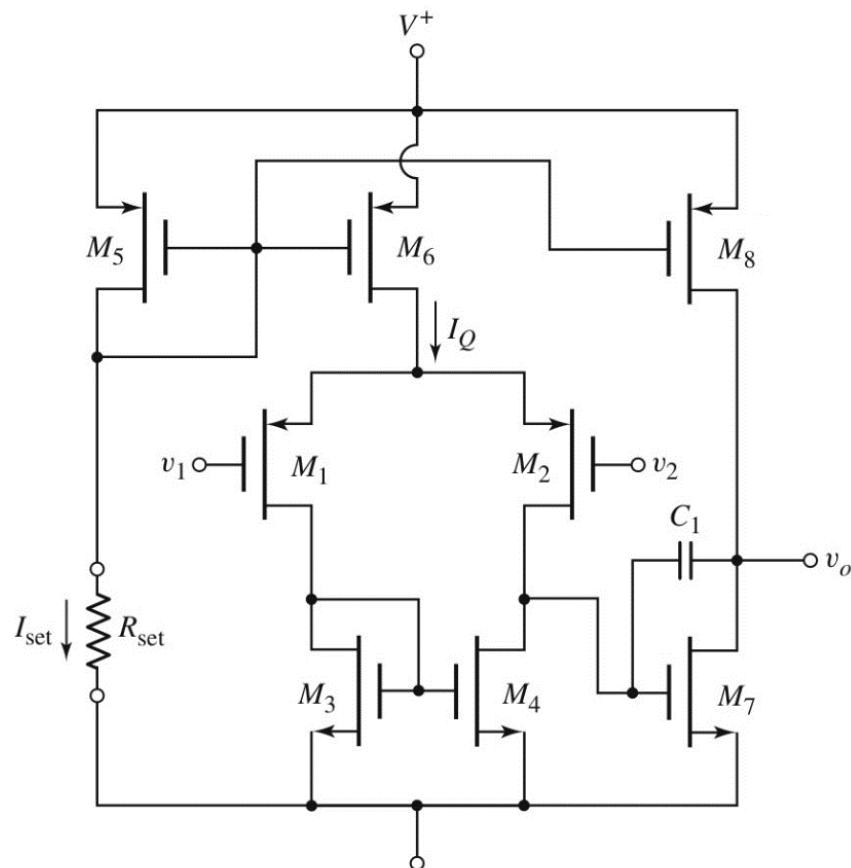


Figure 1

Answer:

; N - MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k_n}{2} \cdot \frac{W}{L}$$

; P - MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k_p}{2} \cdot \frac{W}{L}$$

; Small signal

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$r_o \equiv \frac{1}{\lambda I_{DQ}}$$

Q(a)

$$I_{D5} = K_{p5} (V_{SG5} + V_{TP})^2 = (100) \times (1.5 - 0.5)^2 = 100 \text{ A} \quad [2]$$

$$I_Q = I_{D6} = I_{D7} = I_{D8} = I_{D5} = 100 \text{ A} \quad [1]$$

$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = I_Q / 2 = 50 \text{ A} \quad [1]$$

Q(b)

$$A_d = g_{m2} (r_{o2} \| r_{o4}) \quad [1]$$

$$g_{m2} = \sqrt{2K_p I_Q} = \sqrt{2(100)(100)} = 141.42 \text{ A/V} \quad [0.5]$$

$$r_{o2} = \frac{1}{\lambda_p I_{D2}} = \frac{1}{0.02 \times 50} = 1 \text{ M} \quad [0.5]$$

$$r_{o4} = \frac{1}{\lambda_n I_{D4}} = \frac{1}{0.01 \times 50} = 2 \text{ M} \quad [0.5]$$

$$A_d = (141.42) (1 \text{ M} \| 2 \text{ M}) = 94.286 \quad [0.5]$$

$$A_{v2} = -g_{m7} (r_{o7} \| r_{o8})$$

$$g_{m7} = 2\sqrt{K_{n7} I_{D7}} = 2\sqrt{(125)(100)} = 223.6 \text{ A/V} \quad [0.5]$$

$$r_{o7} = \frac{1}{\lambda_n I_{D7}} = \frac{1}{0.01 \times 100} = 1 \text{ M} \quad [0.5]$$

$$r_{o8} = \frac{1}{\lambda_p I_{D8}} = \frac{1}{0.02 \times 100} = 0.5 \text{ M} \quad [0.5]$$

$$A_{v2} = -(223.6) (1 \text{ M} \| 0.5 \text{ M}) = -74.53 \quad [0.5]$$

$$A_v = A_d A_{v2} = 94.286 \times (-74.53) = -7027.45 \quad [1]$$

Question:

Consider the MC14573 op-amp in **Figure 1**. Assume transistor parameters of $V_{TN} = 0.5$ V, $K_n = 125 \mu\text{A/V}^2$ and $\lambda_n = 0.01 \text{ V}^{-1}$ for N-MOSFET; and $V_{TP} = -0.5$ V, $K_p = 125 \mu\text{A/V}^2$, and $\lambda_p = 0.02 \text{ V}^{-1}$ for P-MOSFET. Given that $V_{SG5} = 1.5$ V:

- (a) Find the quiescent bias currents for all transistors in the **Figure 1**. [4 marks]
 (b) Determine the overall small signal differential-mode voltage gain for the MC14573 op-amp in the **Figure 1**. Gain for the output stage consists of transistor M_7 and M_8 is given by equation:
 $A_{v2} = -g_{m7}(r_{o7} \parallel r_{o8})$. [6 marks]

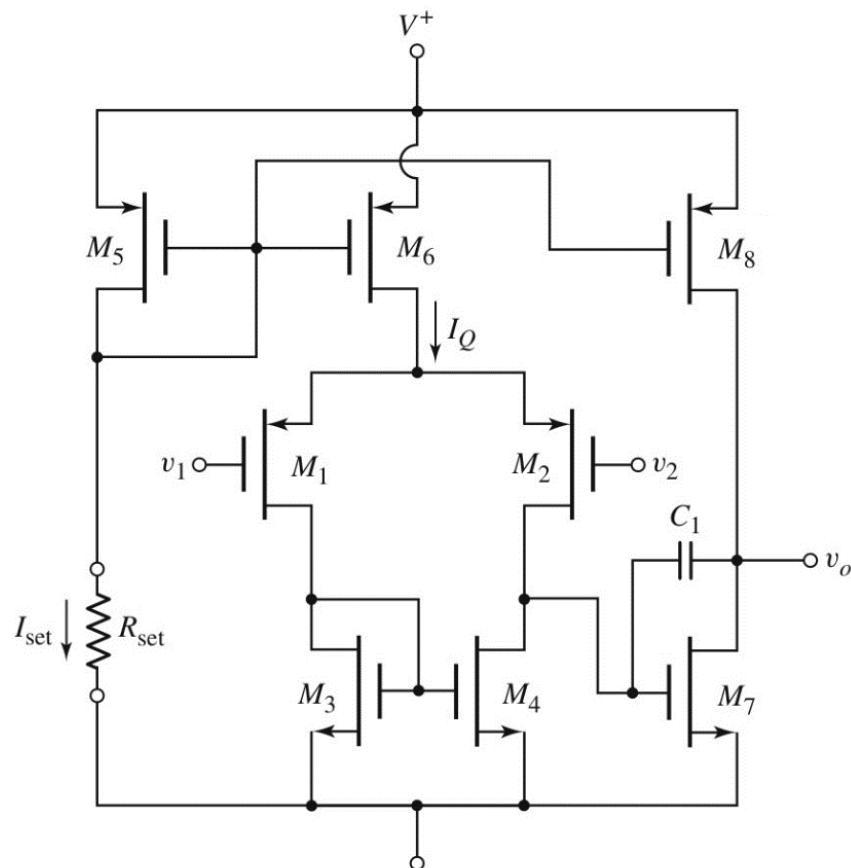


Figure 1

Answer:

; N - MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k_n}{2} \cdot \frac{W}{L}$$

; P - MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k_p}{2} \cdot \frac{W}{L}$$

; Small signal

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$r_o \equiv \frac{1}{\lambda I_{DQ}}$$

Q(a)

$$I_{D5} = K_{p5} (V_{SG5} + V_{TP})^2 = (125) \times (1.5 - 0.5)^2 = 125 \text{ A} \quad [2]$$

$$I_Q = I_{D6} = I_{D7} = I_{D8} = I_{D5} = 125 \text{ A} \quad [1]$$

$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = I_Q / 2 = 62.5 \text{ A} \quad [1]$$

Q(b)

$$A_d = g_{m2}(r_{o2} \| r_{o4}) \quad [1]$$

$$g_{m2} = \sqrt{2K_p I_Q} = \sqrt{2(125)(125)} = 176.77 \text{ A/V} \quad [0.5]$$

$$r_{o2} = \frac{1}{\lambda_p I_{D2}} = \frac{1}{0.02 \times 62.5} = 0.8 \text{ M} \quad [0.5]$$

$$r_{o4} = \frac{1}{\lambda_n I_{D4}} = \frac{1}{0.01 \times 62.5} = 1.6 \text{ M} \quad [0.5]$$

$$A_d = (176.77)(0.8 \text{ M} \| 1.6 \text{ M}) = 94.277 \quad [0.5]$$

$$A_{v2} = -g_{m7}(r_{o7} \| r_{o8})$$

$$g_{m7} = 2\sqrt{K_{n7} I_{D7}} = 2\sqrt{(125)(125)} = 250 \text{ A/V} \quad [0.5]$$

$$r_{o7} = \frac{1}{\lambda_n I_{D7}} = \frac{1}{0.01 \times 125} = 0.8 \text{ M} \quad [0.5]$$

$$r_{o8} = \frac{1}{\lambda_p I_{D8}} = \frac{1}{0.02 \times 125} = 0.4 \text{ M} \quad [0.5]$$

$$A_{v2} = -(250)(0.8 \text{ M} \| 0.4 \text{ M}) = -66.67 \quad [0.5]$$

$$A_v = A_d A_{v2} = 94.277 \times (-66.67) = -6285.13 \quad [1]$$

Question:

Consider the MC14573 op-amp in **Figure 1**. Assume transistor parameters of $V_{TN} = 0.5$ V, $K_n = 100 \mu\text{A/V}^2$ and $\lambda_n = 0.01 \text{ V}^{-1}$ for N-MOSFET; and $V_{TP} = -0.5$ V, $K_p = 100 \mu\text{A/V}^2$, and $\lambda_p = 0.02 \text{ V}^{-1}$ for P-MOSFET. Given that $V_{SG5} = 1.5$ V:

- (a) Find the quiescent bias currents for all transistors in the **Figure 1**. [4 marks]
 (b) Determine the overall small signal differential-mode voltage gain for the MC14573 op-amp in the **Figure 1**. Gain for the output stage consists of transistor M_7 and M_8 is given by equation:
 $A_{v2} = -g_{m7}(r_{o7} \parallel r_{o8})$. [6 marks]

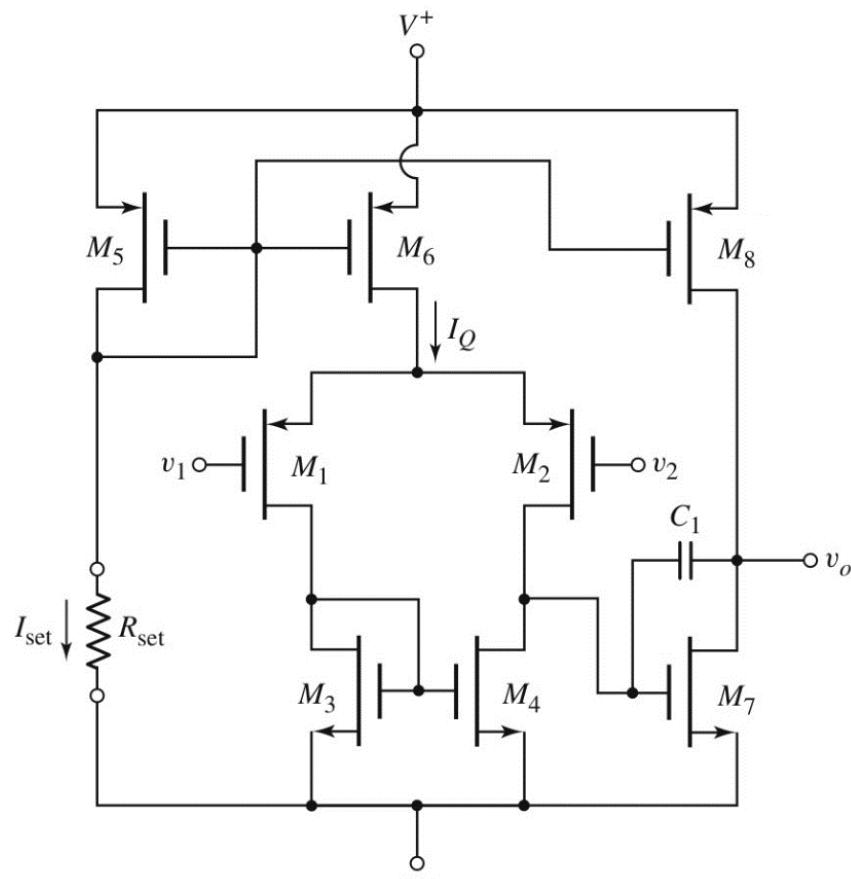


Figure 1

Answer:

; N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k_n}{2} \cdot \frac{W}{L}$$

; P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k_p}{2} \cdot \frac{W}{L}$$

; Small signal

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$r_o \equiv \frac{1}{\lambda I_{DQ}}$$

Q(a)

$$I_{D5} = K_{p5} (V_{SG5} + V_{TP})^2 = (100) \times (1.5 - 0.5)^2 = 100 \text{ A} \quad [2]$$

$$I_Q = I_{D6} = I_{D7} = I_{D8} = I_{D5} = 100 \text{ A} = 0.1 \text{ mA} \quad [1]$$

$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = I_Q / 2 = 50 \text{ A} = 0.5 \text{ mA} \quad [1]$$

Q(b)

$$A_d = g_{m2} (r_{o2} \parallel r_{o4}) \quad [1]$$

$$g_{m2} = \sqrt{2K_p I_Q} = \sqrt{2(100)(100)} = 141.42 \text{ A/V} \quad [0.5]$$

$$r_{o2} = \frac{1}{\lambda_p I_{D2}} = \frac{1}{0.02 \times 50} = 1 \text{ M} \quad [0.5]$$

$$r_{o4} = \frac{1}{\lambda_n I_{D4}} = \frac{1}{0.01 \times 50} = 2 \text{ M} \quad [0.5]$$

$$A_d = (141.42) (1\text{M} \parallel 2\text{M}) = 94.286 \quad [0.5]$$

$$A_{v2} = -g_{m7} (r_{o7} \parallel r_{o8})$$

$$g_{m7} = 2\sqrt{K_{n7} I_{D7}} = 2\sqrt{(100)(100)} = 200 \text{ A/V} \quad [0.5]$$

$$r_{o7} = \frac{1}{\lambda_n I_{D7}} = \frac{1}{0.01 \times 100} = 1 \text{ M} \quad [0.5]$$

$$r_{o8} = \frac{1}{\lambda_p I_{D8}} = \frac{1}{0.02 \times 100} = 0.5 \text{ M} \quad [0.5]$$

$$A_{v2} = -(200) (1\text{M} \parallel 0.5\text{M}) = -66.67 \quad [0.5]$$

$$A_v = A_d A_{v2} = 94.286 \times (-66.67) = -6285.73 \quad [1]$$

Question:

Consider the MC14573 op-amp in **Figure 1**. Assume transistor parameters of $V_{TN} = 0.5$ V, $K_n = 100 \mu\text{A/V}^2$ and $\lambda_n = 0.01 \text{ V}^{-1}$ for N-MOSFET; and $V_{TP} = -0.5$ V, $K_p = 125 \mu\text{A/V}^2$, and $\lambda_p = 0.02 \text{ V}^{-1}$ for P-MOSFET. Given that $V_{SG5} = 1.5$ V:

- (a) Find the quiescent bias currents for all transistors in the **Figure 1**. [4 marks]
 (b) Determine the overall small signal differential-mode voltage gain for the MC14573 op-amp in the **Figure 1**. Gain for the output stage consists of transistor M_7 and M_8 is given by equation:
 $A_{v2} = -g_{m7}(r_{o7} \parallel r_{o8})$. [6 marks]

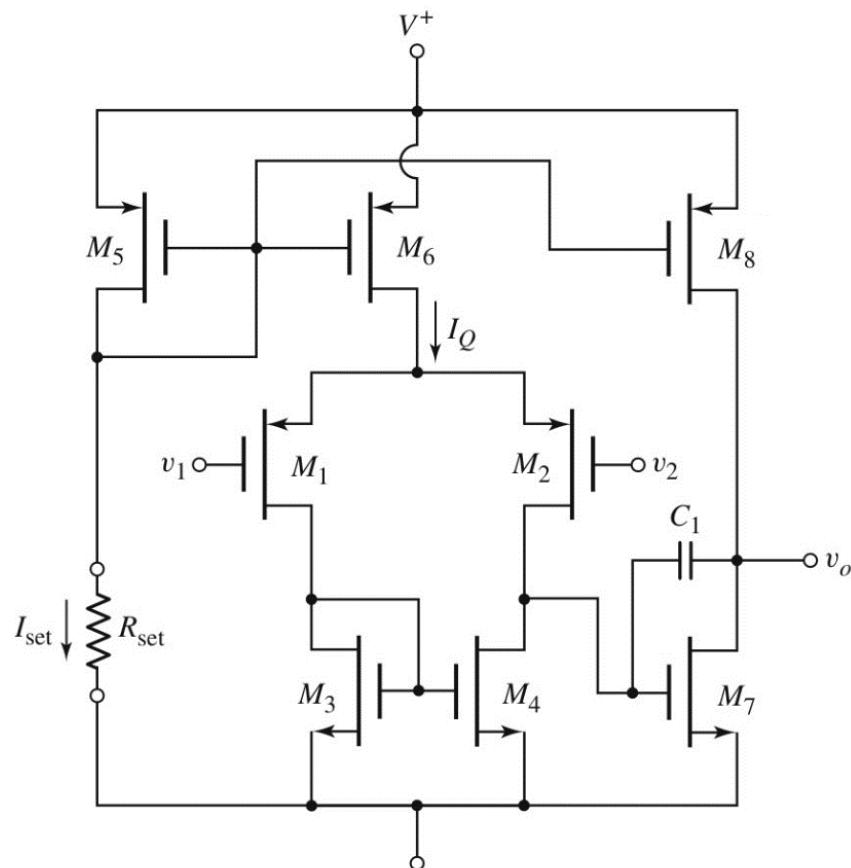


Figure 1

Answer:

; N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k_n}{2} \cdot \frac{W}{L}$$

; P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k_p}{2} \cdot \frac{W}{L}$$

; Small signal

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$r_o \equiv \frac{1}{\lambda I_{DQ}}$$

Q(a)

$$I_{D5} = K_{p5} (V_{SG5} + V_{TP})^2 = (125) \times (1.5 - 0.5)^2 = 125 \text{ A} \quad [2]$$

$$I_Q = I_{D6} = I_{D7} = I_{D8} = I_{D5} = 125 \text{ A} \quad [1]$$

$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = I_Q / 2 = 62.5 \text{ A} \quad [1]$$

Q(b)

$$A_d = g_{m2}(r_{o2} \| r_{o4}) \quad [1]$$

$$g_{m2} = \sqrt{2K_p I_Q} = \sqrt{2(125)(125)} = 176.77 \text{ A/V} \quad [0.5]$$

$$r_{o2} = \frac{1}{\lambda_p I_{D2}} = \frac{1}{0.02 \times 62.5} = 0.8 \text{ M} \quad [0.5]$$

$$r_{o4} = \frac{1}{\lambda_n I_{D4}} = \frac{1}{0.01 \times 62.5} = 1.6 \text{ M} \quad [0.5]$$

$$A_d = (176.77) (0.8 \text{ M} \| 1.6 \text{ M}) = 94.277 \quad [0.5]$$

$$A_{v2} = -g_{m7}(r_{o7} \| r_{o8})$$

$$g_{m7} = 2\sqrt{K_{n7} I_{D7}} = 2\sqrt{(100)(125)} = 223.6 \text{ A/V} \quad [0.5]$$

$$r_{o7} = \frac{1}{\lambda_n I_{D7}} = \frac{1}{0.01 \times 125} = 0.8 \text{ M} \quad [0.5]$$

$$r_{o8} = \frac{1}{\lambda_p I_{D8}} = \frac{1}{0.02 \times 125} = 0.4 \text{ M} \quad [0.5]$$

$$A_{v2} = -(223.6) (0.8 \text{ M} \| 0.4 \text{ M}) = -59.63 \quad [0.5]$$

$$A_v = A_d A_{v2} = 94.277 \times (-59.63) = -5618.61 \quad [1]$$