

EEEE273 - Quiz 7  
 SEMESTER 2, ACADEMIC YEAR 2016/2017  
 Date: 17 January 2017 Time: 15 minutes

**Question:**

Refer to **ideal** inverting op-amp in **Figure 1**. Calculate its absolute minimum and maximum values of the closed-loop voltage gain ( $A_v = v_O/v_I$ ) if  $R_1 = 20 \text{ k}\Omega$ ,  $R_2 = 20 \text{ k}\Omega$ , and potentiometer  $R_{2V} = 0$  to  $30 \text{ k}\Omega$ .

Show your calculation clearly.

[10 marks]

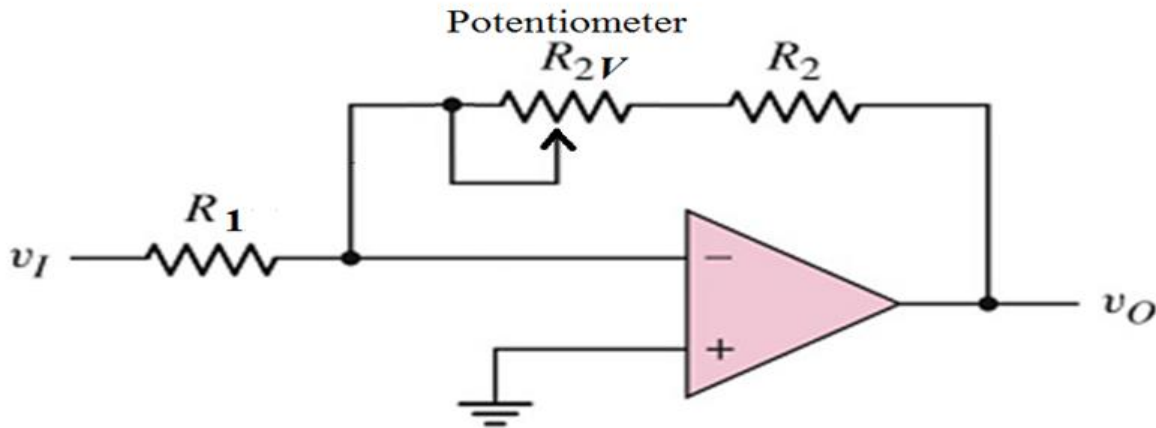


Figure 1

**Answer:**

$$A_v = v_O / v_I = - (R_2 + R_{2V}) / R_1 \quad [1]$$

$$R_2 (\text{min}) = R_2 = 20 \text{ k}\Omega \quad [1]$$

$$R_2 (\text{max}) = R_2 + R_{2V} = 20 \text{ k}\Omega + 30 \text{ k}\Omega = 50 \text{ k}\Omega \quad [1]$$

$$R_1 = 20 \text{ k}\Omega \quad [1]$$

$$A_v(\text{min}) = - R_2 (\text{min}) / R_1 \quad [2]$$

$$\Rightarrow A_v(\text{min}) = -20\text{k}/20\text{k} = -1 \text{ V/V} \quad [1]$$

$$A_v(\text{max}) = - R_2 (\text{max}) / R_1 \quad [2]$$

$$\Rightarrow A_v(\text{max}) = -50\text{k}/20\text{k} = -2.5 \text{ V/V} \quad [1]$$

**Question:**

Refer to **ideal** inverting op-amp in **Figure 1**. Calculate its absolute minimum and maximum values of the closed-loop voltage gain ( $A_v = v_O/v_I$ ) if  $R_1 = 15 \text{ k}\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ , and potentiometer  $R_{2V} = 0$  to  $30 \text{ k}\Omega$ .

Show your calculation clearly.

[10 marks]

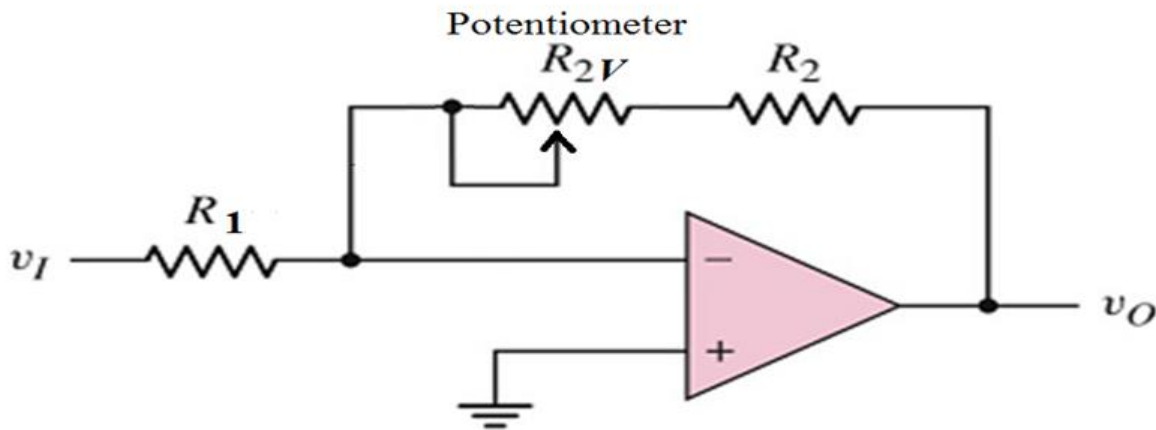


Figure 1

**Answer:**

$$A_v = v_O / v_I = - (R_2 + R_{2V}) / R_1 \quad [1]$$

$$R_2 (\text{min}) = R_2 = 10 \text{ k}\Omega \quad [1]$$

$$R_2 (\text{max}) = R_2 + R_{2V} = 10 \text{ k}\Omega + 30 \text{ k}\Omega = 40 \text{ k}\Omega \quad [1]$$

$$R_1 = 15 \text{ k}\Omega \quad [1]$$

$$A_v(\text{min}) = - R_2 (\text{min}) / R_1 \quad [2]$$

$$\Rightarrow A_v(\text{min}) = -10\text{k}/15\text{k} = -0.667 \text{ V/V} \quad [1]$$

$$A_v(\text{max}) = - R_2 (\text{max}) / R_1 \quad [2]$$

$$\Rightarrow A_v(\text{max}) = -40\text{k}/15\text{k} = -2.667 \text{ V/V} \quad [1]$$

**Question:**

Refer to **ideal** inverting op-amp in **Figure 1**. Calculate its absolute minimum and maximum values of the closed-loop voltage gain ( $A_v = v_O/v_I$ ) if  $R_1 = 25 \text{ k}\Omega$ ,  $R_2 = 20 \text{ k}\Omega$ , and potentiometer  $R_{2V} = 0$  to  $20 \text{ k}\Omega$ .

Show your calculation clearly.

[10 marks]

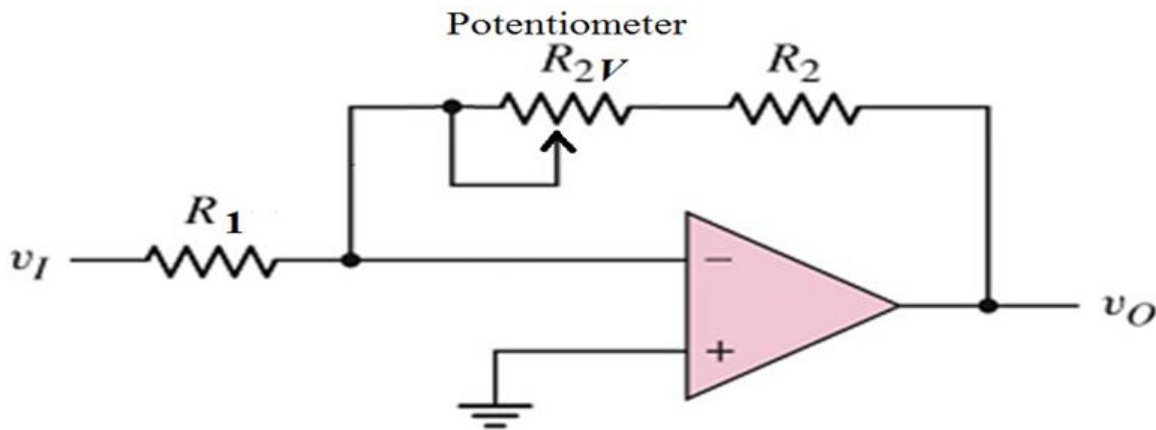


Figure 1

**Answer:**

$$A_v = v_O / v_I = - (R_2 + R_{2V}) / R_1 \quad [1]$$

$$R_2 (\text{min}) = R_2 = 20 \text{ k}\Omega \quad [1]$$

$$R_2 (\text{max}) = R_2 + R_{2V} = 20 \text{ k}\Omega + 20 \text{ k}\Omega = 40 \text{ k}\Omega \quad [1]$$

$$R_1 = 25 \text{ k}\Omega \quad [1]$$

$$A_v(\text{min}) = - R_2 (\text{min}) / R_1 \quad [2]$$

$$\Rightarrow A_v(\text{min}) = -20\text{k}/25\text{k} = -0.8 \text{ V/V} \quad [1]$$

$$A_v(\text{max}) = - R_2 (\text{max}) / R_1 \quad [2]$$

$$\Rightarrow A_v(\text{max}) = -40\text{k}/25\text{k} = -1.6 \text{ V/V} \quad [1]$$

EEEE273 - Quiz 7  
 SEMESTER 2, ACADEMIC YEAR 2016/2017  
 Date: 17 January 2017 Time: 15 minutes

**Question:**

Refer to **ideal** inverting op-amp in **Figure 1**. Calculate its absolute minimum and maximum values of the closed-loop voltage gain ( $A_v = v_O/v_I$ ) if  $R_1 = 20 \text{ k}\Omega$ ,  $R_2 = 25 \text{ k}\Omega$ , and potentiometer  $R_{2V} = 0$  to  $25 \text{ k}\Omega$ .

Show your calculation clearly.

[10 marks]

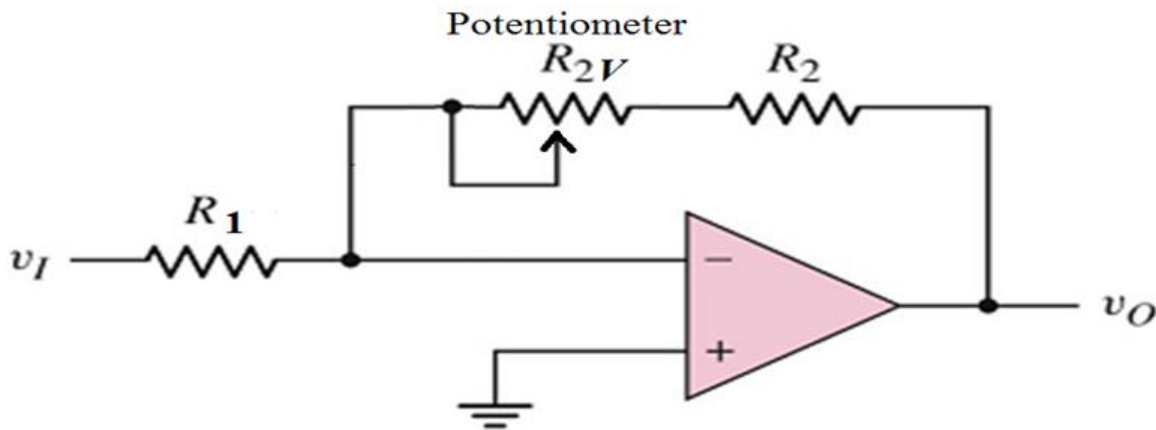


Figure 1

**Answer:**

$$A_v = v_O / v_I = - (R_2 + R_{2V}) / R_1 \quad [1]$$

$$R_2 (\text{min}) = R_2 = 25 \text{ k}\Omega \quad [1]$$

$$R_2 (\text{max}) = R_2 + R_{2V} = 25 \text{ k}\Omega + 25 \text{ k}\Omega = 50 \text{ k}\Omega \quad [1]$$

$$R_1 = 20 \text{ k}\Omega \quad [1]$$

$$A_v(\text{min}) = - R_2 (\text{min}) / R_1 \quad [2]$$

$$\Rightarrow A_v(\text{min}) = -25\text{k}/20\text{k} = -1.25 \text{ V/V} \quad [1]$$

$$A_v(\text{max}) = - R_2 (\text{max}) / R_1 \quad [2]$$

$$\Rightarrow A_v(\text{max}) = -50\text{k}/20\text{k} = -2.5 \text{ V/V} \quad [1]$$