

Name:
 Student ID Number:
 Section Number: 01/02/03/04 A/B
 Lecturer: Dr Jamaludin/ Dr Jehana Ermy/
 Dr Azni Wati
 Table Number:



College of Engineering
 Department of Electronics and Communication Engineering

Test 1 – With Model Answer

SEMESTER 2, ACADEMIC YEAR 2016/2017

Subject Code : **EEEB273**
 Course Title : **Electronics Analysis & Design II**
 Date : **19 November 2016**
 Time Allowed : **2 hours**

Instructions to the candidates:

1. Write your Name and Student ID Number. Indicate your Section Number and Lecturer's Name. Write also your Table Number.
2. **Write all your answers using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS. Show clearly** all your calculations. Every value must be written with its correct Unit.
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.

☺ **GOOD LUCK!** ☺

Question Number	Q1	Q2	Q3	Total
Marks				

QUESTION 1 [40 marks]

(a) Consider the **three-transistor BJT current source** as in **Figure 1(a)**. All transistors have $V_{BE(on)} = 0.6 \text{ V}$ and $V_A = 120 \text{ V}$. Transistors Q_1 and Q_2 are identical with $\beta = 80$, while Q_3 has $\beta_3 = 50$. Given $V^+ = 10 \text{ V}$, $V^- = -10 \text{ V}$, and $I_O = 0.70 \text{ mA}$.

- (i) Calculate all transistor currents in the circuit, I_{REF} , and R_1 . [12 marks]
- (ii) What is the minimum voltage at V_{C2} ? [2 marks]
- (iii) How much reference current differs from the bias current? [2 marks]
- (iv) Describe any similarity and difference of this current source with the Wilson current source. [4 marks]

Answers for Question 1(a)

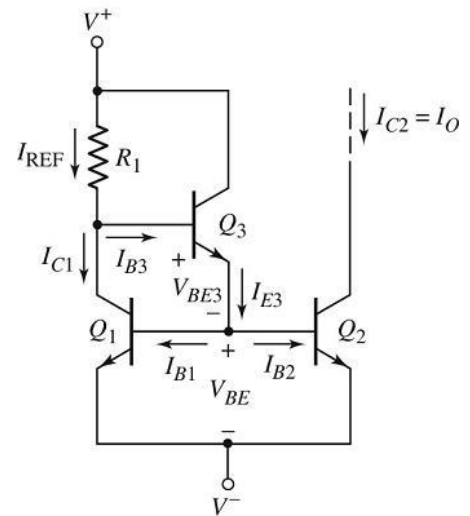


Figure 1(a)

Answers for Question 1(a) (Continued)Answers for Question 1(a)

- (i) **Calculate** all transistor currents in the circuit, I_{REF} , and R_1 . [12 marks]
- $$I_{B1} = I_{B2} \quad [1]$$
- $$I_O = \beta I_{B2} \rightarrow I_{B2} = I_O / \beta = 0.7\text{m}/80 = 8.75\text{uA} \quad [1.5]$$
- $$I_{C1} = \beta I_{B2} \rightarrow I_{C1} = I_O = 0.7\text{mA} \quad [1]$$
-
- $$I_{E3} = 2 I_{B2} = 2(8.75\text{u}) = 17.5\text{uA} \quad [1]$$
- $$I_{B3} = I_{E3} / (1 + \beta_3) = 17.5\text{u}/51 = 0.3431\text{uA} \quad [1.5]$$
-
- $$I_{REF} = I_{C1} + I_{B3} = 0.7\text{m} + 0.3431\text{u} = 700.3431\text{uA} \quad [2]$$
-
- $$R_1 = (V^+ - 2V_{BE(\text{on})} - V^-) / I_{REF} \quad [2]$$
- $$= (20 - 2(0.6)) / (0.7003431\text{m}) \quad [2]$$
- $$= \mathbf{26.84} \text{ k}\Omega$$
-
- (ii) **What** is the minimum voltage at V_{C2} ? [2 marks]
- $$V_{C2} = V^- + v_{CE2(\text{min})} = -10 + 0.6 = -9.4 \text{ V} \quad [2]$$
-
- (iii) **How much** reference current differs from the bias current? [2 marks]
- $$I_{REF} \text{ is } 0.049\% \text{ higher than } I_O \text{ OR differs } \mathbf{0.3431\text{uA}} \quad [2]$$
-
- (iv) **Describe** any similarity and difference of this current source with the Wilson current source. [4 marks]
- 1) Very close approximation of I_O to I_{REF} [2]
 - 2) Lower output resistance by a factor of $(\beta/2)$. [2]

(b) Study a multi-transistor BJT current mirror shown in Figure 1(b) thoroughly and carefully. With circuit analysis, load current for a mirror transistor I_{ON} can be found using

$$I_{ON} = \frac{I_{REF}}{1 + \frac{(1 + N)}{\beta}}$$

where N is the total number of **equivalent** mirror transistors inside Q_1 to Q_N in the circuit. Every **equivalent** mirror transistor is matching with the reference transistor Q_R .

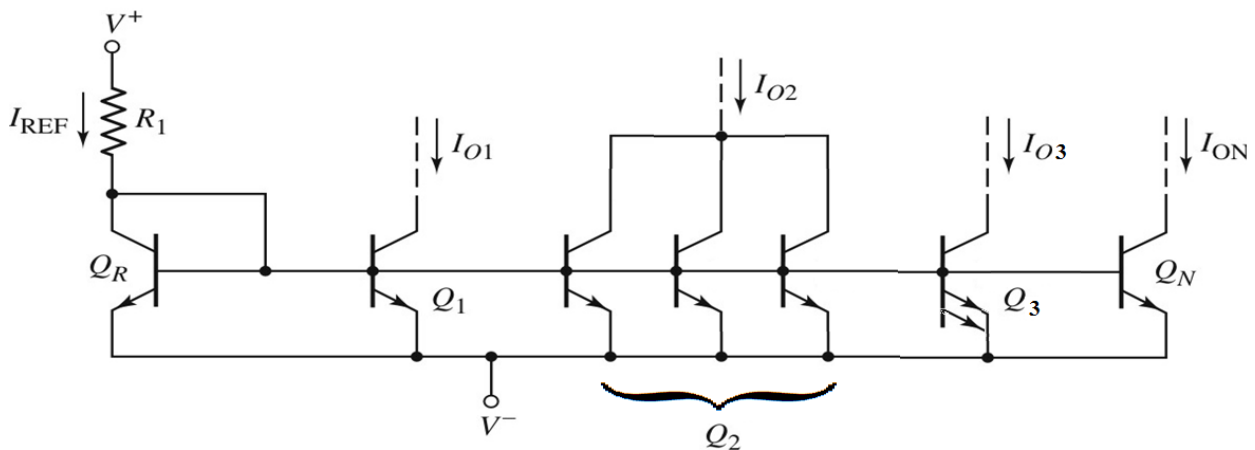


Figure 1(b)

All transistors have $V_{BE(on)} = 0.7 \text{ V}$, $\beta = 40$, and $V_A = 150 \text{ V}$. Given $V^+ = 10 \text{ V}$, $V^- = -10 \text{ V}$, and $R_1 = 10 \text{ k}\Omega$.

- (i) What is the total number of **equivalent** mirror transistors (N) in the circuit? [4 marks]
- (ii) Calculate I_{REF} , I_{O1} , I_{O2} , I_{O3} , and I_{ON} in the circuit. [12 marks]
- (iii) Find output resistance of the current mirror at transistor Q_3 (i.e. R_{O3}). [4 marks]

Answers for Question 1(b)

Answers for Question 1(b) (Continued)**Answers for Question 1(b)**

- (i)
- What**
- is the total number of
- equivalent**
- mirror transistors (
- N
-) in the circuit? [4 marks]

$$N = 1 \text{ (for } Q_1) + 3 \text{ (for } Q_2) + 2 \text{ (for } Q_3) + 1 \text{ (for } Q_N) = 7 \quad [4]$$

- (ii)
- Calculate**
- I_{REF}
- ,
- I_{O1}
- ,
- I_{O2}
- ,
- I_{O3}
- , and
- I_{ON}
- in the circuit. [12 marks]

$$I_{REF} = (V^+ - V_{BE(on)} - V^-) / R_1 \quad [2]$$

$$= (10 - 0.7 - (-10)) / (10k) = 1.93 \text{ mA} \quad [2]$$

$$I_{ON} = I_{REF} / (1 + (1 + N) / \beta)$$

$$= (1.93 \text{ mA}) / (1 + (1 + 7) / 40) = 1.608 \text{ mA} \quad [2] \text{ *Note}$$

$$I_{O1} = I_{ON} = 1.608 \text{ mA} \quad [2] \text{ *Note}$$

$$I_{O2} = 3 I_{ON} = 3 \times 1.608 \text{ mA} = 4.824 \text{ mA} \quad [2] \text{ *Note}$$

$$I_{O3} = 2 I_{ON} = 2 \times 1.608 \text{ mA} = 3.216 \text{ mA} \quad [2] \text{ *Note}$$

*Note: If answer for 1(b)(i) is not $N = 7$, may give [1.5 marks] for values of I_{O1} , I_{O2} , I_{O3} , and I_{ON} based value of N given in 1(b)(i) on condition that respective **formula** is correct.

- (iii)
- Find**
- output resistance of the current mirror at transistor
- Q_3
- (i.e.
- R_{O3}
-). [4 marks]

$$R_{O3} = V_A / I_{O3} \quad [2]$$

$$= 150 / 3.216 \text{ mA} = 46.6418 \text{ k}\Omega \quad [2]$$

QUESTION 2 [30 marks]

Figure 2 shows a MOSFET cascode current source with all transistors are regarded as identical. The transistor parameters are: $V_{TN} = 0.5 \text{ V}$, $K_n = 80 \mu\text{A}/\text{V}^2$, and $\lambda = 0.02 \text{ V}^{-1}$. The circuit parameters are: $V^+ = +7 \text{ V}$, $V^- = -7 \text{ V}$, and $I_{REF} = 120 \mu\text{A}$.

- (a) Calculate the V_{GS} of each transistor and I_O . [10 marks]
- (b) If I_{REF} symbol in the **Figure 2** is replaced by another MOSFET transistor M_5 (but M_5 is **NOT** identical to M_1 to M_4) to act like a resistor, what is the value of V_{GS5} ? [4 marks]
- (c) Determine the percent change in I_O as V_{D4} changes from -3 V to $+3 \text{ V}$. [16 marks]

Answers for Question 2

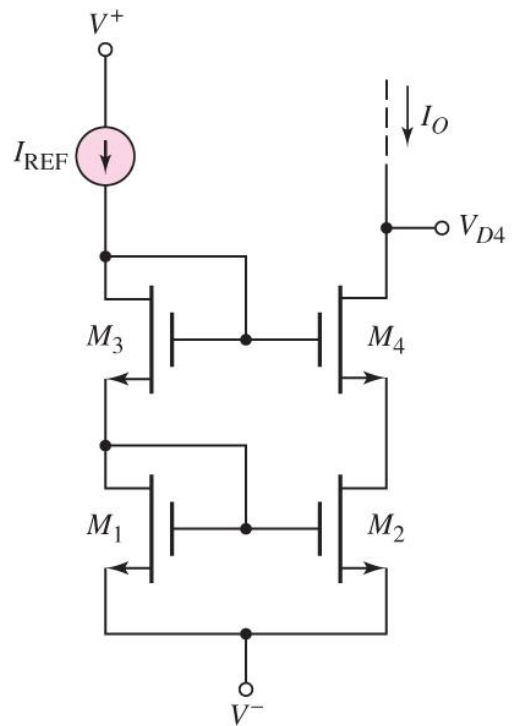


Figure 2

Answers for Question 2 (Continued)

(a) Using the formula of $I_D = K_n (V_{GS} - V_{TN})^2$ [2 marks]

$$I_{REF} = K_n (V_{GS1} - V_{TN})^2 \rightarrow 120\mu = 80\mu (V_{GS1} - 0.5)^2$$
 [2 marks]

$$V_{GS1} = 1.7247 \text{ V}$$
 [2 marks]

$$V_{GS2} = V_{GS3} = V_{GS4} = V_{GS1} = 1.7247 \text{ V}$$
 [2 marks]

$$I_O = I_{D4} = I_{D2} = K_n (V_{GS} - V_{TN})^2 = 120 \mu\text{A}$$
 [2 marks]

(b) $V^+ - V_{GS5} - V_{GS3} - V_{GS1} = V$ [2 marks]

$$V_{GS5} = V^+ - V_{GS3} - V_{GS1} - V = 7 - 1.7247(2) - (-7) = 10.5506 \text{ V}$$
 [2 marks]

(c) $R_O = r_{O4} + r_{O2}(1 + g_m r_{O4})$ [2 marks]

OR $R_O \approx g_m r_{O4} r_{O2}$
 [Because approximation was also taught in the lecture]

$$g_m = 2\sqrt{K_n I_O} = 2\sqrt{(0.08\text{m})(0.12\text{m})} = 0.19596 \frac{\text{mA}}{\text{V}}$$
 [2 marks]

$$r_{O2} = r_{O4} = \frac{1}{\lambda I_O} = \frac{1}{(0.02)(0.12\text{m})} = 416.666 \text{ k}\Omega$$
 [2 marks]

OR $R_O = 416.666\text{k} + 416.666\text{k}[1 + (0.19596\text{m})(416.666\text{k})] = 34.854 \text{ M}\Omega$ [2 marks]
 $R_O = (0.19596\text{m})(416.666\text{k})(416.666\text{k}) = 34.02 \text{ M}\Omega$

$$\Delta I_O = \frac{\Delta V_{D4}}{R_O} = \frac{3 - (-3)}{34.854\text{M}} = 0.1721 \mu\text{A}$$
 [2, 2 marks]

OR $\Delta I_O = \frac{\Delta V_{D4}}{R_O} = \frac{3 - (-3)}{34.02\text{M}} = 0.1764 \mu\text{A}$

$$\therefore \frac{\Delta I_O}{I_O} \times 100\% = \frac{0.1721\mu}{120\mu} \times 100\% = 0.1434\%$$
 [2, 2 marks]

OR $\therefore \frac{\Delta I_O}{I_O} \times 100\% = \frac{0.1764\mu}{120\mu} \times 100\% = 0.1469\%$

QUESTION 3 [30 marks]

Figure 3 shows a circuit diagram for a BJT differential amplifier biased with a current source to provide bias current I_Q . Study the circuit diagram carefully. Transistor parameters are $V_{BE(on)} = 0.7\text{ V}$, $\beta = \infty$, and $V_A = \infty$.

For the circuit diagram also, voltages measured at v_{C1} and v_{C2} are **4.5 V** respectively.

- (a) Calculate the values for v_{cm} and v_d . [6 marks]
- (b) Determine the value of I_Q . [6 marks]
- (c) Find the value for v_{CE2} . [6 marks]
- (d) Determine the differential-mode voltage gain (A_d) of the differential amplifier for a **one-sided output** taken at v_{C2} . [6 marks]
- (e) Draw and label clearly the full circuit diagram if the differential amplifier is biased with a **Widlar** current source. [6 marks]

Show clearly all your calculations. Every parameter must be written with its correct Unit.

Answers for Question 3

- (a) From Figure 3:
 - $v_{B1} = v_{B2} = 0\text{ V}$ [2]
 - $v_{cm} = (v_{B1} + v_{B2}) / 2 = 0\text{ V}$ [2]
 - $v_d = v_{B1} - v_{B2} = 0\text{ V}$ [2]
- (b) Given: $v_{C1} = v_{C2} = 4.5\text{ V}$
 - $10 - I_{C1}R_C = v_{C1} = 4.5\text{ V}$ [2]
 - $I_{C1} = 0.55\text{ mA} = I_{C2}$ [2]
 - $I_Q = I_{C1} + I_{C2} = 1.1\text{ mA}$ [2]
- (c) Given: $v_{C2} = 4.5\text{ V}$
 - $v_{CE2} = v_{C2} - v_E$ [2]
 - $v_E = v_{B2} - V_{BE(on)} = 0 - 0.7 = -0.7\text{ V}$ [2, 1]
 - $v_{CE2} = v_{C2} - v_E = 4.5 - (-0.7) = 5.2\text{ V}$ [1]
- (d) $A_d = (g_{m2} R_C) / 2$ [2]
 - $g_{m2} = I_{C2} / V_T$ [2]
 - $= 0.55\text{m} / 26\text{m} = 21.153\text{ mA/V}$ [1]
 - $A_d = (g_{m2} R_C) / 2$
 - $= (21.153\text{m} \times 10\text{k}) / 2 = 105.76$ [1]


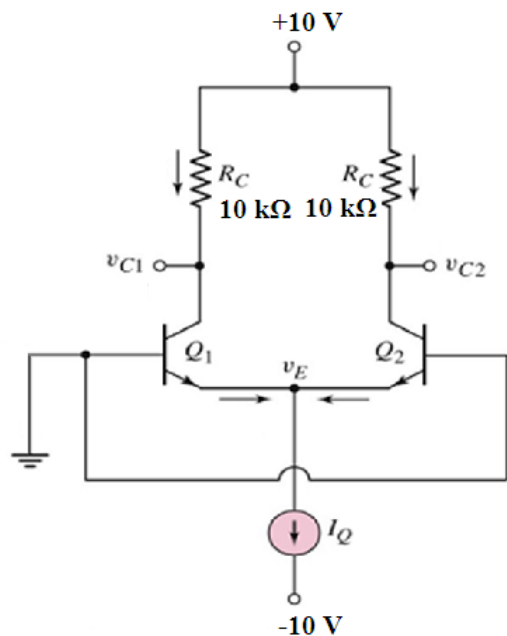


Figure 3

Answers for Question 3 (Continued)

(e)

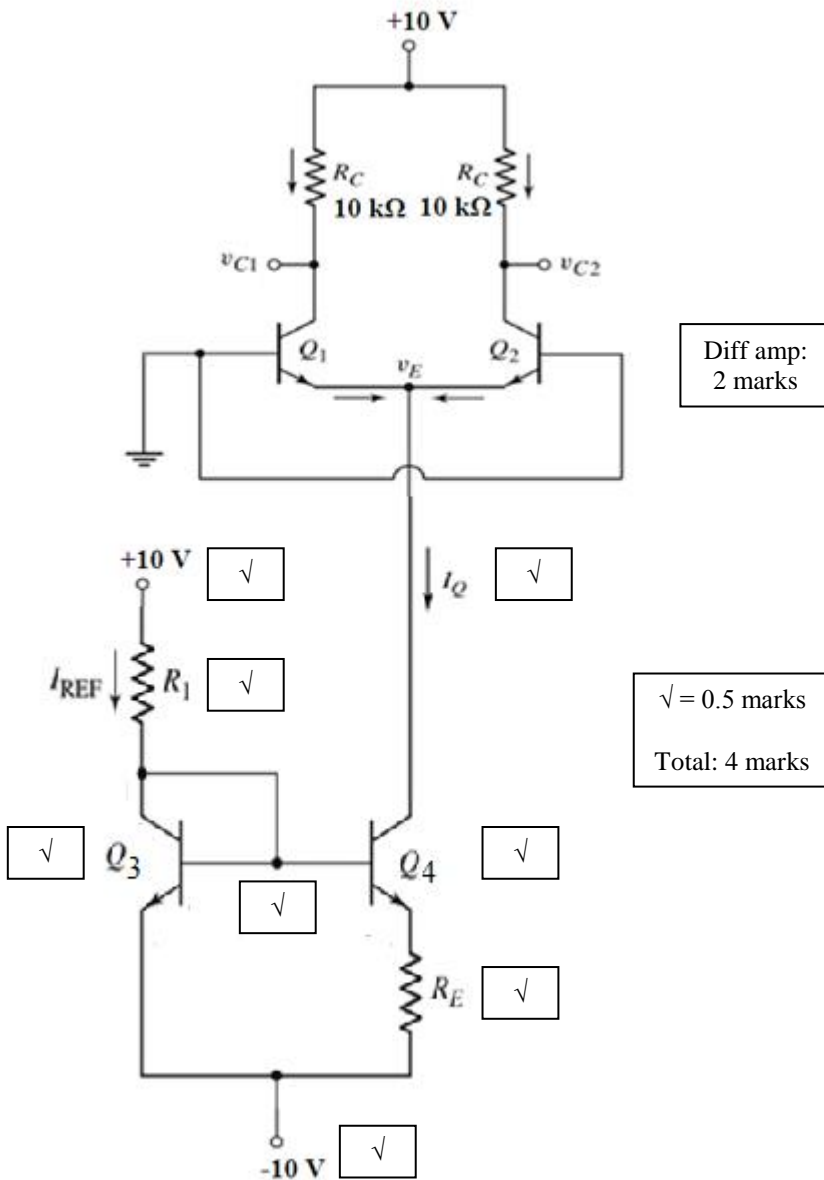

Diff amp:
2 marks

$\checkmark = 0.5$ marks
Total: 4 marks

BASIC FORMULA FOR TRANSISTOR

BJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{nnp}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

;Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

MOSFET

;N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{k'_n}{2} \cdot \frac{W}{L}$$

;P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{k'_p}{2} \cdot \frac{W}{L}$$

;Small signal

$$g_m = 2\sqrt{K_n I_{DQ}}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

Quadratic formula :

$$Ax^2 + Bx + C = 0 \rightarrow x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$