



**COLLEGE OF ENGINEERING
PUTRAJAYA CAMPUS
FINAL EXAMINATION
SEMESTER 1 2017 / 2018**

PROGRAMME : Bachelor of Electrical & Electronics Engineering (Honours)
Bachelor of Electrical Power Engineering (Honours)

SUBJECT CODE : EEEB273

SUBJECT : ELECTRONIC ANALYSIS AND DESIGN II

DATE : September 2017

TIME : 3 hours

INSTRUCTIONS TO CANDIDATES:

1. This paper contains **FIVE** (5) questions in **NINE** (9) pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided. Use **pen** to write your answer.
4. Write answer to different question on a **new page**.

THIS QUESTION PAPER CONSISTS OF NINE (9) PRINTED PAGES INCLUDING THIS COVER PAGE.

Question 3 [20 marks]

The transistor parameters for the circuit in **Figure 3** are: $\beta = 200$, $V_{BE(on)} = 0.7 \text{ V}$, and $V_A = 80 \text{ V}$. For Q_1 and Q_2 , $V_A = \infty$. The diff-amp has a common-mode voltage gain of $A_{cm1} = -0.0749$. It is given that $I_{C3} = 1.886 \text{ mA}$ and $I_{C5} = 1.003 \text{ mA}$.

- (a) Calculate the differential-mode input resistance (R_{id}) and common-mode input resistance (R_{icm}). [7 marks]
- (b) Determine the differential-mode voltage gain $A_d = v_{O3}/v_d$ and the common-mode voltage gain $A_{cm} = v_{O3}/v_{cm}$. [10 marks]
- (c) If $A_{cm} = 0$, determine the **output voltage** v_{O3} if $v_1 = 2.015 \sin \omega t \text{ mV}$ and $v_2 = 1.985 \sin \omega t \text{ mV}$. [3 marks]

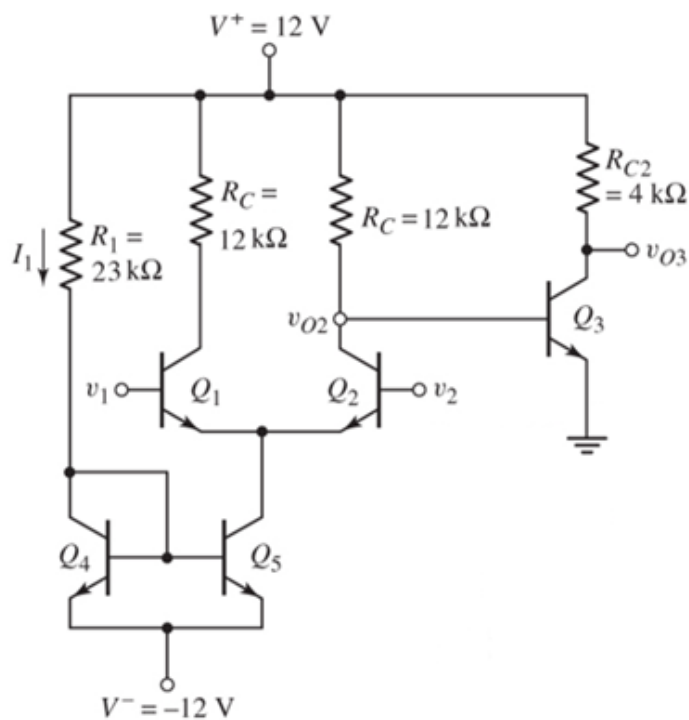


Figure 3

Question 4 [25 marks]

(a) Refer to the output stage circuits shown in **Figure 4(a)** and **Figure 4(b)**.

(i) **Identify** the output stage circuits shown in the **Figure 4(a)** and **Figure 4(b)**. Then, **describe** clearly the differences between the output stages shown in the **Figure 4(a)** and **Figure 4(b)** in terms of advantage(s) and/or disadvantage(s) of the designs.

[5 marks]

(ii) For the output stage shown in **Figure 4(b)**, assume that $V_{CC} = 10 \text{ V}$, $V_{BB} = 1.35 \text{ V}$, and $R_L = 1 \text{ k}\Omega$. Transistor Q_n and Q_p have $I_S = 4 \times 10^{-15} \text{ A}$. Given that output voltage $v_O = -8 \text{ V}$, **calculate** the currents i_L , i_{Cn} , and i_{Cp} , the input voltage v_I , and the power dissipation in the transistors Q_n and Q_p .

[10 marks]

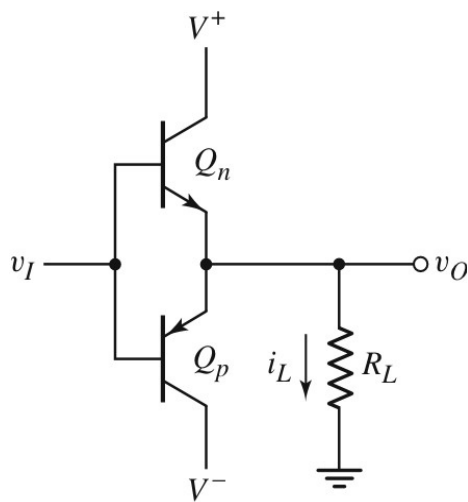


Figure 4(a)

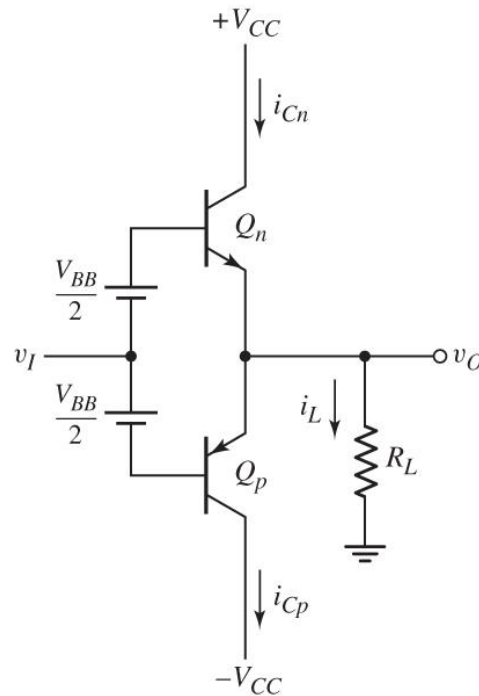
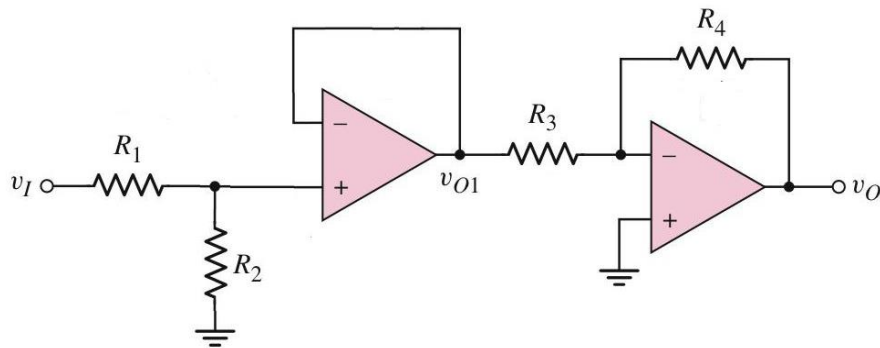


Figure 4(b)

Question 5 [15 marks]

- (a) Consider **two (2)** ideal op-amp circuits connected in cascade as shown in **Figure 6**. Given that $R_1 = 50 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$, $R_3 = 80 \text{ k}\Omega$, and $R_4 = 75 \text{ k}\Omega$. Calculate voltage gain v_O/v_I of the overall circuit. **[5 marks]**

**Figure 6**

- (b) **Figure 7** in the following page shows a design for an **instrumentation amplifier** using op-amps. The instrumentation amplifier has **adjustable differential voltage gain (A_v)**. In the design, R_{1POT} is a **potentiometer** (or a variable resistor) used to **provide variable resistance** so that differential voltage gain of the instrumentation amplifier can be adjustable. With analysis, it can be shown that output voltage (v_O) for the **difference amplifier** constructed using op-amp A_3 , resistors R_3 , and resistors R_4 is

$$v_O = \frac{R_4}{R_3} (v_{O2} - v_{O1})$$

- (i) **Study Figure 7 carefully.** Using same labels for all resistors, voltages and currents given in the **Figure 7**, show that the output voltage (v_O) of the **instrumentation amplifier with adjustable differential voltage gain** is

[7 marks]

$$v_O = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_{1f} + R_{1POT}} \right) (v_{I2} - v_{I1})$$

- (ii) For the circuit in **Figure 7**, given that $R_4 = 2.5 R_3$, $R_2 = 495 \text{ k}\Omega$, $R_{1f} = 15 \text{ k}\Omega$, R_{1POT} is set at $40 \text{ k}\Omega$, $v_{I1} = 0.090 \text{ V}$, and $v_{I2} = 0.115 \text{ V}$. Calculate adjustable differential voltage gain (A_v) and the output voltage (v_O) of the circuit.

[3 marks]

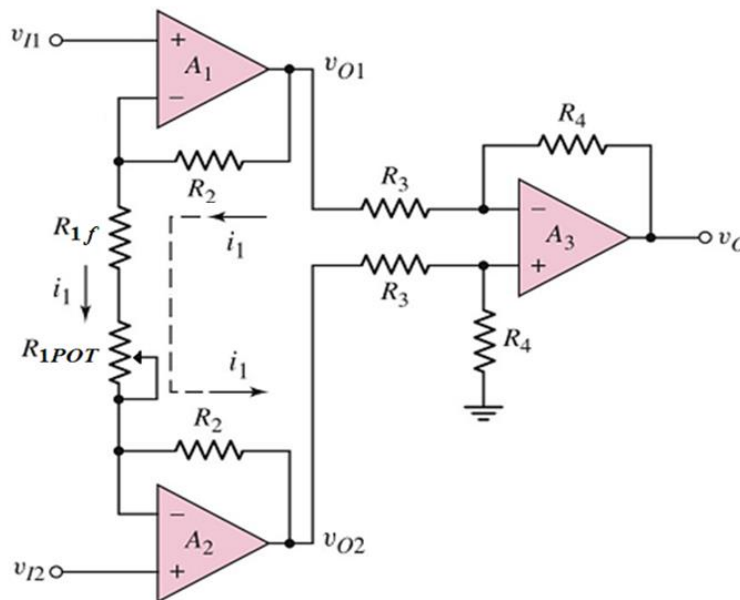


Figure 7

-END OF QUESTION PAPER-

APPENDIX:

A) BASIC FORMULA FOR TRANSISTOR

BJT

$$i_C = I_S e^{v_{BE}/V_T} \quad ; \text{NPN}$$

$$i_C = I_S e^{v_{EB}/V_T} \quad ; \text{PNP}$$

$$i_C = \beta i_B = \frac{\beta}{\beta + 1} i_E$$

$$i_E = i_B + i_C$$

; Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

MOSFET

; N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k'_n}{2} \cdot \frac{W}{L}$$

; P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k'_p}{2} \cdot \frac{W}{L}$$

; Small signal


$$g_m = 2\sqrt{K_n I_{DQ}} \quad ; \text{N – MOSFET}$$

$$g_m = 2\sqrt{K_p I_{DQ}} \quad ; \text{P – MOSFET}$$


$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

B) HYBRID- π EQUIVALENT CIRCUITS

BJT

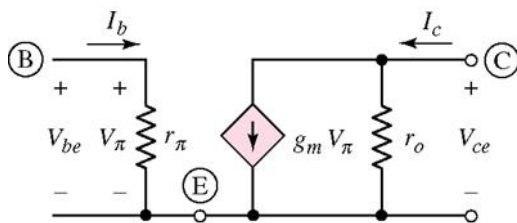

MOSFET

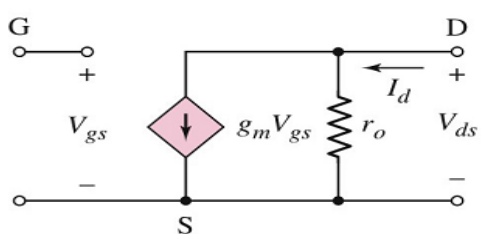

C) QUADRATIC FORMULA

$$Ax^2 + Bx + C = 0 \quad \rightarrow \quad x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$