

EEEE273 - Quiz 7  
 SEMESTER 1, ACADEMIC YEAR 2017/2018  
 Date: 30 August 2017 Time: 15 minutes

**Question:**

Refer to **ideal** inverting op-amp in **Figure 1**. Calculate its absolute minimum and maximum values of the closed-loop voltage gain ( $A_v = v_O/v_I$ ) when  $R_1 = 20 \text{ k}\Omega$ , potentiometer  $R_{1V} = 0 \text{ to } 30 \text{ k}\Omega$ , and  $R_2 = 20 \text{ k}\Omega$ .

Show your calculation clearly.

[10 marks]

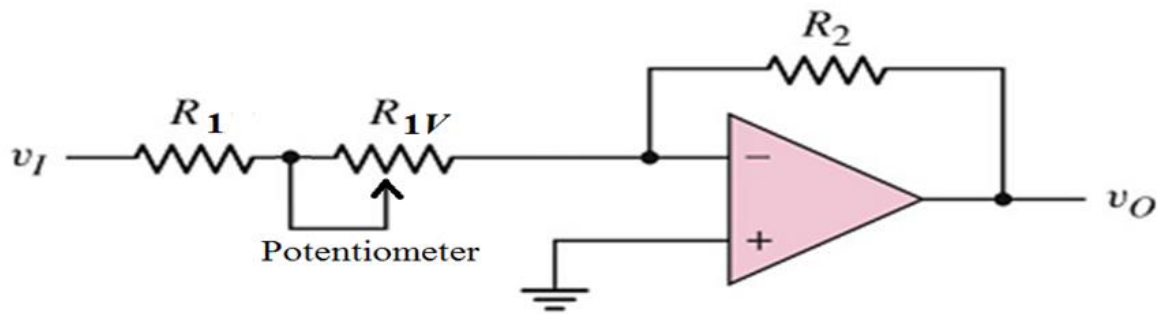


Figure 1

**Answer:**

$$A_d = v_O / v_I = - R_2 / (R_1 + R_{1V}) \quad [1]$$

$$R_1 (\text{min}) = R_1 = 20 \text{ k}\Omega \quad [1]$$

$$R_1 (\text{max}) = R_1 + R_{1V} = 20 \text{ k}\Omega + 30 \text{ k}\Omega = 50 \text{ k}\Omega \quad [1]$$

$$R_2 = 20 \text{ k}\Omega \quad [1]$$

**Absolute value of  $A_v$  is maximum when  $R_{1V}$  is minimum.**

$$A_v(\text{max}) = - R_2 / R_1 (\text{min}) \quad [2]$$

$$\Rightarrow A_v(\text{max}) = -20\text{k}/20\text{k} = -1 \text{ V/V} \quad [1]$$

$$A_v(\text{min}) = - R_2 / R_1(\text{max}) \quad [2]$$

$$\Rightarrow A_v(\text{min}) = -20\text{k}/50\text{k} = -0.4 \text{ V/V} \quad [1]$$

EEEEB273 - Quiz 7  
 SEMESTER 1, ACADEMIC YEAR 2017/2018  
 Date: 30 August 2017 Time: 15 minutes

**Question:**

Refer to **ideal** inverting op-amp in **Figure 1**. Calculate its absolute minimum and maximum values of the closed-loop voltage gain ( $A_v = v_O/v_I$ ) when  $R_1 = 10 \text{ k}\Omega$ , potentiometer  $R_{1V} = 0 \text{ to } 30 \text{ k}\Omega$ , and  $R_2 = 15 \text{ k}\Omega$ .

Show your calculation clearly.

[10 marks]

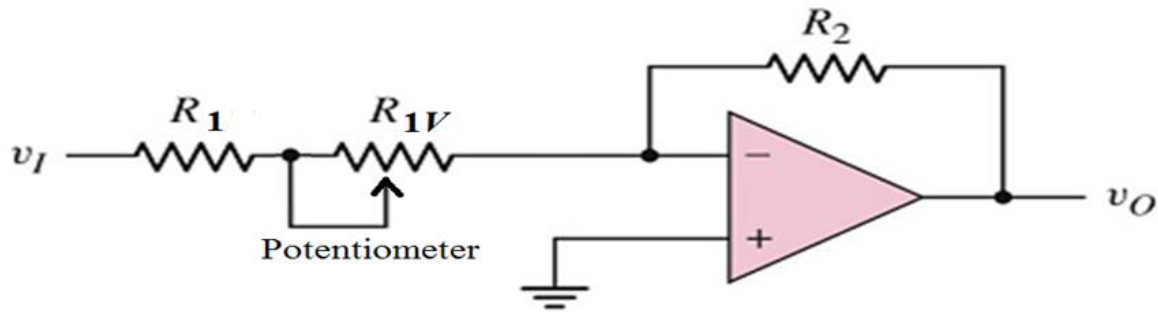


Figure 1

**Answer:**

$$A_d = v_O / v_I = - R_2 / (R_1 + R_{1V}) \quad [1]$$

$$R_1 (\text{min}) = R_1 = 10 \text{ k}\Omega \quad [1]$$

$$R_1 (\text{max}) = R_1 + R_{1V} = 10 \text{ k}\Omega + 30 \text{ k}\Omega = 40 \text{ k}\Omega \quad [1]$$

$$R_2 = 15 \text{ k}\Omega \quad [1]$$

**Absolute value of  $A_v$  is maximum when  $R_{1V}$  is minimum.**

$$A_v(\text{max}) = - R_2 / R_1 (\text{min}) \quad [2]$$

$$\Rightarrow A_v(\text{max}) = -15\text{k}/10\text{k} = -1.5 \text{ V/V} \quad [1]$$

$$A_v(\text{min}) = - R_2 / R_1(\text{max}) \quad [2]$$

$$\Rightarrow A_v(\text{min}) = -15\text{k}/40\text{k} = -0.375 \text{ V/V} \quad [1]$$

EEEE273 - Quiz 7 ;  
 SEMESTER 1, ACADEMIC YEAR 2017/2018  
 Date: 30 August 2017 Time: 15 minutes

**Question:**

Refer to **ideal** inverting op-amp in **Figure 1**. Calculate its absolute minimum and maximum values of the closed-loop voltage gain ( $A_v = v_O/v_I$ ) when  $R_1 = 20 \text{ k}\Omega$ , potentiometer  $R_{1V} = 0 \text{ to } 20 \text{ k}\Omega$ , and  $R_2 = 25 \text{ k}\Omega$ .

Show your calculation clearly.

[10 marks]

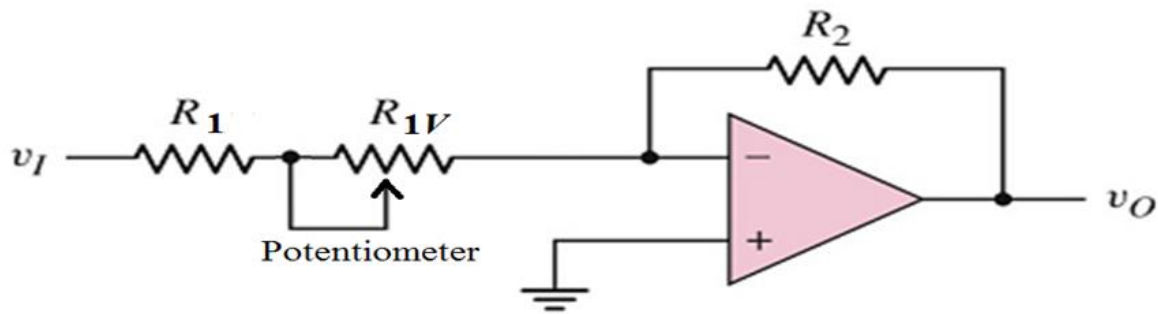


Figure 1

**Answer:**

$$A_d = v_O / v_I = - R_2 / (R_1 + R_{1V}) \quad [1]$$

$$R_1 (\text{min}) = R_1 = 20 \text{ k}\Omega \quad [1]$$

$$R_1 (\text{max}) = R_1 + R_{1V} = 20 \text{ k}\Omega + 20 \text{ k}\Omega = 40 \text{ k}\Omega \quad [1]$$

$$R_2 = 25 \text{ k}\Omega \quad [1]$$

**Absolute value of  $A_v$  is maximum when  $R_{1V}$  is minimum.**

$$A_v(\text{max}) = - R_2 / R_1 (\text{min}) \quad [2]$$

$$\Rightarrow A_v(\text{max}) = -25\text{k}/20\text{k} = -1.25 \text{ V/V} \quad [1]$$

$$A_v(\text{min}) = - R_2 / R_1(\text{max}) \quad [2]$$

$$\Rightarrow A_v(\text{min}) = -25\text{k}/40\text{k} = -0.625 \text{ V/V} \quad [1]$$

EEEEB273 - Quiz 7 :  
 SEMESTER 1, ACADEMIC YEAR 2017/2018  
 Date: 30 August 2017 Time: 15 minutes

**Question:**

Refer to **ideal** inverting op-amp in **Figure 1**. Calculate its absolute minimum and maximum values of the closed-loop voltage gain ( $A_v = v_O/v_I$ ) when  $R_1 = 25 \text{ k}\Omega$ , potentiometer  $R_{1V} = 0 \text{ to } 25 \text{ k}\Omega$ , and  $R_2 = 20 \text{ k}\Omega$ .

Show your calculation clearly.

[10 marks]

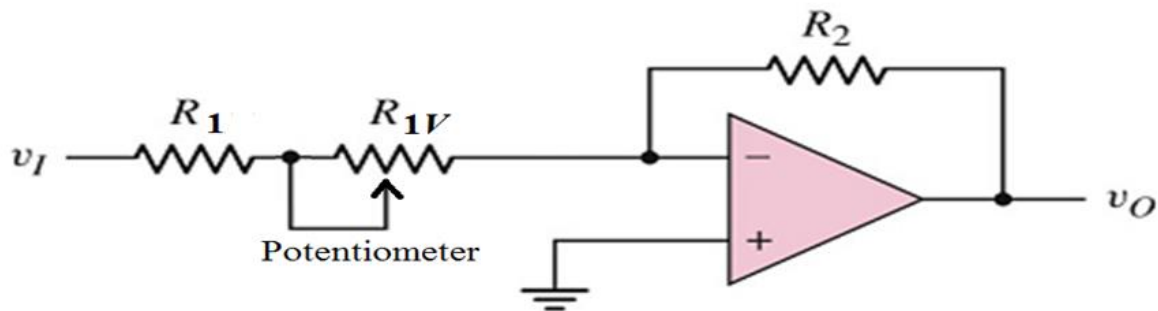


Figure 1

**Answer:**

$$A_d = v_O / v_I = - R_2 / (R_1 + R_{1V}) \quad [1]$$

$$R_1 (\text{min}) = R_1 = 25 \text{ k}\Omega \quad [1]$$

$$R_1 (\text{max}) = R_1 + R_{1V} = 25 \text{ k}\Omega + 25 \text{ k}\Omega = 50 \text{ k}\Omega \quad [1]$$

$$R_2 = 20 \text{ k}\Omega \quad [1]$$

**Absolute value of  $A_v$  is maximum when  $R_{1V}$  is minimum.**

$$A_d(\text{max}) = - R_2 / R_1 (\text{min}) \quad [2]$$

$$\Rightarrow A_d(\text{max}) = -20\text{k}/25\text{k} = -0.8 \text{ V/V} \quad [1]$$

$$A_v(\text{min}) = - R_2 / R_1(\text{max}) \quad [2]$$

$$\Rightarrow A_v(\text{min}) = -20\text{k}/50\text{k} = -0.4 \text{ V/V} \quad [1]$$