



College of Engineering
Department of Electronics and Communication Engineering

Test 1 (Solution)

SEMESTER 1, ACADEMIC YEAR 2017/2018

Subject Code : **EEEB273**
Course Title : **Electronics Analysis & Design II**
Date : **8 July 2017**
Time Allowed : **2 hours**



Instructions to the candidates:

1. Write your Name and Student ID Number. Indicate your Section Number and Lecturer's Name.
Write also your Table Number.
2. **Write all your answers using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.** Show clearly all your calculations. Every value **must** be written with its correct Unit.
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.

(Smiley face) **GOOD LUCK!** (Smiley face)

Question Number	Q1	Q2	Q3	Q4	Total
Marks					

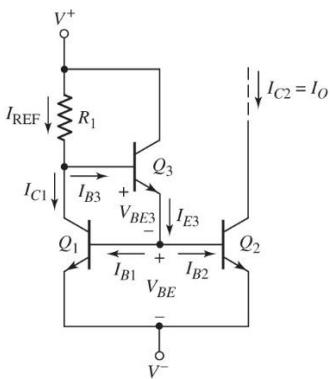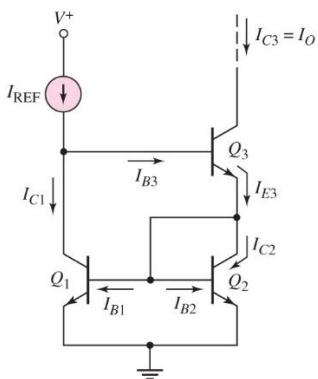Answers for Question 1(i) Three transistor current sourcePlacements of Q_1 , Q_2 and Q_3 [2 marks]Batteries V^+ and V^- labels [2 marks]Currents I_{REF} and I_O labels [2 marks]Wilson current sourcePlacements of Q_1 , Q_2 and Q_3 [2 marks]Batteries V^+ and V^- labels [2 marks]Currents I_{REF} and I_O labels [2 marks](ii) Both three-transistor and Wilson current sources have an increased stability [1.5 marks] with smaller I_O change [1.5 marks].

(iii) For Widlar current source:

Assuming that both Q_1 and Q_2 are identical,

$$I_{REF} \cong I_{C1} = I_S e^{\frac{V_{BE1}}{V_T}} \quad [1 \text{ mark}]$$

$$I_O \cong I_{C2} = I_S e^{\frac{V_{BE2}}{V_T}} \quad [1 \text{ mark}]$$

Solving the V_{BE} voltages,

$$V_{BE1} = V_T \ln\left(\frac{I_{REF}}{I_S}\right) \text{ and } V_{BE2} = V_T \ln\left(\frac{I_O}{I_S}\right) \quad [2 \text{ marks}]$$

$$\text{Combining the equations for VBES, } V_{BE1} - V_{BE2} = V_T \ln\left(\frac{I_{REF}}{I_S}\right) - V_T \ln\left(\frac{I_O}{I_S}\right) \quad [1 \text{ mark}]$$

$$\text{Hence, } V_{BE1} - V_{BE2} = V_T \ln\left(\frac{I_{REF}}{I_O}\right) \quad [1 \text{ mark}]$$

$$\text{From the circuit, } V_{BE1} - V_{BE2} = I_E R_E \cong I_O R_E \quad [2 \text{ marks}]$$

$$\text{Combining the equations, } I_O R_E = V_T \ln\left(\frac{I_{REF}}{I_O}\right) \quad [2 \text{ marks}]$$

$$(iv) \quad R_1 = \frac{V^+ - V_{BE1} - V^-}{I_{REF}} = \frac{3 - 0.6 - (-3)}{0.1m} = 54.00 \text{ k}\Omega \quad [1.5, 1, 1 \text{ marks}]$$

$$R_E = \frac{V_T}{I_O} \ln\left(\frac{I_{REF}}{I_O}\right) = \frac{0.026}{0.02m} \ln\left(\frac{0.1m}{0.02m}\right) = 2.092 \text{ k}\Omega \quad [1.5, 1, 1 \text{ marks}]$$

$$V_{BE2} = V_{BE1} - I_O R_E = 0.6 - (0.02m)(2.092k) = 0.5582 \text{ V} \quad [1, 1, 1 \text{ marks}]$$

Answers for Question 2

Question 2(a)

$$VDS2 (\text{min}) = VD2 - VS2 = -2.1 - (-3) \underline{= 0.9V} = \mathbf{VDS2(\text{sat})} \quad [2]$$

$$VDS2(\text{sat}) = VGS2 - VTN$$

$$VGS2 = VDS2(\text{sat}) + VTN = 0.9 + 0.5 \underline{= 1.4V} \quad [1]$$

$$\text{From circuit, } \underline{\mathbf{VGS1 = VGS2 = 1.4V}} \quad [1]$$

$$\begin{aligned} I_{o1} &= ID_2 = (\frac{1}{2}\mu_n C_{ox})(W/L)_2(VGS2 - VTN)^2 \\ &= (50 \mu)(35)(1.4-0.5)^2 \underline{= 1.418mA} \quad [2] \end{aligned}$$

$$\begin{aligned} I_{REF} &= ID_1 = (\frac{1}{2}\mu_n C_{ox})(W/L)_1(VGS1 - VTN)^2 \\ &= (50 \mu)(20)(1.4-0.5)^2 \underline{= 0.810mA} \quad [1] \end{aligned}$$

$$ID_3 = ID_4 = I_{REF} = 0.810mA \quad [1]$$

$$\begin{aligned} ID_3 &= 0.810mA = (\frac{1}{2}\mu_n C_{ox})(W/L)_3(VGS3 - VTN)^2 \\ &= (50 \mu)(5)(VGS3-0.5)^2 \quad [2] \end{aligned}$$

$$\begin{aligned} ID_4 &= 0.810mA = (\frac{1}{2}\mu_p C_{ox})(W/L)_4(VSG4 + VTP)^2 \\ &= (20 \mu)(10)(VSG4+ (-0.55))^2 \quad [2] \end{aligned}$$

$$\underline{\mathbf{VSG4 = 2.562V}} \quad [2]$$

Question 2(b)

$$dI_o = dVD2/RO \quad [1]$$

$$dVD2 = 0.4 - (-1.6) \underline{= 2V} \quad [1]$$

$$Ro = ro_2$$

$$ro_2 = 1/(\lambda n)(ID_2) = 1/(0.02)(1.418m) = \underline{35.26k\Omega} \quad [2]$$

$$dI_o = 2/35.26k \underline{= 56.72\mu A} \quad [1]$$

Question 2(c)


$$I_o' = I_o + dI_o \quad [1]$$

$$= 1.418mA + 56.72\mu A$$

$$\underline{\mathbf{= 1.475mA}} \quad [2]$$

Answers for Question 3

(a)

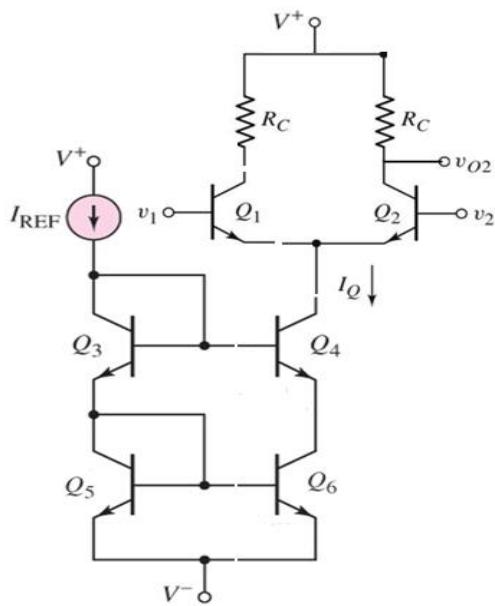

Cascode CS	[2]
Supply connections	[1]
Output and reference connection of CS	[2]

(b) $I_{C2} = I_Q / 2 = 0.5m / 2 = 0.25 \text{ mA}$ [2]

$$R_C = [V^+ - v_{o2}] / I_{C2}$$
 [2]
$$= [12 - 0.4] / 0.25m = 46.4k\Omega$$
 [2]

(c) $v_d = v_1 - v_2$ [2]

$$v_d = (250 - 150) \sin \omega t \mu\text{V} = 100 \sin \omega t \mu\text{V}$$
 [2]

(d) $v_{cm} = (v_1 + v_2)/2$ [2]

$$= [(250+150)/2] \sin \omega t \mu\text{V} = 200 \sin \omega t \mu\text{V}$$
 [2]

(e) $v_o = A_d v_d + A_{cm} v_{cm}$ [2]

$$v_o = (223) 100 \sin \omega t \mu\text{V} + (-10)(200 \sin \omega t \mu\text{V})$$
 [2]

$$= (22.3m - 2m) \sin \omega t \text{ V} = 20.3 \sin \omega t \text{ mV}$$
 [2]

Answers for Question 4

$$V_o = \frac{\beta R_C}{2(r_\pi + R_B)} \cdot V_d - \frac{\beta R_C}{r_\pi + R_B + 2(1+\beta)R_o} \cdot V_{cm}$$

$$R_B = 0$$

$$\Rightarrow V_o = \frac{\beta R_C}{2r_\pi} V_d - \frac{\beta R_C}{r_\pi + 2(1+\beta)R_o} V_{cm} \quad [2]$$

$$V_o = A_d V_d + A_{cm} V_{cm} \quad [2]$$

$$A_d = \frac{\beta R_C}{2r_\pi} = \frac{g_m r_\pi R_C}{2r_\pi} = \frac{g_m R_C}{2} \quad [2]$$

$$g_m = \frac{I_Q}{2V_T} = \frac{(0.8m)}{2(0.026)} = 15.384 \text{ mA/V} \quad [2]$$

$$r_\pi = \frac{2V_T \beta}{I_Q} = \frac{2(0.026)(100)}{(0.8m)} = 6.5 \text{ k}\Omega \quad [2]$$

$$\Rightarrow A_d = \frac{g_m R_C}{2} = \frac{I_Q R_C}{2V_T} = \frac{I_Q R_C}{2(2V_T)} = \frac{I_Q R_C}{4V_T} = \frac{(0.8m)(12k)}{4(0.026)} = 92.3 \quad [2]$$

$$A_{cm} = \frac{-\beta R_C}{r_\pi + 2(1+\beta)R_o} \quad [2]$$

$$\Rightarrow A_{cm} = \frac{-\beta R_C}{r_\pi + 2(1+\beta)R_o} = \frac{-g_m R_C}{1 + \frac{2(1+\beta)R_o g_m}{\beta}} = \frac{-\frac{I_Q R_C}{2V_T} R_C}{1 + \frac{2(1+\beta)R_o I_Q}{\beta} \frac{R_C}{2V_T}} = -0.237 \quad [2]$$

$$CMRR = \left| \frac{A_d}{A_{cm}} \right| = \left| \frac{92.3}{-0.237} \right| = 389 \quad [4]$$