

Name:  
Student ID Number:  
Section Number: 01/02/03/04/05/06 A/B  
Lecturer: Dr Azni Wati/ Dr Fazrena Azlee/  
Dr Jehana Ermy/ Dr Jamaludin  
Table Number:

**UNIVERSITI  
TENAGA  
NASIONAL**



**College of Engineering**  
Department of Electronics and Communication Engineering

**Test 1**

**SEMESTER 1, ACADEMIC YEAR 2017/2018**

Subject Code : **EEEEB273**  
Course Title : **Electronics Analysis & Design II**  
Date : **8 July 2017**  
Time Allowed : **2 hours**

**Instructions to the candidates:**

1. Write your Name and Student ID Number. Indicate your Section Number and Lecturer's Name. Write also your Table Number.
2. **Write all your answers using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS. Show clearly** all your calculations. Every value **must** be written with its correct Unit.
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**

**NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.**



**GOOD LUCK!**




Question Number	Q1	Q2	Q3	Q4	Total
Marks					

**QUESTION 1 [35 marks]**

- (a) Draw the BJT three-transistor and Wilson current sources with clear details of the transistors  $Q_1$ ,  $Q_2$  and  $Q_3$  placements. [12 marks]
- (b) What are the applications of the BJT three-transistor and Wilson current sources? [3 marks]
- (c) **Figure 1** shows a Widlar current source. Derive an equation that gives the relationship between the reference current,  $I_{REF}$ , and the load current,  $I_O$ . [10 marks]
- (d) Consider a Widlar current source with circuit parameters of  $V^+ = 3\text{ V}$ ,  $V^- = -3\text{ V}$ ,  $V_{BE1(\text{on})} = 0.6\text{ V}$ , and  $V_A = \infty$ . Design the circuit such that  $I_O = 20\text{ }\mu\text{A}$  and  $I_{REF} = 100\text{ }\mu\text{A}$ . Neglect the base currents. [10 marks]

**Answers for Question 1**

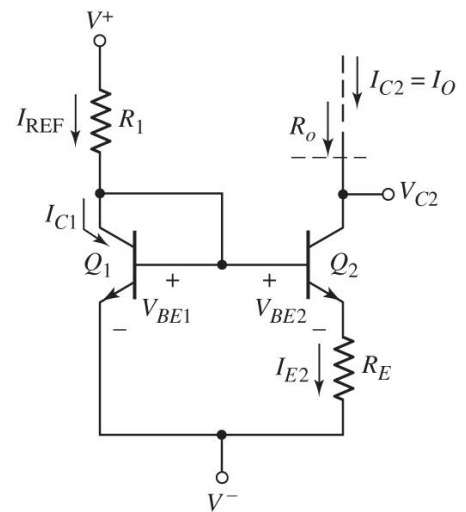

**Figure 1**


**Answers for Question 1 (Continued)**

**QUESTION 2 [20 marks]**

For a MOSFET current source shown in **Figure 2** the circuit parameters are:  $V^+ = 3\text{ V}$  and  $V^- = -3\text{ V}$ . Transistor parameters for N-MOSFET are:  $V_{TN} = 0.5\text{ V}$ ,  $\frac{1}{2}\mu_n C_{ox} = 50\ \mu\text{A/V}^2$  and  $\lambda_n = 0.02\text{ V}^{-1}$ ; and the transistor parameters for P-MOSFET are:  $V_{TP} = -0.55\text{ V}$ ,  $\frac{1}{2}\mu_p C_{ox} = 20\ \mu\text{A/V}^2$  and  $\lambda_p = 0.03\text{ V}^{-1}$ . The transistor aspect ratios are:  $(W/L)_1 = 20$ ,  $(W/L)_2 = 35$ ,  $(W/L)_3 = 5$  and  $(W/L)_4 = 10$ .

- (a) Find  $I_O$ ,  $I_{REF}$  and the  $V_{GS}$  voltages for all transistors if the minimum voltage at the drain of transistor  $M_2$ , i.e.  $V_{D2}$  is **-2.1V**. [12 marks]
- (b) Calculate the change in the output current,  $dI_O$  if  $V_{D2}$  varies from **-1.6V to 0.4V**. [5 marks]
- (c) From the answer calculated in (b) find the output current,  $I_O$  in this condition when  $V_{D2}$  varies from **-1.6V to 0.4V**. [3 marks]

**Answers for Question 2**

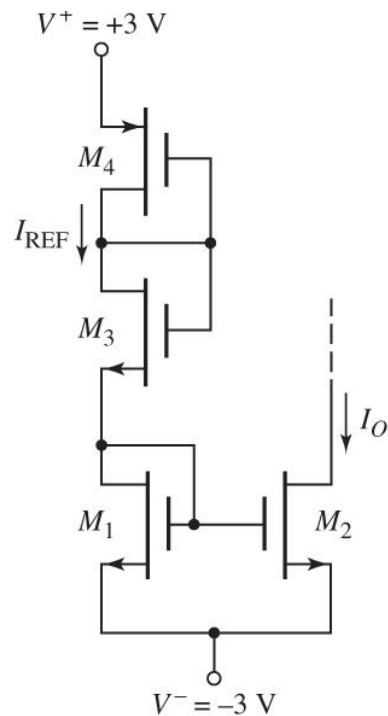

**Figure 2**


**Answers for Question 2 (Continued)**

**QUESTION 3 [25 marks]**

The BJT differential amplifier in Figure 3 is biased by a Cascode current source. Let the biasing current,  $I_Q$ , from the current source is 0.5 mA. The transistor parameters for the circuit shown are  $\beta = 180$ ,  $V_{BE(on)} = 0.7$ , and  $V_A = \infty$  for  $Q_1$  and  $Q_2$ . The differential-mode voltage gain,  $A_d$ , is 223 while the common-mode voltage gain  $A_{cm}$ , is -10.

- (a) Redraw the circuit incorporating the Cascode current source. [5 marks]
- (b) Design the differential amplifier such that  $v_{o2} = 0.4 \text{ V}$  for  $v_1 = v_2 = 0$ . [6 marks]
- (c) Calculate the differential-mode input voltage,  $v_d$ . [4 marks]
- (d) Calculate the common-mode input voltage,  $v_{cm}$ . [4 marks]
- (e) Calculate the output voltage,  $v_o$ , due to  $v_1 = 250 \sin \omega t \text{ } \mu\text{V}$  and  $v_2 = 150 \sin \omega t \text{ } \mu\text{V}$ . [6 marks]

**Answers for Question 3**

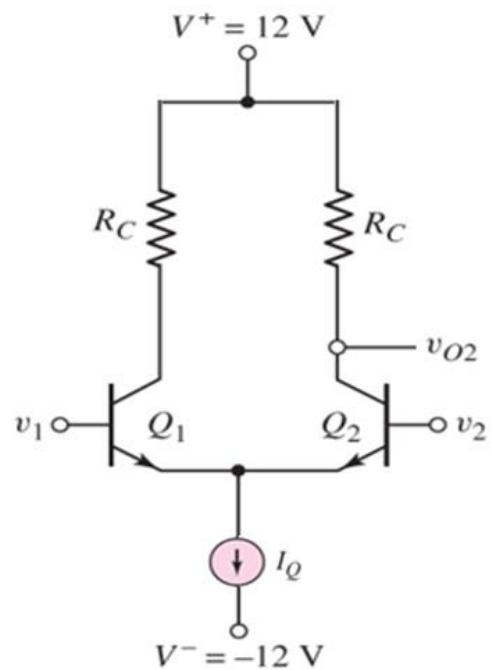


**Figure 3**


**Answers for Question 3 (Continued)**

**QUESTION 4 [20 marks]**

For a **BJT differential amplifier** in **Figure 4 (a)** we can use **Figure 4 (b)** to perform the small-signal circuit analysis.

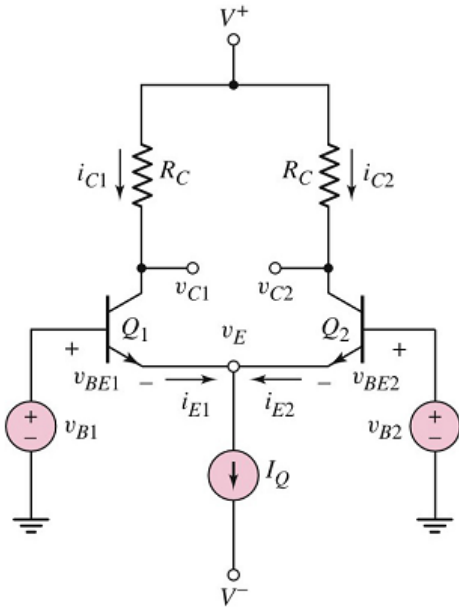

**Figure 4 (a)**

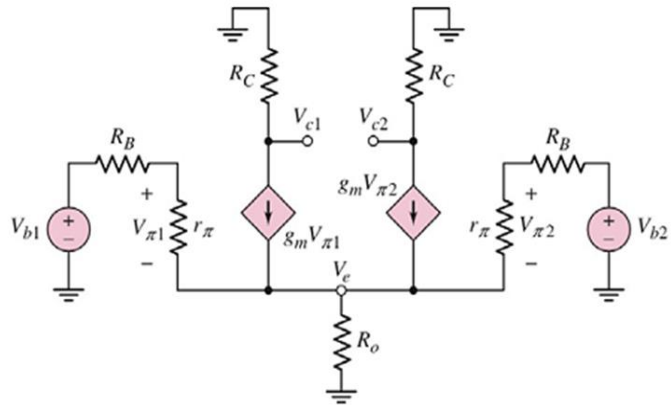

**Figure 4 (b)**

With small-signal circuit analysis, we can derive that **one-sided output voltage ( $V_o$ )** taken at  $V_{c2}$  is given by the following equation:

$$V_o = \frac{\beta R_C}{2(r_{\pi} + R_B)} \cdot V_d - \frac{\beta R_C}{r_{\pi} + R_B + 2(1 + \beta)R_o} \cdot V_{cm}$$

where  $V_d$  is differential-mode input voltage,  $V_{cm}$  is common-mode input voltage,  $R_B$  is output resistance for input signals  $V_{b1}$  and  $V_{b2}$ , and  $R_o$  is output resistance looking into the constant-current source that is biasing the diff-amp.

**Consider** the circuit in the **Figure 4 (a)** with parameters  $V^+ = 10 \text{ V}$ ,  $V^- = -10\text{V}$ ,  $I_Q = 0.8 \text{ mA}$ , and  $R_C = 12 \text{ k}\Omega$ . Transistor parameters are  $\beta = 100$  and  $V_A = \infty$ . Assume  $R_o = 25 \text{ k}\Omega$  and  $R_B = 0$ .

**Calculate** differential-mode gain ( $A_d$ ), common-mode gain ( $A_{cm}$ ), and the common-mode rejection ratio (**CMRR**) of the diff-amp. [20 marks]





**Answers for Question 4**

## BASIC FORMULA FOR TRANSISTOR

### BJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

;Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

Quadratic formula :

$$Ax^2 + Bx + C = 0 \quad \rightarrow \quad x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$

### MOSFET

;N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{k'_n}{2} \cdot \frac{W}{L}$$

;P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{k'_p}{2} \cdot \frac{W}{L}$$

;Small signal

$$g_m = 2\sqrt{K_n I_{DQ}} \quad ; \text{N - MOSFET}$$

$$g_m = 2\sqrt{K_p I_{DQ}} \quad ; \text{P - MOSFET}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$