

Name:
Student ID Number:
Section Number: 01/02/03/04/05/06 A/B
Lecturer: Dr Azni Wati/ Dr Fazrena Azlee/
Dr Jehana Ermy/ Dr Jamaludin
Table Number:

**UNIVERSITI
TENAGA
NASIONAL**



College of Engineering
Department of Electronics and Communication Engineering

Test 2 SOLUTION

SEMESTER 1, ACADEMIC YEAR 2017/2018

Subject Code : **EEEEB273**
Course Title : **Electronics Analysis & Design II**
Date : **19 August 2017**
Time Allowed : **2 hours**

Instructions to the candidates:

1. Write your Name and Student ID Number. Indicate your Section Number and Lecturer's Name. Write also your Table Number.
2. **Write all your answers using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS. Show clearly** all your calculations. Every value **must** be written with its correct Unit.
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.



GOOD LUCK!




Question Number	Q1	Q2	Q3	Q4	Total
Marks					

QUESTION 1 [20 marks]

Answers for Question 1 (Continued)

Answer Guide:

(a)

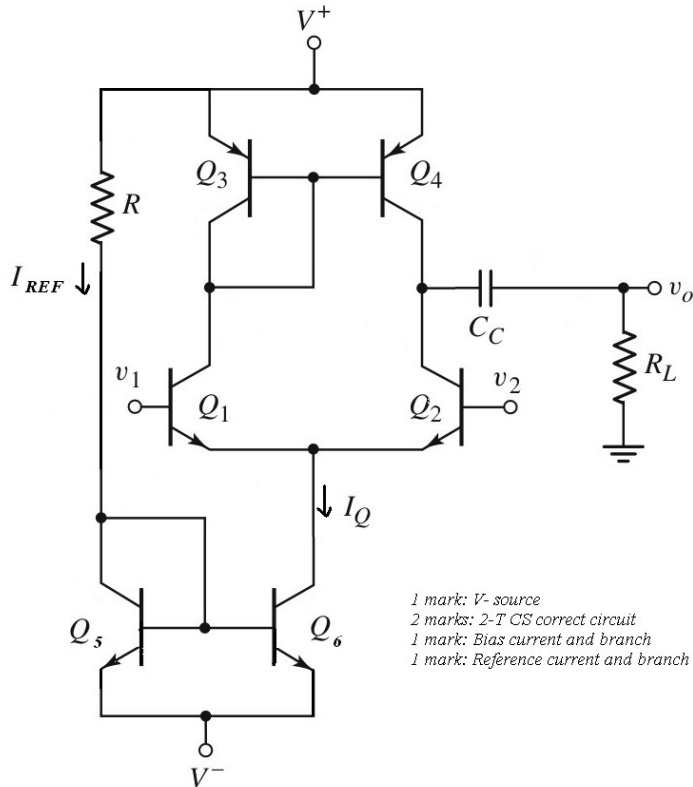

1 mark: V^- source
 2 marks: 2-T CS correct circuit
 1 mark: Bias current and branch
 1 mark: Reference current and branch

(b)

$$v_o = g_m v_d (r_{O2} || r_{O4}) \quad [1.5]$$

$$A_d = \frac{v_o}{v_d} = g_m (r_{O2} || r_{O4}) \quad [1]$$

$$g_m = \frac{I_{Q/2}}{v_T} = \frac{0.25m/2}{0.026} = 4.808mA/V \quad [1.5]$$

$$r_{O2} = \frac{V_{AN}}{I_{Q/2}} = \frac{120}{0.125m} = 960 \text{ k}\Omega \quad [2]$$

$$r_{O4} = \frac{V_{AP}}{I_{Q/2}} = \frac{100}{0.125m} = 800 \text{ k}\Omega \quad [2]$$

$$r_{O2} || r_{O4} \rightarrow \frac{960k \times 800k}{960k + 800k} = 436.4 \text{ k}\Omega \quad [1]$$

$$A_d = 4.808 \text{ m} \times 436.4 \text{ k} = 2098 \quad [1]$$

(c)

$$v_o = g_m v_d (r_{O2} || r_{O4} || R_L) \quad [1]$$

$$A_d = \frac{v_o}{v_d} = g_m (r_{O2} || r_{O4} || R_L) \quad [1]$$

$$r_{O2} || r_{O4} || R_L \rightarrow \frac{436.4k \times 150k}{436.4k + 150k} = 111.63k\Omega \quad [2]$$

$$A_d = 4.808 \text{ m} \times 111.63 \text{ k} = 536.7 \quad [1]$$

QUESTION 2 [35 marks]

Answers for Question 2 (Continued)

2a) 12 marks

$$I_{set} = I_{DF} = \frac{V^+ - V^- - V_{SGF}}{R_{set}} = \frac{5 - (-5) - V_{SGF}}{15k} \quad [1]$$

$$I_{DF} = K_{pF}(V_{SGF} + V_{TP})^2 = 0.5(20u)(10)(V_{SGF} - 2)^2 \quad [1]$$

Simultaneous equation: $10 - V_{SGF} = (15k)(0.5)(20u)(10)(V_{SGF} - 2)^2$
 $\Rightarrow V_{SGF} = 4V, -0.67V. \quad [2]$

Choose $V_{SGF} = 4V$, since $> |V_{TP}| \quad [1]$

$$I_{set} = (10 - 4) / 15k = 0.4mA \quad [1]$$

$I_{set} = I_Q$ since W/L for ME and MF are the same $[1]$

$$I_{DA} = I_{DC} = I_Q / 2 = 0.4mA / 2 = 0.2mA \quad [1]$$

$$I_{DA} = K_{PA}(V_{SGA} + V_{TP})^2 = 0.2mA$$

$$\Rightarrow V_{SGA} = -2 + \text{SQRT}(0.2mA / (10u)(20)) = 3V \quad [2]$$

$$I_{DC} = K_{NC}(V_{GSC} - V_{TN})^2 = 0.2mA$$

$$\Rightarrow V_{GSC} = 2 + \text{SQRT}(0.2mA / (20u)(15)) = 2.82V \quad [2]$$

2b) 8 marks

$$A_d = g_{mA}(r_{oB} \parallel r_{oD}) \quad [2]$$

$$g_{mA} = 2\sqrt{K_{PA}I_{DA}} = 2\sqrt{\left(\frac{k'_p}{2}\right)\left(\frac{W}{L}\right)_A I_{DA}} = 2\sqrt{\left(\frac{20\mu}{2}\right)(20)(0.4mA)} = 0.4mA/V \quad [1]$$

$$r_{oB} = \frac{1}{\lambda_p I_{DB}} = \frac{1}{(0.02)(0.2mA)} = 250\Omega \quad [2]$$

$$r_{oD} = \frac{1}{\lambda_n I_{DD}} = \frac{1}{(0.01)(0.2mA)} = 500k\Omega \quad [2]$$

$$A_d = (0.4mA)(250k \parallel 500k) = 66.67V/V \quad [1]$$

2c) 5 marks

$$A_{dnew} = g_{mA}(r_{oB} \parallel r_{oD} \parallel R_{in2}) \quad [2]$$

$$A_{dnew} = (0.4mA)(167.7k \parallel 200M) \approx 66.67V/V \quad [1]$$

$$A_v = A_d \times A_{v2} = 66.67 \times 80 = 5330 V/V \quad [2]$$


2d) 5 marks

3rd transistor between ME and diff-pair [2]
 Correct connection for Wilson current source [2]
 Correction connection between Wilson output node and diff pair [1]

2e) 5 marks

Advantage of Wilson over 2T:
 Increased R_o , [2] hence CMRR of diff -amp will increase [1]

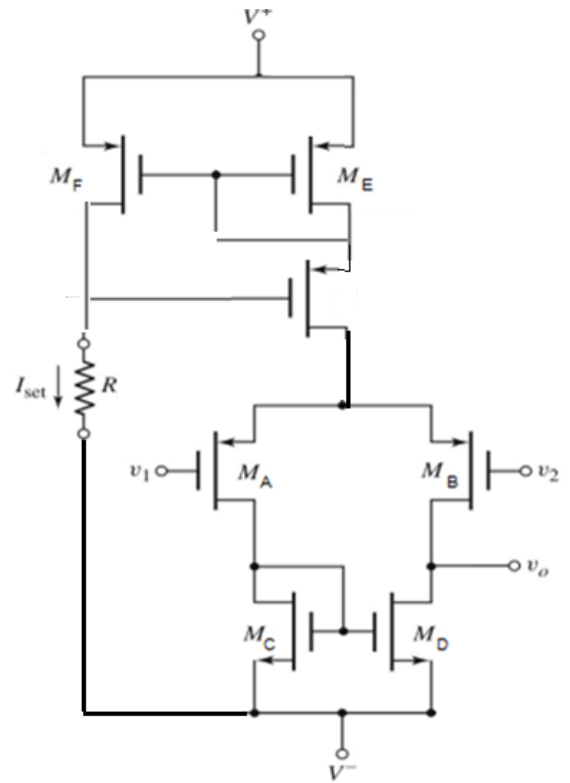Disadvantage of Wilson over 2T:
 Since additional transistor, decreased input and/or output voltage swing [2]



QUESTION 3 [20 marks]

(i) $v_{o(min)} = V + C_{E2(sat)} = -5 + 0.38 = -4.62 \text{ V}$ [2]

$v_{o(max)} = V^+ - C_{EI(sat)} = 7 - 0.38 = 6.62 \text{ V}$

BUT for symmetrical swing of class-A, $v_{o(max)} = |v_{o(min)}| = +4.62 \text{ V}$ [2]

(ii) $I_Q = |v_{o(min)}|/R_L = 4.62/1k = 4.62 \text{ mA}$ [2]

(iii) $i_{E1} = I_Q + I_L$ [1]

$i_{E1} (\text{max}) = I_Q + V_{o(max)}/R_L = 2I_Q = 9.24\text{mA}$ [1.5]

$i_{E1} (\text{min}) = I_Q + V_{o(min)}/R_L = 0$ [1.5]

(iv) $v_{I(max)} = v_{o(max)} + V_{BE} = 4.62 + 0.7 = 5.32 \text{ V}$ [1.5]

$v_{I(min)} = v_{o(min)} + V_{BE} = -4.62 + 0.7 = -3.92 \text{ V}$ [1.5]

(v) $\eta = (\overline{P}_L) / (\overline{P}_S) \times 100 \%$ [1]

$(\overline{P}_L) = V_p^2 / 2R_L = (4.62)^2 / (2)(1k) = 10.67 \text{ mW}$ [3]

$(\overline{P}_S) = (\overline{P}_S^+ + \overline{P}_S^-) = (7) I_Q + 2 (5) I_Q = 2[(0 - (-5))(4.62\text{m})] = 78.54\text{mW}$ [2]

$\eta = 10.67/78.54 \times 100\% = 13.6\%$ [1]

QUESTION 4 [25 marks]**Answers for Question 4**

$$I_{C6} = \frac{\beta}{1+\beta} I_{E6} = \frac{\beta}{1+\beta} I_{B7} = \frac{\beta}{1+\beta} \frac{I_{C7}}{\beta} = \frac{I_{C7}}{1+\beta} \quad [3]$$

$$I_{C6} = \frac{0.2\text{m}}{101} = 0.00198 \text{ mA} = 1.98 \mu\text{A} \quad [2]$$

$$R_i = r_{\pi6} + r_{\pi7}(1+\beta) \quad [2]$$

$$r_{\pi7} = \frac{\beta V_T}{I_{C7}} = \frac{100(26\text{m})}{0.2\text{m}} = 1.3\text{k}\Omega \quad [2]$$

$$r_{\pi6} = \frac{\beta V_T}{I_{C6}} = \frac{(1+\beta)\beta V_T}{I_{C7}} = \frac{(101)100(26\text{m})}{0.2\text{m}} = 1.313\text{M}\Omega \quad [2]$$

$$R_i = \frac{2(1+\beta)\beta V_T}{I_{C7}} = \frac{2(101)(100)(26\text{m})}{0.2\text{m}} = 2.626 \text{ M}\Omega \quad [1]$$

$$R_{L7} = R_{c11} \parallel R_{b8} \quad [2]$$

$$R_{c11} = r_{o11} = V_{A11} / I_{C11} = 100 / 0.2\text{m} = 500 \text{ k}\Omega \quad [3]$$

$$R_{b8} = r_{\pi8} + (1+\beta)R_2 \quad [2]$$

$$r_{\pi8} = \frac{\beta V_T}{I_{C8}} = \frac{100(26\text{m})}{1.3\text{m}} = 2 \text{ k}\Omega \quad [2]$$

$$R_{b8} = 2\text{k} + 101(12\text{k}) = 1.214 \text{ M}\Omega \quad [1]$$

$$R_{L7} = 500\text{k} \parallel 1.214\text{M} = 354.14 \text{ k}\Omega = 0.35414 \text{ M}\Omega \quad [1]$$

$$A_v = \frac{\beta(1+\beta)R_{L7}}{R_i} = \frac{100(101)(0.35414\text{M})}{2.626\text{M}} = 1362.077 \quad [2]$$