

Name:
Student ID Number:
Section Number: 01/02/03/04/05/06 A/B
Lecturer: Dr Azni Wati/ Dr Fazrena Azlee/
Dr Jehana Ermy/ Dr Jamaludin
Table Number:

**UNIVERSITI
TENAGA
NASIONAL**



College of Engineering
Department of Electronics and Communication Engineering

Test 2

SEMESTER 1, ACADEMIC YEAR 2017/2018

Subject Code : **EEEEB273**
Course Title : **Electronics Analysis & Design II**
Date : **19 August 2017**
Time Allowed : **2 hours**

Instructions to the candidates:

1. Write your Name and Student ID Number. Indicate your Section Number and Lecturer's Name. Write also your Table Number.
2. **Write all your answers using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS. Show clearly** all your calculations. Every value **must** be written with its correct Unit.
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.



GOOD LUCK!



Question Number	Q1	Q2	Q3	Q4	Total
Marks					

APPENDIX

A) BASIC FORMULA FOR TRANSISTOR

BJT

$$i_C = I_S e^{v_{BE}/V_T} \quad ; \text{NPN}$$

$$i_C = I_S e^{v_{EB}/V_T} \quad ; \text{PNP}$$

$$i_C = \beta i_B = \frac{\beta}{\beta + 1} i_E$$

$$i_E = i_B + i_C$$

; Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

MOSFET

; N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k'_n}{2} \cdot \frac{W}{L}$$

; P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k'_p}{2} \cdot \frac{W}{L}$$

; Small signal


$$g_m = 2\sqrt{K_n I_{DQ}} \quad ; \text{N – MOSFET}$$

$$g_m = 2\sqrt{K_p I_{DQ}} \quad ; \text{P – MOSFET}$$


$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

B) HYBRID- π EQUIVALENT CIRCUITS

BJT

 

MOSFET

 

C) QUADRATIC FORMULA

$$Ax^2 + Bx + C = 0 \quad \rightarrow \quad x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$

QUESTION 1 [20 marks]

The differential amplifier in **Figure 1** has a pair of transistors forming an active load. A two-transistor current source is added to bias a constant current source of **0.25 mA**. (Note: $I_Q = 0.25$ mA). The transistor parameters are $\beta = 100$, $V_{BE}(\text{on}) = V_{EB}(\text{on}) = 0.7$ V, $V_{AN} = 120$ V, and $V_{AP} = 100$ V.

- (i) Draw a complete circuit for **Figure 1** with the active load and the bias circuit. [5 marks]
- (ii) Determine the differential-mode voltage gain, $A_d = v_o/v_d$. [10 marks]
- (iii) Calculate the differential-mode voltage gain if the load resistance, R_L , is 150 k Ω . [5 marks]

Answers for Question 1

 


Figure 1

Answers for Question 1 (continued)

QUESTION 2 [35 marks]

The MOSFET differential amplifier shown in Figure 2 below is connected to supply voltages of $V^+ = +5V$ and $V^- = -5V$. The value of R_{set} is $15\text{ k}\Omega$. Transistor parameters for **N-MOSFET** are: $V_{TN} = 2\text{ V}$, $k_n' = 40\ \mu\text{A/V}^2$ and $\lambda_n = 0.01\text{ V}^{-1}$; and the transistor parameters for **P-MOSFET** are: $V_{TP} = -2\text{ V}$, $k_p' = 20\ \mu\text{A/V}^2$ and $\lambda_p = 0.02\text{ V}^{-1}$. The transistor aspect ratios are $(W/L)_{A,B} = 20$, $(W/L)_{C,D} = 15$ and $(W/L)_{E,F} = 10$.

- (a) Calculate the values of I_{set} , I_Q , V_{SGA} and V_{SGC} . [12 marks]
- (b) Determine the gain of the differential amplifier. [8 marks]
- (c) Another amplifier is connected at the output of the differential amplifier as a second gain stage, to form a multistage amplifier circuit. If the second gain stage has input impedance R_{in2} of $200\text{M}\Omega$ and gain $A_{V2} = 80\text{ V/V}$, calculate the overall gain of the multistage circuit. [5 marks]
- (d) The biasing current source circuit generating I_Q for the differential amplifier is now changed to a Wilson current source.
 - i) Sketch the circuit in Figure 2 with its new biasing current source circuit. [5 marks]
 - ii) Discuss the advantage and disadvantage of using the Wilson current source over the two-transistor current source for biasing the differential amplifier circuit. [5 marks]

Answers for Question 2

 


Figure 2

Answers for Question 2 (Continued)

QUESTION 3 [20 marks]

Consider the **Class- A** amplifier circuit shown in Figure 3. Assume all transistors are matched with $V_{BE}(\text{on}) = 0.7 \text{ V}$, $V_{CE}(\text{sat}) = 0.38 \text{ V}$, and is very large β is very large. Determine the following:

- (i) The range of the maximum symmetrical output voltage swing. [4 marks]
- (ii) The required bias current I_Q for Class-A operation. [2 marks]
- (iii) Maximum and minimum amplifier current ($i_{E1(\text{max})}$ and $i_{E1(\text{min})}$). [4 marks]
- (iv) Maximum and minimum input voltage ($v_{I(\text{max})}$ and $v_{I(\text{min})}$). [3 marks]
- (v) Power conversion efficiency of the amplifier, η . [7 marks]

Answers for Question 3

 


Figure 3

Answers for Question 3 (Continued)

QUESTION 4 [25 marks]

Consider the circuit shown in **Figure 4**. Study the **Figure 4** thoroughly and *notice that biasing for the amplifiers in the circuit is provided by two-transistor current mirrors*.

The circuit parameters for the **Figure 4** are $I_{C7} = I_{C11} = 0.2 \text{ mA}$, $I_{C8} = 1.3 \text{ mA}$, and $R_2 = 12 \text{ k}\Omega$. Assume $\beta = 100$ for all transistors and the **Early voltage** for Q_{11} is **100 V**.

Using small-signal analysis, the small-signal voltage gain (A_v) for the **Darlington Pair** in the gain stage can be found using the following formula:

$$A_v = \frac{\beta(1 + \beta)R_{L7}}{R_i}$$

Calculate the value of I_{C6} and the value of small-signal voltage gain (A_v) for the Darlington Pair in the gain stage. [25 marks]

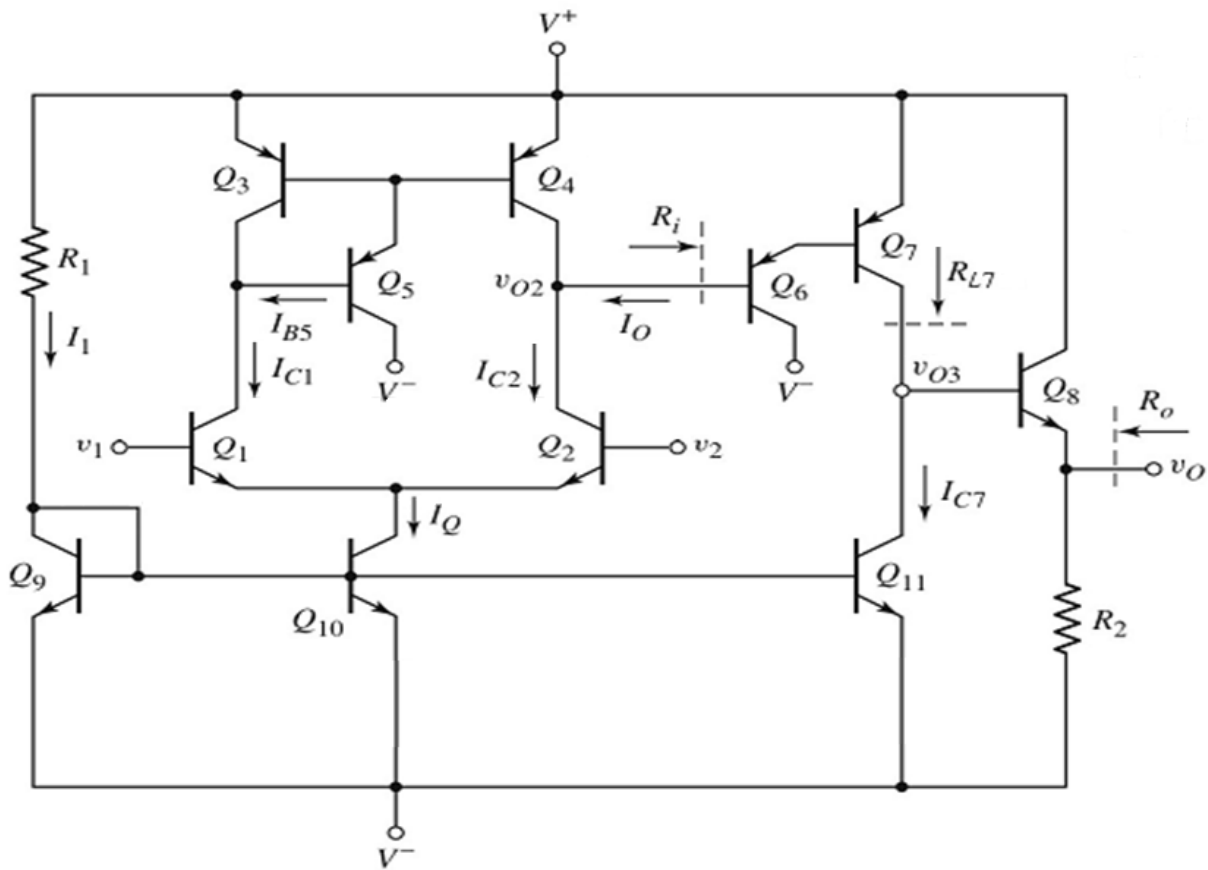


Figure 4

Answers for Question 4