

**COLLEGE OF ENGINEERING
PUTRAJAYA CAMPUS
FINAL EXAMINATION**

SEMESTER 2 2017 / 2018

PROGRAMME : **Bachelor of Electrical & Electronics Engineering (Honours)
Bachelor of Electrical Power Engineering (Honours)**

SUBJECT CODE : **EEEB273**

SUBJECT : **ELECTRONIC ANALYSIS AND DESIGN II**

DATE : **January/February 2018**

TIME : **3 hours**

INSTRUCTIONS TO CANDIDATES:

1. This paper contains **FIVE (5)** questions in **NINE (9)** pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided. Use **pen** to write your answer.
4. Write answer to different question on a **new page**.

THIS QUESTION PAPER CONSISTS OF NINE (9) PRINTED PAGES INCLUDING THIS COVER PAGE.

Question 1 [20 marks]

Answers to QUESTION 1

<p>(a) <u>Two-transistor current source</u></p> <p>Total 5 marks <u>Placement of Q1 and Q2 [2 marks]</u> <u>Resistor R1 [1 marks]</u> <u>IREF and IO labels [2 marks]</u></p>	<p><u>Widlar current source</u></p> <p>Total 5 marks <u>Placement of Q1 and Q2 [2 marks]</u> <u>Resistors R1 and RE [2 marks]</u> <u>IREF and IO labels [1 mark]</u></p>
---	--

- (b) $I_{C1} = I_{REF} = I_S e^{(V_{BE1}/V_T)} \dots(1)$ [1 mark]
 $I_{C2} = I_O = I_S e^{(V_{BE2}/V_T)} \dots(2)$ [1 mark]
 $V_{BE1} - V_{BE2} = I_O R_E \dots (3)$ [1 mark]
 $V_{BE1} = V_T \ln (I_{REF}/I_S)$ and $V_{BE2} = V_T \ln (I_O/I_S)$
 $I_O R_E = V_T \ln (I_{REF}/I_S) - V_T \ln (I_O/I_S)$ [1 mark]
 $= V_T \ln (I_{REF}/I_O)$ (proven) [1 mark]

(c) Using $I_C = I_S e^{\frac{V_{BE}}{V_T}}$;

$$I_S = \frac{I_{C1}}{e^{\frac{V_{BE}}{V_T}}} = \frac{1m}{e^{0.7/0.026}} = \underline{2.03 \times 10^{-15} \text{ A}}$$

At $I_{REF} = 3 \text{ mA}$, $V_{BE} = V_T \ln (I_{REF}/I_S)$
 So $V_{BE} = (0.026) \ln(3m / 2.03 \times 10^{-15}) = \underline{0.7286 \text{ V}}$

Designing for R_I ;

$$V^+ - I_{REF}R_I - V_{BE1} - V^- = 0$$

$$R_I = (20 - 0.7286) / 3m = \underline{6.423 \text{ k}\Omega}$$

Designing for R_E ;

$$I_O R_E = V_T \ln(I_{REF}/I_O)$$

$$R_E = (V_T/I_O) \ln(I_{REF}/I_O) = (0.026/50\mu) \ln(3m/50\mu) = \underline{2.129 \text{ k}\Omega}$$

Question 2 [20 marks]**Answer to Q2(a):**

$$I_{REF} = (V^+ - V_{BE5} - V_{BE3} - V^-) / (R_1) \approx I_Q (\beta = 200) \quad [2 \text{ marks}]$$

$$= (10 - 0.7 - 0.7 - (-10)) / (10k) = 1.86 \text{ mA} \quad [2 \text{ marks}]$$

$$A_d = (g_m RC) / 2 = (I_Q RC) / (4V_T) \quad [2 \text{ marks}]$$

$$g_m = I_Q / (2V_T) = (1.86m) / (2 \times 26m) = 35.7692 \text{ mA/V} \quad [2 \text{ marks}]$$

$$A_d = (35.7692m)(12.8k) / (2) = 228.923 \text{ V/V} \quad [2 \text{ marks}]$$

Answer to Q2(b):*Q2b(i)*

$$A_d = g_{m2}(r_{o2} \parallel r_{o4}) \quad [1]$$

$$g_{m2} = \frac{I_{CQ}}{V_T} = \frac{0.5m/2}{26m} = 9.615 \text{ mA/V} \quad [1]$$

$$r_{o2} = \frac{V_{A2}}{I_{CQ}} = \frac{120}{0.5m/2} = 480 \text{ k}\Omega \quad [1]$$

$$r_{o4} = \frac{V_{A4}}{I_{CQ}} = \frac{80}{0.5m/2} = 320 \text{ k}\Omega \quad [1]$$

$$A_d = (9.615m)(480k \parallel 320k) = 1846.08 \quad [1]$$

Q2b(ii)

$$R_o = r_{o2} \parallel r_{o4} = 480k \parallel 320k = 192 \text{ k}\Omega \quad [2]$$

Q2b(iii)

$$A_d = g_{m2}(r_{o2} \parallel r_{o4} \parallel R_L) \quad [1]$$

$$A_d = (0.75)(1846) = 1384.5 = (9.615m)(480k \parallel 320k \parallel R_L) \quad [1]$$

$$R_L = 1394.5 \text{ k}\Omega \quad [1]$$

Question 3 [20 marks]

Answers:

Q3(a)

$$I_1 = [V^+ - V - V_{BE}] / R_1 = (10 - 0.7) / 18.6k = 0.5 \text{ mA} \quad [1]$$

$$I_Q R_2 = V_T \ln(I_1 / I_Q)$$

$$I_Q (59.6) = (0.026) \ln(0.5 \text{ mA} / I_Q) \rightarrow I_Q = 0.27 \text{ mA} = I_{C8} \quad [2]$$

$$I_{C2} = 0.135 \text{ mA} \quad (\text{Neglect base current in } Q1 \text{ and } Q2) \quad [1]$$

$$I_{R4} = [V^+ - I_{C2} R_C - V_{BE3} - V_{BE4}] / R_4$$

$$I_{R4} = [2.3 - 2(0.7)] / 11.5k = 78.26 \text{ uA} = I_{C4} \quad (\text{Neglect base current}) \quad [2]$$

$$I_{C3} = I_{C4} / (1 + \beta) = (78.26 \text{ u}) / (151) = 0.5217 \text{ uA} \quad [2]$$

$$I_{C6} \cong I_{E6} = (v_o - V) / R_7 = (-0.1316 + 5) / 5k = 0.9737 \text{ mA} \quad [2]$$

Q3(b)

$$A_d = v_o / v_d = (v_{O2} / v_d)(v_{O3} / v_{O2})(v_o / v_{O3}) = A_{d1} A_{v2} A_{v3} \quad [1]$$

$$A_{d1} = (g_{m2} / 2)(R_C \parallel R_{i2}) \quad [1]$$

$$g_{m2} = I_{CQ2} / V_T = I_Q / (2V_T) = (0.27 \text{ mA}) / (2 \times 0.026) = 5.912 \text{ mA/V} \quad [0.5]$$

$$r_{\pi4} = \beta V_T / I_{C4} = (150 \times 26 \text{ m}) / (78.26 \text{ u}) = 49.83 \text{ k}\Omega \quad [0.5]$$

$$r_{\pi3} = \beta V_T / I_{C3} = (150 \times 26 \text{ m}) / (0.5217 \text{ u}) = 7.476 \text{ M}\Omega \quad [0.5]$$

$$R_{i2} = r_{\pi3} + (1 + \beta) r_{\pi4} = 7.476 \text{ M} + (151)(49.83 \text{ k}) = 14.92 \text{ M}\Omega \quad [1.5]$$

$$A_{d1} = (0.5)(5.912 \text{ mA})(20 \text{ k} \parallel 14.92 \text{ M}) = 59.04 \quad [0.5]$$

$$A_{v2} = \frac{\beta(1 + \beta)(R_5 \parallel R_{i3})}{R_{i2}} = \frac{(150)(151)(5 \text{ k})}{14.92 \text{ M}} = 7.59 \quad [2.5]$$

$$A_{v3} \approx 1 \quad [1]$$

$$A_d = (59.04)(7.59)(1) = 448.1 \quad [1]$$

Question 4 [20 marks]

Answers:

Q4(a)

$$P_L(ave) = 10 = (1/2)(V_p^2/R_L) \quad [1]$$

$$V_p = 0.8 V_{CC} = (0.8)(24) = 19.2 \text{ V} \quad [1]$$

$$R_L = (1/2)[V_p^2/P_L(ave)] = \text{SQR}(19.2) / [(2)(10)] = 18.43 \ \Omega \quad [2]$$

$$P_S(ave) = 2V_{CC}I = 2(24)(19.2/[(\pi)(18.43)]) = 15.92 \text{ Watts} \quad [4]$$

$$\eta = P_L(ave) / P_S(ave) = 10/15.92 = 0.628 \text{ or } 62.8\% \quad [2]$$

Q4b(i)

$$I_{D5} = K_{p5}(V_{SG5} + V_{TP})^2 = (125\mu) \times (1.5 - 0.5)^2 = 125 \mu\text{A} \quad [2]$$

$$I_Q = I_{D6} = I_{D7} = I_{D8} = I_{D5} = 125 \mu\text{A} \quad [1]$$

$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = I_Q / 2 = 62.5\mu\text{A} \quad [1]$$

Q4b(ii)

$$A_d = g_{m2}(r_{o2} \parallel r_{o4}) \quad [1]$$

$$g_{m2} = \sqrt{2K_p I_Q} = \sqrt{2(125\mu)(125\mu)} = 176.77 \mu\text{A/V} \quad [0.5]$$

$$r_{o2} = \frac{1}{\lambda_p I_{D2}} = \frac{1}{0.02 \times 62.5\mu} = 0.8 \text{ M}\Omega \quad [0.5]$$

$$r_{o4} = \frac{1}{\lambda_n I_{D4}} = \frac{1}{0.01 \times 62.5\mu} = 1.6 \text{ M}\Omega \quad [0.5]$$

$$A_d = (176.77\mu)(0.8\text{M} \parallel 1.6\text{M}) = 94.277 \quad [0.5]$$

$$A_{v2} = -g_{m7}(r_{o7} \parallel r_{o8})$$

$$g_{m7} = 2\sqrt{K_{n7} I_{D7}} = 2\sqrt{(100\mu)(125\mu)} = 223.6 \mu\text{A/V} \quad [0.5]$$

$$r_{o7} = \frac{1}{\lambda_n I_{D7}} = \frac{1}{0.01 \times 125\mu} = 0.8 \text{ M}\Omega \quad [0.5]$$

$$r_{o8} = \frac{1}{\lambda_p I_{D8}} = \frac{1}{0.02 \times 125\mu} = 0.4 \text{ M}\Omega \quad [0.5]$$

$$A_{v2} = -(223.6\mu)(0.8\text{M} \parallel 0.4\text{M}) = -59.63 \quad [0.5]$$

$$A_v = A_d A_{v2} = 94.277 \times (-59.63) = -5618.61 \quad [1]$$

Question 5 [20 marks]

Answers:

Q5(a)

$$A_v = v_o / v_I = - (R_2 + R_{2V}) / (R_1 + R_{1V}) \quad [2]$$

$$R_1 (\text{min}) = R_1 = 20 \text{ k}\Omega \quad [1]$$

$$R_1 (\text{max}) = R_1 + R_{1V} = 20 \text{ k}\Omega + 30 \text{ k}\Omega = 50 \text{ k}\Omega \quad [1]$$

$$R_2 (\text{min}) = R_2 = 30 \text{ k}\Omega \quad [1]$$

$$R_2 (\text{max}) = R_2 + R_{2V} = 30 \text{ k}\Omega + 40 \text{ k}\Omega = 70 \text{ k}\Omega \quad [1]$$

Absolute value of A_v is maximum when:

$$A_v(\text{max}) = \mathbf{ABS}(- R_2(\text{max}) / R_1 (\text{min})) \quad [1]$$

$$\Rightarrow A_v(\text{max}) = \mathbf{ABS}(-70\text{k}/20\text{k}) = 3.5 \text{ V/V} \quad [1]$$

Absolute value of A_v is minimum when:

$$A_v(\text{min}) = \mathbf{ABS}(- R_2(\text{min}) / R_1(\text{max})) \quad [1]$$

$$\Rightarrow A_v(\text{min}) = \mathbf{ABS}(-30\text{k}/50\text{k}) = 0.6 \text{ V/V} \quad [1]$$

Q5(b)

$$v_o = -10v_{I1} - 5v_{I2} + 2v_{I3} + 5v_{I4}$$

$$R_F / R_1 = 10 \quad \rightarrow R_F = 10 R_1 \quad [1]$$

and $R_F / R_2 = 5 \quad \rightarrow R_F = 5 R_2 \quad [1]$

Given $R_1 = 50 \text{ k}\Omega$,

$$\rightarrow R_F = 10 R_1 = 10 \times 50 \text{ k}\Omega = 500 \text{ k}\Omega \quad [1]$$

and $R_2 = R_F / 5 = 500 \text{ k}\Omega / 5 = 100 \text{ k}\Omega \quad [1]$

$$R_N = R_1 \parallel R_2 = 50 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 33.333 \text{ k}\Omega$$

$$1 + R_F / R_N = 1 + 500\text{k} / (33.333\text{k}) = 16 \quad [0.5]$$

$$(1 + R_F / R_N)(R_P / R_A) = (16) (R_P / R_A) = 3 \quad [1]$$

and $(1 + R_F / R_N)(R_P / R_B) = (16) (R_P / R_B) = 5 \quad [1]$

So, $(R_A / R_B) = 5/3 \quad [1]$

Given $R_A = 240 \text{ k}\Omega$,

then $R_B = (3 R_A) / 5 = 144 \text{ k}\Omega \quad [1]$

$$R_P = (5 R_B) / 16 = (3 R_A) / 16$$

$$\rightarrow R_P = 45 \text{ k}\Omega \quad [0.5]$$

$$R_P = R_A \parallel R_B \parallel R_C$$

$$\rightarrow R_C = 53.34 \text{ k}\Omega \quad [1]$$

APPENDIX:

A) BASIC FORMULA FOR TRANSISTOR

BJT

$$i_C = I_S e^{v_{BE}/V_T} \quad ; \text{NPN}$$

$$i_C = I_S e^{v_{EB}/V_T} \quad ; \text{PNP}$$

$$i_C = \beta i_B = \frac{\beta}{\beta + 1} i_E$$

$$i_E = i_B + i_C$$

;Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

MOSFET

; N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k'_n}{2} \cdot \frac{W}{L}$$

; P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k'_p}{2} \cdot \frac{W}{L}$$

;Small signal


$$g_m = 2\sqrt{K_n I_{DQ}} \quad ; \text{N – MOSFET}$$

$$g_m = 2\sqrt{K_p I_{DQ}} \quad ; \text{P – MOSFET}$$


$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

B) HYBRID- π EQUIVALENT CIRCUITS

BJT

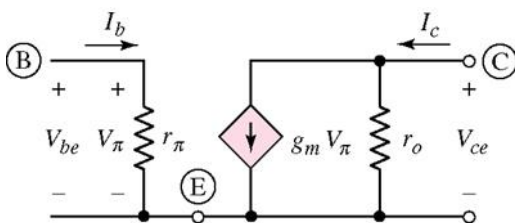

MOSFET

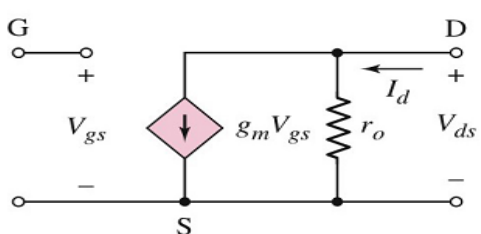

C) QUADRATIC FORMULA

$$Ax^2 + Bx + C = 0 \quad \rightarrow \quad x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$