

**COLLEGE OF ENGINEERING
PUTRAJAYA CAMPUS
FINAL EXAMINATION**

SEMESTER 2 2017 / 2018

PROGRAMME : **Bachelor of Electrical & Electronics Engineering (Honours)
Bachelor of Electrical Power Engineering (Honours)**

SUBJECT CODE : **EEEB273**

SUBJECT : **ELECTRONIC ANALYSIS AND DESIGN II**

DATE : **January/February 2018**

TIME : **3 hours**

INSTRUCTIONS TO CANDIDATES:

1. This paper contains **FIVE (5)** questions in **NINE (9)** pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided. Use **pen** to write your answer.
4. Write answer to different question on a **new page**.

THIS QUESTION PAPER CONSISTS OF NINE (9) PRINTED PAGES INCLUDING THIS COVER PAGE.

Question 1 [20 marks]

- (a) **Draw** the npn BJT **two-transistor** and **Widlar** current sources with clear details of the transistors Q_1 and Q_2 placements. **[10 marks]**
- (b) **Show** that $I_O R_E = V_T \ln\left(\frac{I_{REF}}{I_O}\right)$ for the BJT **Widlar** current source. **[5 marks]**
- (c) **Design** the BJT **Widlar** current source from your drawing in part (a) such that currents $I_{REF} = 3 \text{ mA}$ and $I_O = 50 \text{ }\mu\text{A}$. The circuit parameters are $V^+ = 10 \text{ V}$ and $V^- = -10 \text{ V}$. The transistors are matched with $V_{BE} = 0.7 \text{ V}$ at 1 mA . Neglect the base current. **[5 marks]**

Question 2 [20 marks]

- (a) The basic differential pair biased by a three-transistor current source is shown in **Figure 1**. Assume $\beta = 200$ and $V_{BE(on)} = 0.7 \text{ V}$ for **all** BJTs in the circuit. For $R_1 = 10 \text{ k}\Omega$ and $R_C = 12.8 \text{ k}\Omega$, **find** the differential voltage gain (A_d) of the differential amplifier taken as **one-sided output**. **[10 marks]**

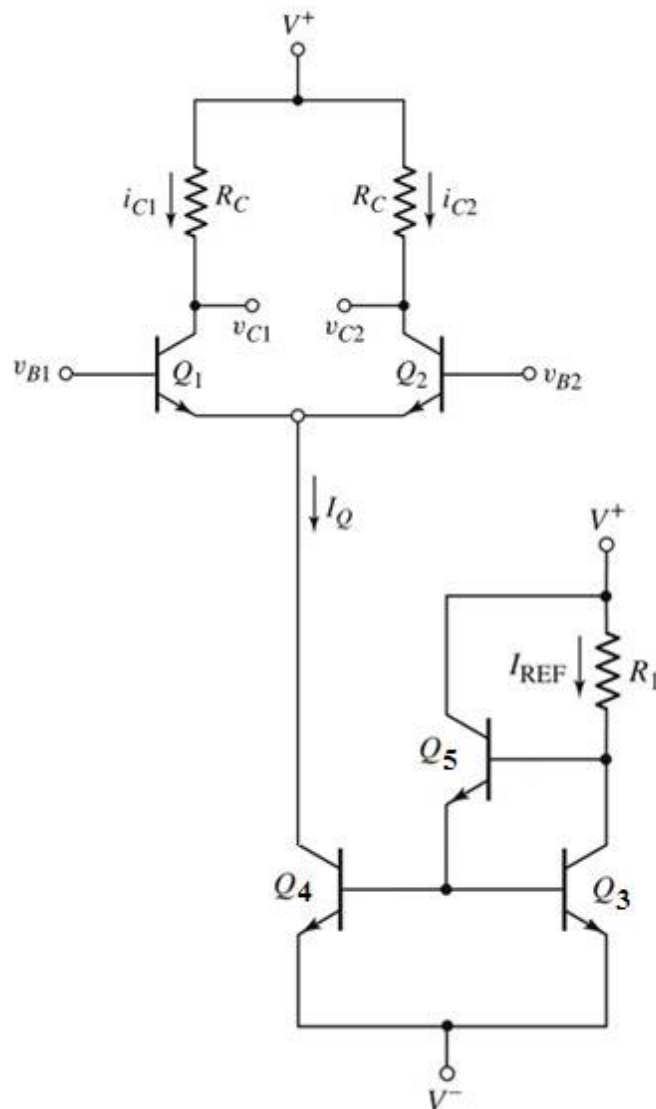


Figure 1

(b) **Figure 2** shows a differential amplifier with **PNP three-transistor** current mirror connected as an active load. The circuit are connected to $V^+ = 3\text{ V}$, $V^- = -3\text{ V}$, and $I_Q = 0.5\text{ mA}$. The transistors parameters are $\beta = 120$, $V_{A1} = V_{A2} = 120\text{ V}$, $V_{A3} = V_{A4} = 80\text{ V}$, and $V_{A5} = \infty$.

- (i) **Determine** the open-circuit differential-mode voltage gain (A_d). **[5 marks]**
- (ii) **What** is the output resistance (R_O) of the differential amplifier? **[2 marks]**
- (iii) **Find** the value of load resistance R_L that reduces the differential-mode gain to **75 percent** of the open-circuit value. **[3 marks]**

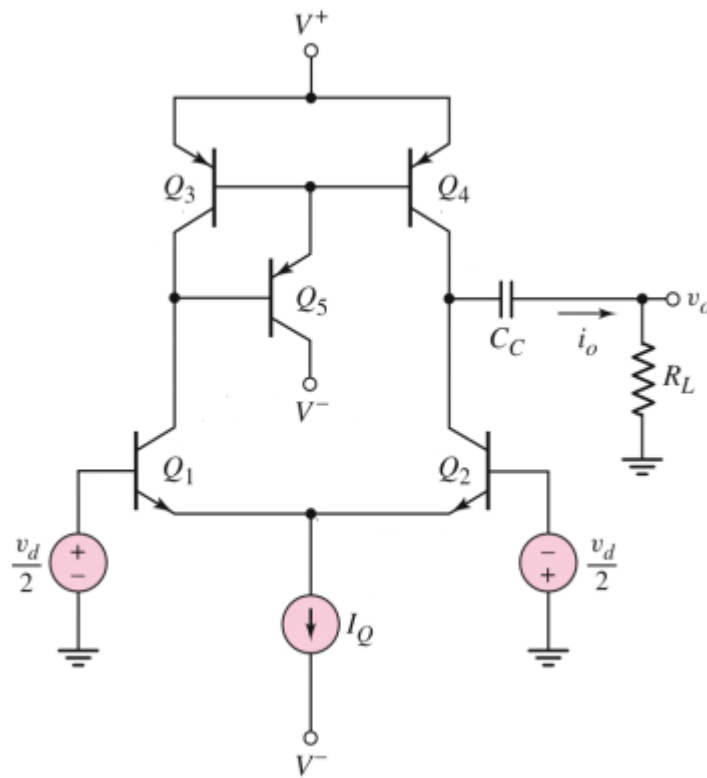


Figure 2

Question 3 [20 marks]

Consider the multi stage bipolar circuit in **Figure 3**. The transistors parameters are: $V_{BE(on)} = 0.7 \text{ V}$, $\beta = 150$ and $V_A = \infty$. When there is no input, $v_O = -0.1316 \text{ V}$.

- (a) **Determine** the transistor quiescent currents: I_{C2} , I_{C3} , I_{C4} , I_{C6} , and I_{C8} . **[10 marks]**
- (b) Assume R_{i3} is very large compared to R_5 , calculate the **overall differential mode voltage gain** (v_O/v_d) of the circuit in **Figure 3**. **[10 marks]**

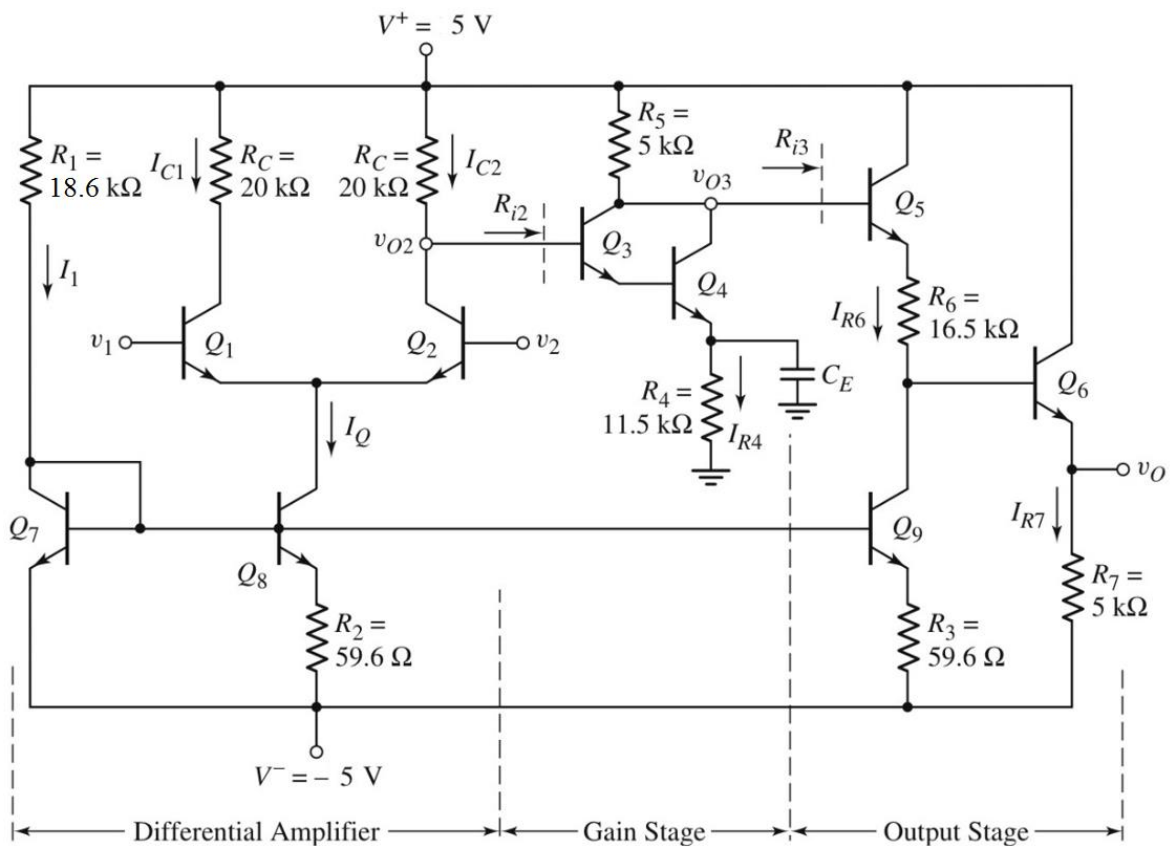


Figure 3

Question 5 [20 marks]

- (a) An **ideal** inverting op-amp with adjustable **closed-loop voltage gain** is shown in **Figure 5**. Calculate its **absolute** minimum A_v and maximum A_v values when $R_1 = 20 \text{ k}\Omega$, potentiometer $R_{1V} = 0 \text{ to } 30 \text{ k}\Omega$, $R_2 = 30 \text{ k}\Omega$, and potentiometer $R_{2V} = 0 \text{ to } 40 \text{ k}\Omega$.

[10 marks]

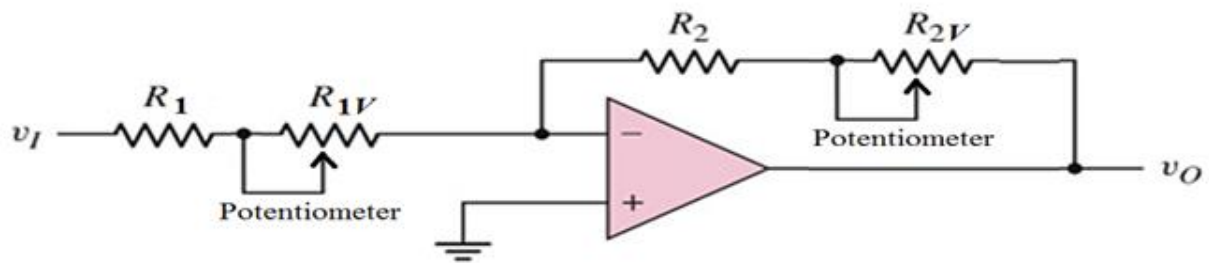


Figure 5

- (b) For a **generalized summing op-amp** shown in **Figure 6** the **total output voltage (v_O)** is the **sum of the individual terms**, or

$$v_O = -\frac{R_F}{R_1} v_{I1} - \frac{R_F}{R_2} v_{I2} + \left(1 + \frac{R_F}{R_N}\right) \left(\frac{R_P}{R_A} v_{I3} + \frac{R_P}{R_B} v_{I4}\right)$$

where

$$R_N = R_1 \parallel R_2$$

$$R_P = R_A \parallel R_B \parallel R_C$$

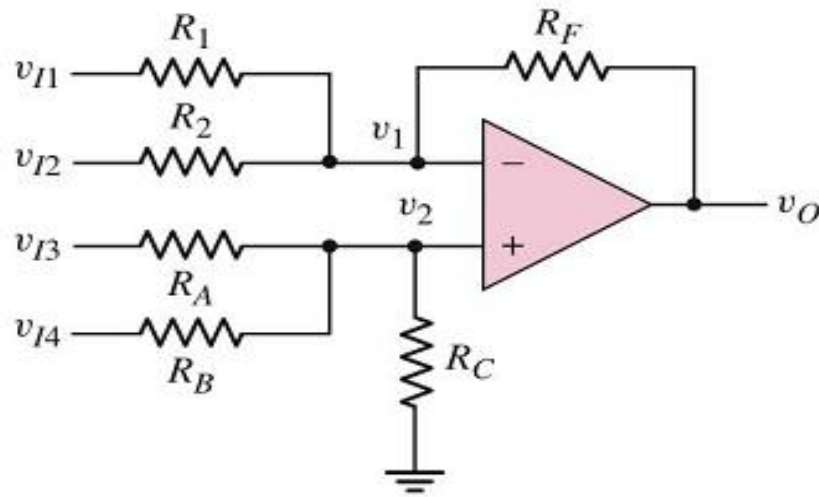


Figure 6

The summing op-amp similar to **Figure 6** is designed to produce the output of

$$v_O = -10v_{I1} - 5v_{I2} + 3v_{I3} + 5v_{I4}$$

Given that $R_1 = 50 \text{ k}\Omega$ and $R_A = 240 \text{ k}\Omega$, calculate the value of R_2 , R_B , R_C , and R_F .

[10 marks]

-END OF QUESTION PAPER-

APPENDIX:

A) BASIC FORMULA FOR TRANSISTOR

BJT

$$i_C = I_S e^{v_{BE}/V_T} \quad ; \text{NPN}$$

$$i_C = I_S e^{v_{EB}/V_T} \quad ; \text{PNP}$$

$$i_C = \beta i_B = \frac{\beta}{\beta + 1} i_E$$

$$i_E = i_B + i_C$$

;Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

MOSFET

; N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k'_n}{2} \cdot \frac{W}{L}$$

; P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k'_p}{2} \cdot \frac{W}{L}$$

;Small signal


$$g_m = 2\sqrt{K_n I_{DQ}} \quad ; \text{N – MOSFET}$$

$$g_m = 2\sqrt{K_p I_{DQ}} \quad ; \text{P – MOSFET}$$


$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

B) HYBRID- π EQUIVALENT CIRCUITS

BJT

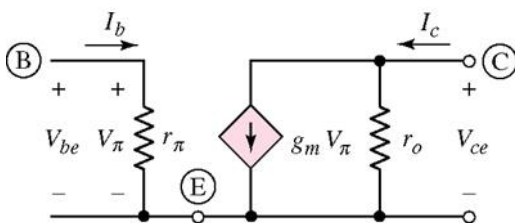

MOSFET

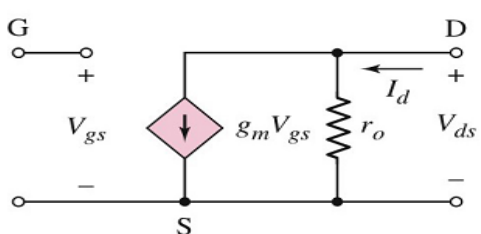

C) QUADRATIC FORMULA

$$Ax^2 + Bx + C = 0 \quad \rightarrow \quad x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$