


Question:

A **Widlar current source** circuit to be designed has the configuration shown in **Figure 1**. The circuit parameters are: $V^+ = +5.5$ V and $V^- = -5.5$ V. The transistor parameters are: $V_{BE1} = 0.6$ V, $V_A = 80$ V, and $\beta = 120$ (Therefore, we can assume that $I_C \approx I_E$).

(a) **Design** the Widlar current source circuit such that $I_{REF} = 1$ mA and $I_O = 12$ μ A. [4 marks]

(b) Calculate the output resistance (R_O) of the Widlar current source in **Figure 1** using the following formula. Use parameters and results from **part (a)** above. [6 marks]

$$R_O = r_{o2} [1 + g_{m2} R'_E] \text{ where } R'_E = R_E \| r_{\pi2} \quad i_C = I_S e^{v_{BE}/V_T}; \text{ npn}$$

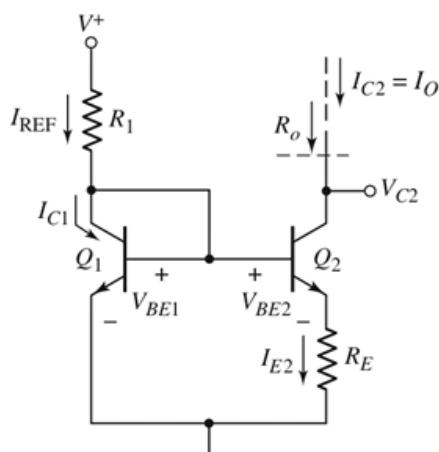

$$i_C = I_S e^{v_{EB}/V_T}; \text{ pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

(a)

$$R_1 = \frac{V^+ - V_{BE1} - V^-}{I_{REF}} = \frac{5.5 - 0.6 - (-5.5)}{1\text{mA}} = 10.4\text{k}\Omega \quad [2]$$

$$R_E = \frac{V_T}{I_O} \ln\left(\frac{I_{REF}}{I_O}\right) = \frac{0.026}{12} \ln\left(\frac{1\text{mA}}{12}\right) = 9.58\text{k}\Omega \quad [2]$$

(b)

$$g_{m2} = \frac{I_O}{V_T} = \frac{12\mu}{0.026} = 0.462\text{mA/V} \quad [1]$$

$$r_{\pi2} = \frac{\beta V_T}{I_O} = \frac{(120)(0.026)}{12\mu} = 260\text{k}\Omega \quad [1]$$

$$r_{o2} = \frac{V_A}{I_O} = \frac{80}{12\mu} = 6.67\text{M}\Omega \quad [1]$$

$$R_O = r_{o2} [1 + g_{m2} (R_E \| r_{\pi2})] \quad [3]$$

$$R_O = (6.67\text{M}) [1 + (0.462\text{mA})(9.58\text{k}\|260\text{k})] = 35.1\text{M}\Omega \quad [3]$$


Question:

A **Widlar current source** circuit to be designed has the configuration shown in **Figure 1**. The circuit parameters are: $V^+ = +5.0 \text{ V}$ and $V^- = -5.0 \text{ V}$. The transistor parameters are: $V_{BE1} = 0.6 \text{ V}$, $V_A = 80 \text{ V}$, and $\beta = 120$ (Therefore, we can assume that $I_C \approx I_E$).

(a) **Design** the Widlar current source circuit such that $I_{REF} = 1.2 \text{ mA}$ and $I_O = 12 \mu\text{A}$. [4 marks]

(b) Calculate the output resistance (R_O) of the Widlar current source in **Figure 1** using the following formula. Use parameters and results from **part (a)** above. [6 marks]

$$R_O = r_{o2} [1 + g_{m2} R'_E] \quad \text{where } R'_E = R_E \| r_{\pi2} \quad i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

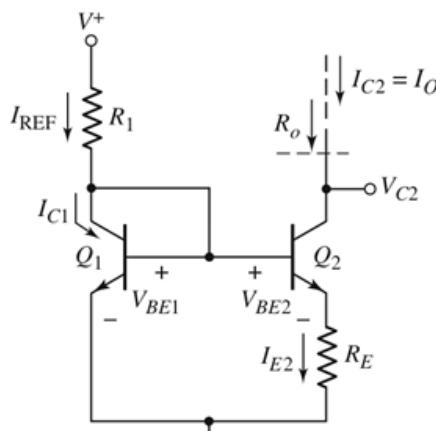

$$i_C = I_S e^{v_{EB}/V_T}; \text{ppn}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

$$(a) R_1 = \frac{V^+ - V_{BE1} - V^-}{I_{REF}} = \frac{5 - 0.6 - (-5)}{1.2 \text{ mA}} = 7.83 \text{ k}\Omega \quad [2]$$

$$R_E = \frac{V_T}{I_O} \ln\left(\frac{I_{REF}}{I_O}\right) = \frac{0.026}{12} \ln\left(\frac{1.2 \text{ mA}}{12}\right) = 9.98 \text{ k}\Omega \quad [2]$$

$$(b) g_{m2} = \frac{I_O}{V_T} = \frac{12 \mu}{0.026} = 0.462 \text{ mA/V} \quad [1]$$

$$r_{\pi2} = \frac{\beta V_T}{I_O} = \frac{(120)(0.026)}{12 \mu} = 260 \text{ k}\Omega \quad [1]$$

$$r_{o2} = \frac{V_A}{I_O} = \frac{80}{12 \mu} = 6.67 \text{ M}\Omega \quad [1]$$

$$R_O = r_{o2} [1 + g_{m2} (R_E \| r_{\pi2})] \quad [3]$$

$$R_O = (6.67 \text{ M}) [1 + (0.462 \text{ mA})(9.98 \text{ k}\Omega \| 260 \text{ k}\Omega)] = 36.2 \text{ M}\Omega \quad [3]$$


Question:

A **Widlar current source** circuit to be designed has the configuration shown in **Figure 1**. The circuit parameters are: $V^+ = +5.0 \text{ V}$ and $V^- = -5.0 \text{ V}$. The transistor parameters are: $V_{BE1} = 0.6 \text{ V}$, $V_A = 100 \text{ V}$, and $\beta = 120$ (Therefore, we can assume that $I_C \approx I_E$).

(a) **Design** the Widlar current source circuit such that $I_{REF} = 1 \text{ mA}$ and $I_O = 10 \mu\text{A}$. [4 marks]

(b) Calculate the output resistance (R_O) of the Widlar current source in **Figure 1** using the following formula. Use parameters and results from **part (a)** above. [6 marks]

$$R_O = r_{o2} [1 + g_{m2} R'_E] \text{ where } R'_E = R_E \| r_{\pi2} \quad i_C = I_S e^{v_{BE}/V_T}; \text{ npn}$$

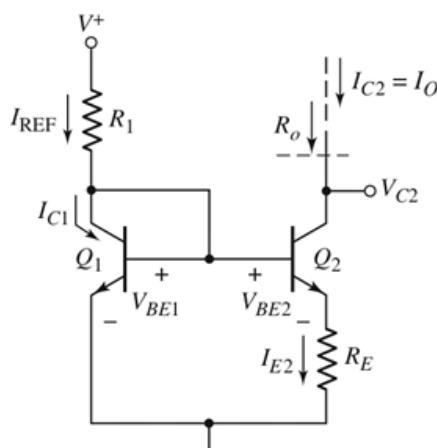

$$i_C = I_S e^{v_{EB}/V_T}; \text{ pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

(a)

$$R_1 = \frac{V^+ - V_{BE1} - V^-}{I_{REF}} = \frac{5 - 0.6 - (-5)}{1\text{m}} = 9.40\text{k}\Omega \quad [2]$$

$$R_E = \frac{V_T}{I_O} \ln\left(\frac{I_{REF}}{I_O}\right) = \frac{0.026}{10} \ln\left(\frac{1\text{m}}{10}\right) = 11.97\text{k}\Omega \quad [2]$$

(b)

$$g_{m2} = \frac{I_O}{V_T} = \frac{10\mu}{0.026} = 0.385\text{mA/V} \quad [1]$$

$$r_{\pi2} = \frac{\beta V_T}{I_O} = \frac{(120)(0.026)}{10\mu} = 312\text{k}\Omega \quad [1]$$

$$r_{o2} = \frac{V_A}{I_O} = \frac{100}{10\mu} = 10.0\text{M}\Omega \quad [1]$$

$$R_O = r_{o2} [1 + g_{m2} (R_E \| r_{\pi2})]$$

$$R_O = (10.0\text{M}) [1 + (0.385)(11.97\text{k} \| 312\text{k})] = 54.3\text{M}\Omega \quad [3]$$


Question:

A **Widlar current source** circuit to be designed has the configuration shown in **Figure 1**. The circuit parameters are: $V^+ = +5.5$ V and $V^- = -5.5$ V. The transistor parameters are: $V_{BE1} = 0.6$ V, $V_A = 100$ V, and $\beta = 120$ (Therefore, we can assume that $I_C \approx I_E$).

(a) **Design** the Widlar current source circuit such that $I_{REF} = 1.2$ mA and $I_O = 10$ μ A. [4 marks]

(b) Calculate the output resistance (R_O) of the Widlar current source in **Figure 1** using the following formula. Use parameters and results from **part (a)** above. [6 marks]

$$R_O = r_{o2} [1 + g_{m2} R'_E] \text{ where } R'_E = R_E \| r_{\pi2} \quad i_C = I_S e^{v_{BE}/V_T}; \text{ npn}$$

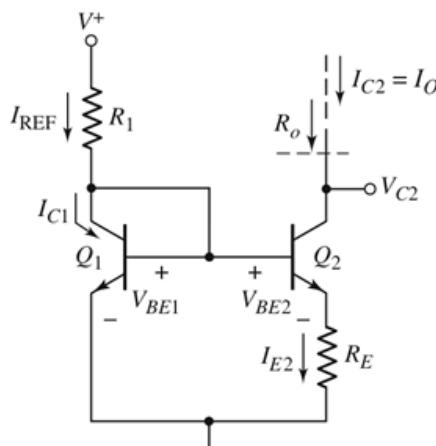

$$i_C = I_S e^{v_{EB}/V_T}; \text{ pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

(a)

$$R_1 = \frac{V^+ - V_{BE1} - V^-}{I_{REF}} = \frac{5.5 - 0.6 - (-5.5)}{1.2 \text{ mA}} = 8.67 \text{ k}\Omega \quad [2]$$

$$R_E = \frac{V_T}{I_O} \ln\left(\frac{I_{REF}}{I_O}\right) = \frac{0.026}{10} \ln\left(\frac{1.2 \text{ mA}}{10}\right) = 12.44 \text{ k}\Omega \quad [2]$$

(b)

$$g_{m2} = \frac{I_O}{V_T} = \frac{10 \mu}{0.026} = 0.385 \text{ mA/V} \quad [1]$$

$$r_{\pi2} = \frac{\beta V_T}{I_O} = \frac{(120)(0.026)}{10 \mu} = 312 \text{ k}\Omega \quad [1]$$

$$r_{o2} = \frac{V_A}{I_O} = \frac{100}{10 \mu} = 10.0 \text{ M}\Omega \quad [1]$$

$$R_O = r_{o2} [1 + g_{m2} (R_E \| r_{\pi2})] \quad [3]$$

$$R_O = (10.0 \text{ M}\Omega) [1 + (0.385 \text{ mA})(12.44 \text{ k}\Omega \| 312 \text{ k}\Omega)] = 56.05 \text{ M}\Omega \quad [3]$$