

EEEE273 - Quiz 7  
 SEMESTER 2, ACADEMIC YEAR 2017/2018  
 Date: 17 January 2018 Time: 15 minutes

**Question:**

Refer to **ideal** inverting op-amp in **Figure 1**. Calculate its absolute minimum and maximum values of the closed-loop voltage gain ( $A_v = v_O/v_I$ ) when  $R_1 = 30 \text{ k}\Omega$ , potentiometer  $R_{1V} = 0 \text{ to } 30 \text{ k}\Omega$ , and  $R_2 = 25 \text{ k}\Omega$ .

Show your calculation clearly.

[10 marks]

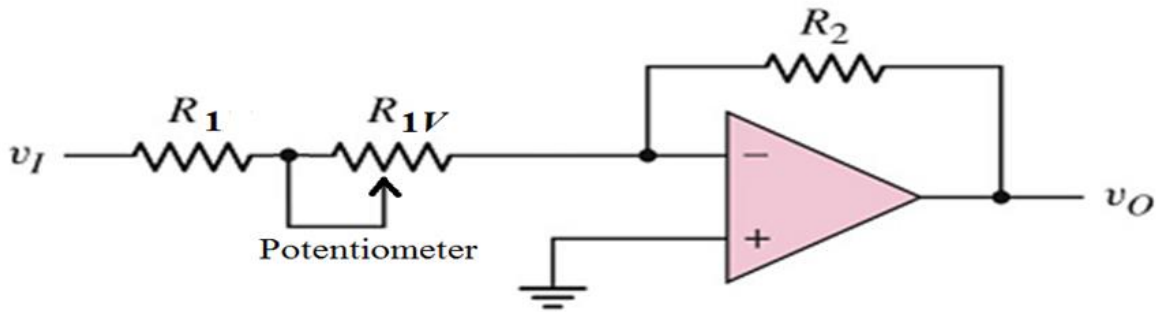


Figure 1

**Answer:**

$$A_d = v_O / v_I = - R_2 / (R_1 + R_{1V}) \quad [1]$$

$$R_1 (\text{min}) = R_1 + R_{1V} (\text{min}) = 30 \text{ k}\Omega \quad [1]$$

$$R_1 (\text{max}) = R_1 + R_{1V} (\text{max}) = 30 \text{ k}\Omega + 30 \text{ k}\Omega = 60 \text{ k}\Omega \quad [1]$$

$$R_2 = 25 \text{ k}\Omega \quad [1]$$

**Absolute value of  $A_v$  is maximum when  $R_{1V} = 0$ .**

$$A_v(\text{max}) = | - R_2 / R_1 (\text{min}) | \quad [2]$$

$$\Rightarrow A_v(\text{max}) = | -25\text{k}/30\text{k} | = 0.6 \text{ V/V} \quad [1]$$

**Absolute value of  $A_v$  is minimum when  $R_{1V} = 30 \text{ k}\Omega$ .**

$$A_v(\text{min}) = | - R_2 / R_1 (\text{max}) | \quad [2]$$

$$\Rightarrow A_v(\text{min}) = | -25\text{k}/60\text{k} | = 0.4167 \text{ V/V} \quad [1]$$

EEEE273 - Quiz 7  
 SEMESTER 2, ACADEMIC YEAR 2017/2018  
 Date: 17 January 2018 Time: 15 minutes

**Question:**

Refer to **ideal** inverting op-amp in **Figure 1**. Calculate its absolute minimum and maximum values of the closed-loop voltage gain ( $A_v = v_O/v_I$ ) when  $R_1 = 40 \text{ k}\Omega$ , potentiometer  $R_{1V} = 0 \text{ to } 30 \text{ k}\Omega$ , and  $R_2 = 45 \text{ k}\Omega$ .

Show your calculation clearly.

[10 marks]

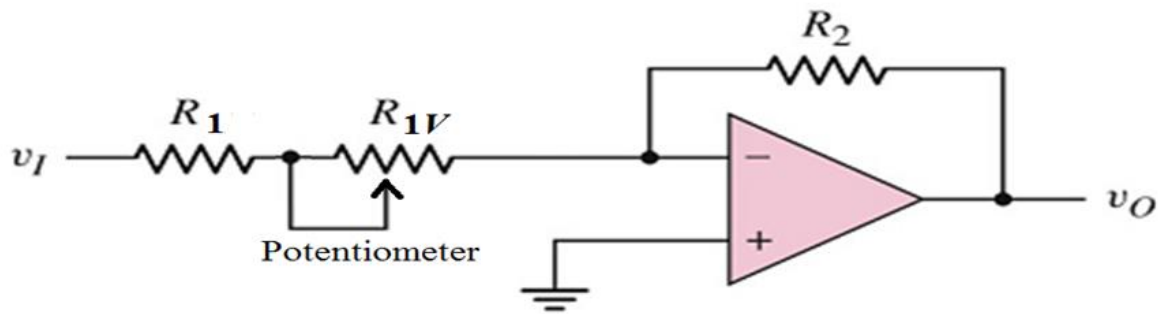


Figure 1

**Answer:**

$$A_d = v_O / v_I = - R_2 / (R_1 + R_{1V}) \quad [1]$$

$$R_1 (\text{min}) = R_1 + R_{1V} (\text{min}) = 40 \text{ k}\Omega \quad [1]$$

$$R_1 (\text{max}) = R_1 + R_{1V} (\text{max}) = 40 \text{ k}\Omega + 30 \text{ k}\Omega = 70 \text{ k}\Omega \quad [1]$$

$$R_2 = 45 \text{ k}\Omega \quad [1]$$

**Absolute value of  $A_v$  is maximum when  $R_{1V}$  is minimum.**

$$A_v(\text{max}) = | - R_2 / R_1 (\text{min}) | \quad [2]$$

$$\Rightarrow A_v(\text{max}) = | -45\text{k}/40\text{k} | = 1.125 \text{ V/V} \quad [1]$$

**Absolute value of  $A_v$  is minimum when  $R_{1V} = 30 \text{ k}\Omega$ .**

$$A_v(\text{min}) = | - R_2 / R_1 (\text{max}) | \quad [2]$$

$$\Rightarrow A_v(\text{min}) = | -45\text{k}/70\text{k} | = 0.6428 \text{ V/V} \quad [1]$$

EEEEB273 - Quiz 7  
 SEMESTER 2, ACADEMIC YEAR 2017/2018  
 Date: 17 January 2018 Time: 15 minutes ;

**Question:**

Refer to **ideal** inverting op-amp in **Figure 1**. Calculate its absolute minimum and maximum values of the closed-loop voltage gain ( $A_v = v_O/v_I$ ) when  $R_1 = 20 \text{ k}\Omega$ , potentiometer  $R_{1V} = 0 \text{ to } 40 \text{ k}\Omega$ , and  $R_2 = 75 \text{ k}\Omega$ .

Show your calculation clearly.

[10 marks]

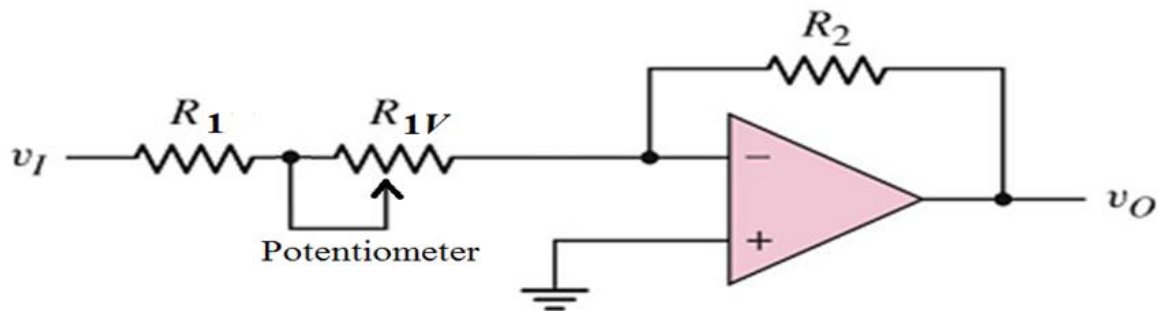


Figure 1

**Answer:**

$$A_d = v_O / v_I = - R_2 / (R_1 + R_{1V}) \quad [1]$$

$$R_1 (\text{min}) = R_1 + R_{1V} (\text{min}) = 20 \text{ k}\Omega \quad [1]$$

$$R_1 (\text{max}) = R_1 + R_{1V} (\text{max}) = 20 \text{ k}\Omega + 40 \text{ k}\Omega = 60 \text{ k}\Omega \quad [1]$$

$$R_2 = 75 \text{ k}\Omega \quad [1]$$

**Absolute value of  $A_v$  is maximum when  $R_{1V}$  is minimum.**

$$A_v(\text{max}) = | - R_2 / R_1 (\text{min}) | \quad [2]$$

$$\Rightarrow A_v(\text{max}) = | -75\text{k}/20\text{k} | = 3.75 \text{ V/V} \quad [1]$$

**Absolute value of  $A_v$  is minimum when  $R_{1V} = 30 \text{ k}\Omega$ .**

$$A_v(\text{min}) = | - R_2 / R_1 (\text{max}) | \quad [2]$$

$$\Rightarrow A_v(\text{min}) = | -75\text{k}/60\text{k} | = 1.25 \text{ V/V} \quad [1]$$

EEEE273 - Quiz 7  
 SEMESTER 2, ACADEMIC YEAR 2017/2018  
 Date: 17 January 2018 Time: 15 minutes

**Question:**

Refer to **ideal** inverting op-amp in **Figure 1**. Calculate its absolute minimum and maximum values of the closed-loop voltage gain ( $A_v = v_O/v_I$ ) when  $R_1 = 25 \text{ k}\Omega$ , potentiometer  $R_{1V} = 0 \text{ to } 35 \text{ k}\Omega$ , and  $R_2 = 80 \text{ k}\Omega$ .

Show your calculation clearly.

[10 marks]

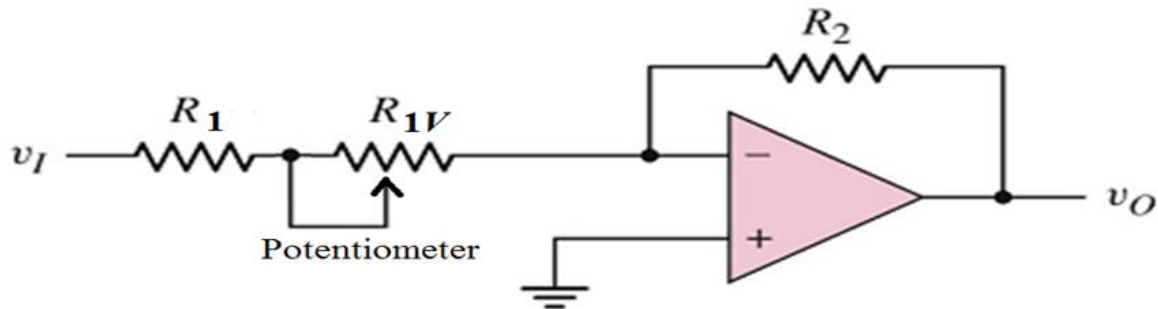


Figure 1

**Answer:**

$$A_d = v_O / v_I = - R_2 / (R_1 + R_{1V}) \quad [1]$$

$$R_1 (\text{min}) = R_1 + R_{1V} (\text{min}) = 25 \text{ k}\Omega \quad [1]$$

$$R_1 (\text{max}) = R_1 + R_{1V} (\text{max}) = 25 \text{ k}\Omega + 35 \text{ k}\Omega = 60 \text{ k}\Omega \quad [1]$$

$$R_2 = 80 \text{ k}\Omega \quad [1]$$

**Absolute value of  $A_v$  is maximum when  $R_{1V}$  is minimum.**

$$A_v(\text{max}) = | - R_2 / R_1 (\text{min}) | \quad [2]$$

$$\Rightarrow A_v(\text{max}) = | -80\text{k}/25\text{k} | = 3.2 \text{ V/V} \quad [1]$$

**Absolute value of  $A_v$  is minimum when  $R_{1V} = 30 \text{ k}\Omega$ .**

$$A_v(\text{min}) = | - R_2 / R_1 (\text{max}) | \quad [2]$$

$$\Rightarrow A_v(\text{min}) = | -80\text{k}/60\text{k} | = 1.333 \text{ V/V} \quad [1]$$