

Name:
Student ID Number:
Section Number: 01/02/03/04 A/B
Lecturer: Dr Jamaludin/Dr Azni Wati/Dr
Jehana Ermy/Prof Md Zaini
Table Number:



College of Engineering
Department of Electronics and Communication Engineering

Test 1

SEMESTER 2, ACADEMIC YEAR 2017/2018

Subject Code : **EEEB273**
Course Title : **Electronics Analysis & Design II**
Date : **18 November 2017**
Time Allowed : **2 hours**

Instructions to the candidates:

1. Write your Name and Student ID Number. Indicate your Section Number and Lecturer's Name. Write also your Table Number.
2. **Write all your answers using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS. Show clearly** all your calculations. Every value **must** be written with its correct Unit.
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**



NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.

☺ **GOOD LUCK!** ☺

Question Number	Q1(a)	Q1(b)	Q2	Q3(a)	Q3(b)	Q4	Total
Marks							

QUESTION 1 [35 marks]

Answers for Question 1
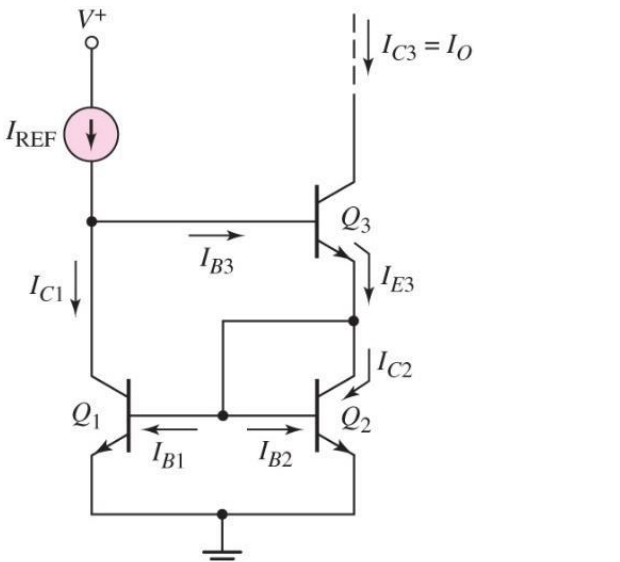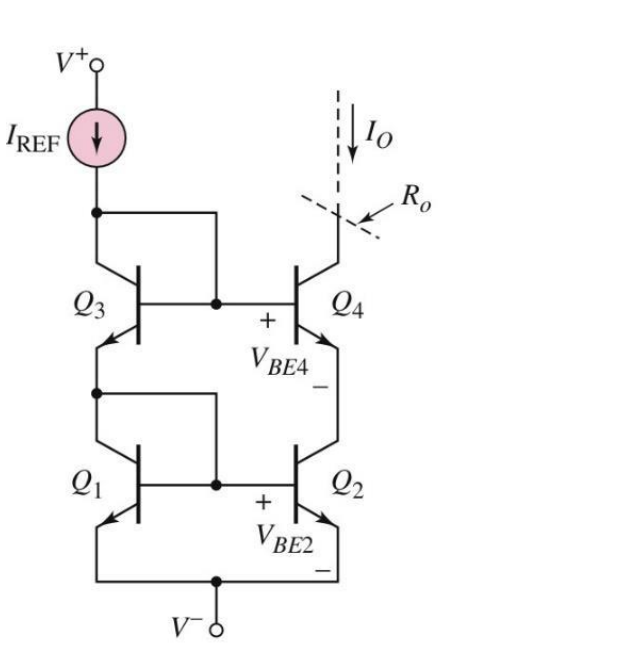
<p>(a) (i) <i>BJT Wilson current source</i></p>  <p>Placements of Q1, Q2 and Q3 [2 marks] I_REF and I_O labels [2 marks] Power supplies labels [1 mark]</p>	<p><i>BJT Cascode current source</i></p>  <p>(a)</p> <p>Placements of Q1, Q2, Q3 and Q4 [2 marks] I_REF and I_O labels [2 marks] Power supplies labels [1 mark]</p>
<p>(a)(ii)</p> <p>At low β values, output current I_o for Wilson is closer to I_{ref} and more stable compared to Cascode,</p> <p>i.e. $I_o = I_{REF} / \left[1 + \frac{2}{\beta(1+\beta_3)} \right]$ for Wilson has better stability compared to $I_o = I_{REF} / \left[1 + \frac{4}{\beta} \right]$ for Cascode at low β values [2.5 marks]</p> <p>At high β values, I_o for Cascode is more stable due to its high output resistance R_o, where R_o for Cascode is given by βr_{o4} compared to R_o for Wilson that is given by $(\beta/2) r_{o3}$. Bigger R_o means better I_o stability [2.5 marks]</p>	

(b)(i)

Summing the currents at $Q1$;

$$I_{REF} = I_{C1} + I_{B3} \quad \dots (1) \quad [2 \text{ marks}]$$

$$I_{B1} = I_{B2} \rightarrow I_{E3} = 2I_{B2} \quad \dots (2) \quad [2 \text{ marks}]$$

$$\text{And } I_{E3} = (1 + \beta_3)I_{B3} \quad \dots (3) \quad [2 \text{ marks}]$$

Combining the equations,

$$I_{REF} = I_{C1} + \frac{I_{E3}}{(1 + \beta_3)} \rightarrow I_{REF} = I_{C1} + \frac{2I_{B2}}{(1 + \beta_3)} \quad [1 \text{ mark}]$$

Replacing I_{C1} with I_{C2} and $I_{B2} = I_{C2}/\beta$;

$$I_{REF} = I_{C2} + \frac{2I_{C2}}{\beta(1 + \beta_3)} \quad [2 \text{ marks}]$$

$$\text{Therefore, } I_O = I_{REF} / \left[1 + \frac{2}{\beta(1 + \beta_3)} \right] \quad [1 \text{ mark}]$$

$$I_{C1} = I_{C2}; I_{B1} = I_{B2}$$

$$I_{C1} = \beta I_{B1} = \beta I_{B2}$$

$$I_{E3} = I_{B1} + I_{B2} = 2I_{B2}$$

$$I_{B3} = (2I_{B2}) / (1 + \beta_3)$$

$$I_{REF} = I_{C1} + I_{B3}$$

$$\rightarrow I_{REF} = (\beta + 2 / (1 + \beta_3)) I_{B2}$$

$$I_O = \beta I_{B2} = \frac{I_{REF}}{\left(1 + \frac{2}{\beta(1 + \beta_3)} \right)}$$

(b)(ii)

For $V_+ = 10 \text{ V}$ and $V_- = 0 \text{ V}$, design the circuit such that $I_O = 0.7 \text{ mA}$. The transistor parameters are: $\beta = 80$, $\beta_3 = 60$, $V_{BE(on)} = 0.7 \text{ V}$ and $V_A = \infty$.

$$\text{Using the 3TCS equation, } I_{REF} = I_O [1 + 2 / (\beta(\beta_3 + 1))] \quad [2 \text{ marks}]$$

$$I_{REF} = (0.7 \text{ mA}) [1 + 2 / (80(60 + 1))] = 0.7003 \text{ mA} \quad [2, 1 \text{ marks}]$$

Using KVL,

$$R1 = (V_+ - v_{BE3} - v_{BE1} - V_-) / I_{REF} = (10 - 2(0.7) - 0) / 0.7003 \text{ mA} = 12.28 \text{ k}\Omega \quad [2, 2, 1 \text{ marks}]$$

QUESTION 2 [20 marks]**Answers for Question 2**

Using the formula,

$$V_{DS2}(sat) = V_{GS2} - V_{TN} \quad [1]$$

At 1 V, $V_{DS2}(sat) = V_{GS2} - V_{TN}$

$$\rightarrow V_{GS2} = 1 + 0.5 = \underline{1.5 \text{ V}} \quad [2]$$

Using the formula,

$$I_D = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_n (V_{GS} - V_{TN})^2 \dots(1)$$

$$I_O = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_2 (V_{GS2} - V_{TN})^2 \quad [2]$$

$$\text{Subs } I_O = 0.15 \text{ mA}, 0.15 \text{ m} = \left(\frac{0.08}{2}\right) \left(\frac{W}{L}\right)_2 (1.5 - 0.5)^2 \rightarrow \left(\frac{W}{L}\right)_2 = \underline{3.75} \quad [3]$$

$$I_{REF} = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TN})^2 \quad [2]$$

$$\text{Subs } I_{REF} = 0.5 \text{ mA}, 0.5 \text{ m} = \left(\frac{0.08}{2}\right) \left(\frac{W}{L}\right)_1 (1.5 - 0.5)^2 \rightarrow \left(\frac{W}{L}\right)_1 = \underline{12.5} \quad [3]$$

With KVL rule, $V_{GS1} + V_{GS3} = V^+ - V^-$

$$\text{Thus, } V_{GS3} = 1.8 - (-1.8) - 1.5 = 2.1 \text{ V} \quad [2]$$

$$\text{So, } I_{REF} = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_3 (V_{GS3} - V_{TN})^2 \quad [2]$$

$$\text{Subs } I_{REF} = 0.5 \text{ mA}, 0.5 \text{ m} = \left(\frac{0.08}{2}\right) \left(\frac{W}{L}\right)_3 (2.1 - 0.5)^2 \rightarrow \left(\frac{W}{L}\right)_3 = \underline{4.88} \quad [3]$$

$$V_{GS2} = V_{DS2}(sat) + V_{TN} = 1 + 0.5 = 1.5 \text{ V}$$

$$I_O = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_2 (V_{GS2} - V_{TN})^2$$

$$0.15 = \left(\frac{0.08}{2}\right) \left(\frac{W}{L}\right)_2 (1.5 - 0.5)^2 \Rightarrow \left(\frac{W}{L}\right)_2 = 3.75$$

$$I_{REF} = 0.5 = \left(\frac{0.08}{2}\right) \left(\frac{W}{L}\right)_1 (1.5 - 0.5)^2 \Rightarrow \left(\frac{W}{L}\right)_1 = 12.5$$

$$V_{GS3} = (V^+ - V^-) - V_{GS1} = 1.8 - (-1.8) - 1.5 = 2.1 \text{ V}$$

$$I_{REF} = 0.5 = \left(\frac{0.08}{2}\right) \left(\frac{W}{L}\right)_3 (2.1 - 0.5)^2 \Rightarrow \left(\frac{W}{L}\right)_3 = 4.88$$

QUESTION 3 [25 marks]

Answers for Question 3

(a)

$$V_{CE4} = V^+ - I_{C4}R_C - V_E \quad [2]$$

$$I_{C4} = \frac{V^+ - V_{CE4} - V_E}{R_C} = \frac{5 - (1.8) - (-0.7)}{5k} = 0.78 \text{ mA} \quad [4]$$

$$I_{E4} = \frac{1+\beta}{\beta} I_{C4} = \left(\frac{41}{40}\right) (0.78\text{m}) = 0.7995\text{mA} \quad [3]$$


$$I_{C2} = 2I_{E4} = 2(0.7995\text{m}) = 1.599\text{mA} \quad [3]$$

$$I_1 = \left(1 + \frac{2}{\beta(1+\beta)}\right) (I_{C2}) = \left(1 + \frac{2}{(40)(41)}\right) (1.599\text{m}) = 1.601\text{mA} \quad [4]$$

$$R_1 = \frac{V^+ - 2V_{BE} - V^-}{I_1} = \frac{5 - 2(0.6) + 5}{1.601\text{m}} = 5497\Omega \quad [4]$$

*Note: use β in current equations [1 mark each time]

(b)

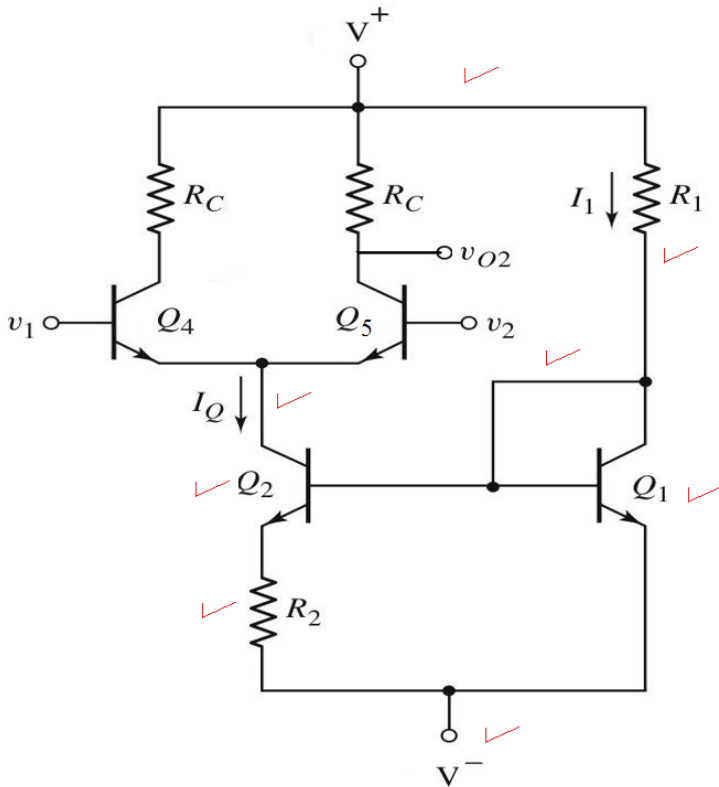

Same diff-amp copied [1]
 V- connection [1/2]
 E4 and C2 connection [1]
 Correct CS output components [1]
 Correct Ref side with diode connection [1]
 CS V+ connection [1/2]

QUESTION 4 [20 marks]**Answers for Question 4**

Q4(a)

$$I_{E2} = \frac{I_Q}{2} = 2mA \quad [1]$$

$$I_{C2} = \frac{\beta}{1+\beta} I_{E2} = 1.983mA \quad [1]$$

$$r_{\pi 2} = \beta \frac{V_T}{I_{C2}} = \frac{(120)(0.026)}{1.983mA} = 1.573k\Omega \quad [2]$$

$$R_{id} = 2r_{\pi 2} = 2(1.573k) = 3.147k\Omega \quad [2]$$

Q4(b)

$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{1.983mA}{(0.026)} = 76.27mA/V \quad [3]$$

$$A_d = \frac{g_{m2}}{2} R_C = (76.27mA/V)(5k) = 190.67 \quad [3]$$

Q4(c)

$$v_d = v_1 - v_2 = 0.35m \sin wt \quad [2]$$

$$v_{cm} = \frac{v_1 + v_2}{2} = 1.075m \sin wt \quad [2]$$

$$v_o = A_d v_d + A_{cm} v_{cm} \quad [2]$$

$$= (190.67)(0.35m) \sin wt + (-0.09912)(1.075m) \sin wt$$

$$= (0.0667 - 0.10655m) \sin wt = 0.0666 \sin wt \text{ V} \quad [2]$$