

Name:  
Student ID Number:  
Section Number: 01/02/03/04 A/B  
Lecturer: Dr Jamaludin/Dr Azni Wati/Dr  
Jehana Ermy/Prof Md Zaini  
Table Number:



**College of Engineering**  
Department of Electronics and Communication Engineering

**Test 1**

**SEMESTER 2, ACADEMIC YEAR 2017/2018**

Subject Code : **EEEB273**  
Course Title : **Electronics Analysis & Design II**  
Date : **18 November 2017**  
Time Allowed : **2 hours**

**Instructions to the candidates:**

1. Write your Name and Student ID Number. Indicate your Section Number and Lecturer's Name. Write also your Table Number.
2. **Write all your answers using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.** Show clearly all your calculations. Every value **must** be written with its correct Unit.
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**

**NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.**



**GOOD LUCK!**




Question Number	Q1(a)	Q1(b)	Q2	Q3(a)	Q3(b)	Q4	Total
Marks							

**QUESTION 1 [35 marks]**

- (a) (i) **Draw the *npn* BJT Wilson and Cascode current sources with clear details of the transistors  $Q_n$  placements. [10 marks]**
- (ii) **Clearly explain and compare the current sources in part a(i) in terms of their output current ( $I_O$ ) stability. [5 marks]**
- (b) (i) **Figure 1 shows a BJT three-transistor current source. Derive the expression of  $I_O$  in terms of  $I_{REF}$ ,  $\beta$  and  $\beta_3$ . [10 marks]**
- (ii) **For  $V^+ = 10\text{ V}$  and  $V^- = 0\text{ V}$ , design the circuit such that  $I_O = 0.7\text{ mA}$ . The transistors parameters are:  $\beta = \beta_3 = 80$ ,  $V_{BE(on)} = 0.7\text{ V}$  and  $V_A = \infty$ . [10 marks]**

**Answers for Question 1**

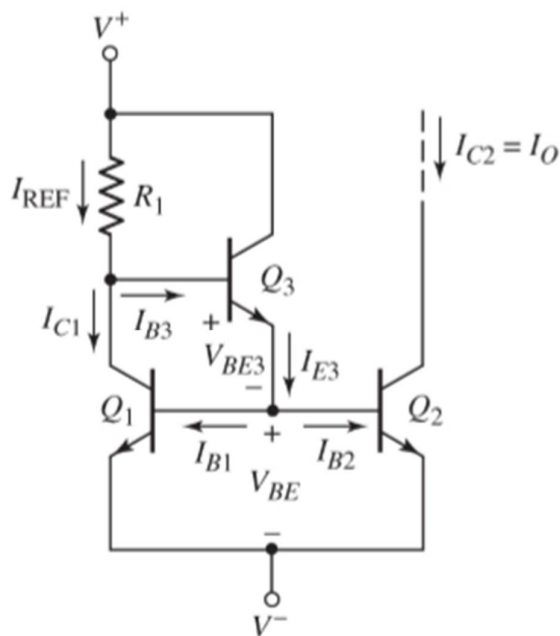

**Figure 1**

**Answers for Question 1 (Continued)**

**QUESTION 2 [20 marks]**


The circuit in **Figure 2** has the following parameters:

$$V^+ = 1.8 \text{ V and } V^- = -1.8 \text{ V.}$$

$$V_{TN} = 0.5 \text{ V, } k'_n = 80 \text{ } \mu\text{A/V}^2, \text{ and } \lambda = 0.$$

**Design** the circuit such that  $I_O = 0.15 \text{ mA}$ ,  $I_{REF} = 0.5 \text{ mA}$  and transistor  $M_2$  remains biased in the saturation region for  $V_{DS2} \geq 1 \text{ V}$ . **[20 marks]**

**Answers for Question 2**

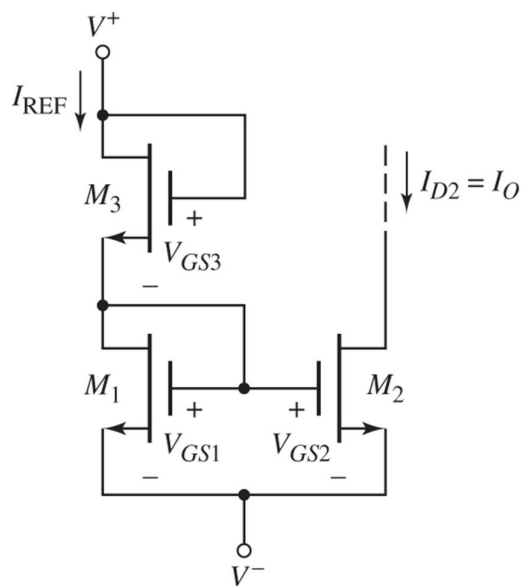


**Figure 2**

**Answers for Question 2 (Continued)**

**QUESTION 3 [25 marks]**

- (a) The differential amplifier in **Figure 3** is biased with a three-transistor current source as shown. The transistor parameters are:  $\beta = 40$ ,  $V_{BE(on)} = 0.6 \text{ V}$ , and  $V_{A4} = V_{A5} = \infty$ . **Determine  $R_1$  if  $V_{CE4} = 1.8 \text{ V}$ .** [20 marks]
- (b) **Redesign** the differential amplifier circuit of **Figure 3** if a **Widlar current source** is used as biasing circuit **instead**. **Draw** the complete differential amplifier circuit. [5 marks]

**Answers for Question 3**

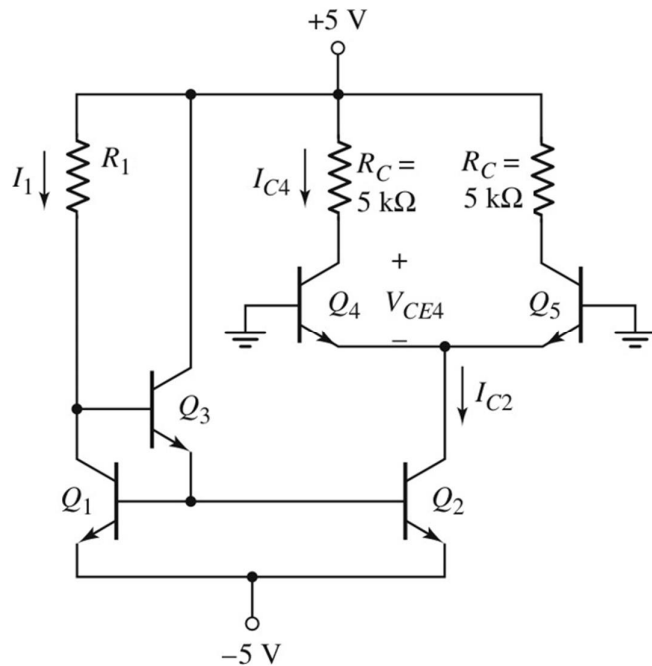

**Figure 3**


**Answers for Question 3 (Continued)**

**QUESTION 4 [20 marks]**

Figure 4 has the transistor parameters of  $\beta = 120$ ,  $V_{BE(on)} = 0.7 \text{ V}$ ,  $V_A = \infty$  for  $Q_1$  and  $Q_2$ , and  $V_A = 100 \text{ V}$  for  $Q_3$  and  $Q_4$ . Given that  $I_Q = 4 \text{ mA}$ .

- (a) **Determine** the differential-mode input resistance ( $R_{id}$ ) of the differential amplifier. [6 marks]
  
- (b) **Determine** the differential-mode voltage gain ( $A_d$ ) of the differential amplifier. Output is **one-sided** taken at collector of  $Q_2$ . [6 marks]
  
- (c) **Determine** the output of the differential amplifier ( $v_o$ ) if the inputs are  $v_1 = 1.25 \sin \omega t \text{ mV}$  and  $v_2 = 0.9 \sin \omega t \text{ mV}$ . Given that  $A_{cm} = -0.09912$ . [8 marks]

**Answers for Question 4**

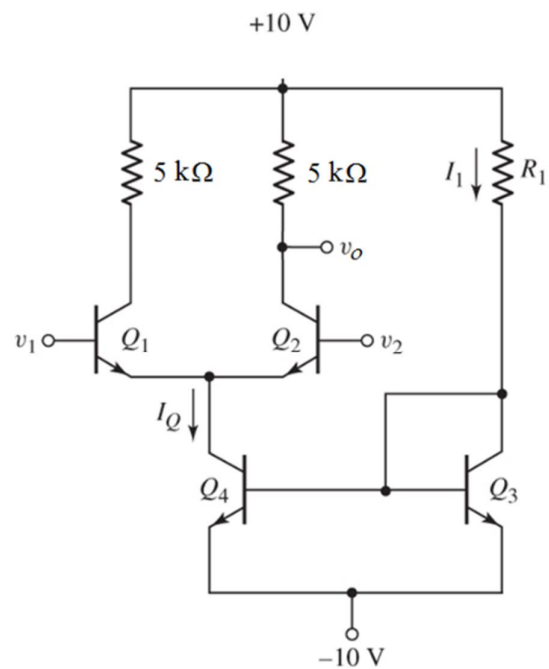

**Figure 4**



**Answers for Question 4 (Continued)**

## BASIC FORMULA FOR TRANSISTOR

### BJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

;Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

### MOSFET

;N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{k'_n}{2} \cdot \frac{W}{L}$$

;P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{k'_p}{2} \cdot \frac{W}{L}$$

;Small signal

$$g_m = 2\sqrt{K_n I_{DQ}} \quad ; \text{N - MOSFET}$$

$$g_m = 2\sqrt{K_p I_{DQ}} \quad ; \text{P - MOSFET}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

Quadratic formula :

$$Ax^2 + Bx + C = 0 \quad \rightarrow \quad x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$