

Name:
Student ID Number:
Section Number: 01/02/03/04 A/B
Lecturer: Dr Jamaludin/ Dr Azni Wati/ Dr
Jehana Ermy/ Prof Md Zaini
Table Number:

**UNIVERSITI
TENAGA
NASIONAL**



College of Engineering
Department of Electronics and Communication Engineering

Test 2

SEMESTER 2, ACADEMIC YEAR 2017/2018

Subject Code : **EEEEB273**
Course Title : **Electronics Analysis & Design II**
Date : **30 December 2017**
Time Allowed : **2 hours**

Instructions to the candidates:

1. Write your Name and Student ID Number. Indicate your Section Number and Lecturer's Name. Write also your Table Number.
2. **Write all your answers using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.** Show clearly all your calculations. Every value **must** be written with its correct Unit.
4. **WRITE ALL YOUR ANSWERS ON THIS QUESTION PAPER.**

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.



GOOD LUCK!



Question Number	Q1a	Q1b-c	Q2a-d	Q2e	Q3	Q4a	Q4b	Total
Marks								

QUESTION 1 [20 marks]

A BJT differential amplifier shown in **Figure 1** is biased by a constant current source with $I_Q = 0.23 \text{ mA}$. The differential amplifier is to be redesigned with an active load. The active load to be used is a **BJT Wilson current source** using *pn*p transistors.

The transistor parameters are $\beta = 120$, $V_{BE(\text{on})} = V_{EB(\text{on})} = 0.7 \text{ V}$, $V_{AN} = 100 \text{ V}$, and $V_{AP} = 120 \text{ V}$.

(a) **Draw** the new differential amplifier circuit added with the active load. **Label** the circuit correctly and clearly with appropriate symbols and numbering for transistors used in circuit.

[4 marks]

(b) **Calculate** the differential-mode voltage gain, (A_d), of the new circuit. [12 marks]

(c) **Calculate** the differential-mode voltage gain, (A_d), of the differential amplifier circuit if the active load is changed to a **three-transistor current source**. Give your comment about values of A_d for the differential amplifier circuit using **Wilson current source** and **three-transistor current source** active loads.

[4 marks]

Answers for Question 1

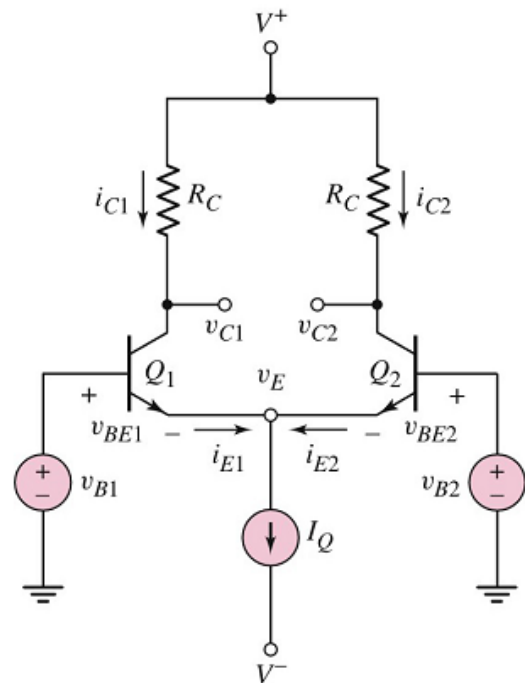


Figure 1

Answers for Question 1 (continued)

QUESTION 2 [35 marks]

Figure 2 shows a differential amplifier circuit with active loads and biased by a current source using MOSFET. Transistors M_1 and M_2 are driven into saturation with $V_{DS}(\text{sat}) = 1.12 \text{ V}$. The active load transistors (M_3 and M_4) are matched with parameters $K_p = 0.1 \text{ mA/V}^2$, $V_{TP} = -2 \text{ V}$, and $\lambda_p = 0.02 \text{ V}^{-1}$. Transistors M_5 , M_6 and M_7 are **identical**. All the NMOS transistors have the same $K_n = 0.2 \text{ mA/V}^2$, $V_{TN} = 2 \text{ V}$, and $\lambda_n = 0.015 \text{ V}^{-1}$.

- (a) Determine I_1 , I_Q , and I_{D1} when $v_1 = v_2 = 0 \text{ V}$. [6 marks]
- (b) Determine the one-sided differential mode voltage gain (A_d) for the differential amplifier if $R_L = 100 \text{ k}\Omega$. [9 marks]
- (c) It is required that the CMRR of the circuit to be 60 dB. What is the common mode voltage gain (A_{cm})? [3 marks]
- (d) Suggest 2 ways to improve the CMRR for the circuit in the **Figure 2**. [2 marks]
- (e) The MOSFET differential amplifier with active load in the **Figure 2** is replaced with the MOSFET differential amplifier with **Cascode active load**. Draw and label clearly all the transistors used in the new circuit. [15 marks]

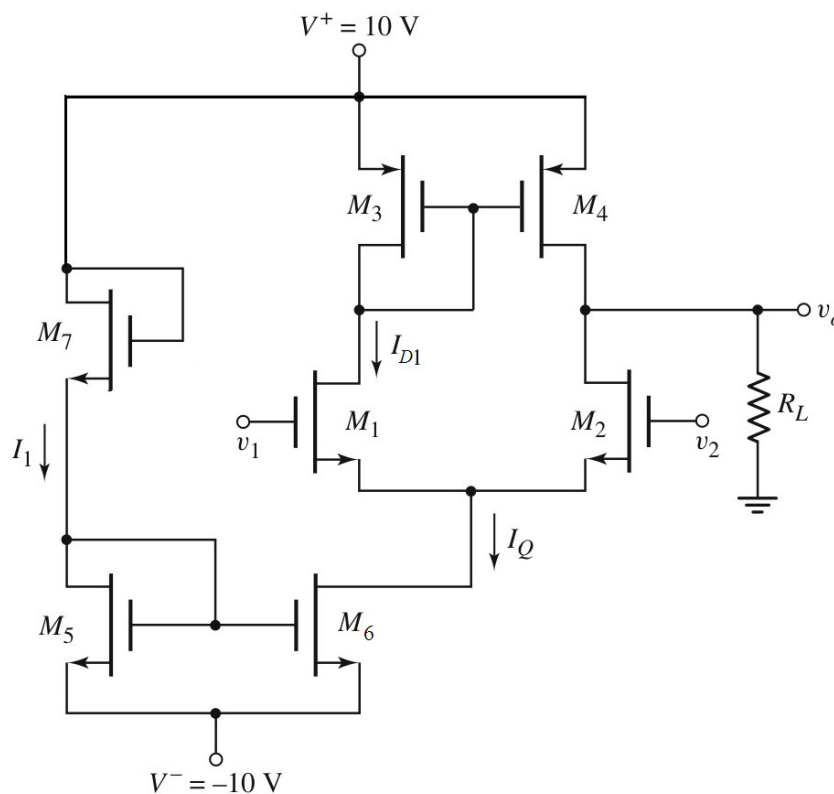


Figure 2

Answers for Question 2

Extra page for Answers – Indicate question number(s)

Extra page for Answers – Indicate question number(s)

QUESTION 3 [20 marks]

Consider the circuit shown in **Figure 3**. Study the **Figure 1** thoroughly. With supply voltage $\pm 10\text{V}$ and circuit parameters $R_1 = 19.3 \text{ k}\Omega$, $R_2 = R_3 = 0.1 \text{ k}\Omega$, and $R_4 = 5 \text{ k}\Omega$ it can be calculated that the value of I_Q is **0.307 mA**.

Assume the quiescent values $I_{C7} = I_Q$; $I_{C1} = I_{E1} = I_{C2} = I_{E2}$; $V_{BE(\text{on})} = 0.7 \text{ V}$, $\beta = 120$, Early voltage is 100 for Q_7 and Q_{11} ; and $v_O = 0$ when $v_1 = v_2 = 0$.

R_i is the input resistance of the Darlington Pair while R_{L7} is the effective resistance connected between collector of Q_7 and signal ground. Calculate the small signal voltage gain of the Darlington Pair (A_{v2}) by using the following relationship: [20 marks]

$$A_{v2} = \frac{V_{o3}}{V_{b6}} = \frac{\beta(1 + \beta)(r_{o7} \parallel R_{L7})}{R_i}$$

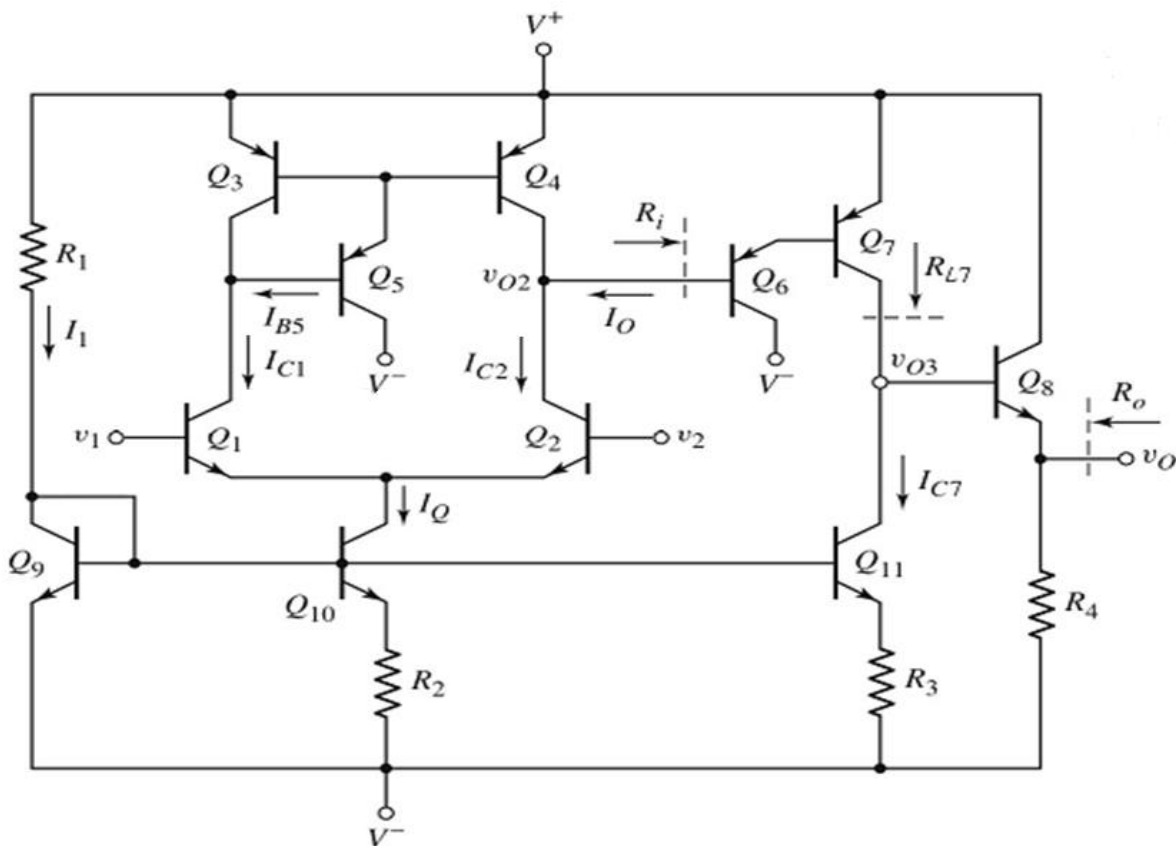


Figure 3

Answers for Question 3

Answers for Question 3 (Continued)

QUESTION 4 [25 marks]

- (a) Draw a **class-A output stage** constructed using **npn** emitter follower with load R_L and biased by a three-transistor current sinking current source. The overall circuit is connected to supply voltages of $V^+ = +5\text{ V}$ and $V^- = -5\text{ V}$. [5 marks]
- (b) A **class-AB** output stage with BJTs is shown in **Figure 4**. Reverse saturation current for every transistor is $I_S = 2 \times 10^{-15}\text{ A}$. Assume $+V_{CC} = +6\text{ V}$ and $-V_{CC} = -6\text{ V}$. Let $R_L = 1\text{ k}\Omega$ and $V_{BB} = 1.40\text{ V}$. For the case of the output voltage $v_O = -4\text{ V}$:
- (i) Determine i_L , i_{Cp} , i_{Cn} , and v_I . [12 marks]
- (ii) Calculate the power dissipated in transistor Q_n and Q_p . [8 marks]

Answers for Question 4

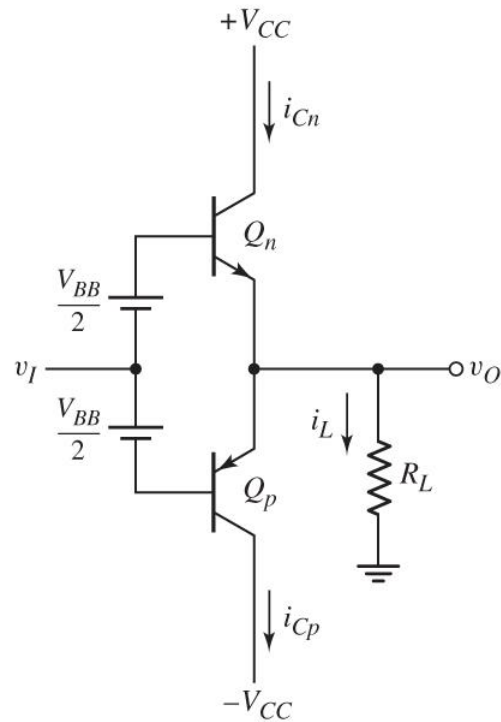


Figure 4

Answers for Question 4 (Continued)

APPENDIX

A) BASIC FORMULA FOR TRANSISTOR

BJT

$$i_C = I_S e^{v_{BE}/V_T} \quad ; \text{NPN}$$

$$i_C = I_S e^{v_{EB}/V_T} \quad ; \text{PNP}$$

$$i_C = \beta i_B = \frac{\beta}{\beta + 1} i_E$$

$$i_E = i_B + i_C$$

; Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

MOSFET

; N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k'_n}{2} \cdot \frac{W}{L}$$

; P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k'_p}{2} \cdot \frac{W}{L}$$

; Small signal


$$g_m = 2\sqrt{K_n I_{DQ}} \quad ; \text{N – MOSFET}$$

$$g_m = 2\sqrt{K_p I_{DQ}} \quad ; \text{P – MOSFET}$$


$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

B) HYBRID- π EQUIVALENT CIRCUITS

BJT

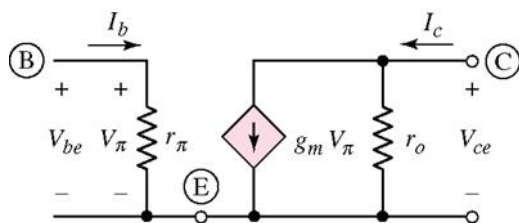

MOSFET

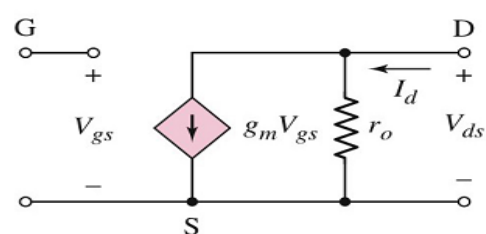

C) QUADRATIC FORMULA

$$Ax^2 + Bx + C = 0 \quad \rightarrow \quad x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$