



The National Energy University

**COLLEGE OF ENGINEERING
PUTRAJAYA CAMPUS
FINAL EXAMINATION**

SEMESTER 1 2018 / 2019

MODEL ANSWERS

PROGRAMME	: Bachelor of Electrical & Electronics Engineering (Honours) Bachelor of Electrical Power Engineering (Honours)
SUBJECT CODE	: EEEB273
SUBJECT	: ELECTRONIC ANALYSIS AND DESIGN II
DATE	: September 2018
TIME	: 3 hours


INSTRUCTIONS TO CANDIDATES:

1. This paper contains **FIVE (5)** questions in **NINE (9)** pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided. **Use pen** to write your answer.
4. Write answer to different question on **a new page**.

THIS QUESTION PAPER CONSISTS OF **NINE (9) PRINTED PAGES INCLUDING THIS COVER PAGE.**

Question 1 [20 marks]**Answers:**

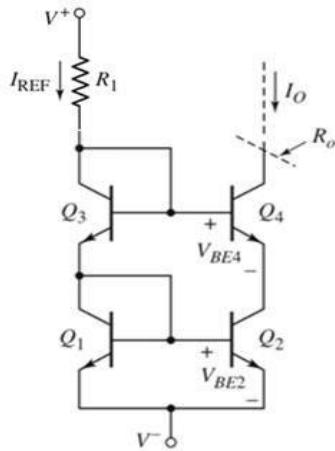(a) [Each component carries 0.5 marks, total 4 marks]



$$\begin{aligned}
 (b) \quad & I_{C2} = \beta I_{B2} = I_{E4} = \beta I_{B1} \\
 & I_{C4} = \alpha I_{E4} = \left(\frac{\beta}{\beta+1}\right)(\beta I_{B1}) = I_O \quad \rightarrow I_{B1} = \left(\frac{\beta+1}{\beta^2}\right)I_O \\
 & I_{B4} = \frac{I_{E4}}{\beta+1} = \left(\frac{1}{\beta+1}\right)(\beta I_{B1}) \\
 & I_{C1} = \beta I_{B1} \text{ and } I_{E3} = (\beta + 2) I_{B1} \\
 & I_{B3} = \left(\frac{1}{\beta+1}\right) I_{E3} = \frac{1}{(\beta+1)} (\beta + 2) I_{B1} \text{ and } I_{C3} = \beta I_{B3} = \left(\frac{\beta}{\beta+1}\right) (\beta + 2) I_{B1} \\
 & I_{REF} = I_{C3} + I_{B3} + I_{B4} \\
 & \Rightarrow I_{REF} = \left(\frac{\beta}{\beta+1}\right) (\beta + 2) I_{B1} + \frac{1}{(\beta+1)} (\beta + 2) I_{B1} + \left(\frac{1}{\beta+1}\right)(\beta I_{B1}) \\
 & I_{REF} = \left[\frac{\beta^2+2\beta+\beta+2+\beta}{\beta+1}\right] I_{B1} \\
 & I_{REF} = \left[\frac{\beta^2+2\beta+\beta+2+\beta}{\beta+1}\right] \left[\left(\frac{\beta+1}{\beta^2}\right) I_O\right] \\
 & \Rightarrow I_O = [I_{REF}/\left[1 + \frac{4}{\beta} + \frac{2}{\beta^2}\right]] \approx I_{REF}/[1 + \frac{4}{\beta}]
 \end{aligned}$$

[Each carries 0.5 marks, total 5 marks]

c) $\beta = 150$, Since β is higher than 100, \therefore Approximation of $I_O = I_{REF}$ [1 mark]

$$\begin{aligned}
 I_{REF} &= \frac{V^+ - V_{BE1} - V_{BE3} - V^-}{R_1} = \frac{5 - 0.7 - 0.7 - (-5)}{6 \times 10^3} = 1.433mA & [2 \text{ marks}] \\
 I_O &= I_{REF} = 1.433mA & [0.5 \text{ mark}] \\
 R_O &= \beta r_O = \beta \left(\frac{V_A}{I_O}\right) = 150 \left(\frac{100}{1.433mA}\right) = 10.465M\Omega & [3.5 \text{ marks}]
 \end{aligned}$$

d)

$g_{m4} = \frac{I_O}{V_T}$	[1 mark]
$g_{m4} = \frac{1.433mA}{26mV} = 55.128mA/V$	[1 mark]
$r_{\pi4} = \frac{\beta V_T}{I_O}$	[1 mark]
$r_{\pi4} = 150 \left(\frac{26mV}{1.433mA}\right) = 2.721k\Omega$	[1 mark]

Question 2 [20 marks]**Answers:**

Q2a(i) Design the circuit such that $I_3 = 400 \mu\text{A}$ and $V_{CE1} = V_{CE2} = 10 \text{ V}$. [5 marks]

Neglect the base currents;

$$I_I = I_3 = 400 \mu\text{A}$$

$$\text{Using KVL, } R_I = (V^+ - V_{BE4} - V^-) / I_I$$

$$R_I = (15 - 0.7 - (-15)) / 0.4\text{m} = \underline{\underline{73.25 \text{ k}\Omega}} \quad [1, 1, 0.5]$$

$$\text{As } V_{CE1} = 10 \text{ V}; V_{CI} = V_{CE1} - V_E = 10 - 0.7 = 9.3 \text{ V}$$

$$R_C = (V^+ - V_{CI}) / I_{CI} = (15 - 9.3) / (400\mu/2) = \underline{\underline{28.5 \text{ k}\Omega}} \quad [1, 1, 0.5]$$

Q2a(ii) Determine A_d and $CMRR_{dB}$ for a one-sided output at v_{O2} . A_{cm} is given as **-0.113**.

[5 marks]


Find r_π ,

$$r_\pi = \beta v_T / I_{CQ} = (100)(0.026) / 200\mu = \underline{\underline{13 \text{ k}\Omega}} \quad [0.5, 0.5]$$

$$\begin{aligned} A_d &= \beta R_C / 2(r_\pi + R_B) \\ &= (100)(28.5\text{k}) / 2(13\text{k} + 10\text{k}) = \underline{\underline{62}} \end{aligned} \quad [1, 1]$$

$$\text{Thus, } CMRR_{dB} = 20 \log_{10} (62/0.113) = \underline{\underline{54.8 \text{ dB}}} \quad [1, 1]$$

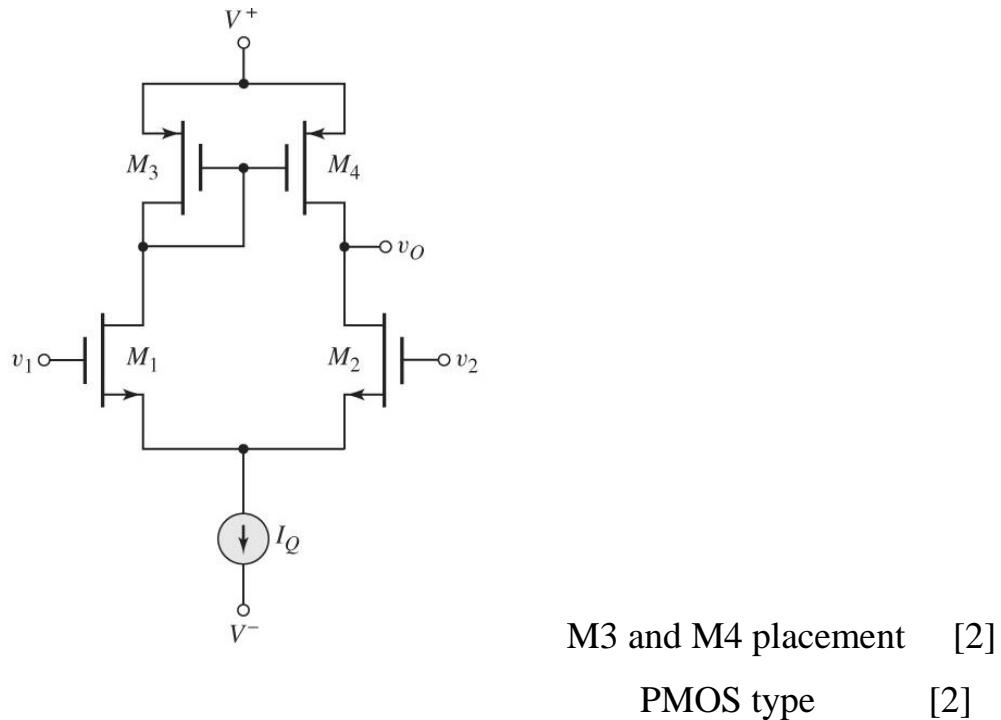Q2b(i) Draw an improved diff-amp for the circuit in **Figure 3**. Use **Table 1** for the transistors specification. [4 marks]



Q2b(ii) Calculate the minimum power supply voltages if the common input voltage is to be in the range of ± 3 V. Assume symmetrical supply voltages.

[6 marks]

$$i_{D3} = K_p (v_{SG3} + V_{TP})^2 \quad [2]$$

$$0.5m/2 = 0.25m (v_{SG3} - 0.4)^2$$

$$v_{SG3} = \underline{1.4 \text{ V}} \quad [1]$$

Then, assuming that $v_{SG3} = v_{GSI}$,

$$v_{DSI(sat)} = v_{GSI} - V_{TN} = 1.4 - 0.4 = \underline{1.0 \text{ V}} \quad [2]$$

$$v_{CM} = V_O - v_{DSI(sat)} + v_{GSI}$$

$$3 = (V^+ - 1.4) - 1.0 + 1.4 \rightarrow \underline{V^+ = 4 \text{ V and } V^- = -4 \text{ V}} \quad [1]$$

Question 3 [20 marks]**Answers:**

Q3(a)

$$\begin{aligned} I_1 &= (V^+ - V_{BE7} - V^-) / (R_I) & [1] \\ &= (10-0.7-(-10)) / (19.3k) & = 1 \text{ mA} & [1] \\ I_Q &= I_1 / (1 + 2/\beta) & = 0.990 \text{ mA} & [2] \\ I_{C2} &= I_Q / 2 & = 0.495 \text{ mA} & [2] \\ v_{O2} &= V^+ - I_{C2} R_C = 10 - (0.495\text{m})(10\text{k}) = 5.05 \text{ V} & [2] \\ I_{R4} &= (v_{O2} - 2 V_{BE}(\text{on})) / (R_4) \\ &= (5.05 - 1.4) / (11.5k) & = 0.3173 \text{ mA} & [0.5] \\ I_{R5} &\approx I_{R4} (\text{neglecting base currents}) = 0.3173 \text{ mA} & [0.5] \\ v_{O3} &= V^+ - I_{R5} R_5 = 10 - (0.348\text{m})(5\text{k}) = 8.413 \text{ V} & [1] \end{aligned}$$

Q3(b) Using $I_{C2} = 0.495 \text{ mA}, I_{R4} = 0.3173 \text{ mA}:$

$$\begin{aligned} A_{d1} &= (g_{m2} / 2)(R_C \parallel R_{i2}) \\ g_{m2} &= I_{C2} / V_T = (0.495\text{mA})/(26\text{mV}) = 19 \text{ mA/V} & [1] \\ r_{\pi4} &= \beta V_T / I_{R4} = (200 \times 26\text{m}) / (0.3173\text{m}) = 16.388 \text{ k}\Omega & [1] \\ r_{\pi3} &\approx \beta r_{\pi4} = 200 \times 16.388\text{k} = 3277.6 \text{ k}\Omega & [1] \\ R_{i2} &= r_{\pi3} + (1 + \beta) r_{\pi4} \\ &= 3277.6\text{k} + (201)(16.388\text{k}) = 6571.59 \text{ k}\Omega & [1] \\ A_{d1} &= (19\text{m}/2)(10\text{k} \parallel 6571.59\text{k}) = 94.85 & [1] \\ A_{v2} &\approx (I_{R4} / 2V_T) R_5 = (0.3173 / (2 \times 26\text{m})) (5\text{k}) = 30.5 & [1] \\ A_3 &\approx 1 \quad (\text{Output stage assume gain} = 1) & [1] \\ A_d &= A_{d1} A_{v2} A_3 \\ &= 94.85 \times 30.5 \times 1 = 2893.8 & [1] \end{aligned}$$

OR

Q3(a)

$$\begin{aligned} I_1 &= (V^+ - V_{BE7} - V^-) / (R_I) & [1] \\ &= (10-0.7-(-10)) / (19.3k) & = 1 \text{ mA} & [1] \\ I_Q &\approx I_1 \quad [\text{Since } \beta=200 \gg 1] & = 1 \text{ mA} & [2] \\ I_{C2} &= I_Q / 2 & = 0.5 \text{ mA} & [2] \\ v_{O2} &= V^+ - I_{C2} R_C = 10 - (0.5\text{m})(10\text{k}) = 5 \text{ V} & [2] \\ I_{R4} &= (v_{O2} - 2 V_{BE}(\text{on})) / (R_4) \\ &= (5 - 1.4) / (11.5k) & = 0.313 \text{ mA} & [0.5] \\ I_{R5} &\approx I_{R4} (\text{neglecting base currents}) = 0.313 \text{ mA} & [0.5] \\ v_{O3} &= V^+ - I_{R5} R_5 = 10 - (0.313\text{m})(5\text{k}) = 8.44 \text{ V} & [1] \end{aligned}$$

Q3(b) Using $I_{C2} = 0.5 \text{ mA}, I_{R4} = 0.313 \text{ mA}:$

$$\begin{aligned} A_{d1} &= (g_{m2} / 2)(R_C \parallel R_{i2}) \\ g_{m2} &= I_{C2} / V_T = (0.5\text{mA})/(26\text{mV}) = 19.23 \text{ mA/V} & [1] \\ r_{\pi4} &= \beta V_T / I_{R4} = (200 \times 26\text{m}) / (0.313\text{m}) = 16.613 \text{ k}\Omega & [1] \\ r_{\pi3} &\approx \beta r_{\pi4} = 200 \times 16.613\text{k} = 3322.6 \text{ k}\Omega & [1] \\ R_{i2} &= r_{\pi3} + (1 + \beta) r_{\pi4} \\ &= 3322.6\text{k} + (201)(16.613\text{k}) = 6661.8 \text{ k}\Omega & [1] \\ A_{d1} &= (19.23\text{m}/2)(10\text{k} \parallel 6661.8\text{k}) = 96 & [1] \\ A_{v2} &\approx (I_{R4} / 2V_T) R_5 = (0.313\text{m} / (2 \times 26\text{m})) (5\text{k}) = 30 & [1] \\ A_3 &\approx 1 \quad (\text{Output stage assume gain} = 1) & [1] \\ A_d &= A_{d1} A_{v2} A_3 \\ &= 96 \times 30 \times 1 = 2880 & [1] \end{aligned}$$

Question 4 [20 marks]


Answers:

Q4a(i)

Figure 4(a) - Approximate class-B output stage [1]

Figure 4(b) - Class-AB output stage [1]

Q4a(ii)

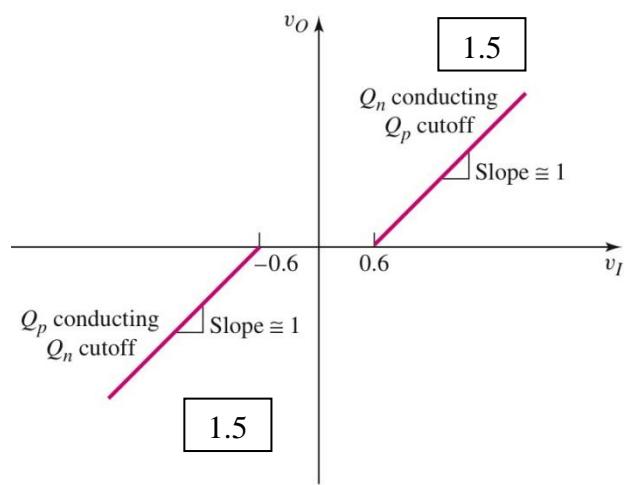

Q4a(iii)

$$i_{Cn} = i_{Cp} = I_s e^{\frac{V_{BB}}{2V_T}}$$

$$i_{Cn} = (4 \times 10^{-13})(e^{\left[\frac{1.2}{(2)(0.026)}\right]}) = 4.210mA$$

$$P_{Qn} = P_{Qp} = v_{CE} i_C$$

$$v_{CE} = 12V$$

$$P_Q = (12)(4.210m) = 50.52mW$$

$$v_{O(\max)} = 12V$$

$$P_{L(\max)} = \frac{1}{2} \frac{V_p^2}{R_L} = (0.5) \left(\frac{12^2}{100} \right) = 0.72W$$

Question 4(b) [10 marks]

To calculate I_{C16} , need to determine I_{C13B}

$$I_{C13B} = 0.75 \quad I_{C12} = (0.75)(0.3m) = 0.225 \text{ mA}$$

$$I_{C17} = I_{C13B} = 0.225 \text{ mA}$$

[1 mark]

[1 mark]

$$I_{C16} \approx I_{E16} = I_{B17} + IR_9 = I_{C17} / \beta + ([I_{C17}R_8 + V_{BE17}] / R_9)$$

$$I_{C16} = (0.225m/200) + ([0.225mx100 + 0.7] / 50k)$$

$$I_{C16} = 1.125\mu + 14.45\mu = 15.575 \mu\text{A}$$

[1 mark]

[1 mark]

$$Rb16 = rpi16 + (1+B)[R9 \parallel Rb17]$$

[1 mark]

$$Rb17 = rpi17 + (1+B)R8$$

[1 mark]

$$Rpi17 = B.VT/IC17 = (200)(26m)/0.225m = 23.11 \text{ kOhm}$$

$$Rpi16 = B.VT/IC16 = (200)(26m) / 15.575\mu = 333.868 \text{ kOhm}$$

[1 mark]

[1 mark]


$$\text{So } Rb17 = 23.11k + (201)100 = 43.21\text{kOhm}$$

$$50k \parallel 43.21k = 23.17k$$

$$\text{So } Rb16 = 333.868 + (201)(50k \parallel 43.21k) = 4.993 \text{ MOhm}$$


[1 mark]

[1 mark]

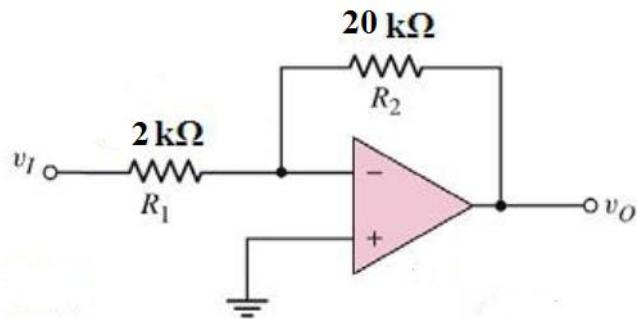Question 5 [20 marks]**Question 5(a) [8 marks]**

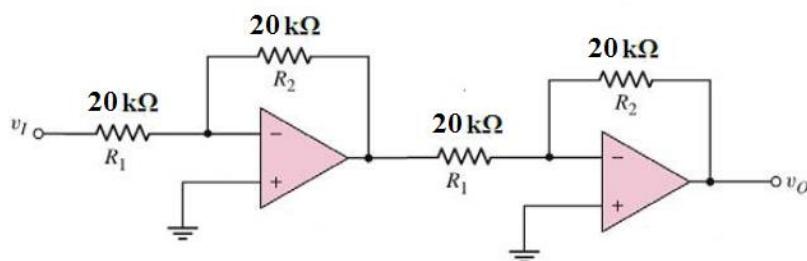(i) $A_v = -R_2/R_1 = -10$
 $R_1 = R_2/15 = 20k/10 = 2k\Omega$ [1.5 marks]

Correct inverting configuration structure [1.5 marks]



(ii) $A_v = -R_2/R_1 = -1$
 $R_1 = R_2/1 = 20k/1 = 20k\Omega$ [2 marks]

Correct inverting configuration structure [2 marks]
 Cascade inverting for 1st stage and 2nd stage [1 mark]

Question 5(b) [12 marks]

$R_2/R_1 = 80k/20k = 4$
 $R_4/R_3 = 85k/20k = 4.25$

[1 mark]
[1 mark]

$$\begin{aligned} V_o &= [1+4][4.25/1+4.25]v_{D2} - 4v_{I1} = 4.048v_{D2} - 4v_{I1} \\ &= 4.048(v_{cm}-v_d/2) - 4(v_{cm}+v_d/2) \\ &= 0.048v_{cm} - 4.024v_d \end{aligned}$$

[2 marks]
[2 marks]
[2 marks]
[2 marks]

Hence, $A_d = 4.024$
 $A_{cm} = 0.048$

And CMRR = $20 \cdot \log(4.024/0.048) = 38.47 \text{ dB}$ [2 marks]