

**COLLEGE OF ENGINEERING
PUTRAJAYA CAMPUS
FINAL EXAMINATION**

SEMESTER 1 2018 / 2019

PROGRAMME : **Bachelor of Electrical & Electronics Engineering (Honours)
Bachelor of Electrical Power Engineering (Honours)**

SUBJECT CODE : **EEEB273**

SUBJECT : **ELECTRONIC ANALYSIS AND DESIGN II**

DATE : **September 2018**

DURATION : **3 hours**

INSTRUCTIONS TO CANDIDATES:

1. This paper contains **FIVE** (5) questions in **NINE** (9) pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided. Use **pen** to write your answer.
4. Write answer to different question on a **new page**.

THIS QUESTION PAPER CONSISTS OF NINE (9) PRINTED PAGES INCLUDING THIS COVER PAGE.

Question 1 [20 marks]

You are one of the selected candidates to attend an interview carried out at Motorola Semiconductor as Product Engineer. As part of the interview you are given the following task:

Design a BJT Current Source that utilized 4 transistors arranged in cascode mode. All transistors in the circuit are matched. The transistor parameters are: $\beta = 150$, $V_A = 100 \text{ V}$, and $V_{BE(\text{on})} = 0.7 \text{ V}$. The power supplies: $V^+ = 5 \text{ V}$, $V^- = -5 \text{ V}$. Resistor $R_1 = 6 \text{ k}\Omega$.

Determine the followings:

- (a) **Draw** the circuit for the current source. [4 marks]
- (b) **Derive** the relationship between I_O and I_{REF} . [5 marks]
- (c) Based on given value of β , use approximate value of I_O to **estimate** the output resistance, R_O , of the current source. [7 marks]
- (d) **Find** g_{m4} and $r_{\pi4}$. [4 marks]

Question 2 [20 marks]

- (a) The differential amplifier in **Figure 1** has transistor parameters as $\beta = 100$ and $V_{BE(on)} = 0.7 \text{ V}$. The Early voltage is $V_A = \infty$ for Q_1 and Q_2 , and is $V_A = 50 \text{ V}$ for Q_3 and Q_4 .
- (i) Design the circuit such that $I_3 = 400 \mu\text{A}$ and $V_{CE1} = V_{CE2} = 10 \text{ V}$. [5 marks]
- (ii) Determine A_d and $CMRR_{dB}$ for a one-sided output at v_{O2} . A_{cm} is given as -0.113 V/V . [5 marks]

 


Figure 1

- (b) The differential amplifier in **Figure 2** is biased at $I_Q = 0.5 \text{ mA}$. The transistor parameters are shown in **Table 1**.

Table 1: MOSFET parameters

N-MOSFET transistor	P-MOSFET transistor
$K_n = 0.25 \text{ mA/V}^2$	$K_p = 0.25 \text{ mA/V}^2$
$V_{TN} = 0.4 \text{ V}$	$V_{TP} = -0.4 \text{ V}$
$\lambda_n = 0.02 \text{ V}^{-1}$	$\lambda_p = 0.02 \text{ V}^{-1}$

- (i) **Draw** an improved diff-amp for the circuit in **Figure 2**. Use **Table 1** for the transistors specification. [4 marks]
- (ii) **Calculate** the minimum power supply voltages if the common input voltages are to be in the range of $\pm 3 \text{ V}$. Assume symmetrical supply voltages. [6 marks]

 


Figure 2

Question 3 [20 marks]

A simple bipolar op-amp is designed as shown in **Figure 3**. Note that biasing for amplifiers in the circuit is provided by **two-transistor current mirrors**. Study the **Figure 3** carefully. Neglect base currents. Assume parameters for all transistors are $V_{BE(on)} = 0.7 \text{ V}$, $\beta = 200$, and $V_A = \infty$.

- (a) Referring to **Figure 3** calculate DC values for I_1, I_Q, I_{C2}, v_{O2} , and v_{O3} . **[10 marks]**
- (b) With small-signal analysis, values for $A_{d1}, r_{\pi3}$, and A_{v2} can be found using the following **Equations (3.1) to (3.3)**, assuming that $R_{i3} \gg R_5$. Calculate A_{d1}, A_{v2} , and the total overall small-signal voltage gain, A_d for the bipolar op-amp. **[10 marks]**

$$A_{d1} = \frac{v_{O2}}{v_d} = \frac{g_{m2}}{2} (R_C || R_{i2}) \quad (3.1)$$

$$r_{\pi3} \cong \beta r_{\pi4} \quad (3.2)$$

$$A_{v2} \cong \frac{I_{R4}}{2V_T} (R_5) \quad (3.3)$$

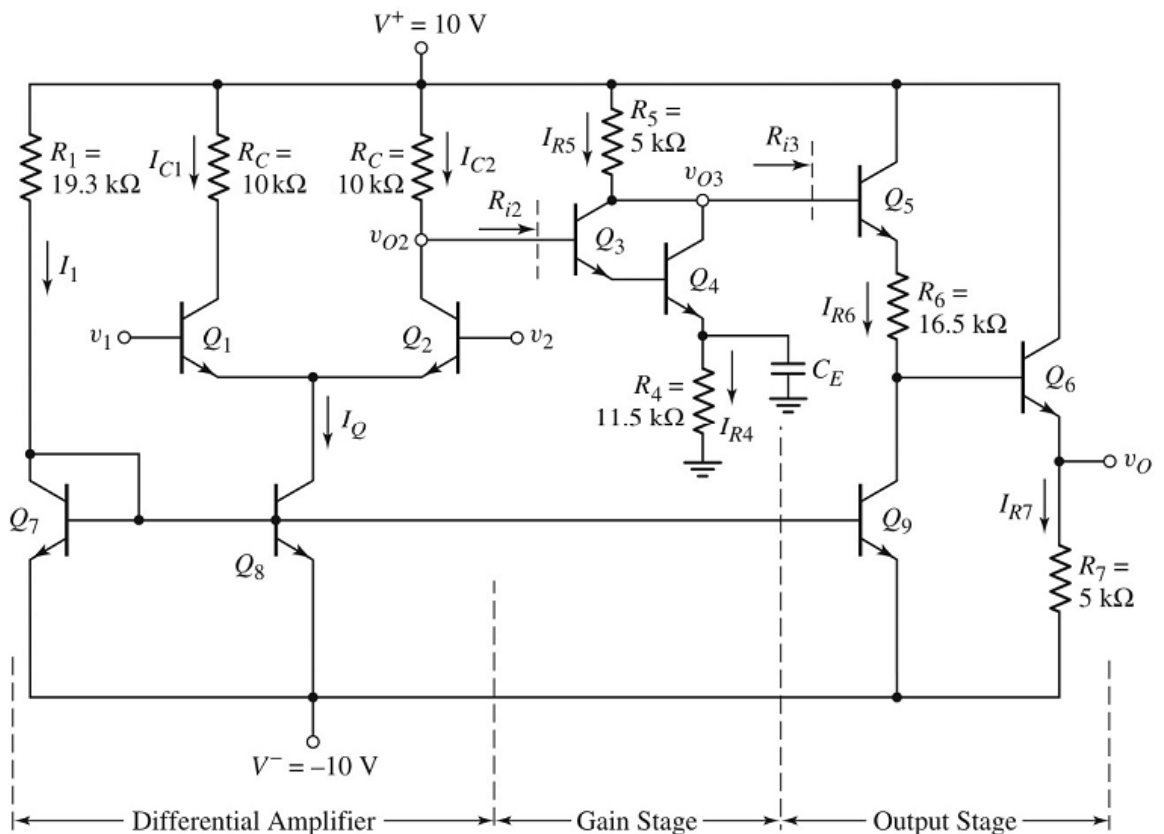


Figure 3

Question 4 [20 marks]

(a) **Figure 4a** and **Figure 4b** show two different designs of output stages.

- (i) **Identify** class of the output stages in the **Figure 4a** and **Figure 4b**. [2 marks]
- (ii) For the output stage circuit in the **Figure 4a** assume the B-E cut-in voltage (i.e. V_{BE} V_{EB}) of **0.6 V** such that v_O remains zero for the interval $-0.6 \text{ V} \leq v_I \leq 0.6 \text{ V}$. **Sketch** the voltage transfer characteristic of the circuit. **Indicate** when Q_n is conducting and when it is not conducting. [3 marks]
- (iii) For the output stage circuit in the **Figure 4b**, the circuit parameters are $V_{CC} = 12 \text{ V}$, $R_L = 100 \Omega$, and $V_{BB} = 1.2 \text{ V}$. Q_n and Q_p are matched with $I_S = 4 \times 10^{-13} \text{ A}$ and $\beta \gg 1$. For input voltage $v_I = 0$, **calculate** the quiescent collector currents, i_{Cn} and i_{Cp} . **What** is the maximum amplitude of the output voltage (v_O) and the corresponding maximum power that can be delivered to the load? [5 marks]

 


Figure 4a

 


Figure 4b

- (b) The **741 op-amp** is shown in **Figure 5**. Assume that $V_{BE(on)} = V_{EB(on)} = 0.7 \text{ V}$, $\beta_n = 200$, $\beta_p = 60$, $V_{AN} = 200 \text{ V}$, and $V_{AP} = 100 \text{ V}$. The area of transistor Q_{13B} is 75% of transistor Q_{12} . It is given that $I_{REF} = I_{C12} = 0.3 \text{ mA}$. Calculate the **small signal input resistance of the Gain stage** (i.e. into the base of Q_{16}). **[10 marks]**

 


Figure 5

Question 5 [20 marks]

(a) Using **feedback resistor of 20 kΩ**, draw the following circuits using **inverting op-amp configuration**:

(i) An **inverting amplifier** with a **closed-loop gain of -10**. [3 marks]

(ii) A **voltage follower**. [5 marks]

(b) A general output equation for a **difference amplifier** shown in **Figure 6** is:

$$v_o = A_d v_d + A_{cm} v_{cm}$$

For the difference amplifier in the **Figure 6**, the circuit parameters are **$R_1 = 20 \text{ k}\Omega$** , **$R_2 = 80 \text{ k}\Omega$** , **$R_3 = 20 \text{ k}\Omega$** , and **$R_4 = 85 \text{ k}\Omega$** and the output voltage (v_o) equation is as follows:

$$v_o = \left[1 + \frac{R_2}{R_1} \right] \left[\frac{R_4/R_3}{1 + R_4/R_3} \right] v_{I2} - \frac{R_2}{R_1} v_{I1}$$

where $v_{I1} = v_{cm} + \frac{v_d}{2}$ and $v_{I2} = v_{cm} - \frac{v_d}{2}$

Calculate the **differential-mode gain (A_d)**, **common-mode gain (A_{cm})**, and the **common-mode rejection ratio (CMRR) in dB** for the circuit. [12 marks]

 


Figure 6

-END OF QUESTION PAPER-

APPENDIX:

A) BASIC FORMULA FOR TRANSISTOR

BJT

$$i_C = I_S e^{v_{BE}/V_T} \quad ; \text{NPN}$$

$$i_C = I_S e^{v_{EB}/V_T} \quad ; \text{PNP}$$

$$i_C = \beta i_B = \frac{\beta}{\beta + 1} i_E$$

$$i_E = i_B + i_C$$

;Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

MOSFET

; N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k'_n}{2} \cdot \frac{W}{L}$$

; P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k'_p}{2} \cdot \frac{W}{L}$$

;Small signal


$$g_m = 2\sqrt{K_n I_{DQ}} \quad ; \text{N – MOSFET}$$

$$g_m = 2\sqrt{K_p I_{DQ}} \quad ; \text{P – MOSFET}$$


$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

B) HYBRID- π EQUIVALENT CIRCUITS

BJT

 

MOSFET

 

C) QUADRATIC FORMULA

$$Ax^2 + Bx + C = 0 \quad \rightarrow \quad x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$