

EEEB273 - Quiz 2
 SEMESTER 1, ACADEMIC YEAR 2018/2019
 Date: 3 July 2018 Time: 15 minutes

Question:

Study **Figure 1** carefully. Assume $V_{BE(ON)} = 0.7 \text{ V}$ and $V_A = \infty$ for all BJTs in the circuit. β for Q_1 and Q_2 is ∞ , but β for Q_3 and Q_4 is 30. For $R_C = 2 \text{ k}\Omega$, $R_1 = 2.7 \text{ k}\Omega$, and $v_{B1} = v_{B2} = 0 \text{ V}$, determine the value of V_{CE1} . Show your solution clearly. [10 marks]

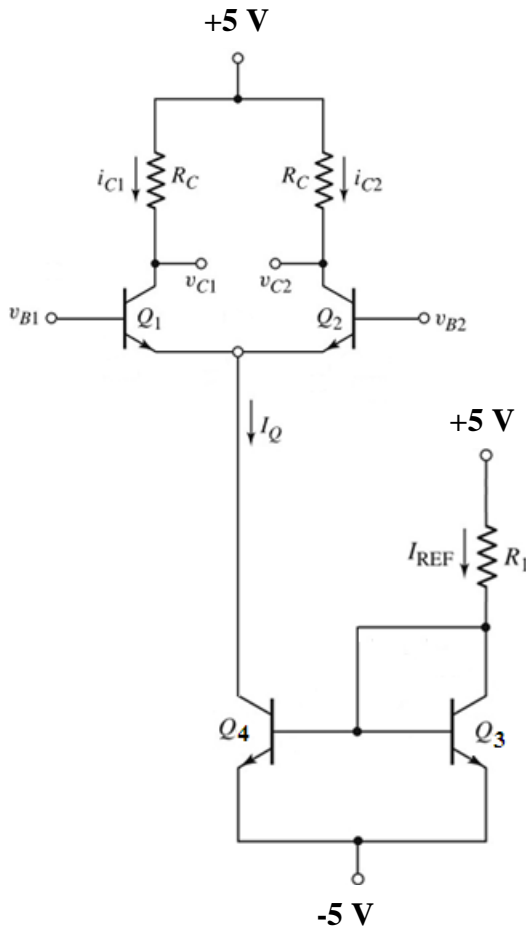


Figure 1

Answer:

2TCS:

$$I_{REF} = (V^+ - V_{BE3(ON)} - V^-) / (R_1) \quad [1]$$

$$= (5 - 0.7 - (-5)) / (2.7k) = 3.444 \text{ mA} \quad [1]$$

$$I_Q = I_{REF} / (1 + 2/\beta) \quad [1]$$

$$= (3.444m) / (1 + 2/30) = 3.2288 \text{ mA} \quad [1]$$

Diff amp:

When $v_{B1} = v_{B2} = 0 \text{ V}$ and β for Q_1 and Q_2 is ∞ :

$$I_Q = i_{C1} + i_{C2} \quad [1]$$

$$i_{C1} = i_{C2} = I_Q / 2 \quad [1]$$

$$= (3.2288m) / 2 = 1.6144 \text{ mA} \quad [1]$$

$$V_{CE1} = v_{C1} - V_{E1} \quad [1]$$

$$V_{E1} = v_{B1} - V_{BE1(ON)} = 0 - 0.7 = -0.7 \text{ V} \quad [1]$$

$$v_{C1} = 5 - i_{C1} R_C \quad [1]$$

$$= 5 - (1.6144m)(2k) = 1.7712 \text{ V} \quad [1]$$

$$V_{CE1} = 1.7712 - (-0.7) = 2.4712 \text{ V} \quad [1]$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

Question:

Study **Figure 1** carefully. Assume $V_{BE(ON)} = 0.7\text{ V}$ and $V_A = \infty$ for all BJTs in the circuit. β for Q_1 and Q_2 is ∞ , but β for Q_3 and Q_4 is 40. For $R_C = 2\text{ k}\Omega$, $R_1 = 2.8\text{ k}\Omega$, and $v_{B1} = v_{B2} = 0\text{ V}$, determine the value of V_{CE2} . Show your solution clearly. [10 marks]

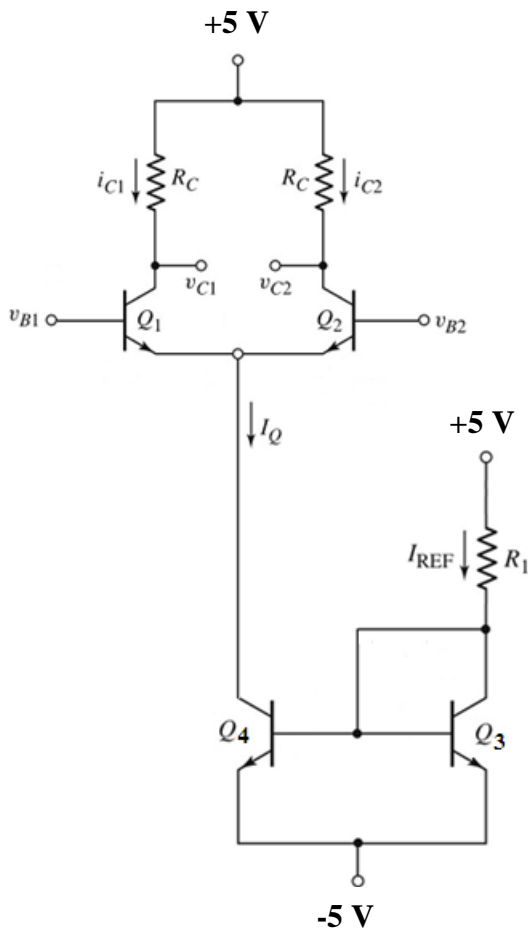


Figure 1

2TCS:

$$I_{REF} = (V^+ - V_{BE3(ON)} - V^-) / (R_1) \quad [1]$$

$$= (5 - 0.7 - (-5)) / (2.8k) = 3.3214\text{ mA} \quad [1]$$

I_Q

$$I_Q = I_{REF} / (1 + 2/\beta) \quad [1]$$

$$= (3.3214\text{m}) / (1 + 2/40) = 3.1632\text{ mA} \quad [1]$$

Diff amp:

When $v_{B1} = v_{B2} = 0\text{ V}$ and β for Q_1 and Q_2 is ∞ :

$$I_Q = i_{C1} + i_{C2} \quad [1]$$

$$i_{C2} = i_{C1} = I_Q / 2 \quad [1]$$

$$= (3.1632\text{m}) / 2 = 1.5816\text{ mA} \quad [1]$$

V_{CE2}

$$V_{CE2} = v_{C2} - V_{E2} \quad [1]$$

$$V_{E2} = v_{B2} - V_{BE2(ON)} = 0 - 0.7 = -0.7\text{ V} \quad [1]$$

$$v_{C2} = 5 - i_{C2} R_C \quad [1]$$

$$= 5 - (1.5816\text{m})(2k) = 1.8368\text{ V} \quad [1]$$

$$V_{CE2} = 1.8368 - (-0.7) = 2.5368\text{ V} \quad [1]$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

Answer:

Question:

Study **Figure 1** carefully. Assume $V_{BE(on)} = 0.7 \text{ V}$ and $V_A = \infty$ for all BJTs in the circuit. β for Q_1 and Q_2 is ∞ , but β for Q_3 and Q_4 is 40. For $R_C = 2.5 \text{ k}\Omega$, $R_1 = 3 \text{ k}\Omega$, and $v_{B1} = v_{B2} = 0 \text{ V}$, determine the value of V_{CE1} . Show your solution clearly. [10 marks]

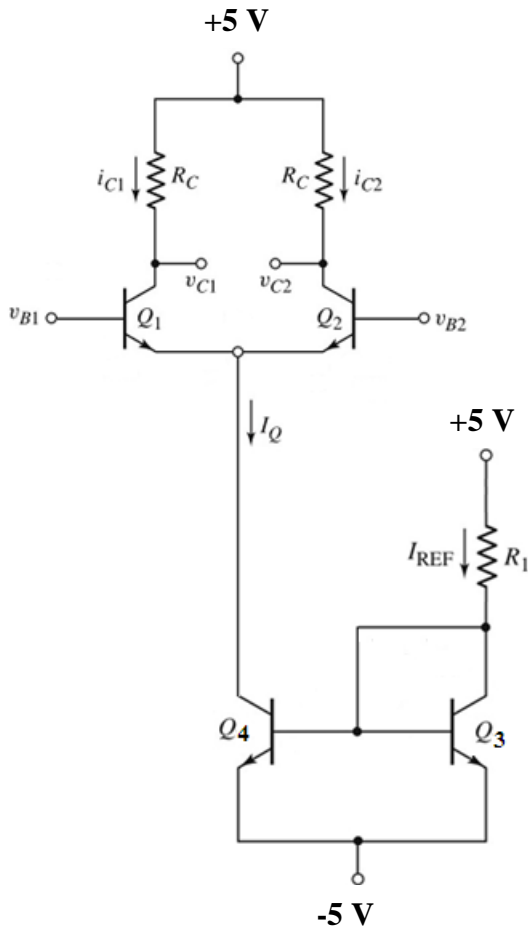


Figure 1

Answer:

2TCS:

$$I_{REF} = (V^+ - V_{BE3(on)} - V^-) / (R_1) \quad [1]$$

$$= (5 - 0.7 - (-5)) / (3k) = 3.1 \text{ mA} \quad [1]$$

$$I_Q = I_{REF} / (1 + 2/\beta) \quad [1]$$

$$= (3.1m) / (1 + 2/40) = 2.9523 \text{ mA} \quad [1]$$

Diff amp:

When $v_{B1} = v_{B2} = 0 \text{ V}$ and β for Q_1 and Q_2 is ∞ :

$$I_Q = i_{C1} + i_{C2} \quad [1]$$

$$i_{C1} = i_{C2} = I_Q / 2 \quad [1]$$

$$= (2.9523m) / 2 = 1.4762 \text{ mA} \quad [1]$$

$$V_{CE1} = v_{C1} - V_{E1} \quad [1]$$

$$V_{E1} = v_{B1} - V_{BE1(on)} = 0 - 0.7 = -0.7 \text{ V} \quad [1]$$

$$v_{C1} = 5 - i_{C1} R_C \quad [1]$$

$$= 5 - (1.4762m)(2.5k) = 1.3095 \text{ V} \quad [1]$$

$$V_{CE1} = 1.3095 - (-0.7) = 2.0095 \text{ V} \quad [1]$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

Question:

Study **Figure 1** carefully. Assume $V_{BE(ON)} = 0.7 \text{ V}$ and $V_A = \infty$ for all BJTs in the circuit. β for Q_1 and Q_2 is ∞ , but β for Q_3 and Q_4 is 30. For $R_C = 2.5 \text{ k}\Omega$, $R_1 = 2.9 \text{ k}\Omega$, and $v_{B1} = v_{B2} = 0 \text{ V}$, **determine** the value of V_{CE2} . Show your solution clearly. [10 marks]

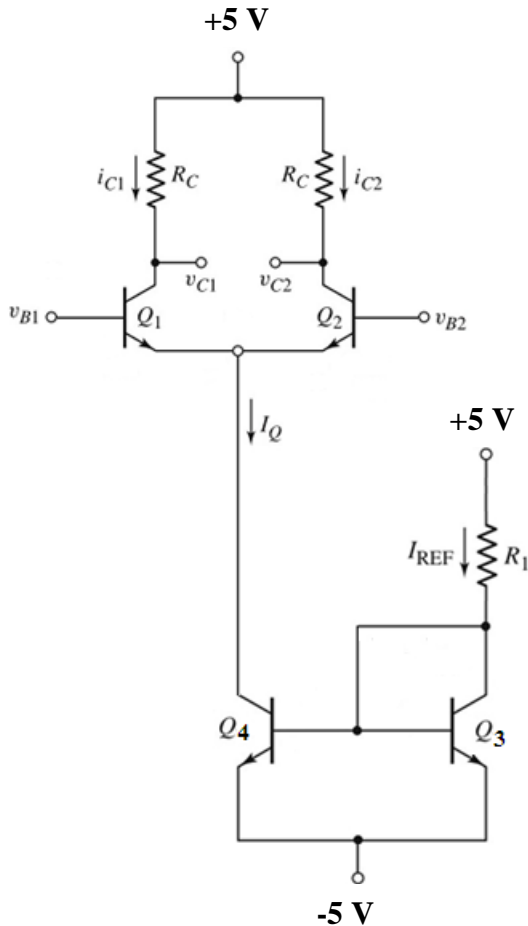


Figure 1

Answer:

2TCS:

$$I_{REF} = (V^+ - V_{BE3(ON)} - V^-) / (R_1) \quad [1]$$

$$= (5 - 0.7 - (-5)) / (2.9k) = 3.2069 \text{ mA} \quad [1]$$

$$I_Q = I_{REF} / (1 + 2/\beta) \quad [1]$$

$$= (3.2069\text{m}) / (1 + 2/30) = 3.0064 \text{ mA} \quad [1]$$

Diff amp:

When $v_{B1} = v_{B2} = 0 \text{ V}$ and β for Q_1 and Q_2 is ∞ :

$$I_Q = i_{C1} + i_{C2} \quad [1]$$

$$i_{C2} = i_{C1} = I_Q / 2 \quad [1]$$

$$= (3.0064\text{m}) / 2 = 1.5032 \text{ mA} \quad [1]$$

$$V_{CE2} = v_{C2} - V_{E2} \quad [1]$$

$$V_{E2} = v_{B2} - V_{BE2(ON)} = 0 - 0.7 = -0.7 \text{ V} \quad [1]$$

$$v_{C2} = 5 - i_{C2} R_C \quad [1]$$

$$= 5 - (1.5032\text{m})(2.5k) = 1.242 \text{ V} \quad [1]$$

$$V_{CE2} = 1.242 - (-0.7) = 1.942 \text{ V} \quad [1]$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$