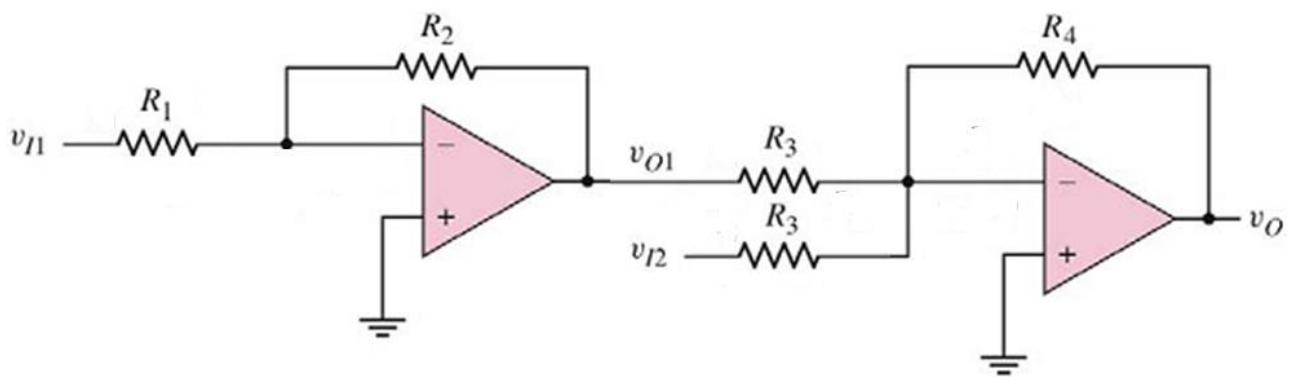


**Question:**

Consider **ideal** inverting op-amp circuits in **Figure 1**. Given  $R_1 = 5 \text{ k}\Omega$ ,  $R_2 = 40 \text{ k}\Omega$ ,  $R_3 = 10 \text{ k}\Omega$ , and  $R_4 = 200 \text{ k}\Omega$ .

- (a) Derive the expression for the output voltage  $v_O$  in terms of input voltages  $v_{I1}$  and  $v_{I2}$ . [6 marks]
- (b) Determine  $v_O$  for  $v_{I1} = +5 \text{ mV}$  and  $v_{I2} = -25 - 50 \sin \omega t \text{ mV}$ . [3 marks]
- (c) What is the maximum value of the output voltage, i.e.  $v_O (\max)$ ? [1 mark]



**Figure 1**

**Answer:**

(a)

$$v_{O1} = - (R_2 / R_1) v_{I1} = - (40\text{k}/5\text{k}) v_{I1} = - 8 v_{I1} \quad [3]$$

$$\begin{aligned} v_O &= - (R_4 / R_3) (v_{O1} + v_{I2}) = - (200\text{k}/10\text{k}) (- 8 v_{I1} + v_{I2}) \\ v_O &= 20 (- 8 v_{I1} + v_{I2}) = 160 v_{I1} - 20 v_{I2} \end{aligned} \quad [3]$$

(b)

$$v_O = 160 v_{I1} - 20 v_{I2} = 160 (+5 \text{ mV}) - 20 (-25 - 50 \sin \omega t \text{ mV}) \quad [2]$$

$$v_O = 800 \text{ mV} + 500 \text{ mV} + 1000 \sin \omega t \text{ mV}$$

$$v_O = 1300 \text{ mV} + 1000 \sin \omega t \text{ mV} = 1.3 + 1 \sin \omega t \text{ V} \quad [1]$$

(c)


$v_O (\max)$  is the value when  $\sin \omega t = 1$ .

$$v_O (\max) = 1.3 + 1 (1) = 2.3 \text{ V.} \quad [1]$$

**Question:**

Consider **ideal** inverting op-amp circuits in **Figure 1**. Given  $R_1 = 15 \text{ k}\Omega$ ,  $R_2 = 45 \text{ k}\Omega$ ,  $R_3 = 8 \text{ k}\Omega$ , and  $R_4 = 240 \text{ k}\Omega$ .

- (a) Derive the expression for the output voltage  $v_O$  in terms of input voltages  $v_{I1}$  and  $v_{I2}$ . [6 marks]
- (b) Determine  $v_O$  for  $v_{I1} = +5 \text{ mV}$  and  $v_{I2} = -25 - 50 \sin \omega t \text{ mV}$ . [3 marks]
- (c) What is the maximum value of the output voltage, i.e.  $v_O (\max)$ ? [1 mark]

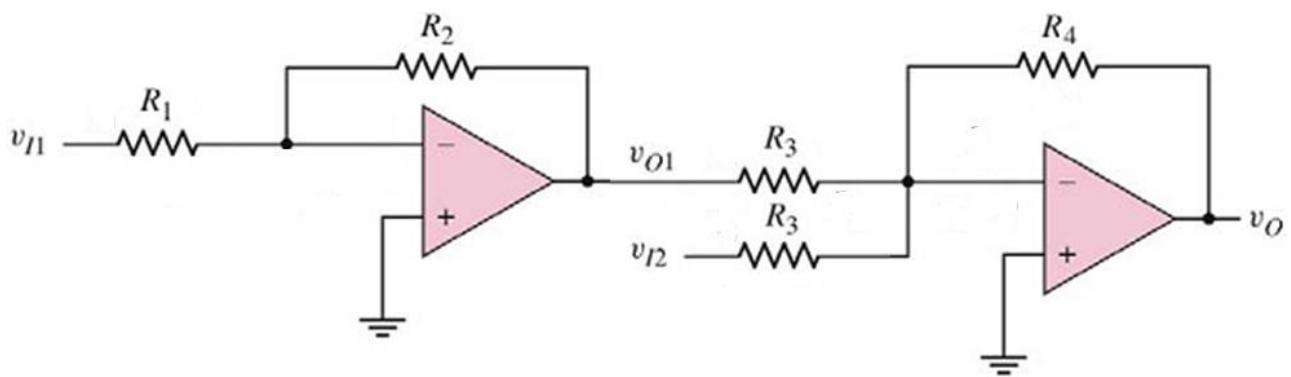

**Figure 1**

**Answer:**

(a)

$$v_{O1} = - (R_2 / R_1) v_{I1} = - (45\text{k}/15\text{k}) v_{I1} = - 3 v_{I1} \quad [3]$$

$$\begin{aligned} v_O &= - (R_4 / R_3) (v_{O1} + v_{I2}) \\ v_O &= - (240\text{k}/8\text{k}) (- 3 v_{I1} + v_{I2}) \\ v_O &= 90 (- 3 v_{I1} + v_{I2}) \end{aligned} \quad [3]$$

(b)

$$v_O = 90 v_{I1} - 30 v_{I2} = 90 (+5 \text{ mV}) - 30 (-25 - 50 \sin \omega t \text{ mV}) \quad [2]$$

$$v_O = 450 \text{ mV} + 750 \text{ mV} + 1500 \sin \omega t \text{ mV}$$

$$v_O = 1200 \text{ mV} + 1500 \sin \omega t \text{ mV} = 1.2 + 1.5 \sin \omega t \text{ V} \quad [1]$$

(c)


$v_O (\max)$  is the value when  $\sin \omega t = 1$ .

$$v_O (\max) = 1.2 + 1.5 (1) = 2.7 \text{ V.} \quad [1]$$

**Question:**

Consider **ideal** inverting op-amp circuits in **Figure 1**. Given  $R_1 = 5 \text{ k}\Omega$ ,  $R_2 = 40 \text{ k}\Omega$ ,  $R_3 = 10 \text{ k}\Omega$ , and  $R_4 = 200 \text{ k}\Omega$ .

- (a) Derive the expression for the output voltage  $v_O$  in terms of input voltages  $v_{I1}$  and  $v_{I2}$ . [6 marks]
- (b) Determine  $v_O$  for  $v_{I1} = +7.5 \text{ mV}$  and  $v_{I2} = -35 - 60 \sin \omega t \text{ mV}$ . [3 marks]
- (c) What is the maximum value of the output voltage, i.e.  $v_O (\max)$ ? [1 mark]

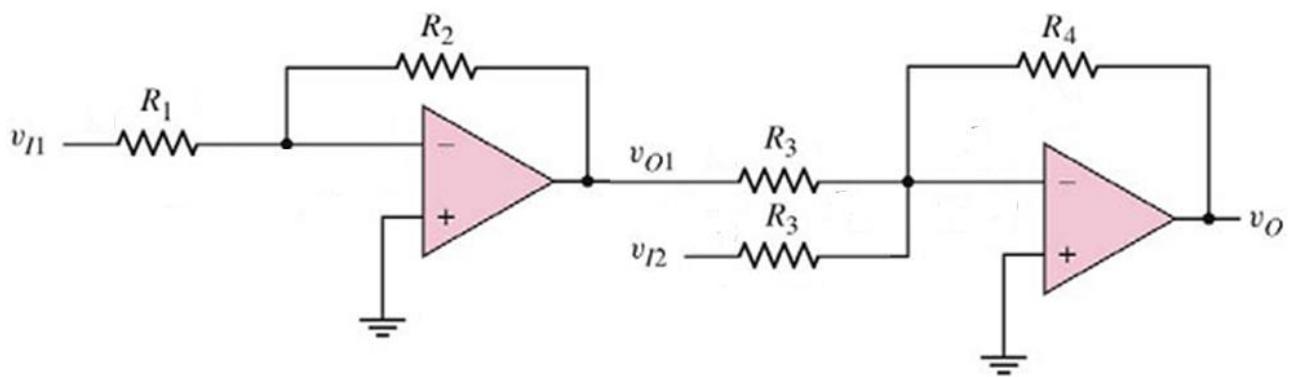

**Figure 1**

**Answer:**

(a)

$$v_{O1} = - (R_2 / R_1) v_{I1} = - (40\text{k}/5\text{k}) v_{I1} = - 8 v_{I1} \quad [3]$$

$$\begin{aligned} v_O &= - (R_4 / R_3) (v_{O1} + v_{I2}) = - (200\text{k}/10\text{k}) (- 8 v_{I1} + v_{I2}) \\ v_O &= 20 (- 8 v_{I1} + v_{I2}) = 160 v_{I1} - 20 v_{I2} \end{aligned} \quad [3]$$

(b)

$$v_O = 160 v_{I1} - 20 v_{I2} = 160 (+7.5 \text{ mV}) - 20 (-35 - 60 \sin \omega t \text{ mV}) \quad [2]$$

$$v_O = 1200 \text{ mV} + 700 \text{ mV} + 1200 \sin \omega t \text{ mV}$$

$$v_O = 1900 \text{ mV} + 1200 \sin \omega t \text{ mV} = 1.9 + 1.2 \sin \omega t \text{ V} \quad [1]$$

(c)


$v_O (\max)$  is the value when  $\sin \omega t = 1$ .

$$v_O (\max) = 1.9 + 1.2 (1) = 3.1 \text{ V.} \quad [1]$$

**Question:**

Consider **ideal** inverting op-amp circuits in **Figure 1**. Given  $R_1 = 15 \text{ k}\Omega$ ,  $R_2 = 45 \text{ k}\Omega$ ,  $R_3 = 8 \text{ k}\Omega$ , and  $R_4 = 240 \text{ k}\Omega$ .

- (a) Derive the expression for the output voltage  $v_O$  in terms of input voltages  $v_{I1}$  and  $v_{I2}$ . [6 marks]
- (b) Determine  $v_O$  for  $v_{I1} = +7.5 \text{ mV}$  and  $v_{I2} = -35 - 60 \sin \omega t \text{ mV}$ . [3 marks]
- (c) What is the maximum value of the output voltage, i.e.  $v_O (\max)$ ? [1 mark]

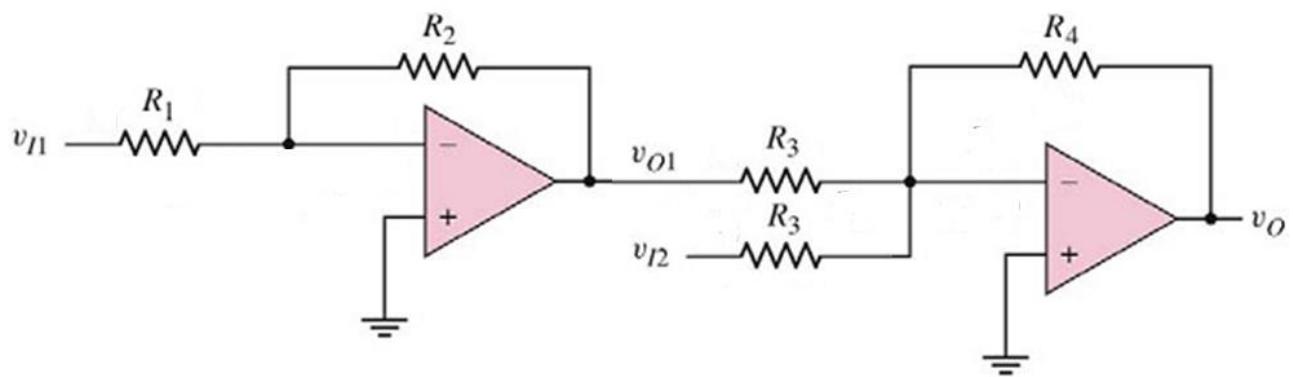

**Figure 1**

**Answer:**

(a)

$$v_{O1} = - (R_2 / R_1) v_{I1} = - (45\text{k}/15\text{k}) v_{I1} = - 3 v_{I1} \quad [3]$$

$$\begin{aligned} v_O &= - (R_4 / R_3) (v_{O1} + v_{I2}) \\ v_O &= - (240\text{k}/8\text{k}) (- 3 v_{I1} + v_{I2}) \\ v_O &= 90 (- 3 v_{I1} + v_{I2}) \end{aligned} \quad [3]$$

(b)

$$v_O = 90 v_{I1} - 30 v_{I2} = 90 (+7.5 \text{ mV}) - 30 (-35 - 60 \sin \omega t \text{ mV}) \quad [2]$$

$$v_O = 675 \text{ mV} + 1050 \text{ mV} + 1800 \sin \omega t \text{ mV}$$

$$v_O = 1725 \text{ mV} + 1800 \sin \omega t \text{ mV} = 1.725 + 1.8 \sin \omega t \text{ V} \quad [1]$$

(c)

$v_O (\max)$  is the value when  $\sin \omega t = 1$ .

$$v_O (\max) = 1.725 + 1.8 (1) = 3.525 \text{ V.} \quad [1]$$