

Name:
Student ID Number:
Section Number: 01/02/03/04 A/B
Lecturer: Dr Jamaludin/ Dr Fazrena Azlee/
 Dr Jehana Ermy/ Prof Md Zaini
Table Number:



College of Engineering
 Department of Electronics and Communication Engineering

Test 2 – Model Answers

SEMESTER 1, ACADEMIC YEAR 2018/2019

Subject Code : **EEEEB273**
 Course Title : **Electronics Analysis & Design II**
 Date : **11 August 2018**
 Duration : **2 hours**

Instructions to the candidates:

1. Write your **Name** and **Student ID Number**. Indicate your **Section Number** and **Lecturer's** Name. Write also your **Table Number**.
2. **Write all your answers using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS.** Show clearly all your calculations. Every value **must** be written with its correct Unit.
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.


☺ **GOOD LUCK!** ☺

Question Number	Q1a	Q1bc	Q2a	Q2b	Q3a	Q3b	Q4a	Q4b	Total
Marks									

QUESTION 1 [20 marks]

Answers for Question 1 (Continued)

Q1(a)

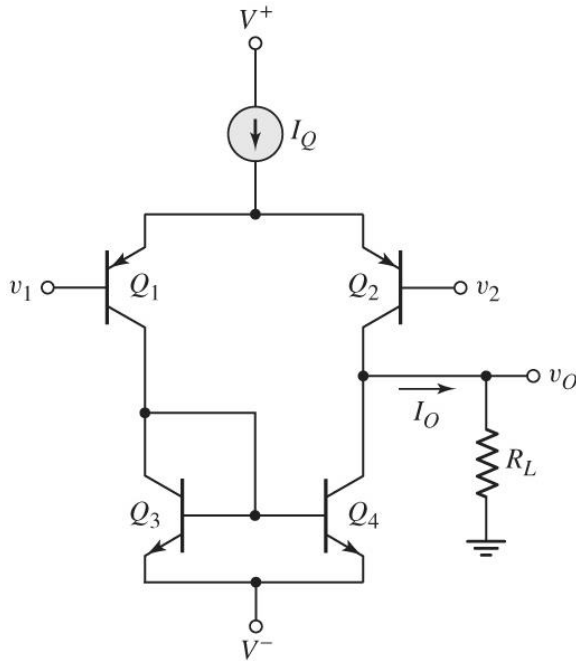

3 marks: correct label
 3 marks: correct placement

Q1(b) $r_{02} = V_A/I_{CQ2} = V_A/(I_Q/2) = 100/(0.15\text{m}/2) = 1.33\text{M}\Omega$ [2]

$r_{04} = V_A/I_{CQ2} = V_A/(I_Q/2) = 100/(0.15\text{m}/2) = 1.33\text{M}\Omega$ [2]

$g_{m2} = I_{CQ2}/V_T = I_Q/2V_T = 0.15\text{m}/[2(26\text{m})] = 2.885\text{mA/V}$ [2]

$A_d = g_{m2} (r_{02} // r_{04}) = 2.885\text{m} (1.33\text{M} // 1.33\text{M}) = 1923 \text{ V/V}$ [2]

Q1(c) $A_d = g_{m2} (r_{02} // r_{04} // R_L)$ [2]


$524 = 2.885\text{m} (1.33\text{M} // 1.33\text{M} // R_L)$ [2]

$R_L = 250\text{k}\Omega$ [2]

QUESTION 2 [35 marks]

Answers for Question 2 (Continued)

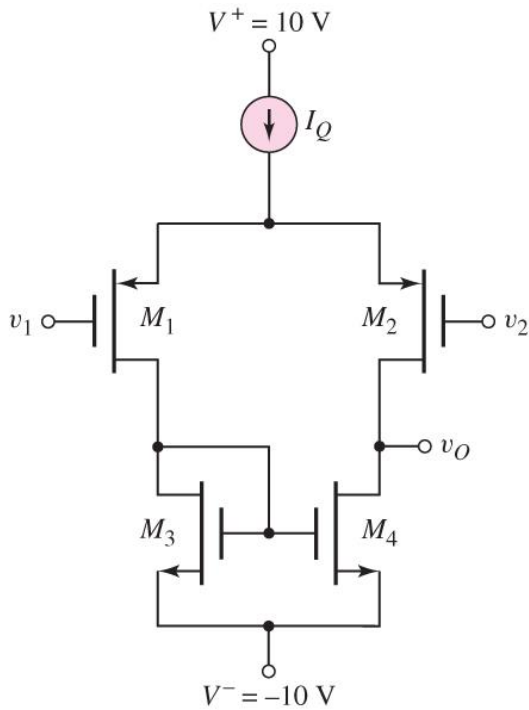- Q2(a) Placements of M_1 and M_2 [5]
 Current source M_3 and M_4 [5]
 Correct label for MOSFET and power supplies [5]



- (b) (i) $R_O = r_{o2} \parallel r_{o4}$ [1]
 $I_{D2} = I_{D4} = I_Q/2 = (0.4\text{mA})/2 = 0.2 \text{ mA}$ [1]
 $r_{o2} = 1/(\lambda_p I_{D2}) = 1/(0.01 \times 0.2\text{mA}) = 500 \text{ k}\Omega$ [1]
 $r_{o4} = 1/(\lambda_n I_{D4}) = 1/(0.02 \times 0.2\text{mA}) = 250 \text{ k}\Omega$ [1]
 $R_O = (500\text{k} \parallel 250\text{k}) = 166.7 \text{ k}\Omega$ [1]
- (ii) $A_d = g_{m2}(r_{o2} \parallel r_{o4}) = g_{m2}(R_O)$ [2]
 $g_{m2} = 2\sqrt{K_p I_{D2}} = 2\sqrt{(60\mu)(0.2\text{mA})} = 0.219 \text{ mA/V}$ [2]
 $A_d = (0.219\text{mA})(166.67\text{k}) = \underline{36.515 \text{ V/V}}$ [1]
- (iii) $v_O = A_d v_d = (36.515) \times 20 \sin(\omega t) = \underline{730 \sin(\omega t) \text{ V}}$ [2, 2, 1]
- (iv) The A_d calculation is changed to $A_d = g_{m2}(r_{o2} \parallel R_{O4c})$ [2]
 where $R_{O4c} = g_{m4} r_{o4} r_{o6}$ by approximation [2]
 and higher than the ordinary R_O . [1]

QUESTION 3 [20 marks]**Answers for Question 3**Q3(a) Derive formula $I_O = I_Q / \beta$ and use it **[5 marks]**

$$I_{B3} + I_{B4} = I_{C3} / \beta + I_{C4} / \beta = (I_{C3} + I_{C4}) / \beta \quad [1]$$

Assuming base currents for transistors in the diff-amp and I_O are small, then

$$I_{C3} + I_{C4} \approx I_{C1} + I_{C2} \approx I_{E1} + I_{E2} = I_Q \quad [1]$$

Then $I_{B3} + I_{B4} = I_Q / \beta$ **[1]**For the DC currents in the diff-amp to be **balanced**

$$I_O = I_{B6} = I_{B3} + I_{B4} = I_Q / \beta \quad [1]$$

$$I_O = I_Q / \beta = 0.307 \text{ mA} / 120 = 0.002558 \text{ mA} = \mathbf{2.558 \mu A} \quad [1]$$

Q3(b) Calculation for A_{v2} : **[15 marks]**

$$I_Q = \mathbf{0.307 \text{ mA}}, \quad I_{B6} = I_O = \mathbf{2.558 \mu A}$$

$$I_{C6} = \beta I_{B6} = \mathbf{120 \times 2.558 \mu = 0.307 \text{ mA}} \quad [1]$$

$$I_{C7} = \beta I_{B7} = \beta I_{E6} = \beta(1 + \beta) I_{B6} \quad [1]$$

$$I_{C7} = \mathbf{120(121)(2.558 \mu) = 37.142 \text{ mA}} \quad [0.5]$$

$$I_{C8} = \frac{v_O - V^-}{R_2} = \frac{0 - (-10)}{5k} = \mathbf{2 \text{ mA}} \quad [1]$$

Calculation for R_i :

$$r_{\pi 6} = \frac{\beta V_T}{I_{C6}} = \frac{120 \times 0.026}{0.307 \text{ m}} = \mathbf{10.16 \text{ k}\Omega} \quad [1]$$

$$r_{\pi 7} = \frac{\beta V_T}{I_{C7}} = \frac{120 \times 0.026}{37.142 \text{ m}} = \mathbf{0.084 \text{ k}\Omega} \quad [1]$$

$$R_i = r_{\pi 6} + (1 + \beta)r_{\pi 7} \quad [1]$$

$$R_i = \mathbf{10.16k + (121)(0.084k) = 20.32 \text{ k}\Omega} \quad [0.5]$$

Calculation for R_{c11} :

$$r_{o11} = V_A / I_{C7} = \mathbf{100/37.142 \text{ m} = 2.692 \text{ k}\Omega} \quad [1]$$

Therefore, $R_{c11} = r_{o11} = \mathbf{2.692 \text{ k}\Omega}$ **[1, 0.5]**Calculation for R_{b8} :

$$r_{\pi 8} = \beta V_T / I_{C8} = (120 \times 0.026) / (2 \text{ m}) = \mathbf{1.56 \text{ k}\Omega} \quad [1]$$

$$R_{b8} = r_{\pi 8} + (1 + \beta)R_2 = \mathbf{1.56k + (121)(5k) = 606.56 \text{ k}\Omega} \quad [1, 0.5]$$

$$R_{L7} = R_{c11} \parallel R_{b8} = \mathbf{2.692k \parallel 606.56k = 2.68 \text{ k}\Omega} \quad [1]$$

$$r_{o7} = r_{o11} = V_A / I_{C7} = \mathbf{100/37.142 \text{ m} = 2.692 \text{ k}\Omega} \quad [1]$$

$$r_{o7} \parallel R_{L7} = \mathbf{2.692k \parallel 2.68k = 1.343 \text{ k}\Omega}$$




$$A_{v2} = \frac{\beta(1 + \beta)(r_{o7} \parallel R_{L7})}{R_i}$$

$$A_{v2} = \mathbf{[(120 \times 121)(2.692k \parallel 2.68k)] / 20.32k = 959.66} \quad [1]$$

QUESTION 4 [25 marks]

Answers for Question 4 (Continued)

Answers to Question 4(a) [5 marks]

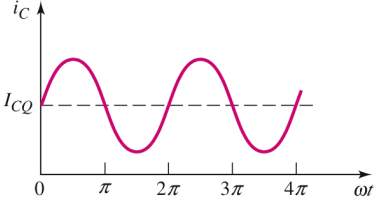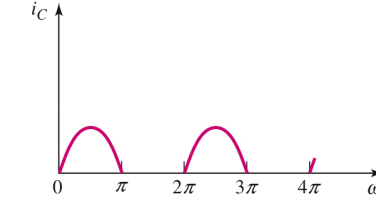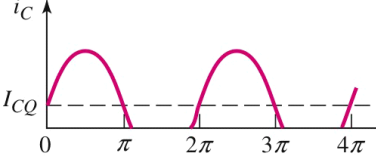Output Stage	Output current waveform	Explanation
<p>Class A</p>	 <p>[1 mark]</p>	<p>output transistor is biased at a quiescent current I_Q [½ mark] and conducts for the entire cycle of the input signal. [½ mark]</p>
<p>Class B</p>	 <p>[½ mark]</p>	<p>output transistor conducts for only one-half of each sine-wave input cycle. [½ mark]</p>
<p>Class AB</p>	 <p>[1 mark]</p>	<p>output transistor biased at a small quiescent current I_Q, [½ mark] and conducts for slightly more than half a cycle [½ mark]</p>

This is extra page for answers. Please indicate question number clearly.

Answers to QUESTION 4(b) [20 marks]

$$(i) \quad \begin{aligned} V_{O(\max)} &= V_{CC} - V_{CE1(\text{sat})} \\ &= 10 - 0.3 = 9.7\text{V} \end{aligned} \quad [2]$$

$$\begin{aligned} V_{O(\min)} &= -V_{CC} + V_{CE2(\text{sat})} \\ &= -10 + 0.3 = -9.7\text{V} \end{aligned} \quad [2]$$

$$\begin{aligned} I_Q &= |I_{L(\text{Min})}| \\ &= |V_{O(\min)} / R_L| = |-9.7 / 1\text{k}| = 9.7 \text{ mA} \end{aligned} \quad [2]$$

$$I_R = I_Q = 9.7\text{mA} \quad [1]$$

$$\begin{aligned} R &= (V_{\text{bias}} - V_{BE(\text{on})} - V_{CC}) / I_R \\ &= (2 - 0.65 - (-10)) / 9.7\text{m} \\ &= 1.17\text{k}\Omega \end{aligned} \quad [2]$$

$$(ii) \quad \eta = P_L(\text{ave}) / P_s(\text{ave}) \times 100\% \quad [1]$$

$$\begin{aligned} P_L(\text{ave}) &= \frac{1}{2} V_{O(\max)}^2 / R_L \\ &= \frac{1}{2} (9.7)^2 / 1\text{k} = 47.045 \text{ mW} \end{aligned} \quad [2]$$

$$\begin{aligned} P_S(\text{ave}) &= (V_{CC} - (-V_{CC})) \times I_Q + (V_{\text{bias}} - (-V_{CC})) \times I_R \\ &= (10 - (-10))(9.7\text{m}) + (2 - (-10))(9.7\text{m}) = 310.4\text{mW} \end{aligned} \quad [2]$$

$$\eta = 47.045\text{m} / 310.4\text{m} \times 100\% = 15.16\% \quad [1]$$

$$(iii) \quad \begin{aligned} P_{Q1} &= V_{CE1} \times I_{C1} = (V_{CC} - V_O) \times (I_Q + I_L) \\ &= (10 - 5) \times (9.7\text{m} + 5/1\text{k}) = (5)(14.7\text{m}) = 73.5\text{mW} \end{aligned} \quad [2]$$

$$= (10 - 5) \times (9.7\text{m} + 5/1\text{k}) = (5)(14.7\text{m}) = 73.5\text{mW} \quad [1]$$