

Name:

Student ID Number:

Section Number: 01/02/03/04 A/B

Lecturer: Dr Jamaludin/ Dr Fazrena Azlee/

Dr Jehana Ermy/ Prof Md Zaini

Table Number:



College of Engineering
Department of Electronics and Communication Engineering

Test 2

SEMESTER 1, ACADEMIC YEAR 2018/2019

Subject Code : **EEEB273**
Course Title : **Electronics Analysis & Design II**
Date : **11 August 2018**
Duration : **2 hours**

Instructions to the candidates:

1. Write your **Name** and **Student ID Number**. Indicate your **Section Number** and **Lecturer's** Name. Write also your **Table Number**.
2. **Write all your answers using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS**. Show clearly all your calculations. Every value **must** be written with its correct Unit.
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.



GOOD LUCK!



Question Number	Q1a	Q1bc	Q2a	Q2b	Q3a	Q3b	Q4a	Q4b	Total
Marks									

BASIC FORMULA FOR TRANSISTOR

BJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{nnp}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

;Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

Quadratic formula :

$$Ax^2 + Bx + C = 0 \quad \rightarrow \quad x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$

MOSFET

;N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{k'_n}{2} \cdot \frac{W}{L}$$

;P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{k'_p}{2} \cdot \frac{W}{L}$$

;Small signal

$$g_m = 2\sqrt{K_n I_{DQ}} \quad ; \text{N - MOSFET}$$

$$g_m = 2\sqrt{K_p I_{DQ}} \quad ; \text{P - MOSFET}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

This is extra page for answers. Please indicate question number clearly.

QUESTION 1 [20 marks]

The differential amplifier with active load shown in **Figure 1** has a pair of **pnp bipolar differential amplifier** as input devices and a pair of **npn bipolar connected as an active load**. The circuit bias is $I_Q = 0.15 \text{ mA}$, and the transistor parameters are $\beta = 100$, and $V_A = 100 \text{ V}$.

- (a) **Draw** the active load circuit to complete the circuit in **Figure 1**. [6 marks]
- (b) **Find** the open-circuit differential-mode voltage gain, A_d . [8 marks]
- (c) **Calculate** the value of a load resistance R_L connected to the output v_O if the differential mode voltage gain A_d is to be reduced to **524 V/V**. [6 marks]

Answers for Question 1

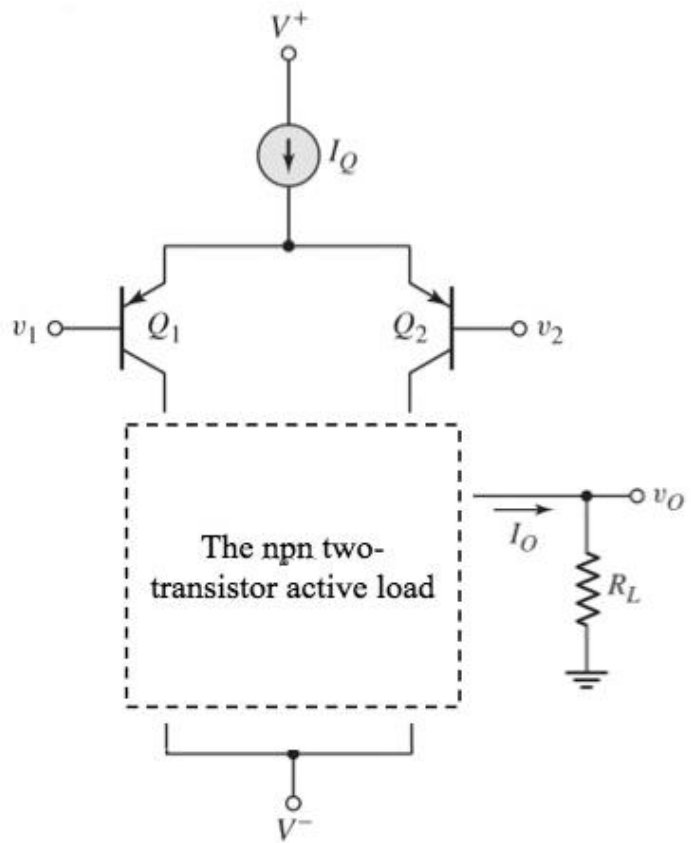


Figure 1

Answers for Question 1 (Continued)

QUESTION 2 [35 marks]

- (a) Draw a PMOS differential amplifier, M_1 and M_2 , with an active load of two-transistor current source, M_3 and M_4 . Label them clearly with $V^+ = 10\text{ V}$ and $V^- = -10\text{ V}$.

[15 marks]

- (b) Consider the drawn figure in part (a). The transistors parameters are $V_{TN} = 1\text{ V}$, $K_n = 90\ \mu\text{A}/\text{V}^2$, $\lambda_n = 0.02\ \text{V}^{-1}$, $V_{TP} = -1\text{ V}$, $K_p = 60\ \text{A}/\text{V}^2$, $\lambda_p = 0.01\ \text{V}^{-1}$, and $I_Q = 0.4\ \text{mA}$. Assume that the differential amplifier transistors M_1 and M_2 , and active load transistors M_3 and M_4 are identical.

- (i) Calculate the output resistance, R_O , of the differential amplifier. [5 marks]

- (ii) Determine the differential-mode gain, A_d . [5 marks]

- (iii) Find the output voltage, v_O , if the differential input voltage is $v_d = 20\ \sin(\omega t)\ \text{V}$.

[5 marks]

- (iv) What will happen to the differential amplifier gain if the active load is changed to cascode current source? [5 marks]

Answers for Question 2

Answers for Question 2 (Continued)

QUESTION 3 [20 marks]

Consider a **multistage amplifier** shown in **Figure 2**. *Take note that one PNP two-transistor current source is used as active load for a differential amplifier. Two other NPN two-transistor current sources are used to bias the differential amplifier and a Darlington Pair respectively.*

Given values of $V^+ = 10\text{ V}$, $V^- = -10\text{ V}$, $I_Q = 0.307\text{ mA}$, and $R_2 = 5\text{ k}\Omega$. Assume $\beta = 120$ for all transistors; **Early voltage** (V_A) for Q_7 and Q_{11} is **100 V**; saturation current (I_S) for Q_7 and Q_{11} is higher than other transistors; $I_{C7} = I_{C11}$; and output voltage $v_O = 0$ when inputs $v_1 = v_2 = 0$.

(a) **Show that** $I_O = I_Q / \beta$ when the DC currents in the differential amplifier are **balanced** (i.e. $I_O = I_{B3} + I_{B4}$) by assuming that base currents for transistors in the differential amplifier and I_O are small. Then **determine** the value of I_O in the **Figure 2**.

[5 marks]

(b) In the **Figure 2** also, R_i is the input resistance of the **Darlington Pair** and R_{L7} is the effective resistance connected between collector of Q_7 and signal ground. **Calculate** the small signal **voltage gain of the Darlington Pair** (A_{v2}) by using the following relationship

$$A_{v2} = \frac{v_{O3}}{v_{O2}} = \frac{\beta(1+\beta)(r_{o7} || R_{L7})}{R_i} \quad [15\text{ marks}]$$

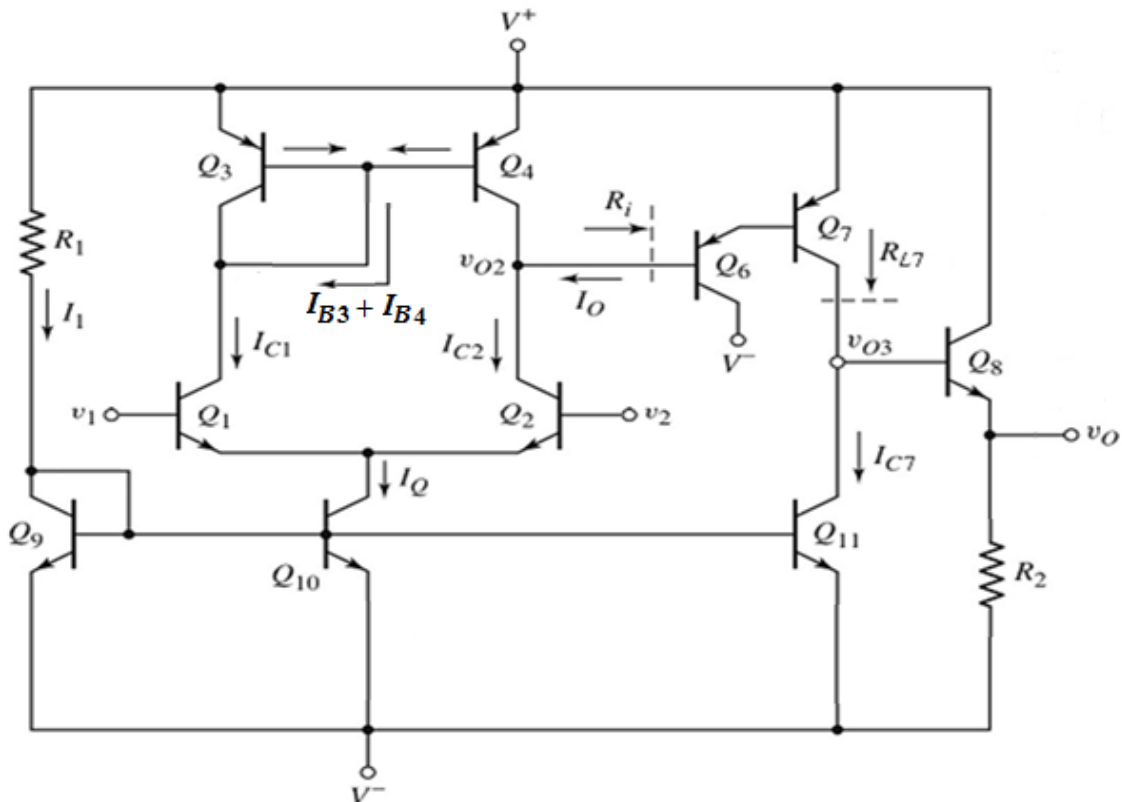


Figure 2

Answers for Question 3

QUESTION 4 [25 marks]

- (a) Briefly **explain** the **classification** of the output stage of **Class-A**, **Class-B** and **Class-AB** by **sketching** the waveform of the relevant transistor current, i_c . [5 marks]
- (b) A **Class-A** output stage circuit using BJTs is shown in **Figure 3**. For the circuit, $V_{CC} = 10\text{ V}$, $V_{bias} = 2\text{ V}$, and $R_L = 1\text{ k}\Omega$. Assume all the transistors are matched with $V_{BE(on)} = 0.65\text{ V}$, $V_{CE(sat)} = 0.3\text{ V}$, and $V_A = \infty$. **Neglect the base currents**.
- (i) **Calculate** the value of I_Q to allow the largest possible output voltage swing. What is the value of resistor R ? [10 marks]
- (ii) **Calculate** the power conversion efficiency (η) of this circuit. [7 marks]
- (iii) **Calculate** the power dissipation in the **emitter follower transistor** Q_1 when output voltage $V_O = 5\text{ V}$. [3 marks]

Answers for Question 4

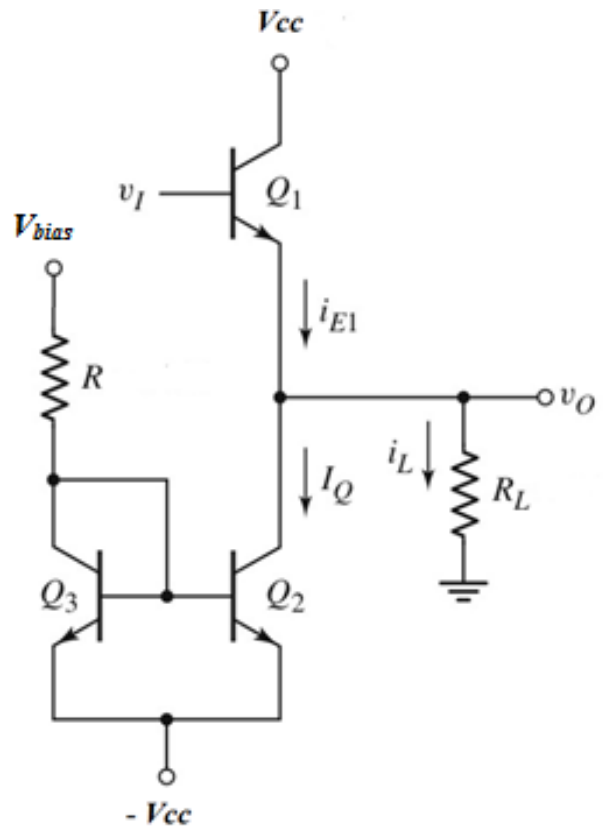


Figure 3

Answers for Question 4 (Continued)

This is extra page for answers. Please indicate question number clearly.