



**COLLEGE OF ENGINEERING
PUTRAJAYA CAMPUS
FINAL EXAMINATION**

SEMESTER 2 2018 / 2019

PROGRAMME : Bachelor of Electrical & Electronics Engineering (Honours)
Bachelor of Electrical Power Engineering (Honours)

SUBJECT CODE : EEEB273/EEEB2014

SUBJECT : ELECTRONIC ANALYSIS AND DESIGN II

DATE : January/February 2019

TIME : 3 hours

INSTRUCTIONS TO CANDIDATES:

1. This paper contains **FIVE** (5) questions in **TEN** (10) pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided. Use **pen** to write your answer.
4. Write answer to different question on a **new page**.

THIS QUESTION PAPER CONSISTS OF TEN (10) PRINTED PAGES INCLUDING THIS COVER PAGE.

Question 1 [20 marks]

- (a) An npn current source is shown in **Figure 1**. The transistor parameters are $\beta = 200$, $V_{BE(on)} = 0.7 \text{ V}$, and $V_A = 250 \text{ V}$. The required **output current** is $20 \mu\text{A}$ and the **reference current** is 0.5 mA . Calculate the percentage change in output current I_O when V_{C2} changes from 0.9 to 5 V . **[8 marks]**

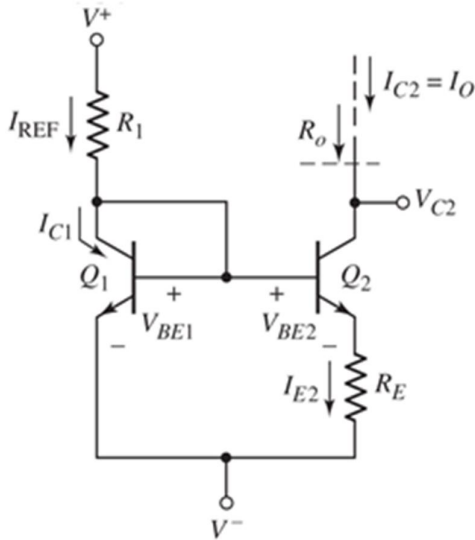


Figure 1

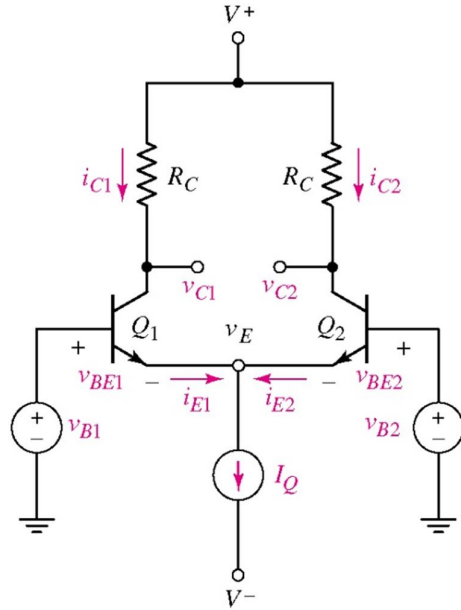


Figure 2

- (b) A **BJT differential amplifier** with passive load is shown in **Figure 2**. The power supplies are $V^+ = 5 \text{ V}$ and $V^- = -5 \text{ V}$. Draw a **pnp** version of the circuit. **[4 marks]**
- (c) For the **pnp** differential amplifier drawn in **part (b)**, the value of $I_Q = 0.5 \text{ mA}$. It is required that when $v_{B1} = v_{B2} = 0 \text{ V}$, the voltage $V_{EC1} = V_{EB(on)} = 0.7 \text{ V}$. Let $\beta = 200$ and $V_A = \infty$ and **neglect the base currents**. Calculate the maximum value of load resistance R_C for this condition and the one-sided differential gain, A_d . **[8 marks]**

Question 2 [20 marks]

Figure 3 shows an N-MOSFET differential amplifier with passive load. The differential amplifier is biased by an N-MOSFET current source constructed by using M_3 , M_4 , and M_5 that produces the bias current $I_Q = 0.20$ mA. Study the **Figure 3** carefully. The overall circuit is powered by $V^+ = 5$ V and $V^- = -5$ V, with $R_D = 40$ k Ω . *Take note that different values of parameters for MOSFET transistors are used in part (a) and part (c) of this Question 2.*

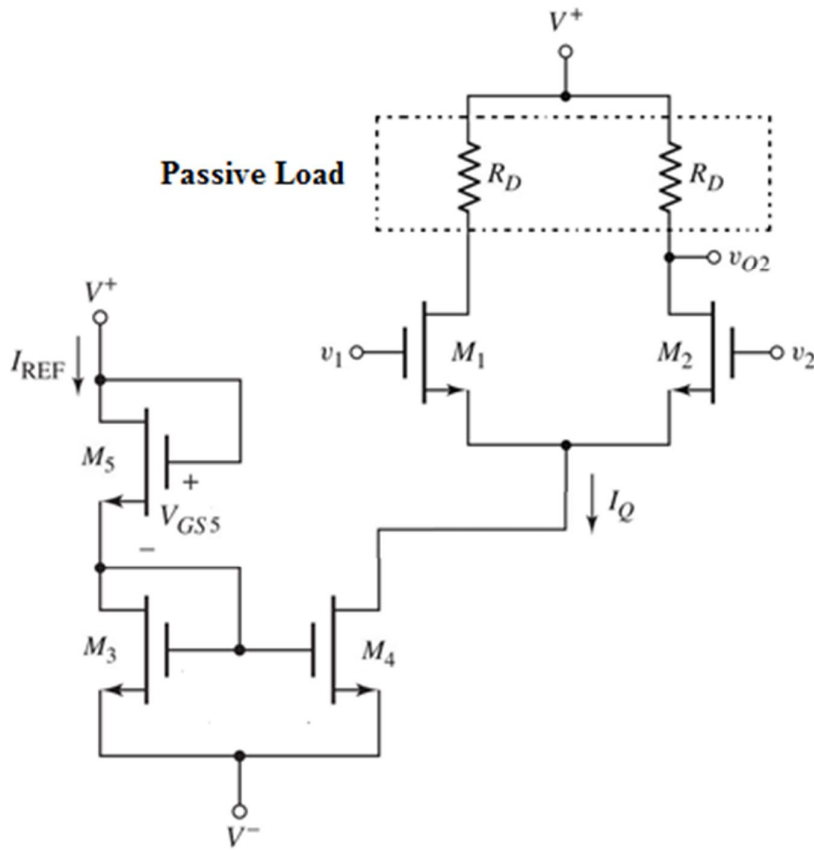


Figure 3

- (a) For the N-MOSFET current source bias circuit in the **Figure 3** the transistors parameters are $V_{TN} = 0.5$ V, $k'_n = 50$ $\mu\text{A}/\text{V}^2$, $(W/L)_3 = (W/L)_4 = 15$, $(W/L)_5 = 3$, and $\lambda_n = 0$. Calculate the value of V_{GS5} . **[5 marks]**

- (b) The differential amplifier with passive load shown in **Figure 3** is to be redesigned to increase its differential-mode voltage gain (A_d) by replacing its passive load (R_D) with an active load constructed using a P-MOSFET Cascode current source. Draw the new

circuit for the differential amplifier incorporating the **active load's full circuit diagram**. Label the new circuit correctly and clearly with appropriate symbols and numbering for the **P-MOSFET** transistors used in the new circuit starts from **M_7** . You are **NOT** required to draw the **N-MOSFET** current source that biased the differential amplifier in the **Figure 3**. **[5 marks]**

- (c) For the differential amplifier circuit in the **Figure 3** and the new circuit with **P-MOSFET** active load in **part (b)**, assume that **N-MOSFET** and **P-MOSFET** devices are available with parameters shown in **Table 1**. For the circuit in **Figure 3**, given **$R_D = 40 \text{ k}\Omega$** . **Determine** how much the **differential-mode voltage gain (A_d)** of the differential amplifier had increased when the active load is used to replace the passive load in the differential amplifier in **Figure 3**. **[10 marks]**

Table 1: MOSFET parameters

N-MOSFET transistor	P-MOSFET transistor
$K_n = 0.4 \text{ mA/V}^2$	$K_p = 0.2 \text{ mA/V}^2$
$V_{TN} = 0.5 \text{ V}$	$V_{TP} = -1 \text{ V}$
$\lambda_n = 0.02 \text{ V}^{-1}$	$\lambda_p = 0.02 \text{ V}^{-1}$

Question 3 [20 marks]

- (a) For circuit in **Figure 4**, given that $I_{C2} = 1.2 \text{ mA}$, $I_{C3} = 5 \text{ mA}$, $R_1 = 50 \text{ k}\Omega$, and $R_2 = 5 \text{ k}\Omega$. Determine the **input resistance (R_i)** and **output resistance (R_o)** of the circuit. Let the transistor parameters $\beta = 60$ and $V_A = \infty$. **[10 marks]**

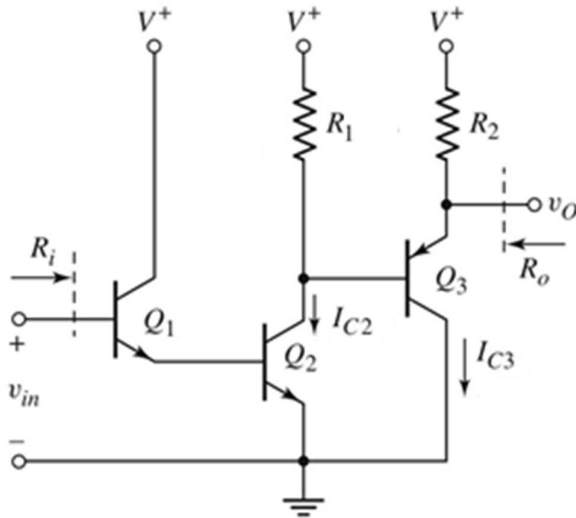


Figure 4

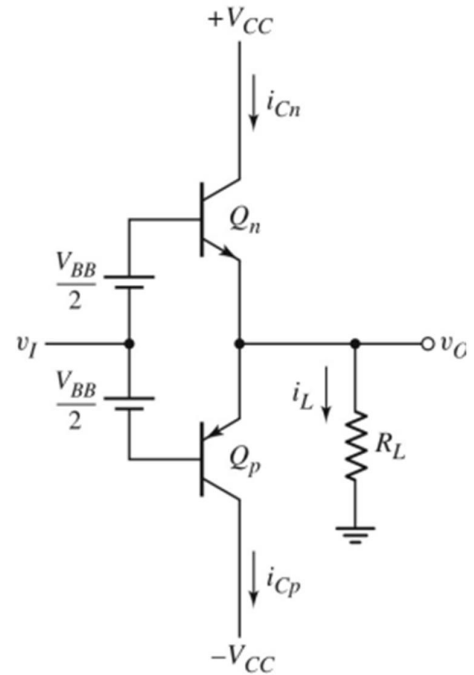


Figure 5

- (b) **Compare and contrast** the Class-A with Class-B, Class-B with Class-AB, and Class-A with Class-AB output stages, **respectively**. **[2 marks]**
- (c) For the **Class-AB** output stage given in **Figure 5**, $V_{CC} = 10 \text{ V}$, $V_{BB} = 1.35 \text{ V}$, $R_L = 100 \Omega$, and for the transistors $I_S = 10^{-13} \text{ A}$. For an output voltage $v_O = 5 \text{ V}$, calculate i_{cn} , i_{cp} and the power dissipated in both Q_n and Q_p transistors. **[8 marks]**

Question 4 [20 marks]

(a) Consider the bias circuit portion of the 741 op-amp in Figure 6. Assume that the transistor parameters of $I_S = 5 \times 10^{-16}$ A. The bias voltages are given as ± 15 V. Neglect the base currents.

(i) Redesign the bias circuit to obtain $I_{REF} = 0.4$ mA and $I_{C10} = 40$ μ A. [4 marks]

(ii) Determine the values of V_{EB12} , V_{BE11} , and V_{BE10} . [6 marks]

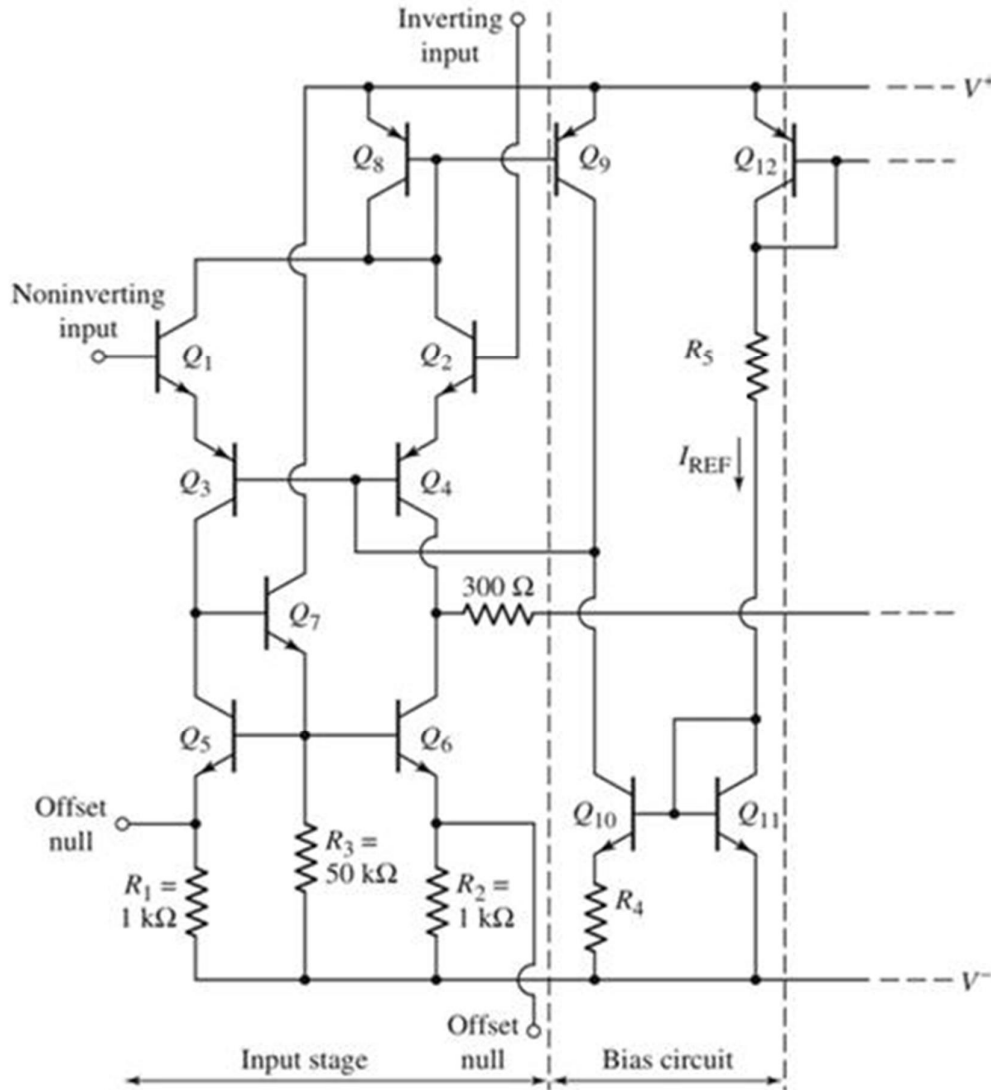


Figure 6

- (b) Consider the MC14573 op-amp in Figure 7. Assume transistor parameters of $V_{TN} = 0.5 \text{ V}$, $V_{TP} = -0.5 \text{ V}$, $K_n = 125 \mu\text{A/V}^2$, $K_p = 100 \mu\text{A/V}^2$, $\lambda_n = 0.01 \text{ V}^{-1}$, and $\lambda_p = 0.02 \text{ V}^{-1}$. Given that bias current for differential amplifier is $I_Q = 0.1 \text{ mA}$.

Determine the overall small signal differential-mode voltage gain for the MC14573 op-amp in the Figure 7. Value for gain of the output stage consists of transistor M_7 and M_8

given by equation $A_{v2} = g_{m7}(r_{o7} \parallel r_{o8})$. [10 marks]

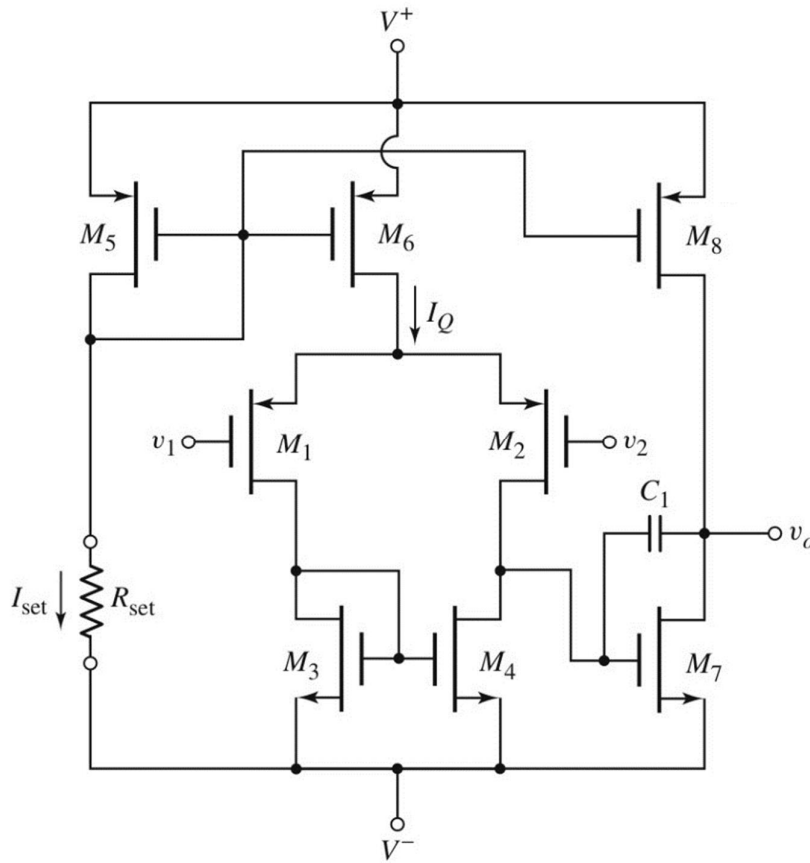


Figure 7

Question 5 [20 marks]

(a) The equivalent circuit of an ideal operational amplifier (op-amp) is given in **Figure 8**.

(i) **Explain** why the op-amp input currents are zero. **[1 mark]**

(ii) **Explain** the ‘virtual short’ concept for the ideal op-amp. **[3 marks]**

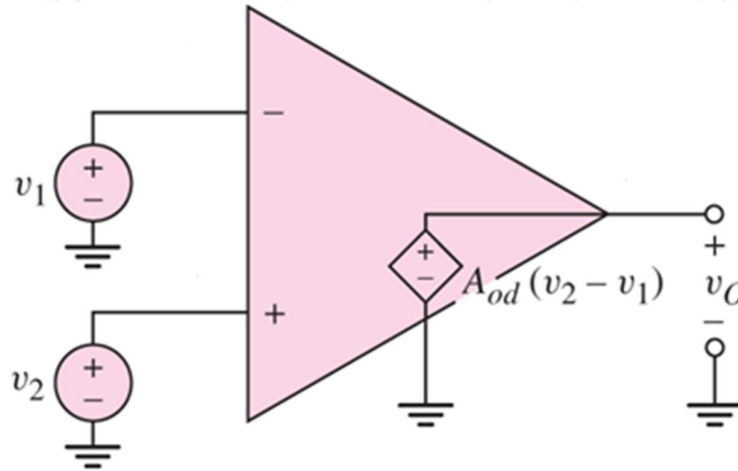


Figure 8

(b) **Figure 9** shows a cascade circuit implemented using ideal op-amps. **Determine** the voltages v_O , v_{O1} and v_{O2} . Given $R = 10 \text{ k}\Omega$, $R_1 = 20 \text{ k}\Omega$, $R_2 = 30 \text{ k}\Omega$, and $v_1 = 1 \text{ mV}$.

[4 marks]

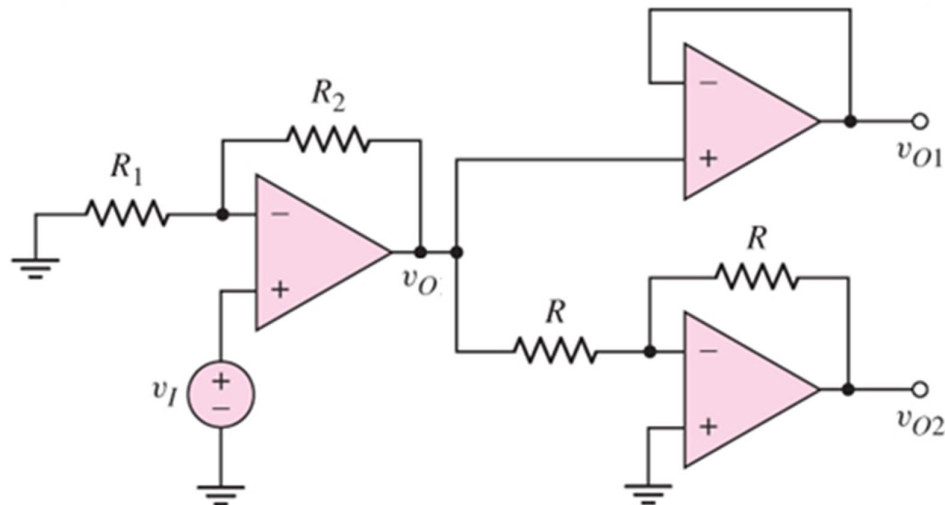


Figure 9

- (c) Refer to the **instrumentation amplifier** in **Figure 10**. With proper analysis using ideal operational amplifier characteristics, it can be found that:

$$v_O = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right) (v_{I2} - v_{I1})$$

Resistor R_1 is such that it consists of a **fixed resistor R_{1f}** in series with a **potentiometer R_{1v}** . **Design** the circuit such that the **differential gain varies between 10 to 500 V/V**. Set the difference amplifier gain to **4**. The maximum current in R_1 is limited to **10 μ A** for a maximum output voltage of **5 V**. What value of potentiometer (R_{1v}) is required?

[12 marks]

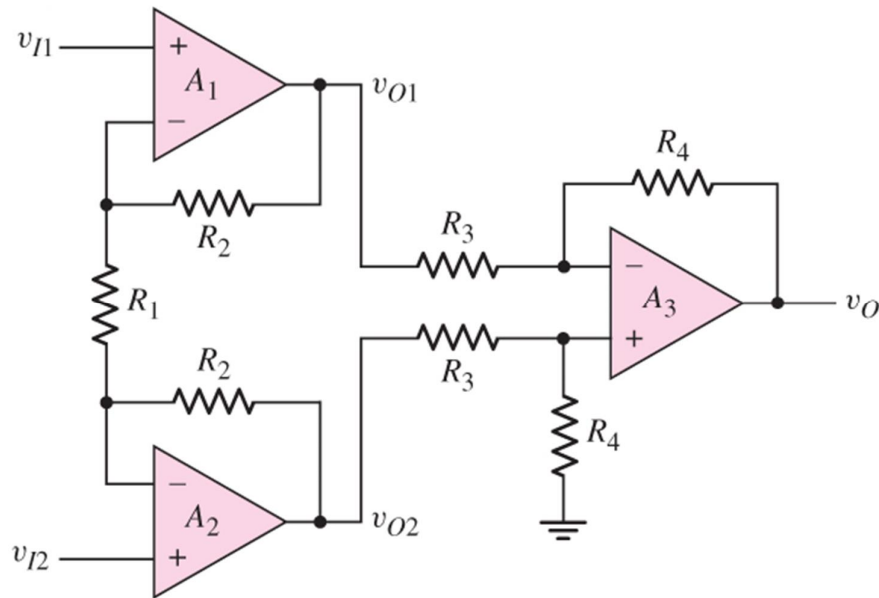


Figure 10

-END OF QUESTION PAPER-

APPENDIX:

A) BASIC FORMULA FOR TRANSISTOR

BJT

$$i_C = I_S e^{v_{BE}/V_T} \quad ; \text{NPN}$$

$$i_C = I_S e^{v_{EB}/V_T} \quad ; \text{PNP}$$

$$i_C = \beta i_B = \frac{\beta}{\beta + 1} i_E$$

$$i_E = i_B + i_C$$

; Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

MOSFET

; N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k'_n}{2} \cdot \frac{W}{L}$$

; P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k'_p}{2} \cdot \frac{W}{L}$$

; Small signal


$$g_m = 2\sqrt{K_n I_{DQ}} \quad ; \text{N – MOSFET}$$

$$g_m = 2\sqrt{K_p I_{DQ}} \quad ; \text{P – MOSFET}$$


$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

B) HYBRID- EQUIVALENT CIRCUITS

BJT

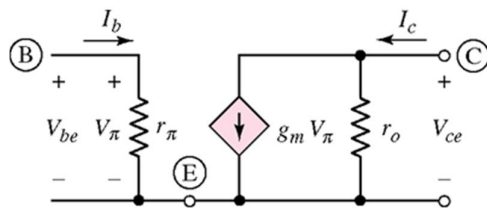

MOSFET

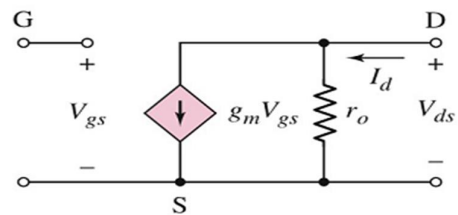

C) QUADRATIC FORMULA

$$Ax^2 + Bx + C = 0 \quad \rightarrow \quad x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$