

Question:

Draw and label clearly a complete circuit diagram for a BJT differential amplifier that is biased with a basic 3-transistor current source at a constant current $I_Q = 1.5 \text{ mA}$. Your drawing must include relevant values for all components in the circuit and power supplies. The BJT diff amp has a differential gain for one-sided output $A_d = 150$. Power supplies are $V^+ = +10 \text{ V}$ and $V^- = -10 \text{ V}$. Assume $\beta = 100$ and $V_{BE(\text{on})} = 0.7 \text{ V}$ for all BJT in the circuit. Hints: You are required to determine the value of R_1 in the basic 3-transistor current source and the value of R_C in the BJT differential amplifier that to be shown in your drawing. **[10 marks]**

Answer:

$$I_{REF} = (V^+ - V_{BE3} - V_{BE5} - V^-) / (R_1) \hat{=} I_Q \quad [0.5 \text{ mark}]$$

$$R_1 = (V^+ - V_{BE3} - V_{BE5} - V^-) / (I_Q) \quad [0.5 \text{ mark}]$$


$$= (10 - 0.7 - 0.7 - (-10)) / (1.5\text{m}) = 12.4 \text{ k} \quad [0.5 \text{ mark}]$$

$$A_d = (g_m R_C) / 2$$

$$R_C = (2 A_d) / g_m \quad [0.5 \text{ mark}]$$

$$g_m = I_Q / (2 V_T) = (1.5\text{m}) / (2 \times 26\text{m}) = 28.846 \text{ mA/V} \quad [0.5 \text{ mark}]$$
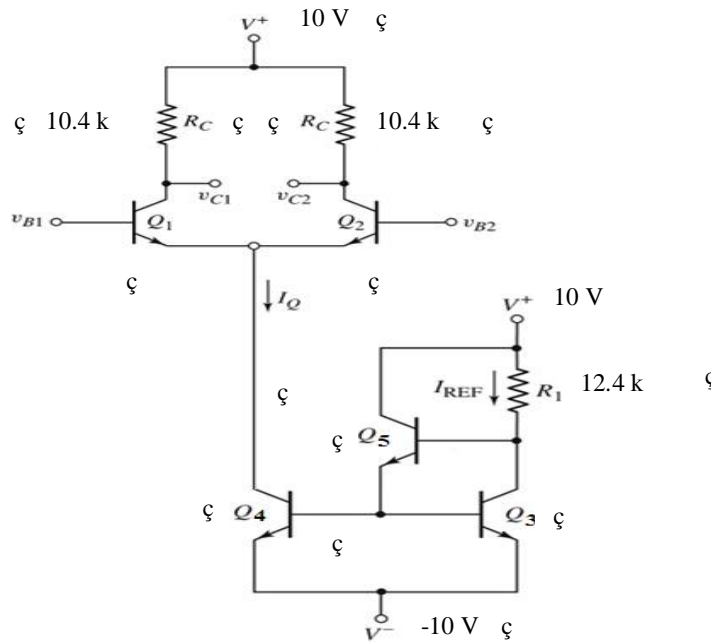
$$R_C = (2 \times 150) / (28.846\text{m}) = 10.4 \text{ k} \quad [0.5 \text{ mark}]$$



ç = ½ mark

EEEB273/EEEB2014 - Quiz 2
 SEMESTER 2, ACADEMIC YEAR 2018/2019
 Date: 29 November 2019

Question:

Draw and label clearly a complete circuit diagram for a BJT differential amplifier that is biased with a **basic 3-transistor** current source at a constant current $I_Q = 1.6 \text{ mA}$. Your drawing **must include relevant values** for all components in the circuit and power supplies. The BJT diff amp has a differential gain for one-sided output $A_d = 150$. Power supplies are $V^+ = +11 \text{ V}$ and $V^- = -11 \text{ V}$. Assume $\beta = 100$ and $V_{BE(\text{on})} = 0.7 \text{ V}$ for all BJT in the circuit. *Hints: You are required to determine the value of R_1 in the basic 3-transistor current source and the value of R_C in the BJT differential amplifier that to be shown in your drawing.* **[10 marks]**

Answer:

$$I_{REF} = (V^+ - V_{BE3} - V_{BE5} - V^-) / (R_1) \hat{=} I_Q \quad [0.5 \text{ mark}]$$

$$R_1 = (V^+ - V_{BE3} - V_{BE5} - V^-) / (I_Q) \quad [0.5 \text{ mark}]$$


$$= (11 - 0.7 - 0.7 - (-11)) / (1.6\text{m}) = 12.875 \text{ k} \quad [0.5 \text{ mark}]$$

$$A_d = (g_m R_C) / 2$$

$$R_C = (2 A_d) / g_m \quad [0.5 \text{ mark}]$$

$$g_m = I_Q / (2 V_T) = (1.6\text{m}) / (2 \times 26\text{m}) = 30.769 \text{ mA/V} \quad [0.5 \text{ mark}]$$
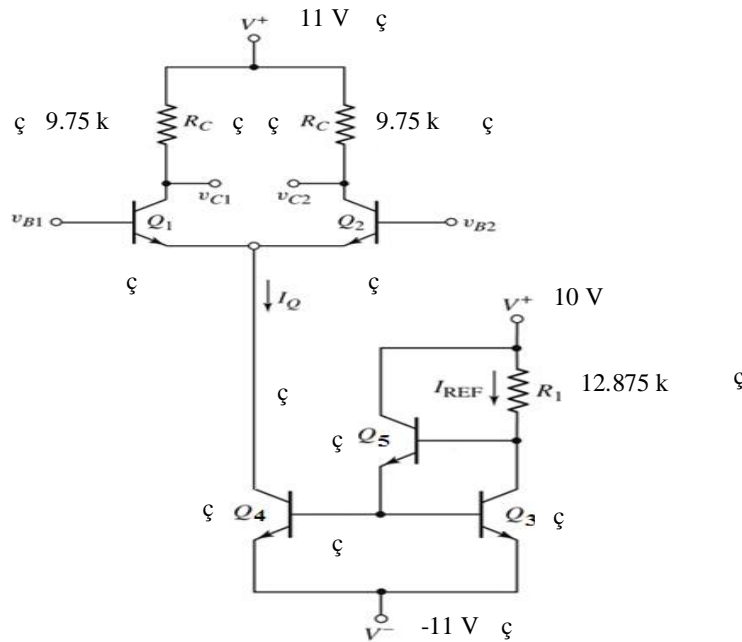
$$R_C = (2 \times 150) / (30.769\text{m}) = 9.75 \text{ k} \quad [0.5 \text{ mark}]$$



ç = ½ mark

EEEB273/EEEB2014 - Quiz 2
 SEMESTER 2, ACADEMIC YEAR 2018/2019
 Date: 29 November 2019 ;

Question:

Draw and label clearly a complete circuit diagram for a BJT differential amplifier that is biased with a **basic 3-transistor** current source at a constant current $I_Q = 1.3 \text{ mA}$. Your drawing **must include relevant values** for all components in the circuit and power supplies. The BJT diff amp has a differential gain for one-sided output $A_d = 160$. Power supplies are $V^+ = +12 \text{ V}$ and $V^- = -12 \text{ V}$. Assume $\beta = 100$ and $V_{BE(\text{on})} = 0.7 \text{ V}$ for all BJT in the circuit. *Hints: You are required to determine the value of R_1 in the basic 3-transistor current source and the value of R_C in the BJT differential amplifier that to be shown in your drawing.* **[10 marks]**

Answer:

$I_{REF} = (V^+ - V_{BE3} - V_{BE5} - V^-) / (R_1) \hat{=} I_Q$ [0.5 mark]

$R_1 = (V^+ - V_{BE3} - V_{BE5} - V^-) / (I_Q)$ [0.5 mark]


$= (12 - 0.7 - 0.7 - (-12)) / (1.3\text{m}) = 17.384 \text{ k}$ [0.5 mark]

$A_d = (g_m R_C) / 2$

$R_C = (2 A_d) / g_m$ [0.5 mark]

$g_m = I_Q / (2 V_T) = (1.3\text{m}) / (2 \times 26\text{m}) = 25 \text{ mA/V}$ [0.5 mark]

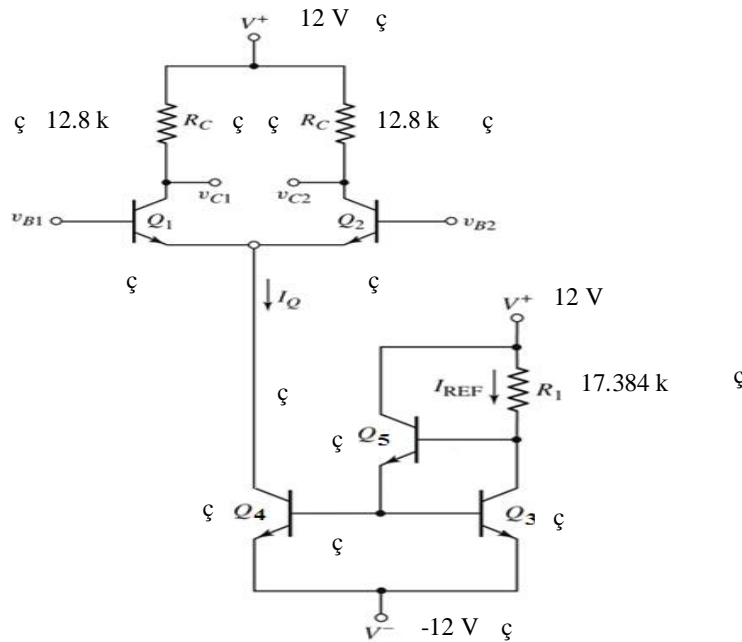$R_C = (2 \times 160) / (25\text{m}) = 12.8 \text{ k}$ [0.5 mark]



ç = ½ mark

Question:

Draw and label clearly a complete circuit diagram for a BJT differential amplifier that is biased with a **basic 3-transistor** current source at a constant current $I_Q = 1.4 \text{ mA}$. Your drawing **must include relevant values** for all components in the circuit and power supplies. The BJT diff amp has a differential gain for one-sided output $A_d = 160$. Power supplies are $V^+ = +13 \text{ V}$ and $V^- = -13 \text{ V}$. Assume $\beta = 100$ and $V_{BE(\text{on})} = 0.7 \text{ V}$ for all BJT in the circuit. *Hints: You are required to determine the value of R_1 in the basic 3-transistor current source and the value of R_C in the BJT differential amplifier that to be shown in your drawing.* **[10 marks]**

Answer:

$I_{REF} = (V^+ - V_{BE3} - V_{BE5} - V^-) / (R_1) \hat{=} I_Q$ [0.5 mark]

$R_1 = (V^+ - V_{BE3} - V_{BE5} - V^-) / (I_Q)$ [0.5 mark]


$= (13 - 0.7 - 0.7 - (-13)) / (1.4\text{m}) = 17.571 \text{ k}$ [0.5 mark]

$A_d = (g_m R_C) / 2$

$R_C = (2 A_d) / g_m$ [0.5 mark]

$g_m = I_Q / (2 V_T) = (1.4\text{m}) / (2 \times 26\text{m}) = 26.923 \text{ mA/V}$ [0.5 mark]

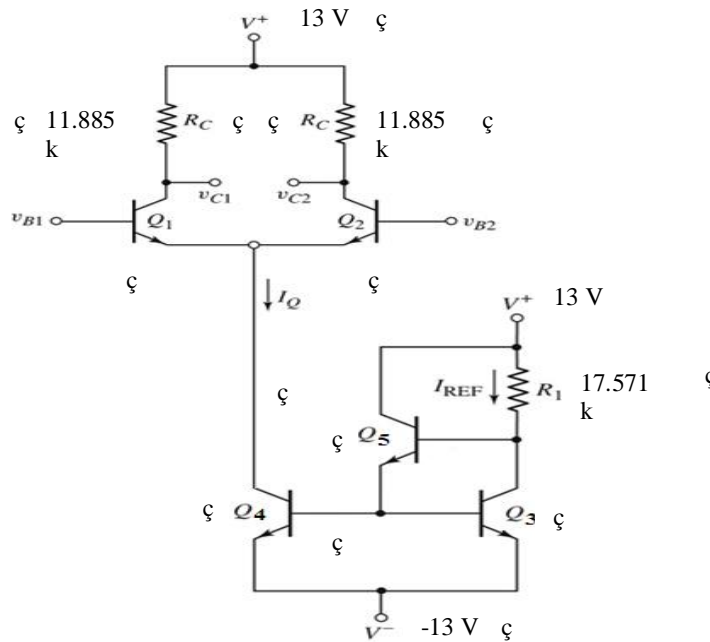$R_C = (2 \times 160) / (26.923\text{m}) = 11.885 \text{ k}$ [0.5 mark]



ç = ½ mark