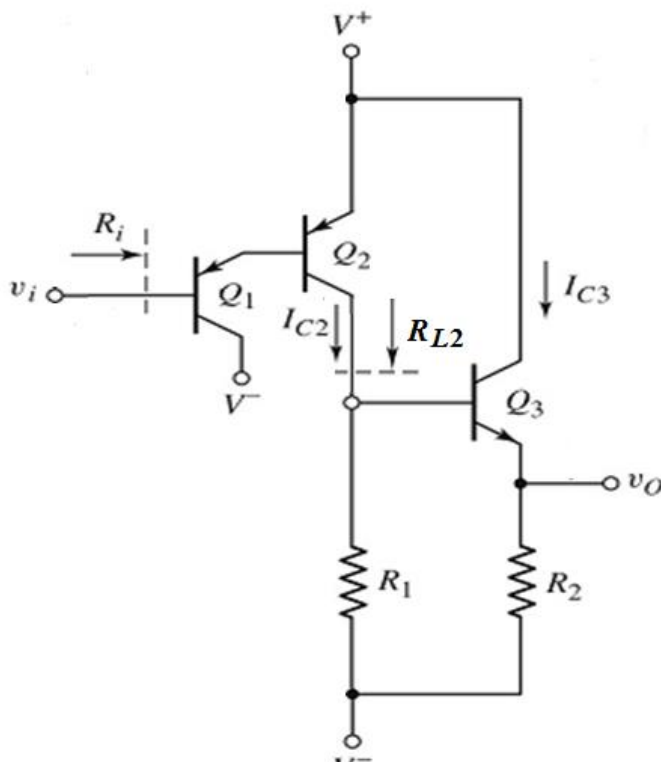


Question:

Study the gain stage and simple output stage circuit shown in Figure 1 carefully. The transistor parameters are: $\beta = 120$ and $V_A = 120$ V. Neglect base currents.

Let $R_1 = 50$ k Ω , $R_2 = 5$ k Ω , $I_{C2} = 0.5$ mA, and $I_{C3} = 1.4$ mA. Determine the input resistance (R_i) of the gain stage and the equivalent load resistance of the gain stage connected to the collector of Q_2 , i.e. R_{L2} shown in the Figure 1. **[10 marks]**

Write your answer using pen, with proper Units for all the parameters.



$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

$$R_i = r_{\pi 1} + (1 + \beta) r_{\pi 2} \quad [2]$$

$$r_{\pi 2} = (\beta V_T) / I_{C2} = (120 \times 0.026) / 0.5\text{m} = 6.24 \text{ k}\Omega \quad [1]$$

$$I_{C1} = (\beta I_{E1}) / (1 + \beta) = (\beta I_{B2}) / (1 + \beta) = (\beta I_{C2} / \beta) / (1 + \beta) = I_{C2} / (1 + \beta) \quad [1]$$

$$r_{\pi 1} = (\beta V_T) / I_{C1} = (\beta V_T) (1 + \beta) / I_{C2} = (120 \times 121 \times 0.026) / 0.5\text{m} = 755.04 \text{ k}\Omega \quad [1]$$

$$R_i = r_{\pi 1} + (1 + \beta) r_{\pi 2} = 755.04\text{k} + (121)(6.24\text{k}) = 1510.8 \text{ k}\Omega \quad [1]$$

$$R_{L2} = R_1 \parallel [r_{\pi 3} + (1 + \beta) R_2] \quad [2]$$

$$r_{\pi 3} = (\beta V_T) / I_{C3} = (120 \times 0.026) / 1.4\text{m} = 2.23 \text{ k}\Omega \quad [1]$$


$$R_{L2} = (50\text{k}) \parallel [2.23\text{k} + (1 + 120)(5\text{k})] = 46.2 \text{ k}\Omega \quad [1]$$

Question:

Study the gain stage and simple output stage circuit shown in Figure 1 carefully. The transistor parameters are: $\beta = 120$ and $V_A = 120$ V. Neglect base currents.

Let $R_1 = 40$ k Ω , $R_2 = 8$ k Ω , $I_{C2} = 0.4$ mA, and $I_{C3} = 1.3$ mA. Determine the input resistance (R_i) of the gain stage and the equivalent load resistance of the gain stage connected to the collector of Q_2 , i.e. R_{L2} shown in the Figure 1. **[10 marks]**

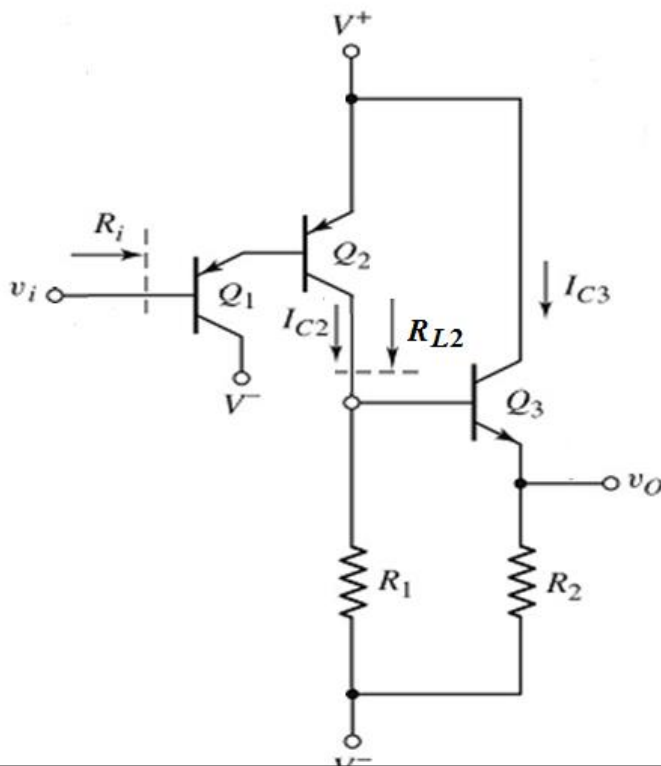Write your answer using pen, with proper Units for all the parameters.



$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

$$R_i = r_{\pi 1} + (1 + \beta) r_{\pi 2} \quad [2]$$

$$r_{\pi 2} = (\beta V_T) / I_{C2} = (120 \times 0.026) / 0.4 \text{ m} = 7.8 \text{ k}\Omega \quad [1]$$

$$I_{C1} = (\beta I_{E1}) / (1 + \beta) = (\beta I_{B2}) / (1 + \beta) = (\beta I_{C2} / \beta) / (1 + \beta) = I_{C2} / (1 + \beta) \quad [1]$$

$$r_{\pi 1} = (\beta V_T) / I_{C1} = (\beta V_T) (1 + \beta) / I_{C2} = (120 \times 121 \times 0.026) / 0.4 \text{ m} = 943.8 \text{ k}\Omega \quad [1]$$

$$R_i = r_{\pi 1} + (1 + \beta) r_{\pi 2} = 943.8 \text{ k} + (121)(7.8 \text{ k}) = 1887.6 \text{ k}\Omega \quad [1]$$

$$R_{L2} = R_1 \parallel [r_{\pi 3} + (1 + \beta) R_2] \quad [2]$$

$$r_{\pi 3} = (\beta V_T) / I_{C3} = (120 \times 0.026) / 1.3 \text{ m} = 2.4 \text{ k}\Omega \quad [1]$$


$$R_{L2} = (40 \text{ k}) \parallel [2.4 \text{ k} + (1 + 120)(8 \text{ k})] = 38.42 \text{ k}\Omega \quad [1]$$

Question:

Study the gain stage and simple output stage circuit shown in **Figure 1** carefully. The transistor parameters are: $\beta = 120$ and $V_A = 120$ V. Neglect base currents.

Let $R_1 = 55$ k Ω , $R_2 = 8$ k Ω , $I_{C2} = 0.3$ mA, and $I_{C3} = 1.2$ mA. Determine the input resistance (R_i) of the gain stage and the equivalent load resistance of the gain stage connected to the collector of Q_2 , i.e. R_{L2} shown in the **Figure 1**. **[10 marks]**

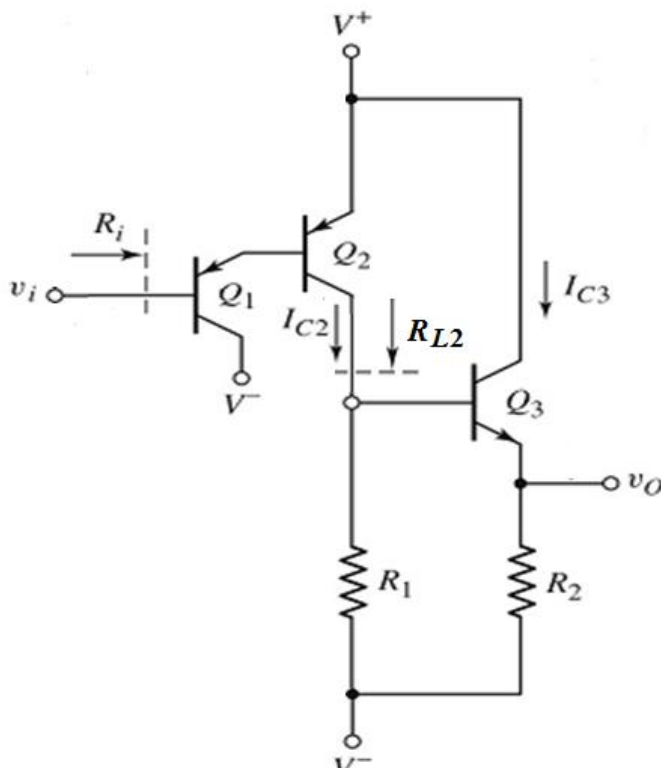Write your answer using pen, with proper Units for all the parameters.



$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

$$R_i = r_{\pi 1} + (1 + \beta) r_{\pi 2} \quad [2]$$

$$r_{\pi 2} = (\beta V_T) / I_{C2} = (120 \times 0.026) / 0.3\text{m} = 10.4 \text{ k}\Omega \quad [1]$$

$$I_{C1} = (\beta I_{E1}) / (1 + \beta) = (\beta I_{B2}) / (1 + \beta) = (\beta I_{C2} / \beta) / (1 + \beta) = I_{C2} / (1 + \beta) \quad [1]$$

$$r_{\pi 1} = (\beta V_T) / I_{C1} = (\beta V_T) (1 + \beta) / I_{C2} = (120 \times 121 \times 0.026) / 0.3\text{m} = 1258.4 \text{ k}\Omega \quad [1]$$

$$R_i = r_{\pi 1} + (1 + \beta) r_{\pi 2} = 1258.4\text{k} + (121)(10.4\text{k}) = 2516.8 \text{ k}\Omega \quad [1]$$

$$R_{L2} = R_1 \parallel [r_{\pi 3} + (1 + \beta) R_2] \quad [2]$$

$$r_{\pi 3} = (\beta V_T) / I_{C3} = (120 \times 0.026) / 1.2\text{m} = 2.6 \text{ k}\Omega \quad [1]$$


$$R_{L2} = (55\text{k}) \parallel [2.6\text{k} + (1 + 120)(8\text{k})] = 52.05 \text{ k}\Omega \quad [1]$$

Question:

Study the gain stage and simple output stage circuit shown in Figure 1 carefully. The transistor parameters are: $\beta = 120$ and $V_A = 120$ V. Neglect base currents.

Let $R_1 = 45$ k Ω , $R_2 = 10$ k Ω , $I_{C2} = 0.6$ mA, and $I_{C3} = 1.1$ mA. Determine the input resistance (R_i) of the gain stage and the equivalent load resistance of the gain stage connected to the collector of Q_2 , i.e. R_{L2} shown in the Figure 1. **[10 marks]**

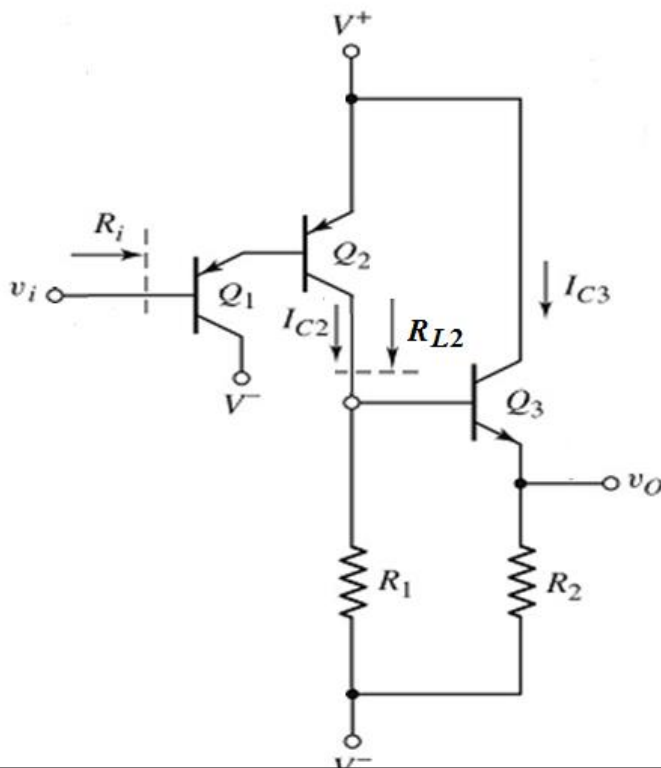Write your answer using pen, with proper Units for all the parameters.



$$i_C = I_S e^{v_{BE}/V_T}; \text{npn}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

$$R_i = r_{\pi 1} + (1 + \beta) r_{\pi 2} \quad [2]$$

$$r_{\pi 2} = (\beta V_T) / I_{C2} = (120 \times 0.026) / 0.6\text{m} = 5.2 \text{ k}\Omega \quad [1]$$

$$I_{C1} = (\beta I_{E1}) / (1 + \beta) = (\beta I_{B2}) / (1 + \beta) = (\beta I_{C2} / \beta) / (1 + \beta) = I_{C2} / (1 + \beta) \quad [1]$$

$$r_{\pi 1} = (\beta V_T) / I_{C1} = (\beta V_T) (1 + \beta) / I_{C2} = (120 \times 121 \times 0.026) / 0.6\text{m} = 629.2 \text{ k}\Omega \quad [1]$$

$$R_i = r_{\pi 1} + (1 + \beta) r_{\pi 2} = 629.2\text{k} + (121)(5.2\text{k}) = 1258.4 \text{ k}\Omega \quad [1]$$

$$R_{L2} = R_1 \parallel [r_{\pi 3} + (1 + \beta) R_2] \quad [2]$$

$$r_{\pi 3} = (\beta V_T) / I_{C3} = (120 \times 0.026) / 1.1\text{m} = 2.84 \text{ k}\Omega \quad [1]$$

$$R_{L2} = (45\text{k}) \parallel [2.84\text{k} + (1 + 120)(10\text{k})] = 43.39 \text{ k}\Omega \quad [1]$$