

EEEB273/EEEB2014 - Quiz 5
SEMESTER 2, ACADEMIC YEAR 2018/2019
Date: 24 January 2019

Question:

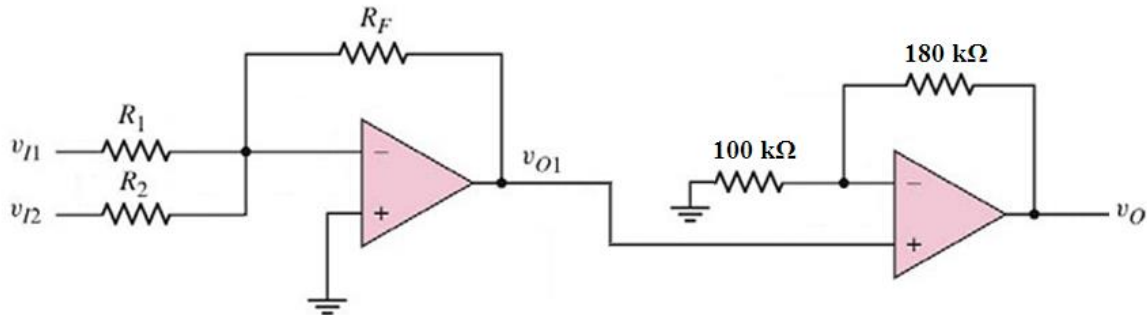


Figure 1

Refer to **Figure 1**. Given that $R_1 = 12 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$, and $R_F = 24 \text{ k}\Omega$. Using ideal properties of the op-amps:

- (a) Determine v_{O1} when $v_{I1} = 15 \text{ mV}$ and $v_{I2} = -20 \text{ mV}$. **[6 marks]**
 (b) Find v_O . **[4 marks]**

Show clearly all calculations in order to get full marks.

Answers:

(a)

Inverting summing amp:

$$v_{O1} = - \left[\left(\frac{R_F}{R_1} \right) (v_{I1}) + \left(\frac{R_F}{R_2} \right) (v_{I2}) \right] \quad [3]$$

$$= - \left[\left(\frac{24\text{k}}{12\text{k}} \right) (15\text{m}) + \left(\frac{24\text{k}}{20\text{k}} \right) (-20\text{m}) \right] = - \left[30\text{m} - 24\text{m} \right] \quad [2]$$

$$= - 6 \text{ mV} \quad [1]$$

(b)

Non-inverting amp:

$$v_O = \left(1 + \frac{180\text{k}}{100\text{k}} \right) (v_{O1}) \quad [2]$$

$$= \left(1 + \frac{180\text{k}}{100\text{k}} \right) (-6\text{m}) = -16.8 \text{ mV} \quad [2]$$

EEEB273/EEEB2014 - Quiz 5
SEMESTER 2, ACADEMIC YEAR 2018/2019
Date: 24 January 2019

Question:

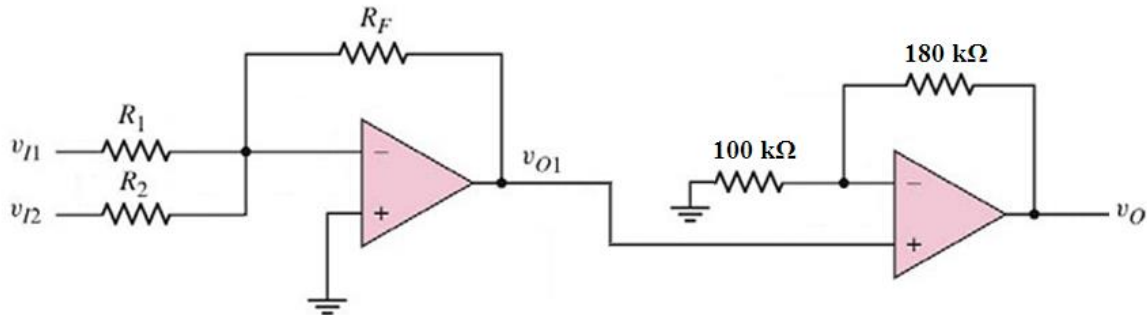


Figure 1

Refer to **Figure 1**. Given that $R_1 = 12 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$, and $R_F = 24 \text{ k}\Omega$. Using ideal properties of the op-amps:

- (a) Determine v_{O1} when $v_{I1} = -15 \text{ mV}$ and $v_{I2} = +20 \text{ mV}$. **[6 marks]**
 (b) Find v_O . **[4 marks]**

Show clearly all calculations in order to get full marks.

Answers:

(a)

Inverting summing amp:

$$v_{O1} = - \left[\left(\frac{R_F}{R_1} \right) (v_{I1}) + \left(\frac{R_F}{R_2} \right) (v_{I2}) \right] \quad [3]$$

$$= - \left[\left(\frac{24\text{k}}{12\text{k}} \right) (-15\text{m}) + \left(\frac{24\text{k}}{20\text{k}} \right) (20\text{m}) \right] = - \left[-30\text{m} + 24\text{m} \right] \quad [2]$$

$$= 6 \text{ mV} \quad [1]$$

(b)

Non-inverting amp:

$$v_O = (1 + \frac{180\text{k}}{100\text{k}}) (v_{O1}) \quad [2]$$

$$= (1 + \frac{180\text{k}}{100\text{k}}) (6\text{m}) = 16.8 \text{ mV} \quad [2]$$

EEEEB273/EEEEB2014 - Quiz 5
SEMESTER 2, ACADEMIC YEAR 2018/2019
Date: 24 January 2019 ;

Question:

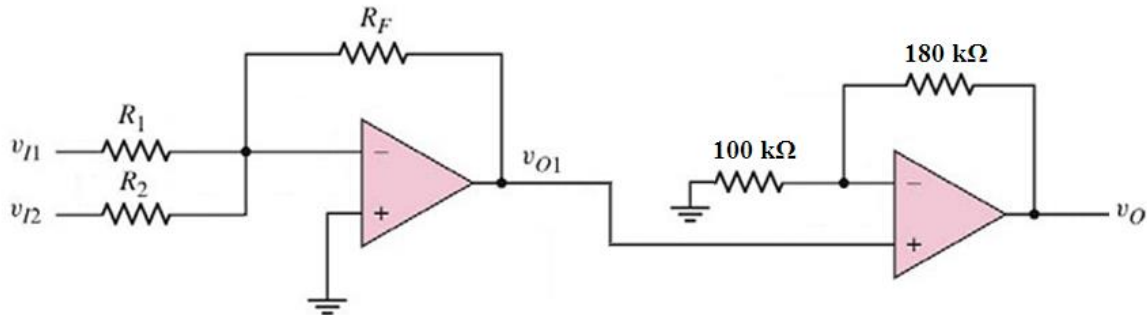


Figure 1

Refer to **Figure 1**. Given that $R_1 = 24 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$, and $R_F = 24 \text{ k}\Omega$. Using ideal properties of the op-amps:

- (a) Determine v_{O1} when $v_{I1} = -15 \text{ mV}$ and $v_{I2} = 20 \text{ mV}$. **[6 marks]**
 (b) Find v_O . **[4 marks]**

Show clearly all calculations in order to get full marks.

Answers:

(a)

Inverting summing amp:

$$v_{O1} = - \left[\left(\frac{R_F}{R_1} \right) (v_{I1}) + \left(\frac{R_F}{R_2} \right) (v_{I2}) \right] \quad [3]$$

$$= - \left[\left(\frac{24\text{k}}{24\text{k}} \right) (-15\text{m}) + \left(\frac{24\text{k}}{20\text{k}} \right) (20\text{m}) \right] = - \left[-15\text{m} + 24\text{m} \right] \quad [2]$$

$$= -9 \text{ mV} \quad [1]$$

(b)

Non-inverting amp:

$$v_O = \left(1 + \frac{180\text{k}}{100\text{k}} \right) (v_{O1}) \quad [2]$$

$$= \left(1 + \frac{180\text{k}}{100\text{k}} \right) (-9\text{m}) = -25.2 \text{ mV} \quad [2]$$

EEEE273/EEEE2014 - Quiz 5
SEMESTER 2, ACADEMIC YEAR 2018/2019
Date: 24 January 2019 :

Question:

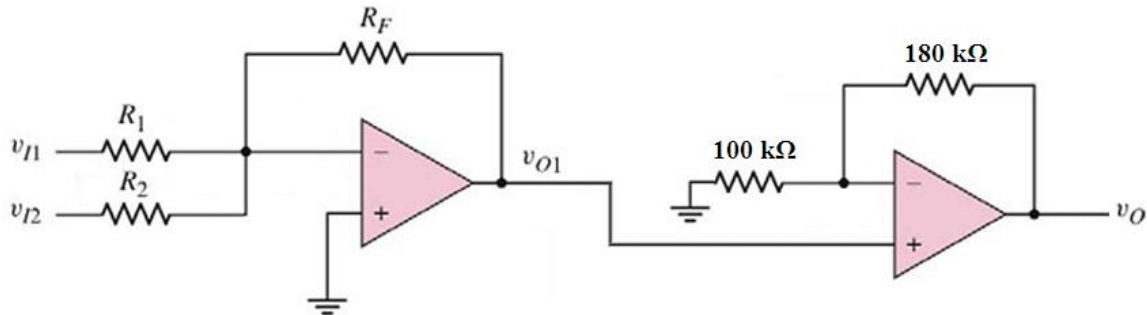


Figure 1

Refer to **Figure 1**. Given that $R_1 = 24 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$, and $R_F = 24 \text{ k}\Omega$. Using ideal properties of the op-amps:

- (a) Determine v_{O1} when $v_{I1} = 15 \text{ mV}$ and $v_{I2} = -20 \text{ mV}$. **[6 marks]**
 (b) Find v_O . **[4 marks]**

Show clearly all calculations in order to get full marks.

Answers:

(a)

Inverting summing amp:

$$v_{O1} = - [(R_F / R_1)(v_{I1}) + (R_F / R_2)(v_{I2})] \quad [3]$$

$$= - [(24\text{k}/24\text{k})(15\text{m}) + (24\text{k}/20\text{k})(-20\text{m})] = - [15\text{m} - 24\text{m}] \quad [2]$$

$$= 9 \text{ mV} \quad [1]$$

(b)

Non-inverting amp:

$$v_O = (1 + 180\text{k}/100\text{k})(v_{O1}) \quad [2]$$

$$= (1 + 180\text{k}/100\text{k})(9\text{m}) = 25.2 \text{ mV} \quad [2]$$