

Name:

Student ID Number:

Section Number: 01/02/03/04 A/B

Lecturer: Dr Jamaludin/ Dr Fazrena Azlee

Table Number:



College of Engineering
Department of Electronics and Communication Engineering

Test 2 – MODEL ANSWERS

SEMESTER 2, ACADEMIC YEAR 2018/2019

Subject Code : **EEEEB273/EEEEB2014**
Course Title : **Electronics Analysis & Design II**
Date : **5 January 2019**
Duration : **2 hours**

Instructions to the candidates:

1. Write your **Name** and **Student ID Number**. Indicate your **Section Number** and **Lecturer's Name**. Write also your **Table Number**.
2. **Write all your answers using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS**. Show clearly all your calculations. Every value **must** be written with its correct Unit.
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.

☺ **GOOD LUCK!** ☺

Question Number	Q1 (a)	Q1 (bc)	Q2 (a)	Q2 (bc)	Q3 (ab)	Q4 (a)	Q4 (b)	Total
Marks								
CO	9	3	9	3	5	9	4	

QUESTION 1 [30 marks]**Answers for Question 1**

(a)

$$I_O = I_{B5} \quad [1]$$

$$I_{B5} = \frac{I_{E5}}{(1+\beta)} = \frac{I_{B3}+I_{B4}}{(1+\beta)} \quad [2]$$

Must indicate currents in Figure 1

$$I_{B5} = \frac{\frac{I_{C3}+I_{C4}}{\beta}}{(1+\beta)} = \frac{\frac{I_{C1}+I_{C2}}{\beta}}{(1+\beta)} \quad [2]$$

$$I_O = I_{B5} = \frac{I_{C1}+I_{C2}}{\beta(1+\beta)} = \frac{I_Q}{\beta(1+\beta)} \quad [2]$$

$$I_O = \frac{I_Q}{\beta(1+\beta)} = \frac{0.24\text{m}}{200 \times 201} = 5.97 \text{ nA} \quad [3]$$

(b)

$$I_{C2} = I_{C4} = \frac{I_Q}{2} = \frac{0.24\text{m}}{2} = 0.12 \text{ mA} \quad [2]$$

$$r_{o2} = \frac{V_{A2}}{I_{C2}} = \frac{100}{0.12\text{m}} = 833.3 \text{ k}\Omega \quad [1]$$

$$r_{o4} = \frac{V_{A4}}{I_{C4}} = \frac{60}{0.12\text{m}} = 500 \text{ k}\Omega \quad [1]$$

$$R_O = r_{o2} || r_{o4} = 833.3\text{k} || 500\text{k} = 312.5 \text{ k}\Omega \quad [1]$$

$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{0.12\text{m}}{0.026} = 4.615 \text{ mA/V} \quad [1]$$

$$A_d = g_{m2}(r_{o2} || r_{o4}) = g_{m2}(R_O) \quad [2]$$

$$A_d = (4.615\text{m})(312.5\text{k}) = 1442 \quad [1]$$

$$A_d(\text{New}) = 80\% \times A_d = 0.8 \times 1442 = 1153.6 \quad [2]$$

$$A_d(\text{New}) = g_{m2}(r_{o2} || r_{o4} || R_L) = g_{m2}(R_O || R_L) \quad [2]$$

$$1153.6 = (4.615\text{m})(312.5\text{k} || R_L) \quad [1]$$

$$R_L = 1286 \text{ k}\Omega \quad [1]$$

(c) Use Cascode **{OR Wilson}** current source as active load. [2]**Draw the circuit** incorporated in diff-amp with New Active load. [1]

Discussion: Increases output resistance of the diff-amp with new active load, help reduces the loading effect when load is connected because output resistance of Cascode configuration is βr_{o4} **{OR Wilson configuration is $\beta r_{o3}/2$ }** which is at least 200X larger for Cascode **{OR 100X larger for Wilson}** than that in the circuit in Figure 1. This larger output resistance of the active load definitely will increase the differential mode voltage gain of the diff-amp. [2]

NOTE: Part (c) can have any other reasonable and logical answer!

QUESTION 2 [30 marks]**Answers for Question 2**

a) State the function of each transistor M1 to M6 in Figure 1. [6 marks]

- M1 & M2: differential-pair , common-**source** amplifiers [2 marks]
- M3 to M6: cascode current mirror [2 marks], active load [2marks]

b) Calculate the voltages VGS1, VSG5 and VD1. [12 marks]

$$ID1 = \frac{1}{2} kn'(W/L)_1(VGS1-V_{TN})^2 \quad [1 \text{ mark}]$$

$$ID1 = \frac{1}{2} IQ = 0.3\text{m}/2 = 0.15\text{m} \quad [1 \text{ mark}]$$

$$0.15\text{m} = \frac{1}{2} (200\mu)(10)(VGS1-0.8)^2 \quad [1 \text{ mark}]$$

$$\rightarrow VGS1 = 1.1873 \text{ V} \quad [1 \text{ mark}]$$

$$ID5 = \frac{1}{2} kp'(W/L)_5(VSG5+V_{TP})^2 \quad [1 \text{ mark}]$$

$$ID5 = \frac{1}{2} IQ = 0.3\text{m}/2 = 0.15\text{m} \quad [1 \text{ mark}]$$

$$0.15\text{m} = \frac{1}{2} (80\mu)(30)(VSG5-0.7)^2 \quad [1 \text{ mark}]$$

$$\rightarrow VSG5 = 1.0536 \text{ V} \quad [1 \text{ mark}]$$

$$VD1 = VD3 = V^+ - VSG5 - VSG3 \quad [1 \text{ mark}]$$

$$VSG3 = VSG5 = 1.0536 \text{ V} \quad [2 \text{ marks}]$$

$$\rightarrow VD1 = 5 - 2(1.0536) = 2.893\text{V} \quad [1 \text{ mark}]$$

c) Calculate the differential gain of the circuit if: (W/L)1-2=10, (W/L)3-6= 30 [12 marks]

$$A_d = gm1 \times [ro2 \parallel Ro4 \text{cascode}] \quad [2 \text{ marks}]$$

$$gm1 = 2\sqrt{K_n1(ID1)} = 2\sqrt{0.5(200\mu)(10)(0.15\text{m})} = 0.7746\text{mA/V} \quad [1 \text{ mark}]$$

$$ro2 = 1/(\lambda_{dn})(ID2) = 1/(0.01 \times 0.15\text{m}) = 666.7\text{k}\Omega \quad [1 \text{ mark}]$$

$$Ro4 \text{cascode} = gm4 ro4 ro6 \quad [2 \text{ marks}]$$

$$gm4 = 2\sqrt{K_p4(ID4)} = 2\sqrt{0.5(80\mu)(30)(0.15\text{m})} = 0.8485\text{mA/V} \quad [1 \text{ mark}]$$

$$ro4 = 1/(\lambda_{dp})(ID4) = 1/(0.015 \times 0.15\text{m}) = 444.4\text{k}\Omega \quad [1 \text{ mark}]$$

$$ro4 = ro6 \quad [1 \text{ mark}]$$

$$Ro4 \text{cascode} = (0.8485\text{m})(444.4\text{k})(444.4\text{k}) = 167.6\text{M}\Omega \quad [1 \text{ mark}]$$

$$A_d = gm1 \times [ro2 \parallel Ro4] = (0.7746\text{m})(666.7 \parallel 167.6\text{M}) = 514.6.8 \text{ V/V} \quad [2 \text{ marks}]$$

QUESTION 3 [20 marks]**Answers for Question 3****(a)**

$$R_{L7} = R_{c11} \parallel R_{b12} \quad [1]$$

$$R_{b12} = r_{\pi12} + (1 + \beta_n) R_{b8}$$

$$R_{b8} = r_{\pi8} + (1 + \beta_n) R_4$$

$$r_{\pi8} = \beta_n V_T / I_{C8} = (120 \times 0.026) / (1.2\text{m}) = 2.6 \text{ k}\Omega \quad [1]$$

$$R_{b8} = r_{\pi8} + (1 + \beta_n) R_4 = 2.6\text{k} + (121)(5\text{k}) = 607.6 \text{ k}\Omega \quad [1]$$

$$\begin{aligned} I_{C12} &= I_{E12} (\beta_n / (1 + \beta_n)) = I_{B8} (\beta_n / (1 + \beta_n)) = (I_{C8} / \beta_n) (\beta_n / (1 + \beta_n)) \\ &= I_{C8} / (1 + \beta_n) = 1.2\text{m} / (121) = 0.009917 \text{ mA} = 9.917 \text{ }\mu\text{A} \end{aligned} \quad [2]$$

$$r_{\pi12} = \beta_n V_T / I_{C12} = (120 \times 0.026) / (9.917\mu) = 314.6 \text{ k}\Omega \quad [1]$$

$$R_{b12} = r_{\pi12} + (1 + \beta_n) R_{b8} = 314.6\text{k} + (121)(607.6\text{k}) = 73.834 \text{ M}\Omega \quad [1]$$

$$R_{c11} = r_{o11} (1 + g_{m11} (r_{\pi11} \parallel R_3)) \quad [1]$$

$$r_{o11} = V_{A11} / I_{C11} = 120 / 0.3\text{m} = 400 \text{ k}\Omega \quad [1]$$

$$g_{m11} = I_{C11} / V_T = 0.3\text{m} / 0.026 = 11.538 \text{ mA/V} \quad [1]$$

$$r_{\pi11} = \beta_n V_T / I_{C11} = (120 \times 0.026) / (0.3\text{m}) = 10.4 \text{ k}\Omega \quad [1]$$

$$R_{c11} = (400\text{k}) (1 + 11.538\text{m} (10.4\text{k} \parallel 0.2\text{k})) = 1.305 \text{ M}\Omega \quad [1]$$

$$R_{L7} = R_{c11} \parallel R_{b12} = 1.305\text{M} \parallel 73.834\text{M} = 1.282 \text{ M}\Omega \quad [1]$$

(b)

$$R_o = R_4 \parallel (r_{\pi8} + Z_1) / (1 + \beta_n) \quad [1]$$

$$Z_1 = (r_{\pi12} + Z) / (1 + \beta_n) \quad [1]$$

$$Z = R_{c11} \parallel R_{c7} \quad [1]$$

$$R_{c7} = r_{o7} = V_{A7} / I_{C7} = 60 / 0.3\text{m} = 200 \text{ k}\Omega \quad [1]$$

$$Z = R_{c11} \parallel R_{c7} = 1.305\text{M} \parallel 200\text{k} = 173.4 \text{ k}\Omega \quad [1]$$

$$Z_1 = (r_{\pi12} + Z) / (1 + \beta_n) = (314.6\text{k} + 173.4\text{k}) / (121) = 4.03 \text{ k}\Omega \quad [1]$$


$$R_o = R_4 \parallel (r_{\pi8} + Z_1) / (1 + \beta_n) = 5\text{k} \parallel ((2.6\text{k} + 4.03\text{k}) / 121) = 54.2 \text{ }\Omega \quad [1]$$

QUESTION 4 [20 marks]

Answers for Question 4

a) Sketch the Class B output stage. Explain the operation. [5 marks]

- Sketch [2 marks]

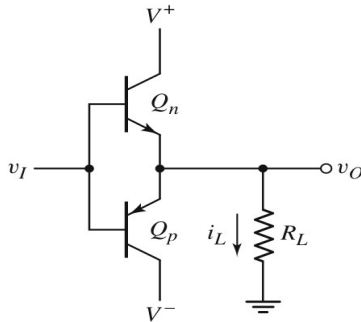

- Operation [3 marks]
 - Assume $V_{BE(on)} = V_{EB(on)} = 0.7V$:
 v_O remains zero as long as $-0.7 \leq v_I \leq 0.7$ [1]
 - Q_n conducts during the positive half of the input cycle:
 v_I positive and $> 0.7V$, Q_n turns on. [1]
 - Q_p conducts during the negative half-cycle:
 v_I negative and $< -0.7V$, Q_p turns on. [1]

b) Class A

i) Calculate the maximum possible output voltage range of the circuit. [2 marks]

$$v_{o(max)} = V^+ - V_{CE1(sat)} = 5 - 0.3 = 4.7V \quad [1 \text{ mark}]$$

$$v_{o(min)} = V^- + V_{CE2(sat)} = -5 + 0.3 = -4.7V \quad [1 \text{ mark}]$$

ii) Determine the minimum required biasing current I_Q . [3 marks]

$$I_Q(\min) = |I_L(\min)| = |v_{o(min)}/R_L| \quad [1 \text{ mark}]$$

$$= |-4.7/100| = 47mA \quad [2 \text{ marks}]$$

iii) For $-4V \leq v_O \leq +4V$. Determine the required range of the input voltage v_I . [10 marks]

$$v_I = v_O + V_{BE1} \quad [2 \text{ marks}]$$

$$I_{C1} = I_{E1}, I_{E1} = I_Q + I_L \quad [1 \text{ mark}]$$

$$I_{C1} = I_Q + v_O/R_L \quad [1 \text{ mark}]$$

For $v_O = v_{O(max)} = +4V$,

$$V_{BE1} = V_T \cdot \ln(I_{C1}/I_S) = V_T \cdot \ln[(I_Q + v_O/R_L) / I_S] \quad [1 \text{ mark}]$$

$$= 26m \cdot \ln[(47m + (4/100))/9 \times 10^{-15}] = 0.7774V \quad [1 \text{ mark}]$$

$$v_I(\max) = v_O(\max) + V_{BE1} = 4 + 0.7774 = 4.7774V \quad [1 \text{ mark}]$$

For $v_O = v_{O(min)} = -4V$,

$$V_{BE1} = V_T \cdot \ln(I_{C1}/I_S) = V_T \cdot \ln[(I_Q + v_O/R_L) / I_S] \quad [1 \text{ mark}]$$

$$= 26m \cdot \ln[(47m + (-4/100))/9 \times 10^{-15}] = 0.7119V \quad [1 \text{ mark}]$$

$$v_I(\max) = v_O(\max) + V_{BE1} = -4 + 0.7119 = -3.2881V \quad [1 \text{ mark}]$$