

Name:

Student ID Number:

Section Number: 01/02/03/04 A/B

Lecturer: Dr Jamaludin/ Dr Fazrena Azlee

Table Number:



College of Engineering
Department of Electronics and Communication Engineering

Test 2

SEMESTER 2, ACADEMIC YEAR 2018/2019

Subject Code : **EEEEB273/EEEEB2014**
Course Title : **Electronics Analysis & Design II**
Date : **5 January 2019**
Duration : **2 hours**

Instructions to the candidates:

1. Write your **Name** and **Student ID Number**. Indicate your **Section Number** and **Lecturer's Name**. Write also your **Table Number**.
2. **Write all your answers using pen. DO NOT USE PENCIL** except for the diagram.
3. **ANSWER ALL QUESTIONS**. Show clearly all your calculations. Every value **must** be written with its correct Unit.
4. **WRITE YOUR ANSWER ON THIS QUESTION PAPER.**

NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.

☺ **GOOD LUCK!** ☺

Question Number	Q1 (a)	Q1 (bc)	Q2 (a)	Q2 (bc)	Q3 (ab)	Q4 (a)	Q4 (b)	Total
Marks								
CO	9	3	9	3	5	9	4	

BASIC FORMULA FOR TRANSISTOR

BJT

$$i_C = I_S e^{v_{BE}/V_T}; \text{nnp}$$

$$i_C = I_S e^{v_{EB}/V_T}; \text{pnp}$$

$$i_C = \alpha i_E = \beta i_B$$

$$i_E = i_B + i_C$$

$$\alpha = \frac{\beta}{\beta + 1}$$

; Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

Quadratic formula :

$$Ax^2 + Bx + C = 0 \quad \rightarrow \quad x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$

MOSFET

; N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{k'_n}{2} \cdot \frac{W}{L}$$

; P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{k'_p}{2} \cdot \frac{W}{L}$$

; Small signal

$$g_m = 2\sqrt{K_n I_{DQ}} \quad ; \text{N - MOSFET}$$

$$g_m = 2\sqrt{K_p I_{DQ}} \quad ; \text{P - MOSFET}$$

$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

This is extra page for answers. Please indicate question number clearly.

QUESTION 1 [30 marks]

The circuit in **Figure 1** has a pair of NPN transistors as input devices and three PNP transistors connected as an active load. The differential amplifier circuit is biased with a constant current source $I_Q = 0.24 \text{ mA}$ that has output resistance $R_{OCS} = 50 \text{ M}\Omega$.

The transistor parameters are: $\beta = 200$, $V_{A1} = V_{A2} = 100 \text{ V}$, $V_{A3} = V_{A4} = 60 \text{ V}$, and $V_{A5} = \infty$.

- (a) The DC currents in the differential amplifier are **balanced**, that is $I_1 = I_2 = I_3 = I_4$. **Show that** $I_O \cong \frac{I_Q}{\beta(1+\beta)}$ and **calculate** the value of I_O . **[10 marks]**
- (b) **Determine** R_L such that the differential-mode voltage gain (A_d) of the differential amplifier with active load in the **Figure 1** is reduced to **80%** of its **open-circuit differential-mode voltage gain value**. **[15 marks]**
- (c) **Design a better active load circuit** that can replace the active load in the **Figure 1**. **Discuss** why your design is better than the circuit in **Figure 1**. **[5 marks]**

Answers for Question 1

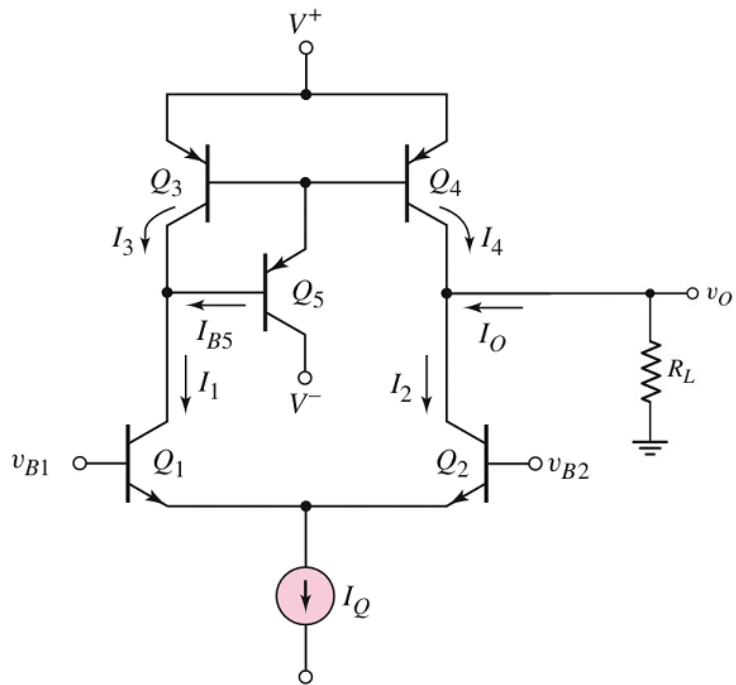


Figure 1

Answers for Question 1 (Continued)

Answers for Question 2 (Continued)

Answers for Question 3

QUESTION 4 [20 marks]

- (a) **Sketch** the **Class-B** output stage circuit employing NPN and PNP BJTs of Q_n and Q_p . **Explain** the operation of the **Class-B** circuit. [5 marks]
- (b) A **Class-A** output stage with BJTs is shown in **Figure 4**. It is given that $V^+ = 5\text{ V}$, $V^- = -5\text{ V}$, and $R_L = 100\ \Omega$. Assume all the transistors are matched with $I_S = 9 \times 10^{-15}\text{ A}$, $V_{CE(\text{sat})} = 0.3\text{ V}$, and $V_A = \infty$. Neglect the base currents.
- (i) **Calculate** the maximum possible output voltage range of the circuit. [2 marks]
- (ii) **Determine** the **minimum** required biasing current I_Q for Class A operation. [3 marks]
- (iii) The output voltage range is now limited to $-4\text{ V} \leq v_O \leq +4\text{ V}$. **Calculate** the required range of the input voltage v_I . [10 marks]

Answers for Question 4

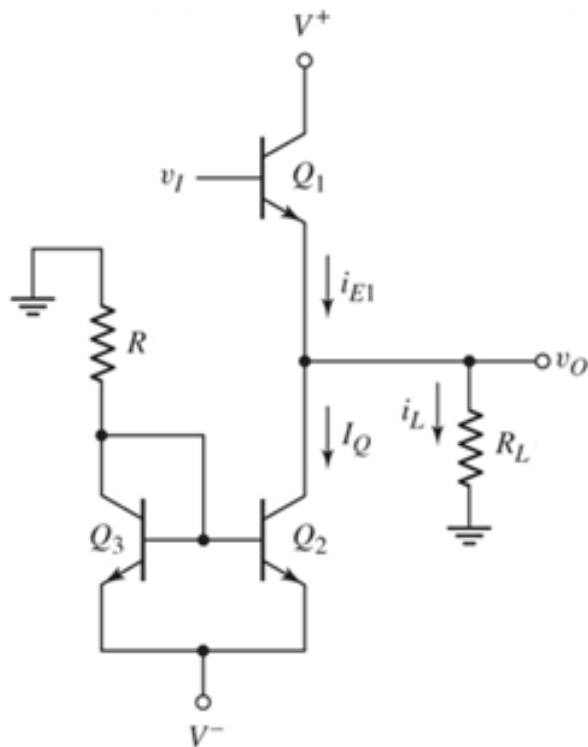


Figure 4

Answers for Question 4 (Continued)

This is extra page for answers. Please indicate question number clearly.