



*The National Energy University*

**COLLEGE OF ENGINEERING  
PUTRAJAYA CAMPUS  
FINAL EXAMINATION – MODEL ANSWER  
SEMESTER 3 2018 / 2019**

PROGRAMME : Bachelor of Electrical & Electronics Engineering (Honours)  
Bachelor of Electrical Power Engineering (Honours)

SUBJECT CODE : EEEB273/EEEB2014

SUBJECT : ELECTRONIC ANALYSIS AND DESIGN II

DATE : April/May 2019

DURATION : 3 hours

---

**INSTRUCTIONS TO CANDIDATES:**

1. This paper contains **FIVE** (5) questions in **EIGHT** (8) pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided. Use **pen** to write your answer.
4. Write answer to different question on a **new page**.

---

***THIS QUESTION PAPER CONSISTS OF EIGHT (8) PRINTED PAGES INCLUDING THIS COVER PAGE.***

**Question 1 [20 marks]**

**Answers:**

**Q1(a) [10 marks]**

$$M_1: \quad I_{REF} = \left(\frac{k'_p}{2}\right) \left(\frac{W}{L}\right)_1 (V_{SG1} + V_{TP})^2 \quad [0.5]$$

$$M_3: \quad I_{REF} = \left(\frac{k'_p}{2}\right) \left(\frac{W}{L}\right)_3 (V_{SG3} + V_{TP})^2 \quad [0.5]$$

$$M_1 = M_3: \quad \left(\frac{60\mu}{2}\right) (25)_1 (V_{SG1} - 0.4)^2 = \left(\frac{60\mu}{2}\right) (5)_3 (V_{SG3} - 0.4)^2 \quad [1]$$

$$\text{KVL:} \quad V_{SG1} + V_{SG3} = V_+ - V_- = 3, \quad V_{SG3} = 3 - V_{SG1} \quad [1]$$

$$\sqrt{\frac{25}{5}} (V_{SG1} - 0.4) = (3 - V_{SG1}) - 0.4 \quad [1]$$

$$3.26 V_{SG1} = 3.499 \rightarrow V_{SG1} = 1.08 \text{ and } V_{SG3} = 1.92 \text{ V} \quad [2]$$

$$I_{REF} = \left(\frac{60m}{2}\right) (25)_1 (1.08 - 0.4)^2 = 0.347 \text{ mA} \quad [2]$$

$$I_Q = \left(\frac{60m}{2}\right) (15)_2 (1.08 - 0.4)^2 = 0.208 \text{ mA} \quad [2]$$

**Q1(b)(i) [6 marks]**

$$R_O = r_{O4} + r_{O6} (1 + g_{m4} r_{O4}) \quad \text{OR} \quad R_O \approx g_{m4} r_{O4} r_{O6} \quad [1]$$

$$I_{DQ} = I_Q / 2 = 0.2\text{m}/2 = 0.1 \text{ mA} \quad [1]$$

$$r_{O4} = r_{O6} = 1/(\lambda_p I_{DQ}) = 1/[(0.02)(0.1\text{m})] = 500 \text{ k}\Omega \quad [1.5]$$

$$g_{m4} = 2\sqrt{(K_p I_{DQ})} = 2\sqrt{[(0.5)(k'_p (W/L)_p)(I_{DQ})]}$$

$$g_{m4} = 2\sqrt{[(0.5)(40\mu)(20)(0.1\text{m})]} = 0.4 \text{ mA/V} \quad [1.5]$$

$$R_O = r_{O4} + r_{O6} (1 + g_{m4} r_{O4}) = 500\text{k} + 500\text{k}(1 + 0.4\text{m} \times 500\text{k}) = 101 \text{ M}\Omega$$

$$\text{OR } R_O \approx g_{m4} r_{O4} r_{O6} = 0.4\text{m} \times 500\text{k} \times 500\text{k} = 100 \text{ M}\Omega \quad [1]$$

**Q1(b)(ii) [4 marks]**

$$A_d = g_{m2} (r_{O2} \parallel R_O) \quad [1]$$

$$r_{O2} = 1/(\lambda_n I_{DQ}) = 1/[(0.02)(0.1\text{m})] = 500 \text{ k}\Omega \quad [1]$$

$$g_{m2} = 2\sqrt{(K_n I_{DQ})} = 2\sqrt{[(0.5)(k'_n (W/L)_2)(I_{DQ})]}$$

$$g_{m2} = 2\sqrt{[(0.5)(80\mu)(10)(0.1\text{m})]} = 0.4 \text{ mA/V} \quad [1.5]$$

$$A_d = (0.4\text{m})(500\text{k} \parallel 101\text{M}) = 199 \text{ V/V} \quad [0.5]$$


**Question 2 [20 marks]**

**Model Answers**

**Q2(a) [10 marks]**

$$\begin{aligned}
 I_{REF} &= I_O [1 + 2/\beta(\beta+1)] && [2] \\
 &= [(0.8\text{m})(1 + 2/(50 \times 51))] && [0.5] \\
 &= (0.8\text{m})(1.00078) = 0.80006 \text{ mA} && [0.5] \\
 R_1 &= (V^+ - V_{EB3} - V_{EB2} - V^-) / I_{REF} && [2] \\
 &= (7.5 - 0.6 - 0.6 - (-7.5)) / (0.80006\text{m}) && [0.5] \\
 &= 17.25 \text{ k}\Omega && [0.5]
 \end{aligned}$$

Each parameter is 0.25 marks

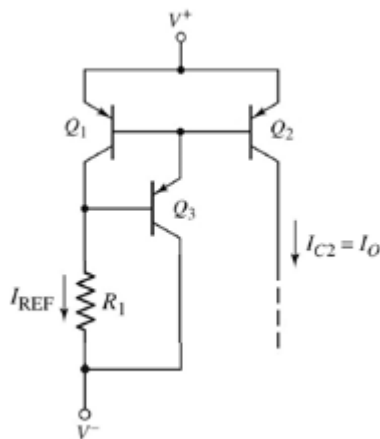

[4]

**Q2(b)(i) [2 marks]**


$$\begin{aligned}
 A_d &= (g_{m2} R_C) / 2 && [0.5] \\
 g_{m2} &= I_{C2} / V_T = I_Q / 2V_T = (2\text{m}) / (2 \times 26\text{m}) = 38.46 \text{ mA/V} && [1] \\
 A_d &= (38.46\text{m} \times 5\text{k}) / 2 = 96.15 \text{ V/V} && [0.5]
 \end{aligned}$$

**Q2(b)(ii) [2 marks]**

$$\begin{aligned}
 R_o \text{ of } 2\text{TCS} &= r_{O2} \text{ in Bias circuit} = V_A / I_Q = 100/2\text{m} = 50 \text{ k}\Omega && [1] \\
 r_{\pi 2} &= \beta V_T / I_{C2} = (100 \times 26\text{m})/1\text{m} = 2.6 \text{ k}\Omega && [0.5]
 \end{aligned}$$

$$A_{cm} = \frac{-g_m R_C}{1 + \frac{2(1 + \beta)R_o}{r_{\pi} + R_B}}, \text{ substitute values, } A_{cm} = -49.5 \times 10^{-3} \quad [0.5]$$

**Q2(b)(iii) [6 marks]**

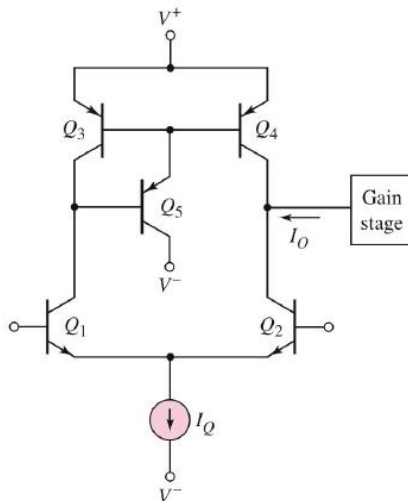

Draw PNP 3TCS active load correctly [2]  
 connected to diff amp [1]

$$A_d = g_{m2} (r_{O2} \parallel R_{OActiveLoad}) \quad [0.5]$$

$$g_{m2} = 38.46 \text{ mA/V}$$

$$r_{O2} = 2 V_A / I_Q = (2 \times 100) / 2\text{m} = 100 \text{ k}\Omega \quad [0.5]$$

$$R_{OActiveLoad} = R_O \text{ of } 3\text{TCS} = r_{O4} \text{ in Active Load} = 2 V_A / I_Q$$

$$\rightarrow R_{OActiveLoad} = (2 \times 100) / 2\text{m} = 100 \text{ k}\Omega \quad [0.5]$$

$$\rightarrow A_d = 38.46\text{m}(100\text{k} \parallel 100\text{k}) = 1923 \text{ V/V} \quad [0.5]$$

$$\text{Thus, } A_d \text{ had increased} = 1923 - 96.15 = 1826.85 \text{ V/V} \quad [1]$$

**Question 3 [20 marks]****Answers:****Q3(a) [10 marks]**

$$\begin{aligned}
 I_Q &= 1.2 \text{ mA} \\
 I_{C2} &= I_Q / 2 = 0.6 \text{ mA} & [0.5] \\
 v_{O2} &= V^+ - I_{C2} R_C = 12 - (0.6\text{m})(10\text{k}) = 6 \text{ V} & [0.5] \\
 I_{R4} &= (v_{O2} - 2 V_{BE(\text{on})}) / (R_4) \\
 &= (6 - 1.4) / (11.5\text{k}) = 0.4 \text{ mA} & [0.5]
 \end{aligned}$$

Using  $I_{C2} = 0.6 \text{ mA}$ ,  $I_{R4} = 0.4 \text{ mA}$ :

$$\begin{aligned}
 A_{d1} &= (g_{m2} / 2)(R_C \parallel R_{i2}) \\
 g_{m2} &= I_{C2} / V_T = (0.6\text{mA}) / (26\text{mV}) = 23.077 \text{ mA/V} & [1] \\
 r_{\pi4} &= \beta V_T / I_{R4} = (200 \times 26\text{m}) / (0.4\text{m}) = 13 \text{ k}\Omega & [1] \\
 r_{\pi3} &\approx \beta r_{\pi4} = 200 \times 13\text{k} = 2600 \text{ k}\Omega & [1] \\
 R_{i2} &= r_{\pi3} + (1 + \beta) r_{\pi4} & [1] \\
 &= 2600\text{k} + (201)(13\text{k}) = 5213 \text{ k}\Omega & [0.5] \\
 A_{d1} &= (23.077\text{m}/2)(10\text{k} \parallel 5213\text{k}) = 115.16 & [0.5] \\
 A_{v2} &\approx (I_{R4} / 2V_T) R_5 = (0.4\text{m} / (2 \times 26\text{m}))(5\text{k}) = 38.46 & [1] \\
 A_3 &\approx 1 \quad (\text{Output stage assume gain} = 1) & [1] \\
 A_d &= A_{d1} A_{v2} A_3 & [1] \\
 &= 115.16 \times 38.46 \times 1 = 4429 \text{ V/V} & [0.5]
 \end{aligned}$$

**Q3(b) [10 marks]**

$$\begin{aligned}
 V_P &= 0.8 V_{CC} = (0.8)(24) = 19.2 \text{ V} & [1] \\
 P_{L(\text{ave})} &= 10 = (1/2)(V_p^2 / R_L) & [1] \\
 R_L &= (1/2)[V_p^2 / P_{L(\text{ave})}] = (19.2)^2 / [(2)(10)] = 18.43 \Omega & [1, 1] \\
 I(\text{ave}) &= V_p / (\pi R_L) = 19.2 / [(\pi)(18.43)] = 0.3316 \text{ A} & [1, 1] \\
 P_{S(\text{ave})} &= 2 V_{CC} I(\text{ave}) = 2(24)(0.3316) = 15.92 \text{ Watts} & [1, 1] \\
 \eta &= P_{L(\text{ave})} / P_{S(\text{ave})} = 10 / 15.92 = 0.628 \text{ or } 62.8\% & [1, 1]
 \end{aligned}$$

**Question 4 [20 marks]**

**Answer to Question 4(a) [10 marks]**

To calculate  $I_{C16}$ , need to determine  $I_{C13B}$

$$I_{C13B} = 0.75 I_{C12} = (0.75)(0.4\text{m}) = 0.3 \text{ mA} \quad [1]$$

$$I_{C17} = I_{C13B} = 0.3 \text{ mA} \quad [1]$$

$$I_{C16} \cong I_{E16} = I_{B17} + I_{R9} = I_{C17} / \beta + ([I_{C17} R_8 + V_{BE17}] / R_9) \quad [1]$$

$$I_{C16} = (0.3\text{m}/200) + ([0.3\text{m} \times 100 + 0.7] / 50\text{k}) \quad [1]$$

$$I_{C16} = 1.5\mu + 14.6\mu = 16.1 \mu\text{A} \quad [1]$$

$$R_{b16} = r_{\pi 16} + (1 + \beta n) [R_9 \parallel R_{b17}] \quad [1]$$

$$R_{b17} = r_{\pi 17} + (1 + \beta n) R_8 \quad [1]$$

$$r_{\pi 17} = \beta n V_T / I_{C17} = (200 \times 26\text{m}) / 0.3\text{m} = 17.333 \text{ k}\Omega \quad [1]$$

$$r_{\pi 16} = \beta n V_T / I_{C16} = (200 \times 26\text{m}) / 16.1\mu = 322.981 \text{ k}\Omega \quad [1]$$

$$\text{So } R_{b17} = 17.333\text{k} + (201)100 = 37.433 \text{ k}\Omega \quad [1]$$

$$50\text{k} \parallel 37.433\text{k} = 21.4 \text{ k}\Omega$$

$$\text{So } R_{b16} = 322.981\text{k} + (201)(50\text{k} \parallel 37.433\text{k}) = 4.624 \text{ M}\Omega \quad [1]$$

**Answer to Question 4(b) [10 marks]**

**Q4b(i) [4 marks]**

$$I_{D5} = K_{p5} (V_{SG5} + V_{TP})^2 = 125\mu(1.5 - 0.5)^2 = 125 \mu\text{A} \quad [2]$$

$$I_Q = I_{D6} = I_{D7} = I_{D8} = I_{D5} = 125 \mu\text{A} \quad [1]$$

$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = I_Q / 2 = 62.5 \mu\text{A} \quad [1]$$

**Q4b(ii) [6 marks]**

$$A_d = g_{m2} (r_{o2} \parallel r_{o4}) \quad [1]$$

$$g_{m2} = 2\sqrt{K_{p2} I_{D2}} = 2\sqrt{(125\mu)(62.5\mu)} = 176.77 \mu\text{A/V} \quad [0.5]$$

$$r_{o2} = \frac{1}{\lambda_p I_{D2}} = \frac{1}{0.02(62.5\mu)} = 0.8 \text{ M}\Omega \quad [0.5]$$

$$r_{o4} = \frac{1}{\lambda_n I_{D4}} = \frac{1}{0.01(62.5\mu)} = 1.6 \text{ M}\Omega \quad [0.5]$$

$$A_d = (176.77\mu)(0.8\text{M} \parallel 1.6\text{M}) = 94.277 \text{ V/V} \quad [0.5]$$

$$A_{v2} = -g_{m7} (r_{o7} \parallel r_{o8})$$

$$g_{m7} = 2\sqrt{K_{n7} I_{D7}} = 2\sqrt{(100\mu)(125\mu)} = 223.6 \mu\text{A/V} \quad [0.5]$$

$$r_{o7} = \frac{1}{\lambda_n I_{D7}} = \frac{1}{0.01(125\mu)} = 0.8 \text{ M}\Omega \quad [0.5]$$

$$r_{o8} = \frac{1}{\lambda_p I_{D8}} = \frac{1}{0.02(125\mu)} = 0.4 \text{ M}\Omega \quad [0.5]$$

$$A_{v2} = -(223.6\mu)(0.8\text{M} \parallel 0.4\text{M}) = -59.63 \text{ V/V} \quad [0.5]$$

$$A_v = A_d A_{v2} = (94.277)(-59.63) = -5621 \text{ V/V} \quad [1]$$

**Question 5 [20 marks]**

Answers:

**Q5(a) [2 marks]**


**Select 2 of the following:**

- $A_{od}$ : Internal differential gain (open loop gain) is considered to be  $\infty$ .
- $(v_2 - v_1)$ : Differential input voltage is assumed to be 0. If  $A_{od} \rightarrow \infty$  and  $v_O$  is finite, then  $v_2 \approx v_1$ .
- $R_i$ : Effective input resistance is assumed to be  $\infty$ , so input currents  $i_1$  and  $i_2$  are essentially 0.
- $R_o$ : Effective output resistance is assumed to be 0, so output voltage is independent of any load connected to the output.
- Bandwidth  $\rightarrow \infty$ .
- $CMRR$ : Common mode rejection ratio =  $\infty$ .

⇒ Each answer above give [1] mark, 2 marks total

**Q5(b) [10 marks]**

**Using superposition theorem**

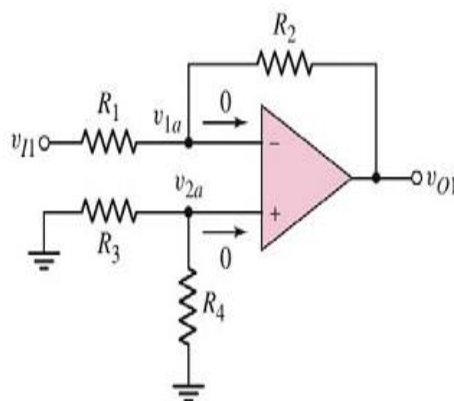


(b)

Let  $v_{I2} = 0$ ,

[1]

$$\rightarrow v_{O1} = -\frac{R_2}{R_1}(v_{I1})$$

[2]

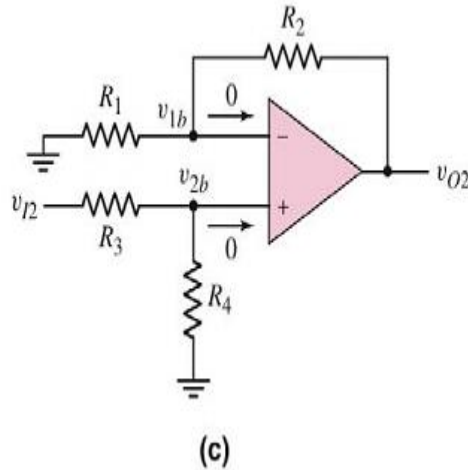

$$v_{2b} = \left( \frac{R_4}{R_3 + R_4} \right) v_{I2} \quad \boxed{1}$$

$$v_{O2} = \left( 1 + \frac{R_2}{R_1} \right) v_{1b} \quad \boxed{1}$$

$$\rightarrow v_{O2} = \left( 1 + \frac{R_2}{R_1} \right) v_{2b} \quad \boxed{1}$$

$$v_{O2} = \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{R_4}{R_3 + R_4} \right) v_{I2}$$

$$v_{O2} = \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{R_4 / R_3}{1 + R_4 / R_3} \right) v_{I2} \quad \boxed{1}$$

Let  $v_{I1} = 0$ ,

$$\boxed{1}$$

$$v_O = v_{O1} + v_{O2} \quad \boxed{1}$$

→

$$v_O = \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{R_4 / R_3}{1 + R_4 / R_3} \right) v_{I2} - \left( \frac{R_2}{R_1} \right) v_{I1} \quad \boxed{1}$$

**Q5(c) [8 marks]**

$$R_2 / R_1 = 120k / 12k = 10 \text{ and } R_4 / R_3 = 440k / 40k = 11 \quad \boxed{1}$$

$$v_O = (1+10)[(11)/(1+11)] v_{I2} - 10 v_{I1}$$

$$\rightarrow v_O = 10.083 v_{I2} - 10 v_{I1} \quad \boxed{1}$$

From  $v_d = v_{I2} - v_{I1}$  and  $v_{cm} = (v_{I2} + v_{I1})/2$

$$\rightarrow v_{I1} = v_{cm} - v_d / 2 \text{ and } v_{I2} = v_{cm} + v_d / 2 \quad \boxed{1}$$

Thus,  $v_O = 10.083 (v_{cm} + v_d / 2) - 10 (v_{cm} - v_d / 2)$

$$\rightarrow v_O = 10.042 v_d + 0.083 v_{cm} \quad \boxed{1}$$

**In general form**

$$v_O = A_d v_d + A_{cm} v_{cm} \quad \boxed{1}$$

Then  $A_d = 10.042$  and  $A_{cm} = 0.083$   $\boxed{1}$

Thus,

$$CMRR(\text{dB}) = 20 \log_{10}(A_d / A_{cm}) \quad \boxed{1}$$

$$CMRR(\text{dB}) = 20 \log_{10}(10.042 / 0.083) = 41.6 \text{ dB} \quad \boxed{1}$$