

**COLLEGE OF ENGINEERING  
PUTRAJAYA CAMPUS  
FINAL EXAMINATION**

**SEMESTER 3 2018 / 2019**

PROGRAMME : **Bachelor of Electrical & Electronics Engineering (Honours)  
Bachelor of Electrical Power Engineering (Honours)**

SUBJECT CODE : **EEEB273**

SUBJECT : **ELECTRONIC ANALYSIS AND DESIGN II**

DATE : **April/May 2019**

DURATION : **3 hours**

---

**INSTRUCTIONS TO CANDIDATES:**

1. This paper contains **FIVE** (5) questions in **EIGHT** (8) pages.
2. Answer **ALL** questions.
3. Write **all** answers in the answer booklet provided. Use **pen** to write your answer.
4. Write answer to different question on a **new page**.

---


***THIS QUESTION PAPER CONSISTS OF EIGHT (8) PRINTED PAGES INCLUDING  
THIS COVER PAGE.***

**Question 1 [20 marks]**


- (a) **Figure 1** shows a two-transistor MOSFET current mirror. The transistor parameters are assumed to be  $V_{TP} = -0.4 \text{ V}$ ,  $k'_p = 60 \mu\text{A}/\text{V}^2$ , and  $\lambda = 0$ . The transistor width-to-length ratios are  $(W/L)_1 = 25$ ,  $(W/L)_2 = 15$ , and  $(W/L)_3 = 5$ .

Calculate  $I_O$ ,  $I_{REF}$ ,  $V_{SG1}$ , and  $V_{SG3}$ .

**[10 marks]**

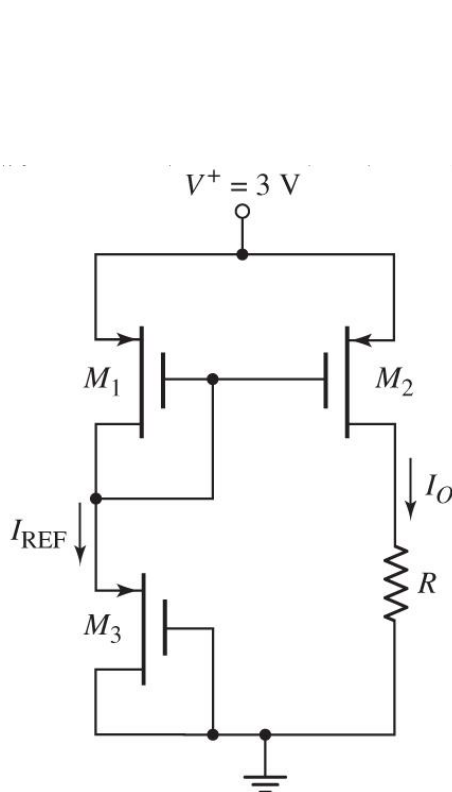

**Figure 1**

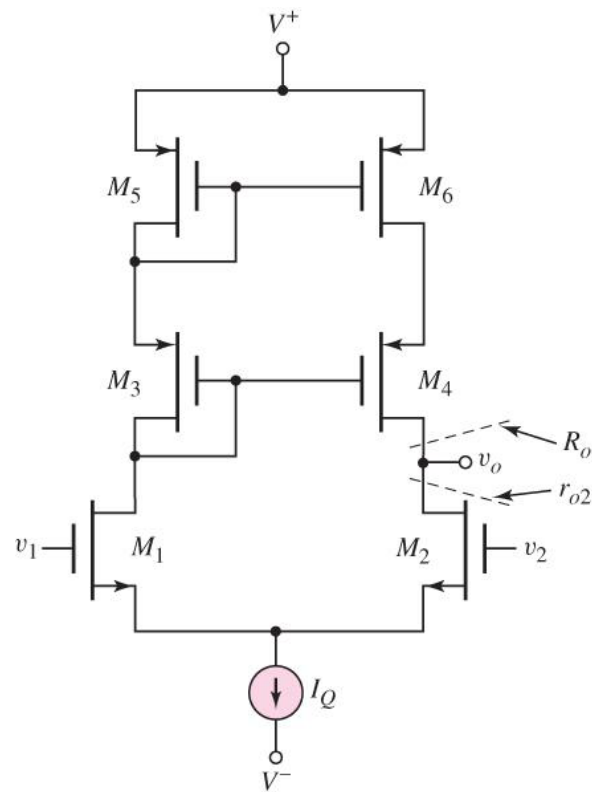


**Figure 2**

- (b) **Figure 2** shows a MOSFET diff-amp with a Cascode active load. Assume that NMOS devices are available with the following parameters:  $V_{TN} = 0.5 \text{ V}$ ,  $k'_n = 80 \mu\text{A}/\text{V}^2$ ,  $\lambda_n = 0.02 \text{ V}^{-1}$ , and  $(W/L)_1 = (W/L)_2 = 10$ . Assume that PMOS devices are available with the following parameters:  $V_{TP} = -1.0 \text{ V}$ ,  $k'_p = 40 \mu\text{A}/\text{V}^2$ ,  $\lambda_p = 0.02 \text{ V}^{-1}$ , and  $(W/L)_p = 20$ . The circuit parameters are  $V^+ = 5 \text{ V}$  and  $V^- = -5 \text{ V}$ . The bias current is  $I_Q = 0.2 \text{ mA}$ .

- (i) **Determine** the output resistance,  $R_O$ , of the **Cascode** active load. **[6 marks]**
- (ii) **Find** the differential-mode voltage gain,  $A_d$ . **[4 marks]**

**Question 2 [20 marks]**

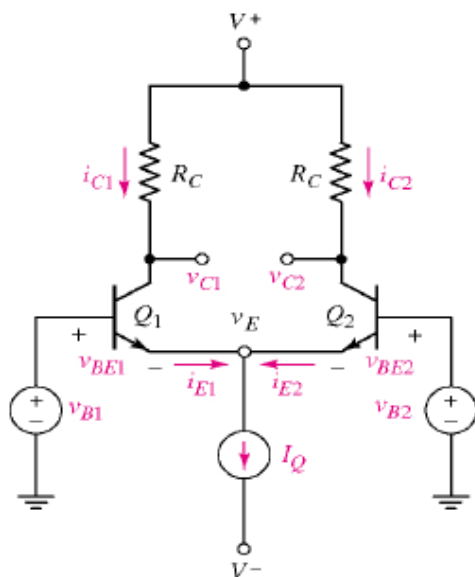- (a) **Design** a three-transistor BJT current source using **PNP** transistors so that **its output current ( $I_O$ ) is 0.8 mA**. All transistors are matched. The transistor parameters are  $\beta = 50$ ,  $V_{EB(on)} = 0.6 \text{ V}$ , and  $V_A = \infty$ . The circuit parameters are  $V^+ = 7.5 \text{ V}$  and  $V^- = -7.5 \text{ V}$ . **Draw the circuit diagram of your design. Show clearly all calculations and values in the circuit diagram** as marks are given according to this. **[10 marks]**
- (b) A **basic differential pair** is shown in **Figure 3**. It is given that  $V^+ = 15 \text{ V}$ ,  $V^- = -15 \text{ V}$ , resistor  $R_C = 5 \text{ k}\Omega$ ,  $I_Q = 2 \text{ mA}$ , and transistor parameters are  $\beta = 100$ , voltages  $V_A = 100 \text{ V}$ ,  $V_{BE(on)} = 0.7 \text{ V}$ , and  $V_{CE(sat)} = 0.3 \text{ V}$ .



$$A_{cm} = \frac{-g_m R_C}{1 + \frac{2(1+\beta)R_Q}{r_\pi + R_B}} \quad (2.1)$$

**Figure 3**

- (i) **Calculate the one-sided small-signal differential voltage gain ( $A_d$ ) of the differential amplifier.** **[2 marks]**
- (ii) The constant current source of **Figure 3** that is providing the current  $I_Q$  is implemented using the **basic two transistor current source**. **Find the value of  $A_{cm}$ , the common-mode voltage gain of the differential-amplifier, using Equation (2.1) given above near the Figure 3. Assume  $R_B = 0$ .** **[2 marks]**
- (iii) The differential amplifier shown in **Figure 3** has a **PNP three-transistor current mirror** connected as an **active load**. **Redraw Figure 3 with the new active load. Assume same values of  $\beta$  and  $V_A$  for PNP. Determine the differential mode gain ( $A_d$ ) and how much the  $A_d$  had changed using the new active load.** **[6 marks]**

**Question 3 [20 marks]**

(a) A simple bipolar op-amp is shown in **Figure 4**. Study the **Figure 4** carefully.

**Neglect base currents.** Assume parameters for all transistors are  $V_{BE(on)} = 0.7 \text{ V}$ ,  $\beta = 200$ , and  $V_A = \infty$ . **Bias current** for the differential amplifier can be calculated to be  $I_Q = 1.2 \text{ mA}$ .

With small-signal analysis, values of gain  $A_{d1}$  for the differential amplifier,  $r_{\pi3}$ , and gain  $A_{v2}$  for the gain stage can be found using the following **Equations (3.1) to (3.3)**.


$$A_{d1} = \frac{v_{O2}}{v_d} = \frac{g_{m2}}{2} (R_C || R_{i2}) \quad (3.1)$$

$$r_{\pi3} \cong \beta r_{\pi4} \quad (3.2)$$

$$A_{v2} \cong \frac{I_{R4}}{2V_T} (R_5) \quad (3.3)$$

Calculate the **total overall small-signal voltage gain ( $A_d$ )** for the bipolar op-amp.

[10 marks]

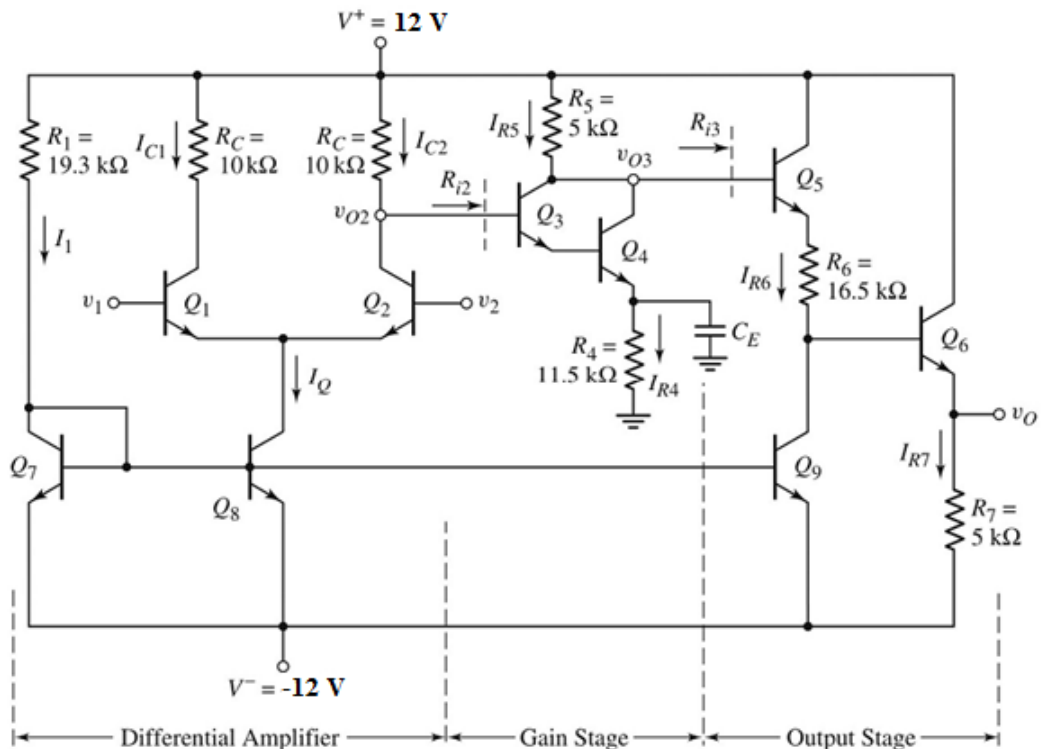


**Figure 4**

(b) An **idealized Class-B output stage** is to deliver **10 Watts of average power** to a load for a symmetrical input sine wave. The maximum output voltage ( $V_p$ ) required should be **80%** of the power supply voltage  $V_{CC}$ . Given that the power supply voltage  $V_{CC}$  is **24 V** and the average current in the circuit is  $I(ave) = V_p / (\pi R_L)$ , where  $R_L$  is the load. Calculate the value of the output stage's **power conversion efficiency ( $\eta$ )**.

[10 marks]

**Question 4 [20 marks]**

- (a) The 741 op-amp is shown in Figure 5. Assume that  $V_{BE(on)} = V_{EB(on)} = 0.7 \text{ V}$ ,  $\beta_n = 200$ ,  $\beta_p = 60$ ,  $V_{AN} = 200 \text{ V}$ , and  $V_{AP} = 100 \text{ V}$ . The area of transistor  $Q_{13B}$  is 75% of transistor  $Q_{12}$ . It is given that  $I_{REF} = I_{C12} = 0.4 \text{ mA}$ . Calculate the small signal input resistance of the Gain stage (i.e. equivalent resistance looking into the base of  $Q_{16}$ ). [10 marks]

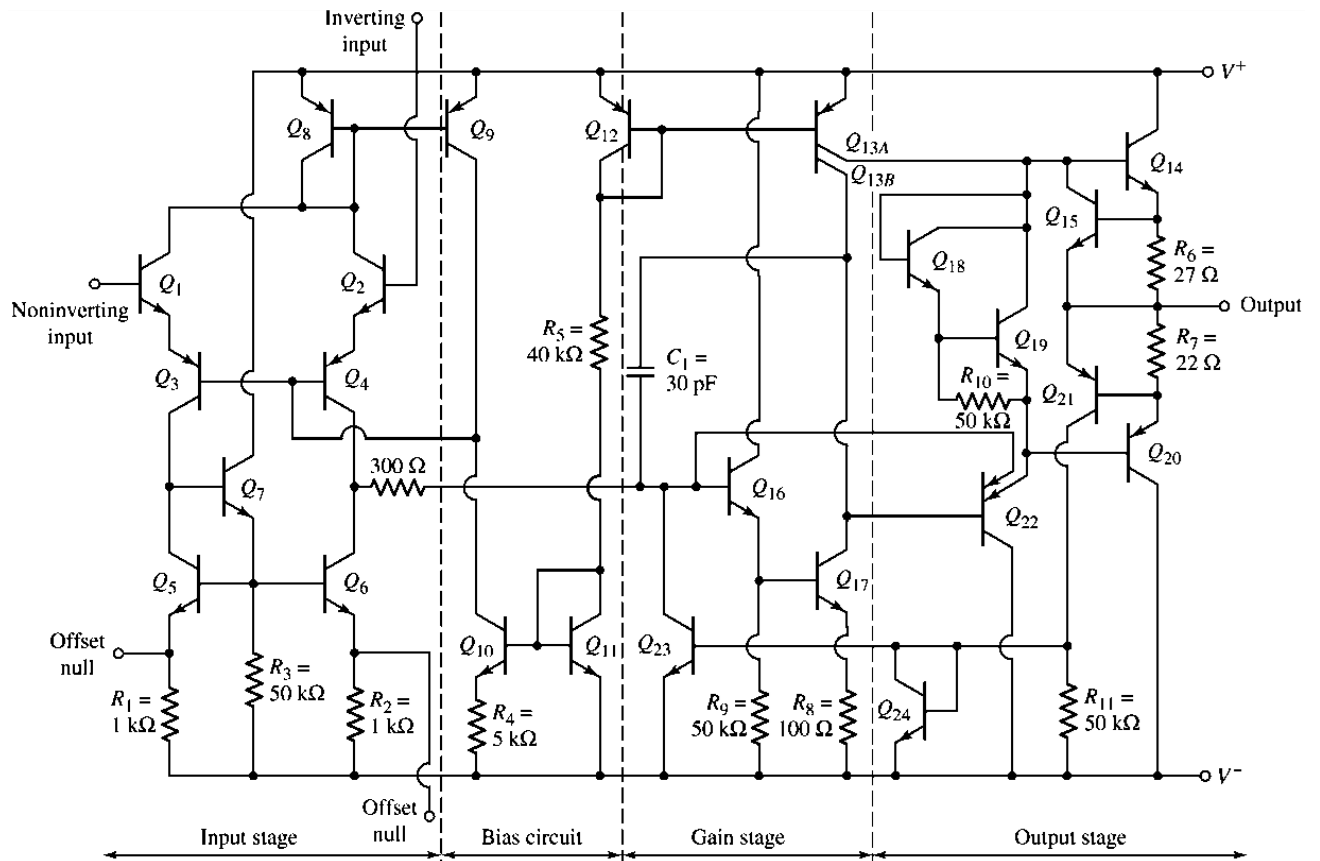


**Figure 5**

**Question 4 (Continue)**

(b) Consider the **MC14573** op-amp in **Figure 6**. Assume transistor parameters for **N-MOSFET** are  $V_{TN} = 0.5 \text{ V}$ ,  $K_n = 100 \mu\text{A/V}^2$  and  $\lambda_n = 0.01 \text{ V}^{-1}$ ; and transistor parameters for **P-MOSFET** are  $V_{TP} = -0.5 \text{ V}$ ,  $K_p = 125 \mu\text{A/V}^2$ , and  $\lambda_p = 0.02 \text{ V}^{-1}$ .

**Given** that  $V_{SG5} = 1.5 \text{ V}$ :


- (i) **Find the quiescent bias currents** for all transistors in the **Figure 6**. [4 marks]
- (ii) **Determine the overall small signal differential-mode voltage gain** for the **MC14573** op-amp in the **Figure 6**. Gain for the output stage consists of transistor  $M_7$  and  $M_8$  is given by equation  $A_{v2} = -g_{m7}(r_{o7} || r_{o8})$ . [6 marks]

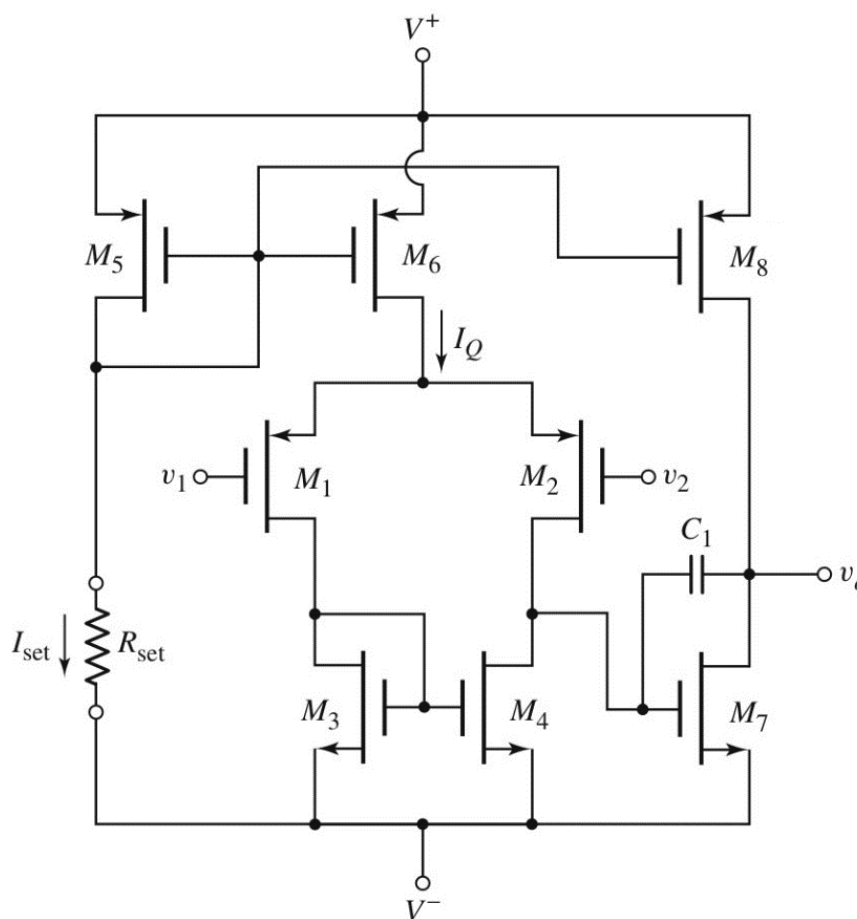

**Figure 6**

**Question 5 [20 marks]**

- (a) **List two** (2) ideal op-amp characteristics. **[2 marks]**
- (b) **Figure 7** shows a **difference amplifier** using ideal op-amps.

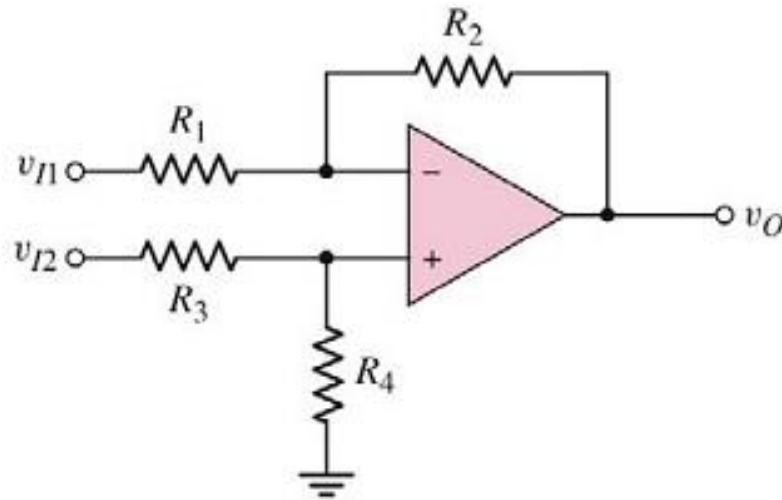

**Figure 7**

With proper analysis, **show that** **[10 marks]**

$$v_O = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 / R_3}{1 + R_4 / R_3}\right) v_{I2} - \left(\frac{R_2}{R_1}\right) v_{I1}$$

- (c) For the difference amplifier in the **Figure 7**, let  $R_1 = 12 \text{ k}\Omega$ ,  $R_2 = 120 \text{ k}\Omega$ ,  $R_3 = 40 \text{ k}\Omega$ , and  $R_4 = 440 \text{ k}\Omega$ . **Determine CMRR(dB).** **[8 marks]**

**-END OF QUESTION PAPER-**

**APPENDIX:**

**A) BASIC FORMULA FOR TRANSISTOR**

**BJT**

$$i_C = I_S e^{v_{BE}/V_T} \quad ; \text{NPN}$$

$$i_C = I_S e^{v_{EB}/V_T} \quad ; \text{PNP}$$

$$i_C = \beta i_B = \frac{\beta}{\beta + 1} i_E$$

$$i_E = i_B + i_C$$

; Small signal

$$\beta = g_m r_\pi$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_T = 26 \text{ mV}$$

**MOSFET**

; N – MOSFET

$$v_{DS}(\text{sat}) = v_{GS} - V_{TN}$$

$$i_D = K_n [v_{GS} - V_{TN}]^2$$

$$K_n = \frac{\mu_n C_{ox} W}{2L} = \frac{k'_n}{2} \cdot \frac{W}{L}$$

; P – MOSFET

$$v_{SD}(\text{sat}) = v_{SG} + V_{TP}$$

$$i_D = K_p [v_{SG} + V_{TP}]^2$$

$$K_p = \frac{\mu_p C_{ox} W}{2L} = \frac{k'_p}{2} \cdot \frac{W}{L}$$

; Small signal


$$g_m = 2\sqrt{K_n I_{DQ}} \quad ; \text{N – MOSFET}$$

$$g_m = 2\sqrt{K_p I_{DQ}} \quad ; \text{P – MOSFET}$$


$$r_o \cong \frac{1}{\lambda I_{DQ}}$$

**B) HYBRID- $\pi$  EQUIVALENT CIRCUITS**

**BJT**

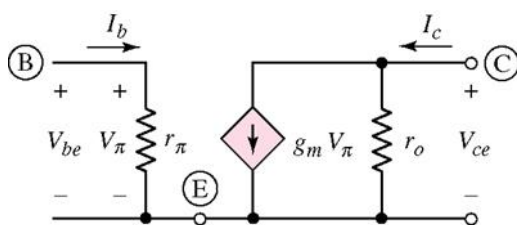

**MOSFET**

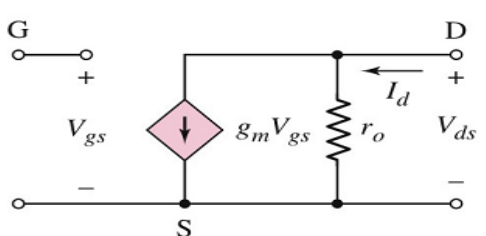

**C) QUADRATIC FORMULA**

$$Ax^2 + Bx + C = 0 \quad \rightarrow \quad x = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A}$$