

Name:
Student ID Number:
Section Number: 01A
Lecturer: Dr Jamaludin/ Prof Md Zaini
Table Number:



The National Energy University

College of Engineering

Department of Electrical Engineering

Midterm Test – Model Answer

SEMESTER 3, ACADEMIC YEAR 2018/2019

Subject Code : **EEB273**
Course Title : **Electronics Analysis & Design II**
Date : **5 April 2019**
Duration : **2 hours**

Instructions to the candidates:

1. Write your Name and Student ID Number.
2. Write all your answers using pen. DO NOT USE PENCIL except for the diagram.
3. ANSWER ALL QUESTIONS. Show clearly all your calculations. Every value must be written with its correct Unit.
4. WRITE YOUR ANSWER ON THIS QUESTION PAPER.



NOTE: DO NOT OPEN THE QUESTION PAPER UNTIL INSTRUCTED TO DO SO.

☺ GOOD LUCK! ☺

Question Number	Q1 (a)	Q1 (bcd)	Q2 (abc)	Q3 (ab)	Q4 (ab)	Total
Marks						
CO	9	1	3	1	2	

QUESTION 1 [25 marks]**Answers for Question 1****Q1(a) [4 marks]**

Each component, V_{BE} , I_{REF} , I_O , and power supplies will be given 0.25 marks.
Total = 4 marks.

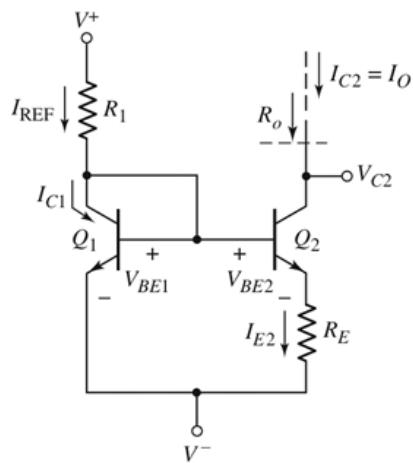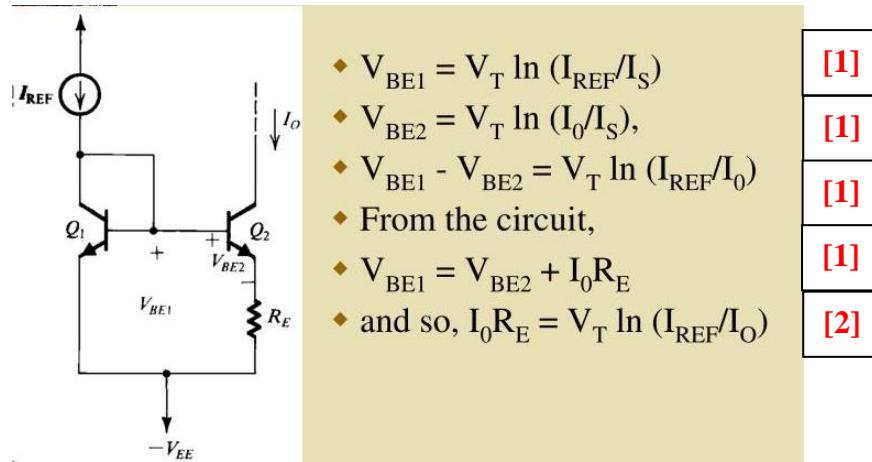**Q1(b) [6 marks]**

Answers for Question 1 (Continued)

Q1(c) [10 marks]

$$\text{Basic formula: } I_C = I_S \exp(V_{BE} / V_T)$$

$$V_{BE} = V_T \ln(I_{REF} / I_S)$$

From the given information $V_{BE} = 0.7$ V at 1 mA,

$$I_S = I_C / \{\exp(V_{BE} / V_T)\} \quad [1]$$

$$= (1m) / \{\exp(0.7 / 0.026)\} = 2.03 \times 10^{-15} \text{ A} \quad [1.5]$$

For $I_{REF} = I_{C1} = 2$ mA,

$$V_{BE1} = V_T \ln(I_{REF} / I_S) \quad [1]$$

$$= (0.026) \ln(2m / 2.03 \times 10^{-15}) = 0.718 \text{ V} \quad [1.5]$$

$$I_{REF} = (V^+ - V_{BE1} - 0) / R_1$$

$$R_1 = (V^+ - V_{BE1} - 0) / I_{REF} \quad [1]$$

$$= (15 - 0.718) / (2m) = 7.14 \text{ k}\Omega \quad [1.5]$$

$$I_O R_E = V_T \ln(I_{REF} / I_O)$$

$$R_E = (V_T / I_O) \ln(I_{REF} / I_O) \quad [1]$$

$$= (26m / 50\mu) \ln(2m / 50\mu) = 1.92 \text{ k}\Omega \quad [1.5]$$

Q1(d) [5 marks]

$$R_O = r_{o2}[1 + g_m(R_E / r_{\pi2})] \quad [1]$$

$$r_{\pi2} = \beta V_T / I_O = [50(26m)] / 50\mu = 26 \text{ k}\Omega \quad [1]$$

$$r_{o2} = V_A / I_O = 100 / 50\mu = 2 \text{ M}\Omega \quad [1]$$

$$g_m = I_O / V_T = 50\mu / 26m = 1.923 \text{ mA/V} \quad [1]$$

$$R_O = 2M [1 + 1.923m (1.92k || 26k)] = 8.88 \text{ M}\Omega \quad [1]$$

QUESTION 2 [25 marks]**Answers for Question 2 (Continued)**

Q2(a) Calculate I_O such that the DC currents in the diff-amp are balanced. [6 marks]

Derive formula $I_O = I_Q / \beta$ and use it

$$I_{B3} + I_{B4} = I_{C3} / \beta + I_{C4} / \beta = (I_{C3} + I_{C4}) / \beta \quad [1]$$

Assuming base currents for transistors in the diff-amp and I_O are small, then

$$I_{C3} + I_{C4} \approx I_{C1} + I_{C2} \approx I_{E1} + I_{E2} = I_Q$$

$$\text{Then } I_{B3} + I_{B4} = I_Q / \beta \quad [1]$$

For the DC currents in the diff-amp to be balanced

$$I_O = I_{B3} + I_{B4} = I_Q / \beta \quad [2]$$

$$I_O = I_Q / \beta = 0.2 \text{ mA} / 100 = 0.002 \text{ mA} = 2 \mu\text{A} \quad [2]$$

Q2(b) Determine the open-circuit differential-mode voltage gain, A_d . [12 marks]

$$r_{o2} = V_A / I_{CQ2} = V_A / (I_Q/2) = 100/(2\mu/2) = 1 \text{ M}\Omega \quad [2]$$

$$r_{o4} = V_A / I_{CQ4} = V_A / (I_Q/2) = 100/(2\mu/2) = 1 \text{ M}\Omega \quad [2]$$

$$g_{m2} = I_{CQ2}/V_T = I_Q / 2V_T = 2 \mu/[2(26m)] = 3.846 \text{ mA/V} \quad [4]$$

$$A_d = g_{m2} (r_{o2} \parallel r_{o4}) = (3.846m) (1M \parallel 1M) = 1923 \text{ V/V} \quad [4]$$

Q2(c) Find the differential-mode voltage gain if load resistance $R_L = 250 \text{ k}\Omega$ [7 marks]

$$A_d = g_{m2} (r_{o2} \parallel r_{o4} \parallel R_L) \quad [3]$$

$$A_d = (3.846m) (1M \parallel 1M \parallel 250k) = 641 \text{ V/V} \quad [4]$$

QUESTION 3 [25 marks]**Answers for Question 3 (Continued)****Q3(a) [15 marks]**

$$M_1: \quad I_{REF} = I_{D1} = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TN})^2 \quad [1]$$

$$M_3: \quad I_{REF} = I_{D3} = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_3 (V_{GS3} - V_{TN})^2 \quad [1]$$

$$\begin{aligned} \text{KVL: } & V_{GS1} + V_{GS3} = V_+ - V_- = 5 - (-5) \\ \Rightarrow & V_{GS3} = 10 - V_{GS1} \end{aligned} \quad [1]$$

$$\begin{aligned} M_1 = M_3: \quad & \left(\frac{70\mu}{2}\right) (20)_1 (V_{SG1} - 0.7)^2 = \left(\frac{70\mu}{2}\right) (3)_3 (V_{SG3} - 0.7)^2 \\ & \sqrt{\frac{20}{3}} (V_{GS1} - 0.7) = (10 - V_{GS1}) - 0.7 \end{aligned} \quad [1]$$

$$\begin{aligned} \text{Solve the equation clearly to find } V_{GS1} &= 3.1 \text{ V} \\ \Rightarrow V_{GS3} &= 10 - V_{GS1} = 10 - 3.1 = 6.9 \text{ V} \end{aligned} \quad [1] \quad [2]$$

$$I_{REF} = I_{D1} = \left(\frac{70\mu}{2}\right) (20)_1 (3.1 - 0.7)^2 = 4.032 \text{ mA} \quad [2]$$

$$V_{GS2} = V_{GS1} = 3.1 \text{ V} \quad [1]$$

$$M_2: \quad I_O = I_{D2} = \left(\frac{k'_n}{2}\right) \left(\frac{W}{L}\right)_2 (V_{GS2} - V_{TN})^2 \quad [1]$$

$$I_O = I_{D2} = \left(\frac{70\mu}{2}\right) (12.5)_2 (3.1 - 0.7)^2 = 2.520 \text{ mA} \quad [2]$$

$$V_{DS2} = V_{DS1} = V_{GS1} = 3.1 \text{ V} \quad [2]$$

Q3(b) [10 marks]

R_o is calculated at $V_{DS2} = V_{DS1} = V_{GS1} = 3.1 \text{ V}$ where $I_o = 2.520 \text{ mA}$

$$R_o = \frac{1}{I_o} = \frac{1}{0.015 \times 2.520} = 26.455 \text{ k}\Omega \quad [2]$$

$\boxed{\text{Io at } V_{DS2} = 2.5 \text{ V} \text{ is given by Io at } V_{DS2} = 3.1 \text{ V} \text{ plus change in Io (i.e. } dI_o \text{) when } V_{DS2} \text{ changes from } 3.1 \text{ V to } 2.5 \text{ V.}}$ [2]

$$dI_o = \frac{dV_{DS2}}{R_o} = \frac{2.5 - 3.1}{26.455k} = -0.02268 \text{ mA} \quad [3]$$

$$\Rightarrow \boxed{\text{Io at } V_{DS2} = 2.5 \text{ V}} = 2.520 \text{ mA} + (-0.02268 \text{ mA}) = 2.4973 \text{ mA} \quad [3]$$

QUESTION 4 [25 marks]**Answers for Question 4 (Continued)****Q4(a) [15 marks]**

$$I_1 = \frac{V^+ - V^- - V_{GS4}}{R_1} = \frac{20 - V_{GS4}}{R_1}$$
1

$$I_1 = K_{n3} (V_{GS4} - V_{TN})^2$$
1

$$9V_{GS4}^2 - 17V_{GS4} - 11 = 0$$

$$V_{GS4} = 2.40 \text{ V}$$
2

$$I_1 = 0.587 \text{ mA}$$
2

$$I_Q = I_1 = 0.587 \text{ mA}$$
[2]

The quiescent drain currents in M_1 and M_2 :

$$I_{D1} = I_{D2} = I_Q / 2 \approx 0.293 \text{ mA}$$
[2]

The gate-to-source voltages are then

$$V_{GS1} = V_{GS2} = \sqrt{\frac{I_{D1}}{K_{n1}}} + V_{TN} = \sqrt{\frac{0.293}{0.1}} + 1 = 2.71 \text{ V}$$
[2]

The quiescent values of v_{o1} and v_{o2} are

$$v_{o1} = v_{o2} = V^+ - I_{D1} R_D$$
[2]

$$= 10 - (0.293 \text{ mA})(16 \text{ k}) = 5.31 \text{ V}$$
[1]

Q4(b) [10 marks]

The maximum common-mode input voltage, v_{CM} (max), is the value at v_1 when M_1 and M_2 reach the saturation point,

$$v_{CM}(\text{max}) = V_{S1}(\text{max}) + V_{GS1} = (v_{o1} - V_{DS1}(\text{sat})) + V_{GS1}$$
[2]

$$V_{DS1}(\text{sat}) = V_{GS1} - V_{TN} = 2.71 - 1 = 1.71 \text{ V}$$
[1]

Therefore,

$$v_{CM}(\text{max}) = 5.31 - 1.71 + 2.71 = 6.31 \text{ V}$$
[2]

The minimum common-mode input voltage, v_{CM} (min), is the value at v_1 when M_4 reaches the saturation point,

$$v_{CM}(\text{min}) = V_{S1}(\text{min}) + V_{GS1} = (V^- + V_{DS4}(\text{sat})) + V_{GS1}$$
[2]

$$V_{DS4}(\text{sat}) = V_{GS4} - V_{TN} = 2.4 - 1 = 1.4 \text{ V}$$
[1]

Therefore,

$$v_{CM}(\text{min}) = (-10) + 1.4 + 2.71 = -5.89 \text{ V}$$
[2]